

A CAHNERS PUBLICATION

FEBRUARY 16, 1989

EDN[®]

Design Ideas
Special Issue
VOLUME III

ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS






The ultimate in components partnering. Which supplier can deliver all the elements?

Dale has been perfecting the elements of partnering for nearly three decades. We began with a commitment to be the absolute best supplier of fixed resistors and associated components. The best at a technology which many said couldn't be improved. But we've done it.

When the industry was ready to surface mount, we were ahead of the game with the largest selection of resistive components available. When ship-to-stock came on the scene, our ZIP® program was the first to eliminate the need for receiving inspection while guaranteeing on-time delivery. And, since 1972, our inno-

Dale® Can.

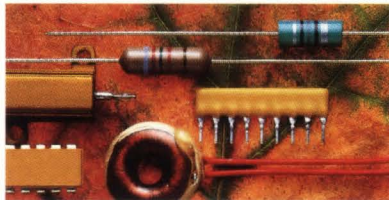

vatve electronic data interchange (EDI) system has grown into an international network.

Behind this solid supply commitment is a quality structure for which perfection is seen as an attainable goal. It encompasses

everything from Certified Suppliers to Quality Circles to fully integrated Statistical Process Control.

Partnering. There's only one components supplier with the experience, size and commitment to make it work to your ultimate advantage. Dale can. Contact your Dale Representative or phone our Corporate Marketing Department at (402) 563-6359.



Dale Makes Your Basics Better

SURFACE MOUNT SUPERSOURCE.



4S-8116

SPRAGUE HAS IT ALL IN SURFACE MOUNT COMPONENTS.

You'll find what you need in state-of-the-art surface-mount passive components at Sprague . . . the SMD leader. No one offers you a broader choice: **TANTAMOUNT®** Solid Tantalum Chip Capacitors with the highest capacitance in the smallest package in the industry. **MONOLITHIC®** Ceramic Chip Capacitors in general purpose, high-voltage, high-temperature and high-frequency types, and low-profile chips for IC decoupling. **SORN®** Small-Outline Resistor Networks — reduce board space requirements. **CAPSTRATE®** Capacitor and R-C Networks — smaller and more reliable than conventional networks.







To build systems for tomorrow, depend on Sprague today . . . for rugged, reliable, competitively priced surface-mount passive components. All Sprague SMD components are available taped and reeled. For complete information, write for our surface-mount data package to Technical Literature Service, Sprague Electric Company, P.O. Box 9102, Mansfield, MA 02048-9102.



Hybrid Reliability Begins Here

Whether you're producing...computers...computer peripherals...telecommunications...medical equipment...terminals...office machines...or NC machine tools...Taiyo Yuden hybrid circuits are your best investment in reliability. **Why?** The reason is simple. In thick film hybrids, design, manufacturing and rigid testing is critical. Taiyo Yuden — **with almost 50 years in electronics** — is the international leader in hybrid circuit assembly. Whatever your requirements, our U.S.-based engineering staff will work with you to transform your hybrid design into a working product incorporating the latest in leading-edge technology, with the same high quality delivered the world over. And like the rest of our electronic components, they're available at very competitive prices. To find out more about Taiyo Yuden hybrids, write or call today:

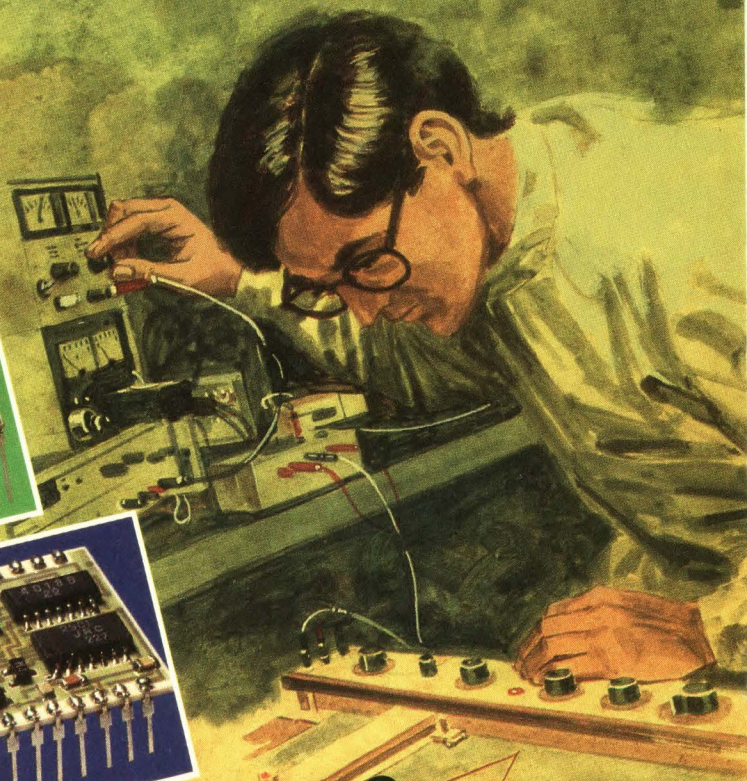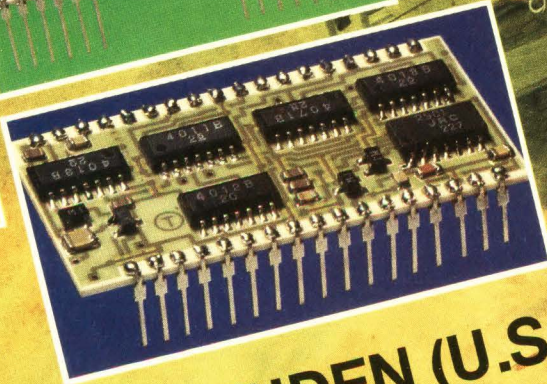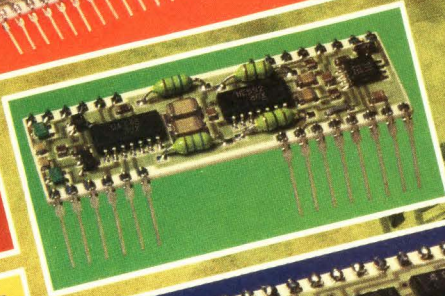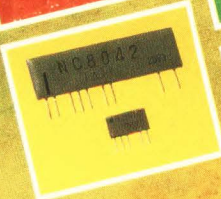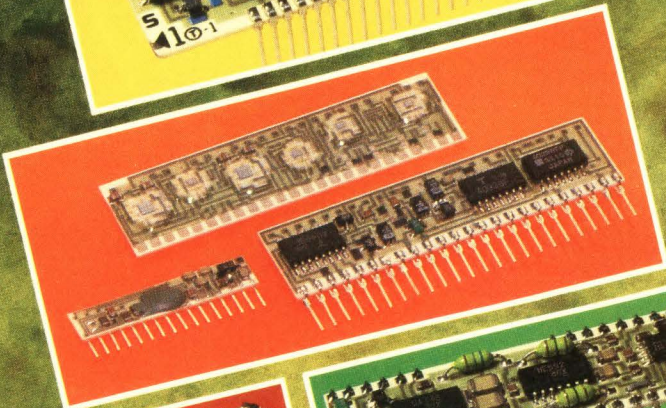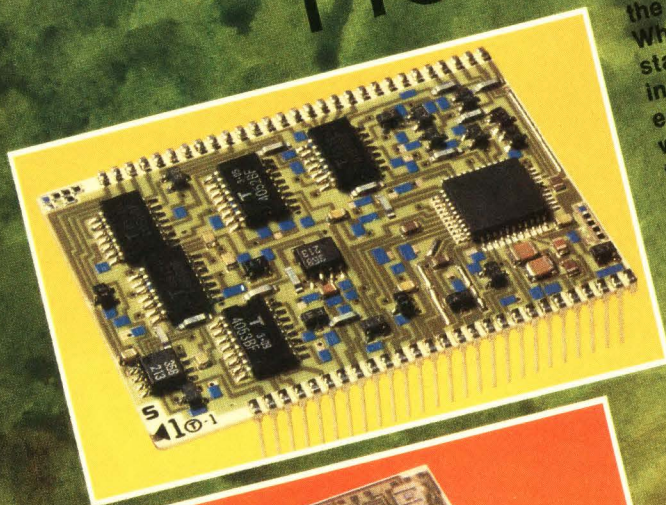TAIYO YUDEN (U.S.A.) INC.
714 West Algonquin Road
Arlington Heights, IL 60005
Tel: 1-312-364-6104
Telex: 910-687-0378 TAIYO U.S.A. ARHT



TAIYO YUDEN (U.S.A.) INC

714 West Algonquin Road • Arlington Heights, IL 60005
Tel.: 1-312-364-6104 • Telex: 910-687-0378 TAIYO U.S.A. ARHT



(Photography by Mike Blake;
art direction by Chinsoo Chung)

INTRODUCTION 7

AMPLIFIERS

- Amp provides 100V common-mode range 67
- Feedforward amplifier reduces distortion 53
- Improve voltage-controlled current source 57
- Op amp provides a current and voltage source . . 69
- Variable-gain amplifier uses matched FETs 53

CONTROLLERS

- AC circuit breaker has adjustable threshold 50
- Analog delay line uses digital techniques 13
- Baseline restorer is voltage-programmable 18
- Bidirectional tachometer offers low error 40
- Counter controls its own clock frequency 16
- IC replaces mechanical-interlock switches 61
- Microphone controls voice-actuated switch 15
- Tachometer circuit reduces parts count 12
- Thermistor bridge senses air flow 47

CONVERTERS

- Circuit converts voltage ratio to frequency 14
- Digital ICs form programmable divider 31
- Power-reset circuit provides four functions 28

Continued on page 5

EDN® (ISSN 0012-7515) is published 49 times a year (biweekly with 2 additional issues a month, except for February, which has 3 additional issues and July and December which have 1 additional issue) by Cahners Publishing Company, A Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158-1630. Terrence M McDermott, President; Frank Sibley, Electronics/Computer Group Vice President; Jerry D Neth, Vice President/Publishing Operations; J J Walsh, Financial Vice President/Magazine Division; Thomas J Dellamaria, Vice President/Production and Manufacturing. Circulation records are maintained at Cahners Publishing Company, 44 Cook Street, Denver, CO 80206-5800. Telephone: (303) 388-4511. Second-class postage paid at Denver, CO 80206-5800 and additional mailing offices. POSTMASTER: Send address corrections to EDN® at the Denver address. EDN® copyright 1989 by Reed Publishing USA; Saul Goldweitz, Chairman; Ronald G Segel, President and Chief Executive Officer; Robert L Krakoff, Executive Vice President; William M Platt, Senior Vice President. Annual subscription rates for nonqualified people: USA, \$105/year; Canada/Mexico, \$125/year; Europe air mail, \$150/year; all other nations, \$150/year for surface mail and \$230/year for air mail. Single copies are available for \$10. Please address all subscription mail to Eric Schmierer, 44 Cook Street, Denver, CO 80206-5800.



**We have solutions
to your toughest
microcircuit problems...**


**And many
are coming
right off
our shelves.**

For over twenty years, CTI has been providing design and manufacturing solutions for some of the most complex black box requirements in the most demanding markets—military and government, avionics, telemetry, navigation, communications, guidance and control systems, among others.

Our products range from custom hi-rel hybrid microcircuits, to Standard Electronic Modules (SEMs) in high-density configurations, to miniaturized subsystems for military and space applications. We have in-house hybrid and monolithic design, manufacturing, and technology expertise to convert the toughest requirements into high-performance microcircuits.

And we've used our experience to build a host of standard circuits. These pre-engineered "off-the-shelf" packages include MIL-STD-1553 standard data bus products, and MIL-STD-1397 interfaces.

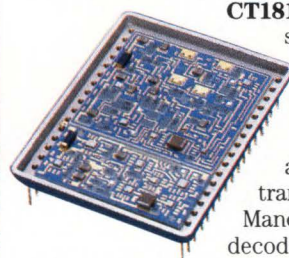One new standard product is the CT1815, a 10MB/Sec serial communication hybrid. The circuit incorporates an encoder, transceiver and Manchester decoder in one



package providing transmission and reception of data over cable lengths of up to 1000 feet.

So, whether your project is in the early design stage or is approaching production, call on CTI. Solutions to some of your requirements may have to be invented. Others may already be on our shelves. We offer you the advantage of either—or both. Call or write us today.

CTI

Circuit Technology Inc.

160 Smith Street, Farmingdale, New York 11735
Tel: (516) 293-8686 FAX: (516) 293-8622

CIRCLE NO 153

VP/Publisher
Peter D Coley

VP/Associate Publisher/Editorial Director
Roy Forsberg

Editor
Jonathan Titus

Managing Editor
John S Haystead

Assistant Managing Editor
Joan Morrow

Special Projects
Gary Legg

Home Office Editorial Staff
275 Washington St, Newton, MA 02158
(617) 964-3030

Tom Ormond, *Senior Editor*
Joanne De Oliveira, *Associate Editor*
John A Gallant, *Associate Editor*
Clare Mansfield, *Associate Editor*
Michael C Markowitz, *Associate Editor*
Christine McElvenny, *Associate Editor*
Dave Pryce, *Associate Editor*
Cynthia B Rettig, *Associate Editor*
Julie Anne Schofield, *Associate Editor*
Charles Small, *Associate Editor*
Dan Strassberg, *Associate Editor*
Anne Watson Swager, *Associate Editor*
Chris Terry, *Associate Editor*
Helen McElwee, *Staff Editor*
James P Scanlan, *Staff Editor*
Steven Paul, *Senior Production Editor*
Flo E Evans, *Production Editor*

Editorial Field Offices
Margery S Conner, *Regional Editor*
Los Osos, CA: (805) 528-0833
Doug Conner, *Regional Editor*
Los Osos, CA: (805) 528-0865
Steven H Leibson, *Regional Editor*
Boulder, CO: (303) 494-2233
J D Mosley, *Regional Editor*
Arlington, TX: (817) 465-4961
Richard A Quinell, *Regional Editor*
San Jose, CA: (408) 296-0868
David Shear, *Regional Editor*
San Jose, CA: (408) 997-5452
Maury Wright, *Regional Editor*
San Diego, CA: (619) 748-6785
Peter Harold, *European Editor*
0603-630782
(St Francis House, Queens Rd,
Norwich, Norfolk NR1 3PN, UK)

Contributing Editors
Robert Pease, Bob Peterson,
Don Powers, Bill Travis

Editorial Services
Kathy Leonard, *Office Manager*
Nancy Weiland, Helen Benedict

Art Staff
Ken Racicot, *Senior Art Director*
Chinsoo Chung, *Associate Art Director*
Cathy Filipski, *Staff Artist*
Martha Crowell, *Staff Artist*

Production/Manufacturing Staff
William Tomaselli, *Production Supervisor*
Danielle M Biviano, *Production Assistant*
Deborah Hodin, *Production Assistant*
Diane Malone, *Composition*

Director of Art Department
Joan Kelly
Norman Graf, *Associate*

VP/Production/Manufacturing
Wayne Hulitzky

Director of Production/Manufacturing
John R Sanders

Business Director
Deborah Virtue

Marketing Communications
Anne Foley, *Promotion Manager*
Sara Morris, *Marketing Services*
Gordon Keegan, *Promotion Specialist*

GENERATORS

Burglar-alarm circuit uses one chip	62
Driver circuit boosts 3-state outputs	23
Electronic thermometer has a 10-mV/°F output	20
Frequency divider generates 50% duty cycle	56
Low-power RS-232C driver operates from 5V	64
Reconstruct missing sync pulses for VCR	51
Simple circuit supplies relay hold current	32

SOFTWARE

Algorithm produces base-2 logarithms	33
Fortran program calculates op-amp noise	49
Program speeds best-fit 1% resistor calculations	35
Run Z80 software on an 8085 system	37
Simpson's rule solves double integrals	38


TEST

Circuit deletes power-line cycles	44
Circuit lets you analyze NiCd batteries	11
Simple calculator acts as low-speed counter	26
Tachometer measures low frequencies	27

Career Opportunities	74
Business/Corporate Staff	75
Advertisers Index	76

Cahners Publishing Company, A Division of Reed Publishing USA ☐ Specialized Business Magazines for Building & Construction ☐ Manufacturing ☐ Foodservice & Lodging ☐ Electronics & Computers ☐ Interior Design ☐ Printing ☐ Publishing ☐ Industrial Research & Technology ☐ Health Care ☐ and Entertainment. Specialized Consumer Magazines: ☐ American Baby ☐ and Modern Bride.

Now... **MORE POWER** in small packages.

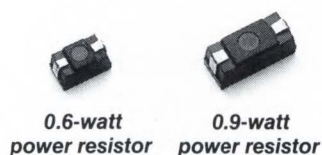


Ohmite expands surface mount line with 0.6 and 0.9 watt resistors.

Now you can get the same high performance and easy application you find in Ohmite's 1.5- and 2.5-watt power resistors in two new ratings: 0.6- and 0.9-watt.

Both are metal film resistors which improve reliability in general purpose applications.

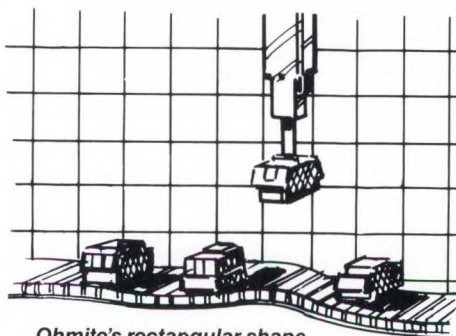Resistance volume ranges from 10 Ohms to 100 Kilohms for the 0.6-watt resistors. And from 1 Ohm to 1 Megohm for the 0.9-watt resistors.



Ohmite's rectangular shape eliminates the need for special pipettes and allows for better vacuum pickup in pick-and-place.

For compatibility with major pick-and-place applications, Ohmite's 0.6-watt resistors can be supplied in 12mm tape reels containing 2000 pieces, and the 0.9-watt resistors can be supplied on 16mm tape reels containing 1500 pieces.

Ohmite® — has the answers in surface mount technology.



To get the latest in surface mount resistor technology and proven performance, contact:

Ohmite Manufacturing Co.

3601 Howard St., Skokie, IL 60076 Tel 312/675-2600 TWX 910-223-0805 Telex 72-4433 FAX 312-675-1505

INTRODUCTION

Every batch of Reader Service cards we receive contains many comments about our Design Ideas section. Most often, readers tell us that they've found a particularly useful circuit that helped them solve a tricky design problem. But readers also want to know how they can get a complete set of past circuits and software. Alas, such a compendium doesn't exist. But this Design Ideas Special Issue represents the next best thing—a collection of 33 of the best Design Ideas published in EDN from 1985 through June 1988.

This collection of designs reflects your preferences, not necessarily those of our technical editors. You and your colleagues voted for these winning ideas by circling the Reader Service numbers that appear at the end of each Design Idea we publish. Of the circuit-design tips in this Design Ideas Special Issue, 21 garnered Best-of-Issue honors based on reader preference. The remaining Design Ideas received the second-highest number of reader votes over the 1985 to 1987 time frame.

In planning these Design Ideas Special Issues, EDN hoped to be able to present a good mixture from the standpoint of design disciplines. Happily, our readers' choices made it easy to achieve this goal. This issue contains 16 analog circuit designs and 12 digital designs, and the remaining five ideas highlight programming tips. To achieve some semblance of order, we've divided the ideas into some generic categories and provided an index that lists design and circuit categories. Although the index is a handy place to look for a special circuit, we'll bet that most readers will want to read the ideas one by one, just to see what circuits are available.

As you read these Design Ideas, remember that each one came from a reader who thought someone else might benefit from his or her work. So, if you find this issue helpful, thank your fellow engineers who submitted the ideas we've published over the years. And the next time you have an interesting and useful circuit, consider sharing it with others by submitting it for publication in EDN's regular Design Ideas section.

Besides seeing your name in print and earning \$100, you might find your idea has been selected as the issue winner. Each issue winner collects an extra \$100. Keep in mind, too, that EDN's editors also choose a grand-prize winner each year. The grand prize includes a check for \$1500. Your idea may also be selected to appear in a future Design Ideas Special Issue. You'll find an entry form in the Design Ideas section of most issues of EDN.

If you enjoy this Design Ideas Special Issue and find it useful, we'd like to hear from you. If you have suggestions for improvements and changes, we'd like to hear those, too. Just send us a note or give us a call. We'd also like to thank all the readers who have submitted Design Idea entries over the years.

Enough introduction. Here are more of the ideas you've been clamoring for. Good reading.


EDN



Tom Ormond
Senior Editor

SAMSUNG
NOW

NEW SAMSUNG MICRO BECAUSE YOU'RE EITHER

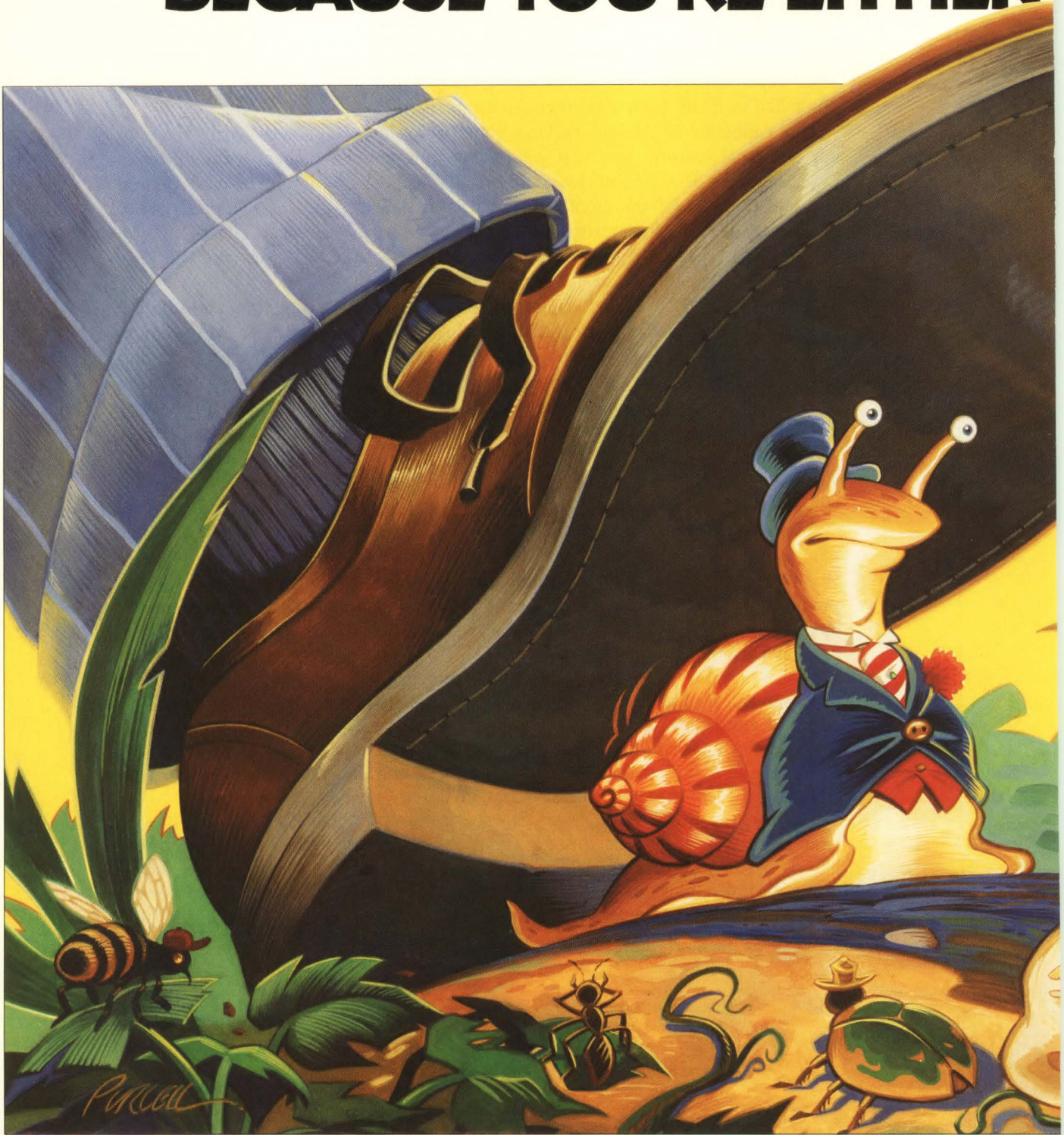

PROCESSOR PERIPHERALS. QUICK OR YOU'RE DEAD.

Samsung's hot new microprocessor peripherals are the fastest industry-standard family made by anyone.

We offer these CMOS parts with top speeds of 10 Mhz, 12 Mhz, and even 16 Mhz.

And in a world where the drive for speed takes no prisoners, that kind of performance can just about save your life.

8086/286/386 microprocessors have steadily gotten faster. But today, they're slowed down by microprocessor peripherals that haven't.

Our new parts change that. They will let your fast CPU run the way it was meant to—fast.

Besides being fast, Samsung's peripherals are in CMOS, which means they're low in power dissipation and will keep your designs cool. And unlike most peripherals, they're available through the entire line in PLCC surface mount packaging, in addition to DIP.

Best of all, these speedy peripherals are for real: you can get

as many of them as you want, because we're a high-volume supplier and we have parts ready for immediate delivery in quantity.

Of particular note: our 82C37 DMA Controller, which at 10

Mhz is the fastest made. Also: our 53C80 SCSI Interface, and our blow-the-doors-off, performance-boosting 1- and 4-Mb DRAM Controller, affectionately known as the System Accelerator.

Microprocessor peripherals from Samsung. The fastest family made, they're designed to let your CPU run at the speeds it was meant to.

In a world where you're either quick or you're dead, we think you'll find them extremely helpful.

Call Microprocessor Peripheral Marketing now for samples, databooks, or application notes, at 1-800-669-5400 or 408-922-7754. Or write to Microprocessor Peripheral Marketing, Samsung Semiconductor Inc., 3725 No. First Street, San Jose, CA 95134-1708.

SAMSUNG'S CMOS MICROPROCESSOR PERIPHERALS

PART	SPEED	AVAILABLE
KS53C80 SCSI Interface	1.5 Mbyte/sec.	Now
KS82C37A DMA Controller	5, 8, 10 Mhz	Now
KS82C50A UART	8, 10 Mhz	Now
KS82C52 Serial Controller Interface	8, 10 Mhz	Now
KS82C54A Interval Timer	8, 10 Mhz	Now
KS82C55A Programmable Peripheral Interface	8, 10 Mhz	Now
KS82C59A Interrupt Controller	8, 10 Mhz	Now
K82C84A Clock Generator	8, 10 Mhz	Now
KS82C88 Bus Controller	8, 10 Mhz	Now
KS82C284 80286 Clock Generator	10, 12, 16 Mhz	Now
KS82C288 80286 Bus Controller	10, 12, 16 Mhz	Now
KS82C289 80286 Bus Arbiter	10, 12, 16 Mhz	Now
KS68C45S CRT Controller	4, 6 Mhz	Now
KS84C21/22 DRAM Controller	25, 40 Mhz	Now
KS85C30 SCC	6, 8, 10 Mhz	June



SAMSUNG
Semiconductor



PHILIPS



More ways to get in touch.

We've added a new color screen to our full line of touch control operator interfaces.

Fluke gives you more ways to improve the operator interface of your computer-based machine. Prompting operators through the sequence of your machine, touch control from Fluke reduces both input error and training time. Your customers will appreciate the value these state-of-the-art interfaces add to computer-based products. Our broad line spans a variety of models, from the economical to the most sophisticated, from panel mount to bench top—and now we've added color. The new 1050 gives you a palette of 32 brilliant colors—more ways to

create effective displays, with the same confidence in quality.

Every Fluke Touch Control Screen offers the advantages of an integrated subsystem, eliminating costly and time consuming integration of touch panel, display and logic components. Our rigorous quality-control procedures ensure that every unit operates reliably. And our touch control screens operate under the toughest of environmental conditions.

Fluke has been designing and manufacturing quality touch control subsystems for the past ten years. As an experienced OEM vendor, we understand your needs. You'll find us a reliable business partner, ready with the support you need: competitive discounts,

complete documentation, powerful software tools and worldwide service.

When you want to get customers in touch with your machine, get in touch with Fluke. Contact your local Fluke Sales Engineer or call **1-800-44-FLUKE**.

John Fluke Mfg. Co., Inc., P.O. Box C9090, M/S 250C, Everett, WA 98206
U.S.: 206-356-5400 CANADA: 416-890-7600
OTHER COUNTRIES: 206-356-5500

© Copyright 1988 John Fluke Mfg. Co., Inc. All rights reserved.
Ad No. 0282-F1050

THE FIRST CHOICE
IN TOUCH CONTROL



CIRCLE NO 155

DESIGN IDEAS

EDITED BY STEVE COGGER

Circuit lets you analyze NiCd batteries

Mike Scaglione

Todd Medical Products, North Canton, OH

Because NiCd batteries maintain a constant output voltage, it is difficult to determine how much of the battery's charge remains. The **Fig 1** circuit provides a way of determining the capacity of a battery by draining it at a preset current to its depleted voltage of 1V/cell. You measure the discharge time of the cells and perform a simple calculation to obtain the battery's capacity.

You set the drain current (I_D) to 0.5C (C=battery capacity in mAh) by selecting an appropriate value for R_4 . Choose R_5 such that $I_D \times R_5 = 1V$. V_{REF} is set so the comparator turns off the drain current and timer when the battery reaches its depleted voltage, V_B (usually 1V/cell). You calculate V_{REF} as follows:

$$V_{REF} = \frac{R_3[R_2(V_S - 1.3) + R_1V_B]}{R_1R_2 + R_2R_3 + R_1R_3}$$

With the battery in place, activate the circuit by grounding V_{REF} with the momentary switch. The battery drains at I_D until it reaches V_B , turning off the drain circuit and the timer. Hysteresis keeps the circuit from restarting.

Determine the battery's capacity using the following equation:

$$C_{(mAh)} = \text{Time of Cycle} \times I_D$$

The circuit shown tests 4.8V, 180-mAh batteries. I_D is 100 mA and V_B is 4V.

EDN

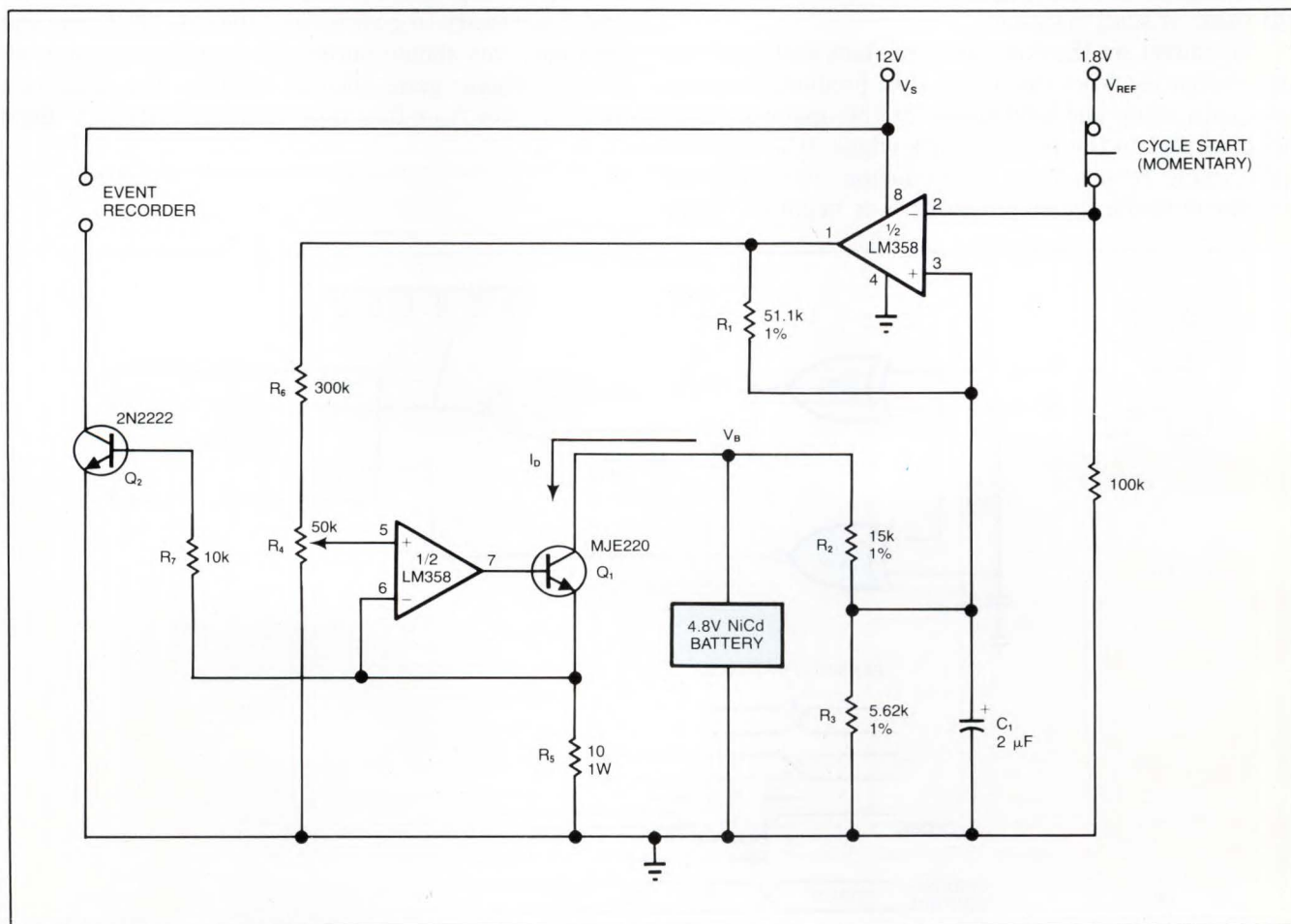


Fig 1—This circuit drains NiCd batteries and controls a timer to test the battery's capacity. When the battery voltage (V_B) reaches 1V/cell, the test stops and the timer turns off.

Tachometer circuit reduces parts count

William McClelland

Stahl Research, Port Chester, NY

The tachometer circuit of **Fig 1** requires only one IC (besides the counter), yet it achieves the same resolution and eliminates backlash just as the 3-IC circuit of an earlier Design Idea did ("Improved tachometer eliminates backlash," March 31, 1987, pg 210).

A standard shaft encoder's A and B ports generate square waves with the same frequency as the shaft turns. The phase of A will lead or lag that of B by 90° , depending on the direction of rotation. To obtain maximum resolution, the tachometer circuit must count every change of state for the A and B signals. Each such change causes a change of state at IC_{1A}'s output, followed by a 1- μ sec negative pulse at the output of IC_{1C}. These clock pulses' positive (trailing) edges cause the counter to count up or down according to the direction of shaft rotation.

You should set the R_1C_1 time constant such that it is approximately twice that of the R_2C_2 product, to ensure adequate setup and hold times for the up/down signal with respect to the positive clock edges. IC_{1C} supports this timing requirement by producing clock pulses of similar duration for either positive or negative transi-

tions from IC_{1A}.

The exclusive-NOR logic of IC_{1B} generates the correct polarity of the up/down signal when necessary—at the positive clock edges—by combining the A value with the B value just prior to a transition of either A or B. C₁ provides memory by storing the B value voltage for about 2 μ sec. (To understand this single-gate encoding, note that, because the phase relationship of B and A is $+ \text{ or } -90^\circ$, adding -90° to B makes the phase difference 0 or -180° , depending on the direction of rotation. Therefore, an exclusive-NOR operation on A and a phase-shifted B produces a logic 1 when the inputs are in phase, or a logic 0 when they are 180° out of phase.)

If necessary, you can invert the up/down signal's polarity by swapping the A and B connections or by using a fourth X-NOR gate as a selectable inverter buffer. To invert the clock signal, substitute identical-pinout, X-OR gates (4070s) for the 4077 X-NOR gates. And if necessary to guarantee standard CMOS rise and fall times, you should buffer the A and B signals with Schmitt-trigger gates such as 74C914s. The maximum frequency for A or B is approximately $(4R_1C_1)^{-1}$. **EDN**

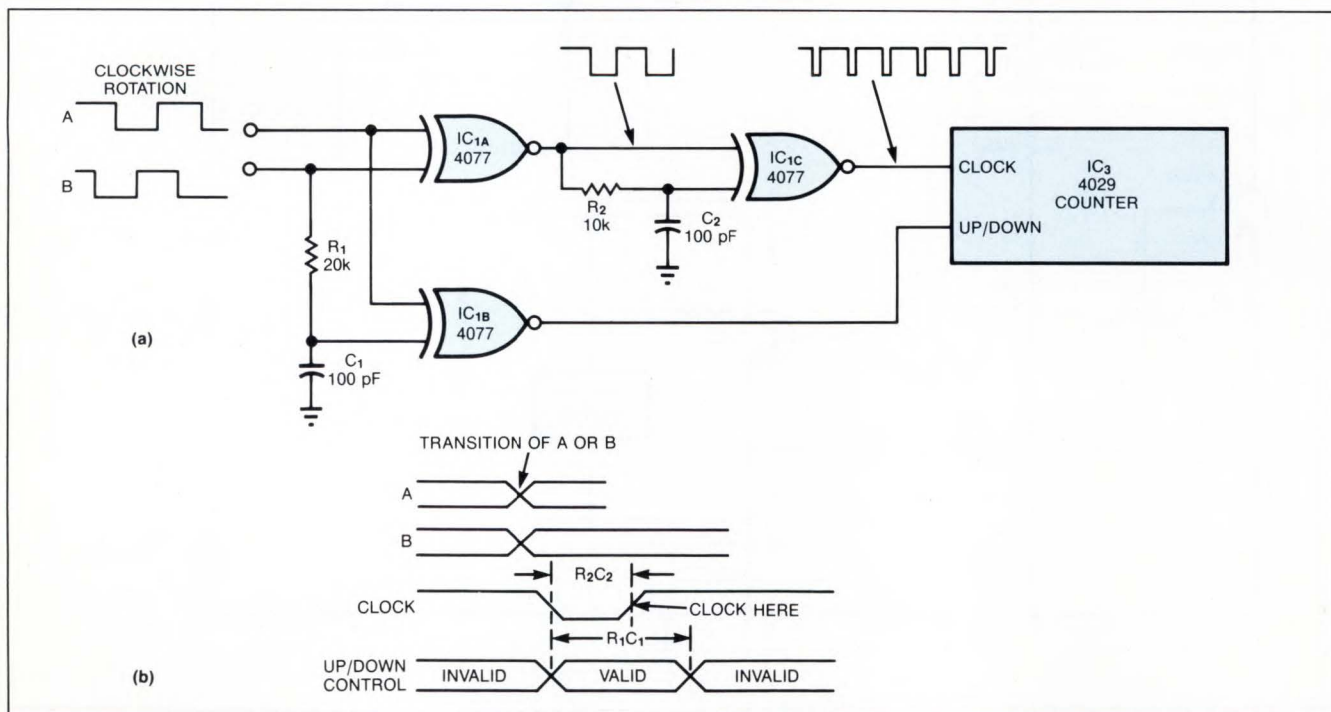


Fig 1—This 1-chip tachometer circuit drives the counter up or down, according to the speed and direction of shaft rotation (the shaft encoder isn't shown).

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Analog delay line uses digital techniques

T G Barnett and J Millar
*The London Hospital Medical College,
London, UK*

The analog delay line of **Fig 1** uses a digital technique to delay an analog signal for as long as two seconds, reconstructing the signal with 8-bit resolution. The product of the delay time and the bandwidth is a constant: For a 1.024-kHz clock frequency (2-sec delay), the analog bandwidth is 100 Hz; for the maximum 40.96-kHz clock frequency (50-msec delay), the analog bandwidth is 4 kHz. There is no lower limit for the clock frequency.

The clock signal drives a binary counter (IC_2), which then scans the address inputs of a 2048-byte \times 8-bit RAM (IC_3). The RAM writes the contents of each memory location to the D/A converter (IC_4) and then reads out the results of a just-completed conversion by the 8-bit A/D converter IC_1 . The RAM reads out each data sample 2048 cycles after it is read in, so the delay is 2048 times the clock period, or 2048 divided by the clock frequency.

The clock signal also drives two monostable multi-

brators in parallel (IC_{5A} and IC_{5B}). IC_{5A} triggers on the clock's rising edge; IC_{5B} triggers on the clock's falling edge. You choose the timing components R and C so that each device produces a pulse of approximately 1 μ sec. These pulses have the proper polarity and phase to control the A/D converter, D/A converter, and RAM as shown.

You should scale the analog input for a range of 0 to 2.5V. The 100-pF capacitor sets the A/D converter's internal clock to its maximum rate of 900 kHz; you should monitor the \overline{BUSY} signal (pin 1) and adjust the capacitor value as required to achieve 900 kHz. Both converters include a 2.5V voltage reference, but to improve accuracy use the A/D converter's reference for both. Power consumption is 120 mA from the 5V supply and 50 μ A from the -5V supply. You can greatly reduce current drain from the positive supply by adding logic to control the RAM's chip-enable input (pin 18).

EDN

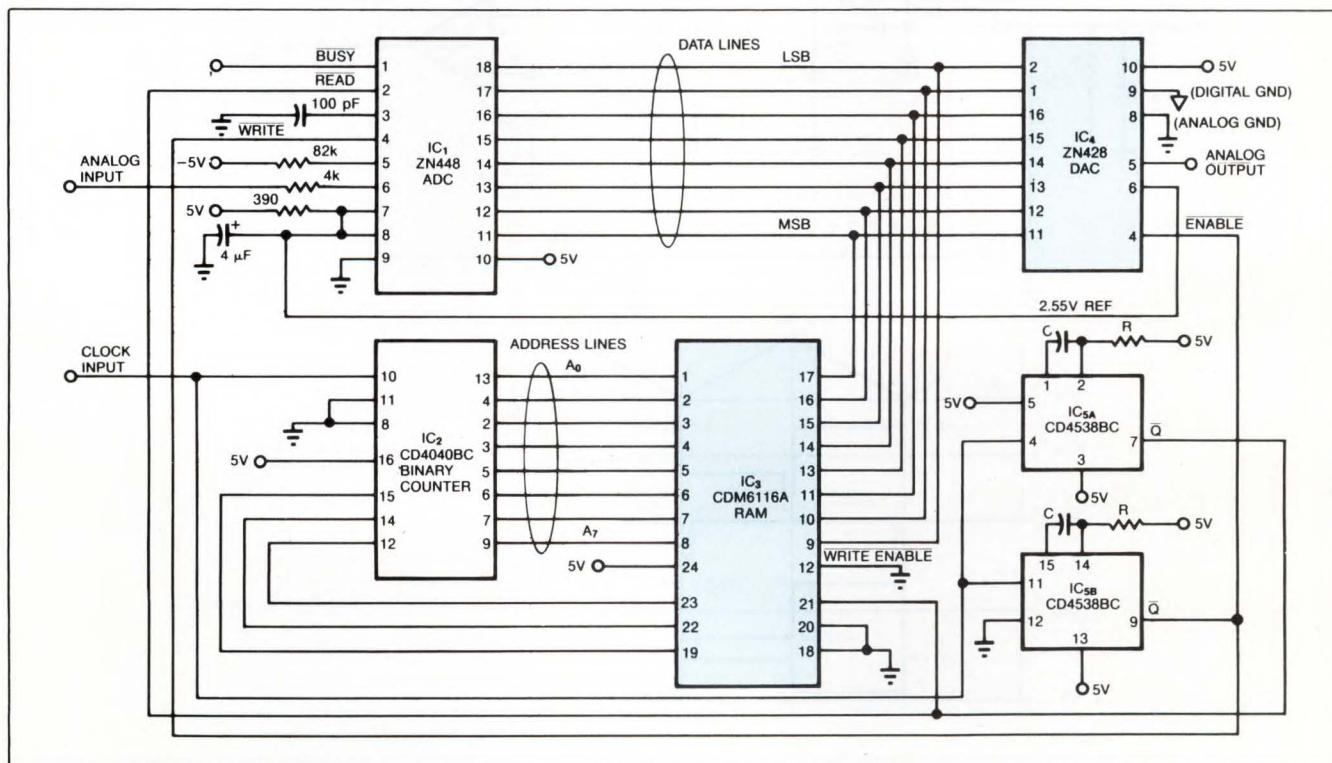


Fig 1—This analog delay line digitizes a signal once per clock cycle, stores the result in a 2048-word RAM, and converts one sample per clock cycle with a D/A converter. The resulting delay equals 2048 divided by the clock frequency.

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Circuit converts voltage ratio to frequency

Bobircă Florin Daniel

*The Electronic Research Institute,
Bucharest, Rumania*

The circuit of **Fig 1** accepts two positive-voltage inputs V_N and V_D and provides a TTL-compatible output pulse train whose repetition rate is proportional to the ratio V_N/V_D . Full-scale output frequency is about 100 Hz, and linearity error is below 0.5%.

The output F_O equals KV_N/V_D , where $K=1/(4R_2C_1)$ and provided $R_1=R_3$. Op amp IC_{1A} alternately integrates $V_N/2$ and $-V_N/2$, producing a sawtooth output that ramps between the V_D level and ground. When transistor Q_1 is on, for example, IC_{1A} integrates $-V_N/2$

until its output equals V_D . At that time, the IC_{1B} comparator switches low, causing IC_{1D} 's bistable output to go low, which turns off Q_1 . IC_{1A} 's output then ramps in the negative direction. When the output reaches 0V, the IC_{1C} comparator switches, Q_1 turns on, and the cycle repeats. Transistor Q_2 converts the IC_{1D} output to TTL-compatible output logic levels.

Setting V_D to 1.00V yields a linear V/F converter ($F_O=KV_N$), and setting V_N to 1.00V yields a reciprocal V/F converter ($F_O=K/V_D$).

EDN

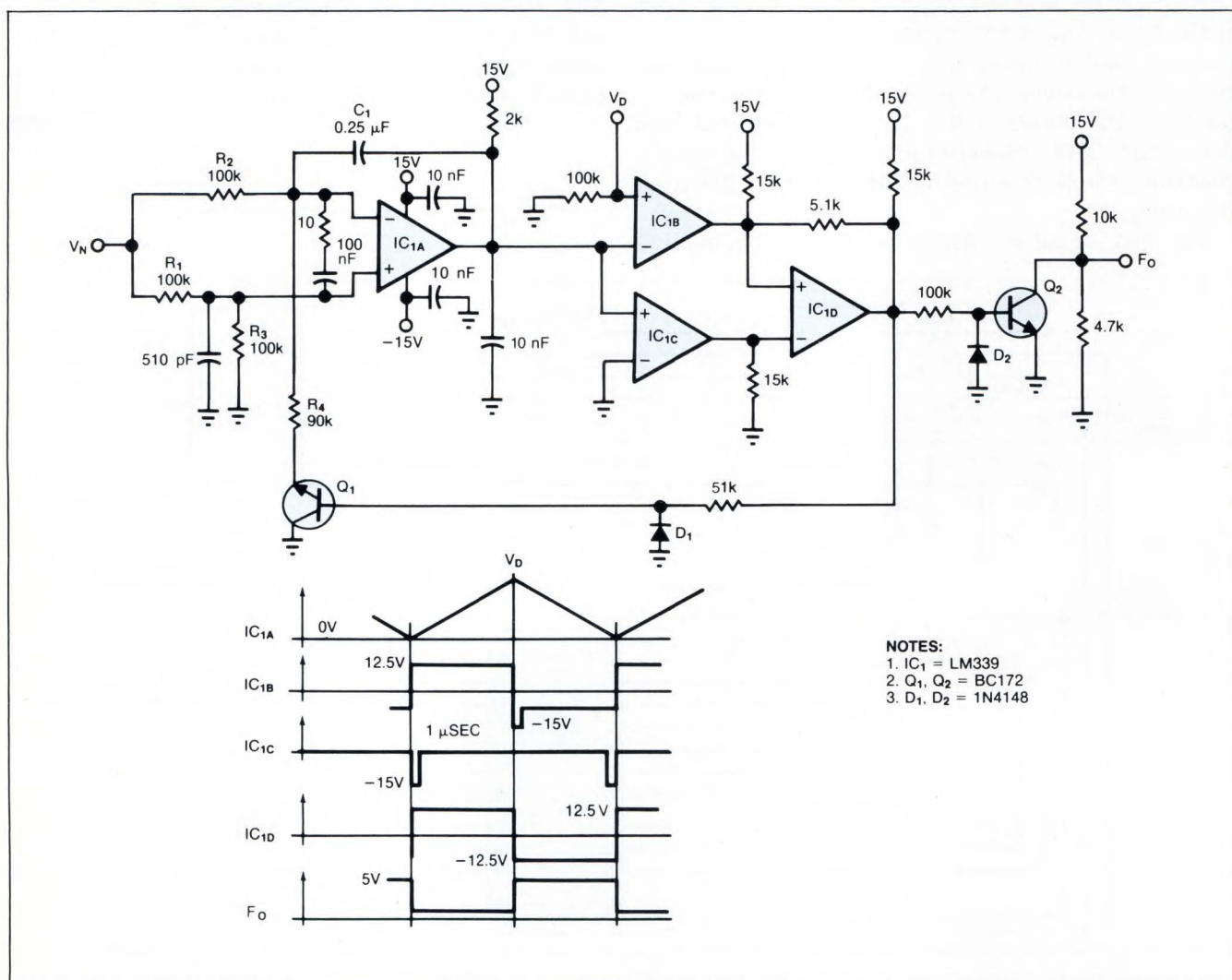


Fig 1—This voltage-ratio/frequency converter produces a TTL-compatible output pulse train that equals KV_N/V_D , where V_N and V_D are the inputs and $K=4R_2C_1$. Linearity error is less than 0.5%.

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Microphone controls voice-actuated switch

Jonathan Audy

Precision Monolithics Inc, Santa Clara, CA

The Fig 1 circuit is a speech-actuated switch that enables voice operation of a radio transceiver or similar device. Low-current consumption and 5V operation make the circuit suitable for battery-operated applications. (The original application involved hands-free control of a radio on a hang glider.)

The input stage (IC_{1A}), a bandpass filter with gain, responds to the speech components that are most reliable for actuating the output switch—those at 800 Hz. The main speech components fall in the 200- to 300-Hz range, but centering the bandpass at these frequencies would make the circuit too sensitive to wind noise, breathing, and “banging-door-type” noises. Fortunately, normal speech includes harmonic peaks every 100 Hz or so, to beyond 1 kHz. Centering the filter's bandpass at 800 Hz provides a good compromise between sensitivity and the suppression of false signals.

To ensure the detection of two harmonics, the filter must provide at least 40 dB of gain over a 400-Hz bandwidth. The component values shown for R_1 , R_2 , C_1 , and C_2 give the desired gain and 800-Hz center frequency. (Although not recommended, IC_{1A} can operate with-

out feedback in this application because the op amp's open-loop gain attenuation acts as a lowpass filter.)

The microphone produces 5- to 10-mV signals, which undergo just enough amplification to trip the comparator's (IC_{1B} 's) output high, turning on Q_1 . D_1 , R_6 , R_7 , and C_4 make up a peak detector that stores this high state long enough to delay the turnoff of Q_1 for about 0.7 sec—long enough to allow pauses between spoken words. The $R_3/R_4/R_5$ voltage divider sets the comparator's threshold and the filter's dc reference level; adjusting R_4 determines the circuit's sensitivity. C_3 removes noise that might otherwise appear at the high-impedance node that serves as a reference for the gain stage.

The circuit's input connects directly to a microphone jack. For radio applications, connect the circuit output directly to the nongrounded side of the radio's transmit switch (or you can add a 5-k Ω pullup resistor, which allows Q_1 to drive a TTL-logic input). For transceiver applications, you don't need a voice-on/off switch because the circuit's open-collector output allows the transmit switch to operate normally when you remove the voice headset.

EDN

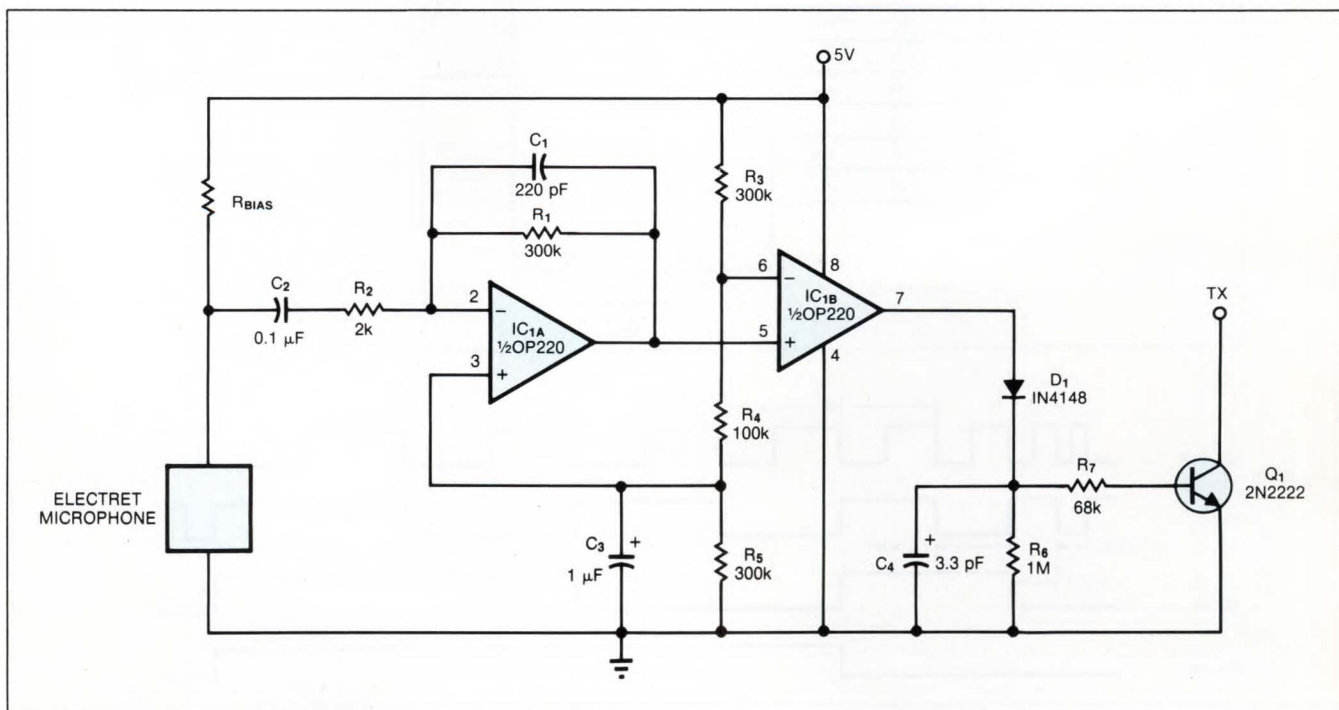


Fig 1—Speaking into this circuit's microphone drives the TX output low. The output remains low for about 0.7 sec following the last word spoken.

Counter controls its own clock frequency

Shantha Fernando

Arthur C Clarke Centre, Moratuwa, Sri Lanka

You can implement a finite-state machine by properly decoding the outputs of a binary counter. Driving the counter with a constant-frequency clock signal produces output states of equal duration. **Fig 1's** circuit, however, produces output states with different time intervals, as most applications require.

The analog multiplexer, IC₃, selects a timing resistor for the timer, IC₁. The timer's output clocks the counter

(IC₂) and the counter outputs drive the multiplexer's address inputs. The resistor values shown (R_{T0} through R_{T7}) produce a chirped clock and an ascending sequence of output-state durations, but you can generate arbitrary durations by choosing other resistor values. You can obtain longer durations by increasing the resistor values or by inserting a digital divider between the timer and the counter.

EDN

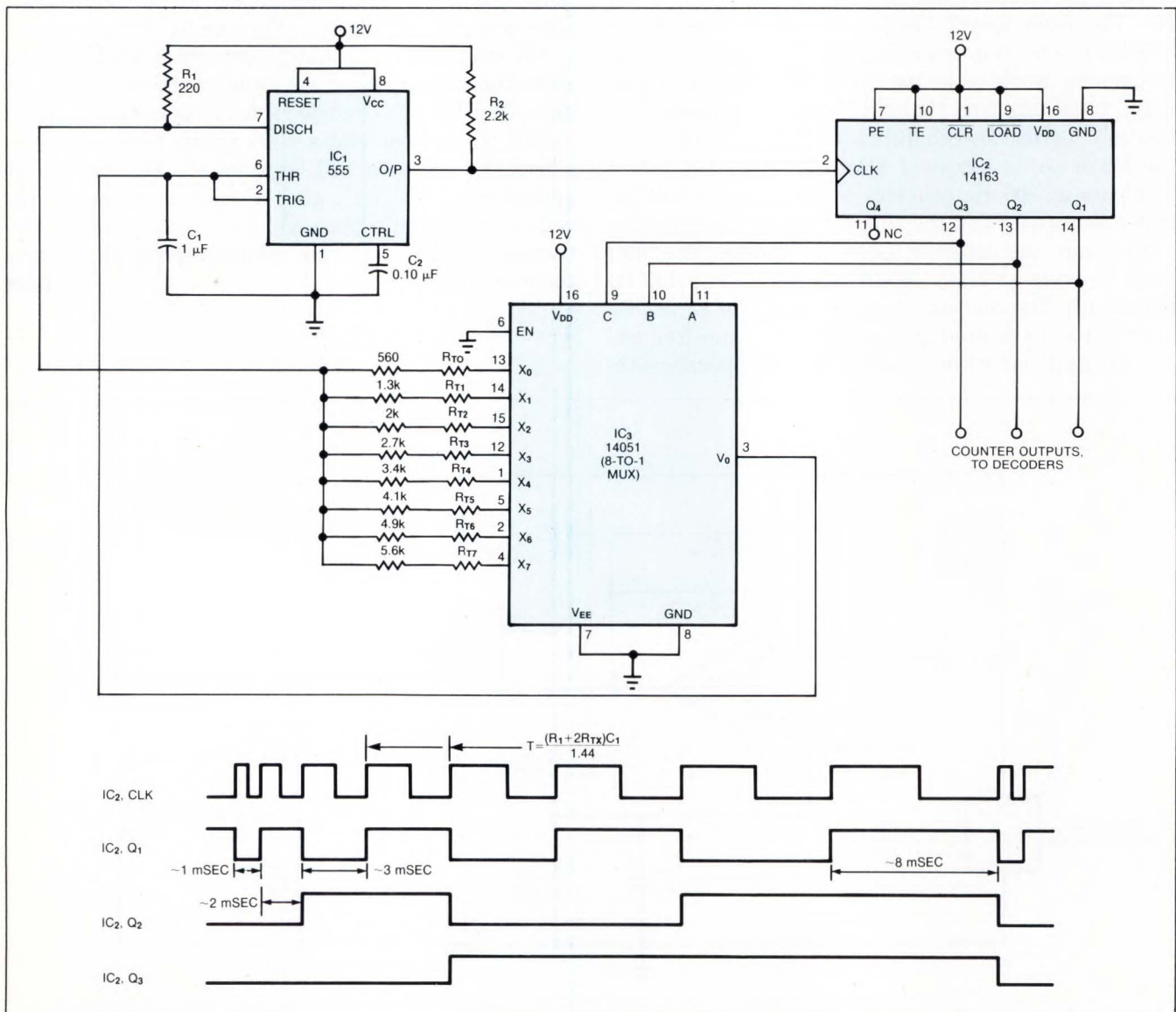


Fig 1—In this loop, the multiplexer selects a timing resistor for the timer, which clocks the counter, IC₂. The counter's resulting output-state durations depend on the values you select for resistors R_{T0} through R_{T7}.

Introducing OrCAD Verification and Simulation Tools

Logic Simulation

IS ONLY \$995

Easy to use menu driven commands speed and simplify design verification.

OrCAD / VST The Next Logical Step

Introducing OrCAD / VST, a full featured verification and simulation tool that is designed to place the performance of an expensive workstation on your PC.

OrCAD / VST is integrated with the popular OrCAD /SDT schematic capture package, with easy-to-use menus and powerful keyboard macros. Your valuable time is used to simulate designs without investing the time, money and resources to built prototypes.

With unsurpassed performance on a PC, you'll discover that nothing comes close to OrCAD's features and price. Benchmark the specifications for yourself. We guarantee satisfaction, or your money back!

- Event driven, 12-state functional simulator
- Exceeds 10,000 events/sec. on an 8 MHz AT without additional hardware
- Over 14,000 gate capacity

- Logic analyzer display format. Virtual screen displays 50 channels
- 10 breakpoints can be set as AND/OR condition of up to 16 signals
- User selectable minimum and maximum delays
- Input stimulus is easily defined with an integrated pop-up editor
- Includes component models of TTL, ECL, CMOS, Memory devices, and easy to use utility for creating custom models

- Of course, OrCAD's excellent support: technical staff to answer questions, 1 year of free product updates, and a trained sales and support network


Call or write today for our FREE Demo Disk and brochure.

OrCAD™
Systems Corporation

1049 S.W. Baseline St. Suite 500
Hillsboro, Oregon 97123
(503) 640-9488

Contact your local OrCAD Representative for further information

- | | | |
|------------------------------------------------------------------------|------------------------------------------------------------------------|----------------------------------------------------------------------|
| 1. WA, OR, MT, ID, AK
Seltech, Inc.
(206) 746-7970 | 6. NE, KS, IA, MO
Walker Engineering, Inc.
(913)888-0089 | 11. FL
High Tech Support
(813) 920-7564 |
| 2. N. CA, Reno NV
Elcor Associates Inc.
(408) 980-8868 | 7. TX, OK, AR, LA
Abcor, Inc.
(713)486-9251 | 12. DE, VA, MD, DC
MGM Visuals
(301) 738-1206 |
| 3. So. CA
Advanced Digital Group
(714) 897-0319 | 8. MI, E. WI, IL
Cad Design Systems, Inc.
(312) 882-0114 | 13. MS, AL, GA
Electro-Cadd
(404) 446-7523 |
| 4. Las Vegas, UT, AZ,
NM, CO
Tusar Corporation
(602) 998-3688 | 9. IN, OH, KY, WV, W. PA
Frank J. Campisano, Inc.
(513) 574-7111 | 14. E. PA, NJ, NY
Beta Lambda, Inc.
(201) 446-1100 |
| 5. ND, SD, MN, W. WI
Comstrand, Inc.
(612)788-9234 | 10. TN, NC, SC
Tingen Technical Sales
(919) 878-4440 | 15. CT, RI, MA, VT, NH, ME
DGA Associates, Inc.
(617) 935-3001 |

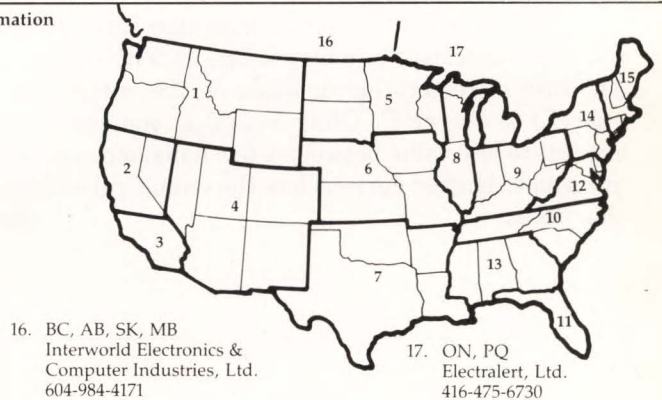

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Baseline restorer is voltage-programmable

Peter Henry

Precision Monolithics Inc, Santa Clara, CA

The Fig 1 circuit is a nonlinear, highpass filter that acts as an active baseline restorer (Fig 2). Baseline restoration improves the signal-to-noise ratio for pulse or ac measurements by counteracting the dc errors caused by amplifier drift and electromagnetic pickup. The circuit is particularly useful for signals derived from a high-impedance source such as the human body.

Unlike standard frequency-domain filters, this one acts on the slew rate rather than the frequency of the input signal. At V_{OUT} , the circuit restores the base level of input-signal pulses to an arbitrary level set by V_{REF} . You set the filter's slew-rate cutoff by adjusting $V_{PROGRAM}$, which in turn sets the currents I_1 and I_2 . (In applications such as analog adaptive filtering, you can set $V_{PROGRAM}$ using a voltage-output D/A converter, or you can remove $R_{PROGRAM}$ and set the currents using a current-output D/A converter.)

To understand the circuit operation, first note the action of the transistor current mirrors: Collector current in Q_2 (I_1) mirrors the collector current in Q_1 , and the transistors Q_5 and Q_6 mirror this current again. Transistors Q_3 and Q_4 each mirror the I_1 current as well, producing the current $I_2=2I_1$. This $2\times$ relationship assures symmetric operation, in which the restoration rates are equal for positive and negative excursions from the baseline.

Assume the capacitor C has charged to the input signal's baseline voltage. If the baseline level of V_{OUT} attempts to rise, the IC_2 output swings low, decreasing the current through D_1 . This action causes a flow of current from capacitor C and thus restores equilibrium by lowering the voltage on C . Conversely, a tendency for the baseline to fall causes charge to flow onto the capacitor.

The IC_2 op amp must have a high slew rate to ensure that the restoration circuitry keeps up with the pulses. The rate of restoration depends on the current available (I_1) to charge C . Using $V_{PROGRAM}$, you can set this current to any value between a few nanoamps and a few milliamps. Higher current lets the circuit reject higher slew rates.

EDN

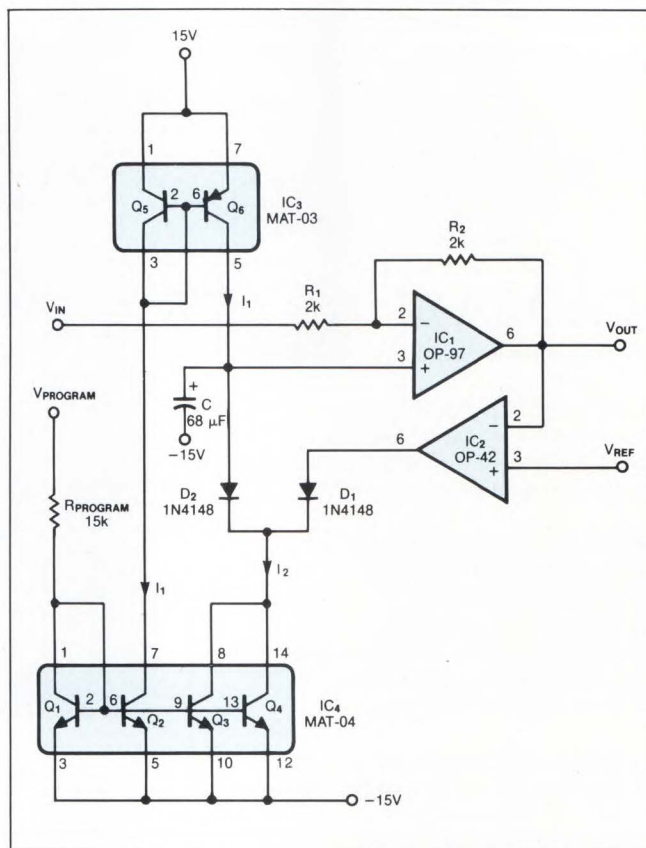


Fig 1—This circuit forces the bases of pulses in V_{IN} to the arbitrary level V_{REF} , and it rejects pulses on the basis of slew rate according to the voltage $V_{PROGRAM}$.


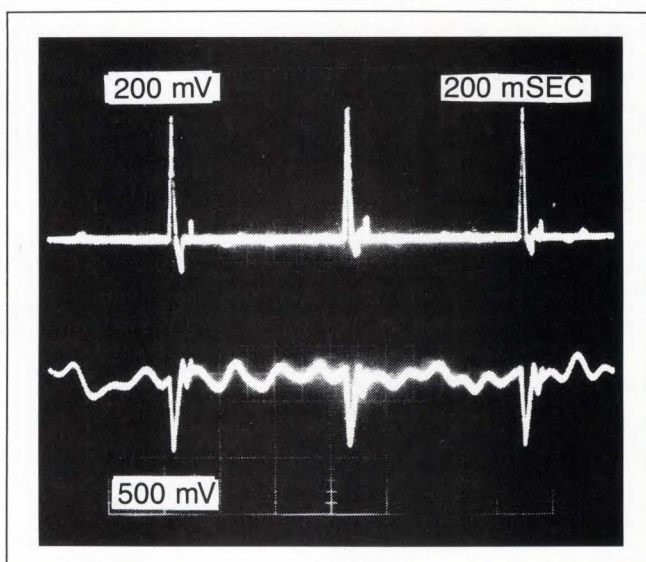


Fig 2—These waveforms show that the Fig 1 circuit's output (upper trace) inverts V_{IN} (lower trace) while filtering and restoring the signal's baseline voltage level.

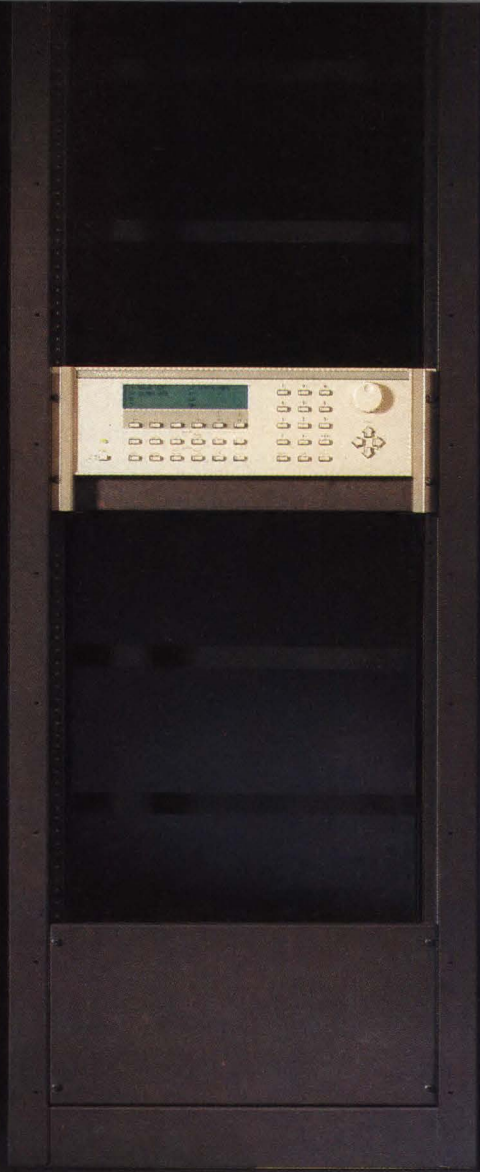

Tests great. Less filling.

Available now.

A high-performance modular instrument system that packs up to eight instruments into a single 7" chassis!

Modules include a 20 MHz Arbitrary/Waveform Generator, a 100 MHz Pulse Generator, a high-accuracy 6½ digit DMM and a 160 MHz Frequency Time Interval Counter.

All backed by one company—

Wavetek, the experts in source technology.

And all for less money than you'd pay for the individual instruments.

Buy just the instruments you need today, and add more later. An internal analog summing bus lets you combine outputs from multiple Arbitrary Generators and Pulse Generators to create complex sources.

With its functional front

panel for debugging, GPIB and optional MATE-CIIL interfaces, and built-in testing, calibration and reference, Model 680 is ideal for ATE applications.

And think of the ways you can use the extra rack space!

Call (619) 279-2200 today for detailed literature, application assistance, or to arrange a demo of the Model 680.

CIRCLE NO 157 FOR LITERATURE

© Copyright 1988 Wavetek Corporation

CIRCLE NO 158 FOR DEMO

WAVETEK

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Electronic thermometer has 10-mV/°F output

Bill Donofrio and Dennis R Bernard
Moore Research Ctr, Grand Island, NY

Using type-K thermocouple wire, you can build an inexpensive electronic thermometer that generates 10 mV/°F (**Fig 1**). Because type-K thermocouples are reasonably linear for the range of 0 to 660°C, you can obtain a moderately accurate temperature measurement for this range by adding a scaling voltage to the cold-junction reference voltage.

The 9V battery powers a bridge circuit in which the temperature sensor, IC₂, and the 2.5V reference, IC₃, provide a signal and reference voltage, respectively. You should place the cold-junction thermocouple close to the temperature sensor. Note that the chromel wires form secondary junctions where they attach to the circuit (nodes A and B). To avoid introducing dc errors, you should maintain these junctions at the same temperature by placing them close together. Bypass capaci-

tors C_6 and C_7 guard against errors due to RF pickup.

Potentiometer R_5 produces a temperature-dependent scaling voltage, and the chopper-stabilized op amp, IC₁, amplifies (with a gain of 1001) the sum of the scaling and thermocouple voltages. As a result, the output V_T equals the sum of the thermocouple cold-junction voltage plus the scaling voltage (0.744 mV), divided by 0.0226. Potentiometer R_6 determines the 0.0226 figure.

To calibrate the circuit, first adjust R_4 for 2.554V across IC_3 . Then adjust R_3 so the voltage across IC_2 equals 10 mV times the ambient temperature (in °K). Place the hot-junction thermocouple in a well-stirred mixture of crushed ice and water, and adjust R_5 so that the op-amp output (across R_6) equals 0.744V. To complete the calibration, adjust V_T to 0.32V using R_6 . **EDN**

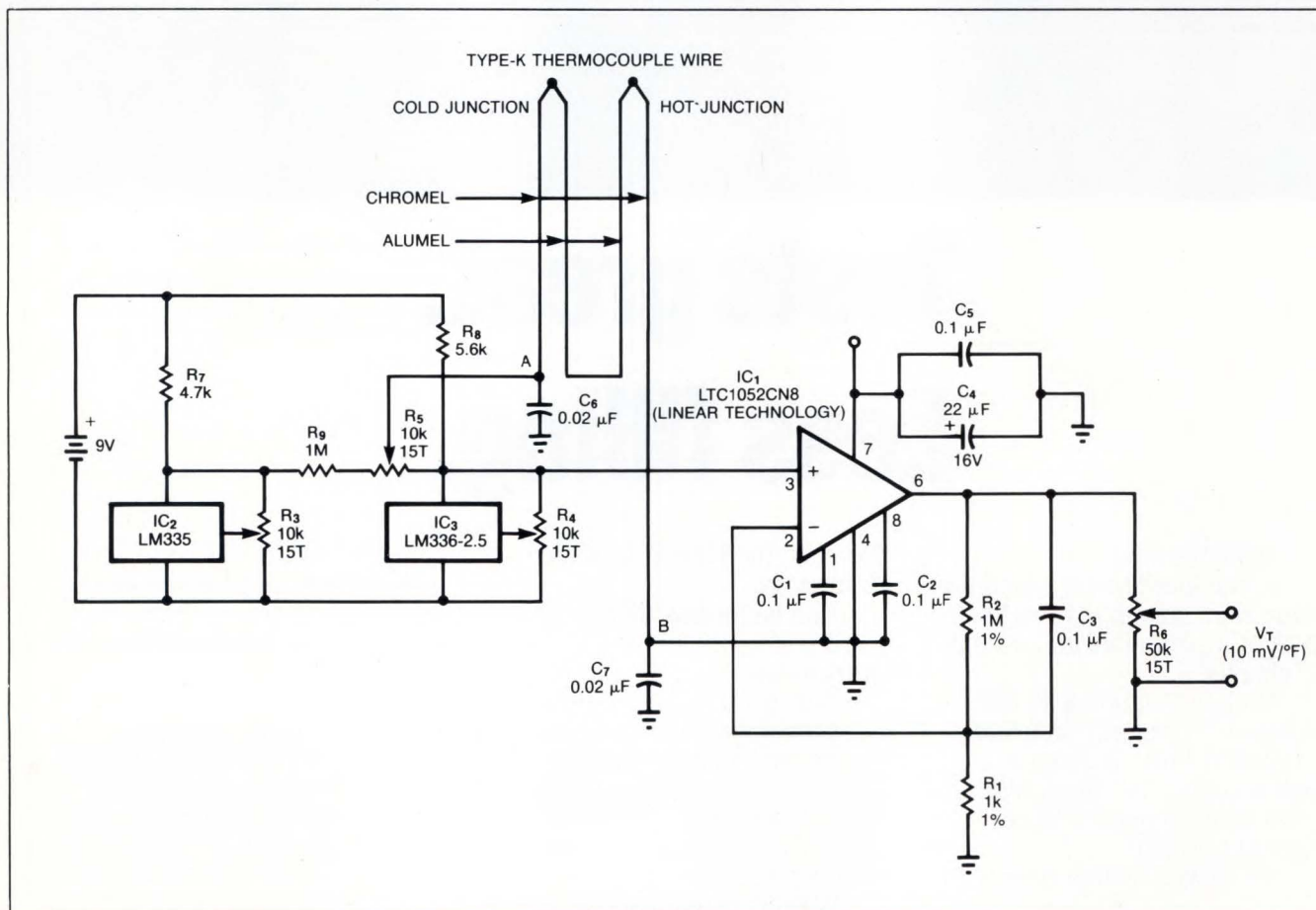


Fig 1—This circuit adds a linearizing voltage to the thermocouple voltage and produces an output V_T of 10 mV/°F.

Target VISHAY For Precision Resistive Components

VISHAY

PRECISION BULK METAL® FOIL RESISTIVE COMPONENTS CIRCLE NO 159

Temperature Coefficient of Resistance (TCR)

To 0.1ppm/°C

Temperature Coefficient of

Resistance, Tracking

To 0.2ppm/°C

Absolute Initial Resistance

To 0.001% (10ppm)

Resistance Ratio Stability

To 0.001% (10ppm)

Stability – Load Life To 0.0025% (25ppm)

Shelf Life To 0.0005% (5ppm)

Thermal Electro Motive Force (Th. EMF)

To 0.03 μ V/°C

Resistors, Trimmers, Networks, Chips, Specials.

VISHAY

...to be precise®

VISHAY

THIN FILM PRODUCTS CIRCLE NO 160

SIPS, DIPS, Chips & Specials.

ANGSTROHM

METAL FILM
RESISTIVE
COMPONENTS

Established Reliability,

Hermetically Sealed Metal Film

Resistors Styles RNR RNN,

Characteristics C&E.

Resistors, Networks, Specials. CIRCLE NO 161



ANGSTROHM

POWER RHEOSTATS CIRCLE NO 162

ELLIOTT/JORDAN

PRECISION WIREWOUND COMPONENTS

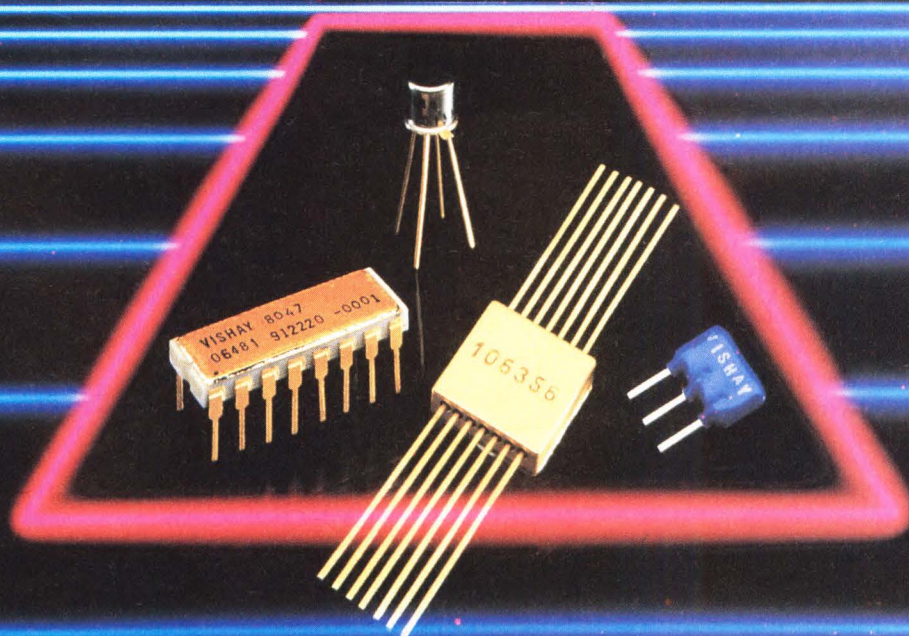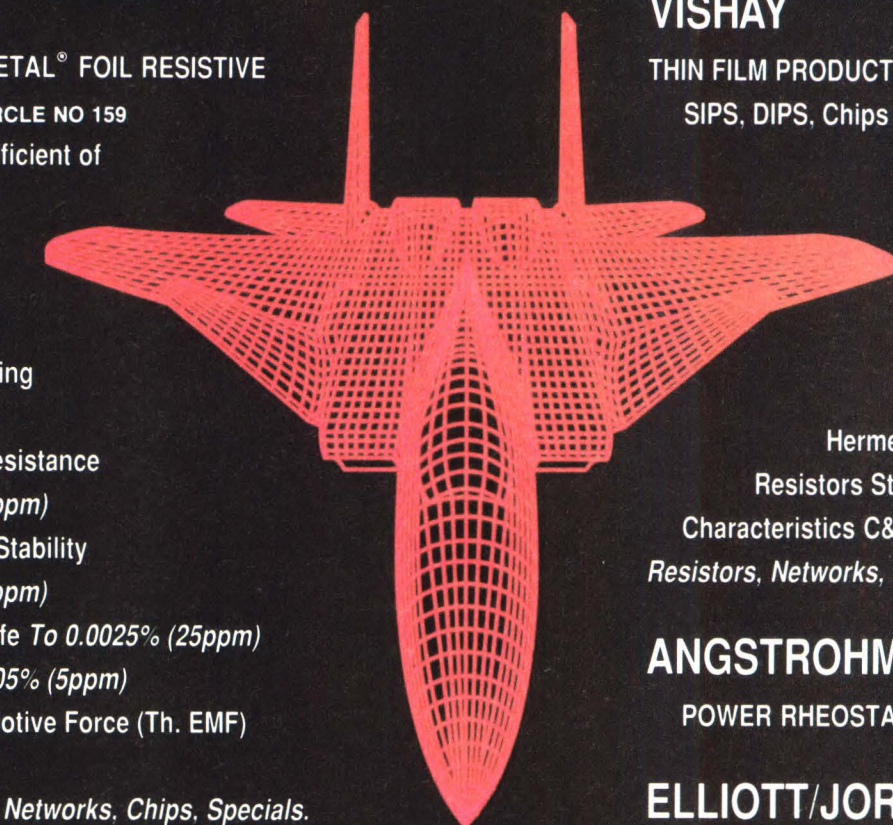*Resistors, Networks, Temperature Sensing
and Compensating.* CIRCLE NO 163



VISHAY Resistive Systems Group

Of VISHAY Intertechnology, Inc.

63 Lincoln Hwy., Malvern PA 16355 (215) 644-1300 / FAX (215) 640-9081

Unitrode announces a new generation of Ultra-fast Rectifiers, with voltage rating to 1000V and recovery times of less than 30 nanoseconds. It's called the HV^{Plus} series.

High voltage, high frequency power supply performance will never be the same again.

HV Plus advantages include unique high voltage, very fast recovery characteristics, very low leakage at high temperature, 8pf capacitance, and an array of other features that just weren't available until now.

HV Plus allows you to do things you've never been able to do before. You'll find improved performance in difficult applications: for example, using an HV Plus as a clamp diode to protect high voltage power mosfets, or using them as output rectifiers for high frequency converters.

HV Plus is available in both high-rel and industrial versions, in two axial leaded body sizes, with 2.0 amp and 4.0 amp ratings. Prices are reasonable and performance is unmatched.

Just look at these sample specs:

Part Number	Voltage	t _{rr}	C _J	IR @ 150°C	Output Current
1N6622	600V	30nS	8pf	200μA	2.0A
1N6623	800V	50nS	8pf	200μA	1.5A
1N6625	1000V	50nS	8pf	200μA	1.5A
1N6628	600V	30nS	30pf	500μA	4.0A
1N6629	800V	50nS	30pf	500μA	3.0A
1N6631	1000V	50nS	30pf	500μA	3.0A

HV Plus data sheets are available now. Call or write today for your copy. Your competition will.

Highest voltage + fastest recovery = HV^{Plus}



**SEMICONDUCTOR
PRODUCTS**

UNITRODE

580 Pleasant Street
Watertown, MA 02172
(617) 926-0404

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Driver circuit boosts 3-state outputs

Einar Abell

ADA Instruments, Burlington, VT

The power booster in **Fig 1** allows an ordinary 3-state gate to drive 50Ω loads to several volts peak-to-peak. Rise and fall times are only a few nanoseconds for a properly terminated coaxial cable. Employing two switched current sources of opposite polarity, the booster converts the gate's unipolar output to a bipolar one. Further, the booster output shuts off when the gate goes to a high-impedance state; this feature is particularly useful when the gate must drive inductive and capacitive loads.

When the 3-state gate output is enabled and in a high state, transistor Q_1 turns on the upper current source (D_1 , D_2 , R_6 , and Q_3); when the 3-state gate output is enabled and in a low state, Q_2 turns on the lower current source (D_3 , D_4 , R_7 , and Q_4). When the 3-state gate is disabled (in a high-impedance state) both sources are off and the booster output discharges to

zero through R_8 .

Fig 1's circuit is simple because its transistors are biased so that they don't saturate. If the transistors were allowed to saturate, you'd need to add components to the circuit to compensate for the unequal turn-on and turn-off times that would result.

To prevent Q_3 and Q_4 from saturating, you must set R_8 to limit the output within 2V of either supply rail. The output current I_0 equals $0.7 R$, where R is the value of R_6 and R_7 . To obtain greater output current, you can replace the output transistors with Darlington pairs. If necessary, you can improve I_0 's temperature stability by thermally coupling D_2 to Q_3 and D_3 to Q_4 and by replacing D_1 and D_4 with low-voltage zener diodes. R_4 and R_5 bias the input transistors to the midpoint of the 3-state gate output and set the drive current to Q_3 and Q_4 .

EDN


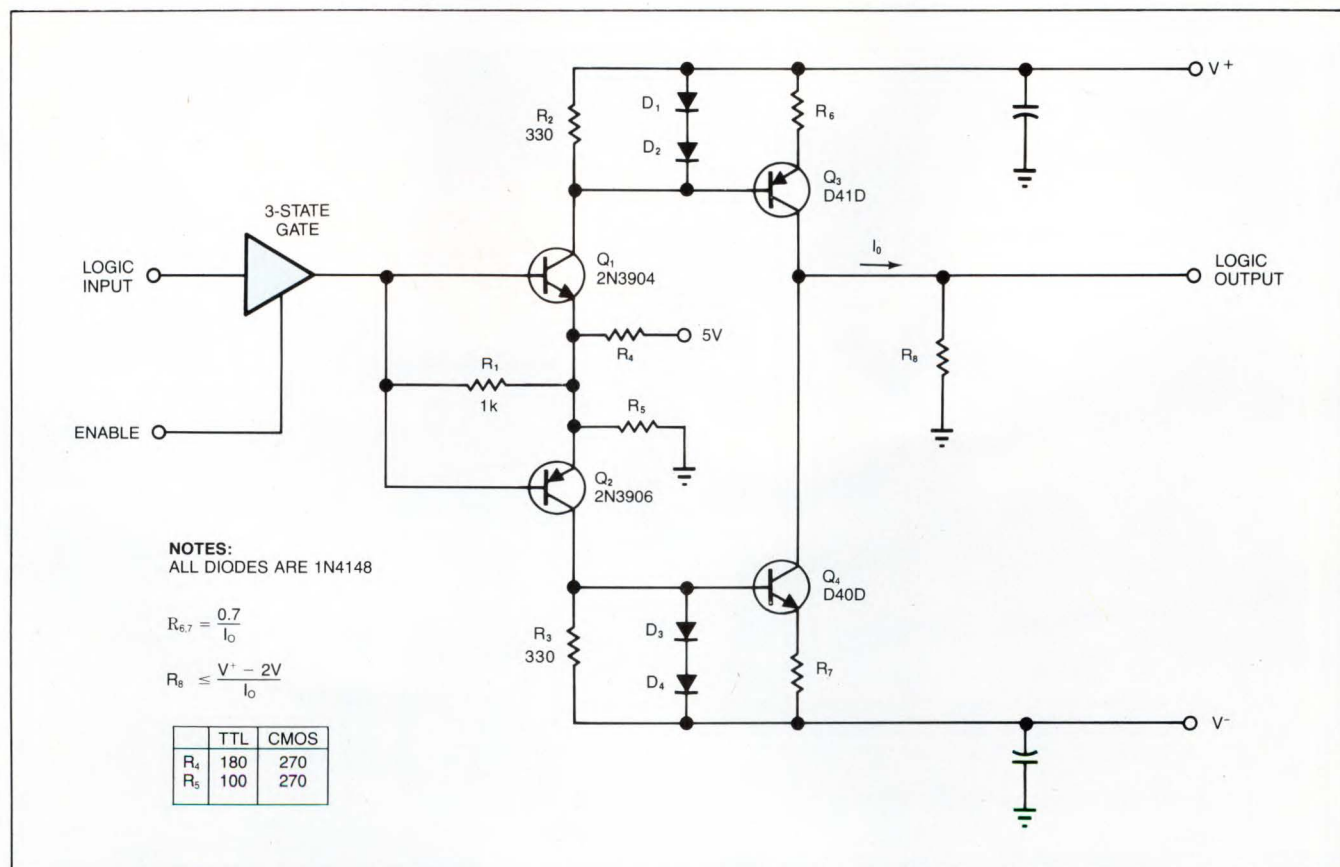


Fig 1—With this discrete driver circuit, any 3-state gate can drive 50Ω loads with ease. Output resistance equals the value of R_8 when the gate is in a high-impedance state.

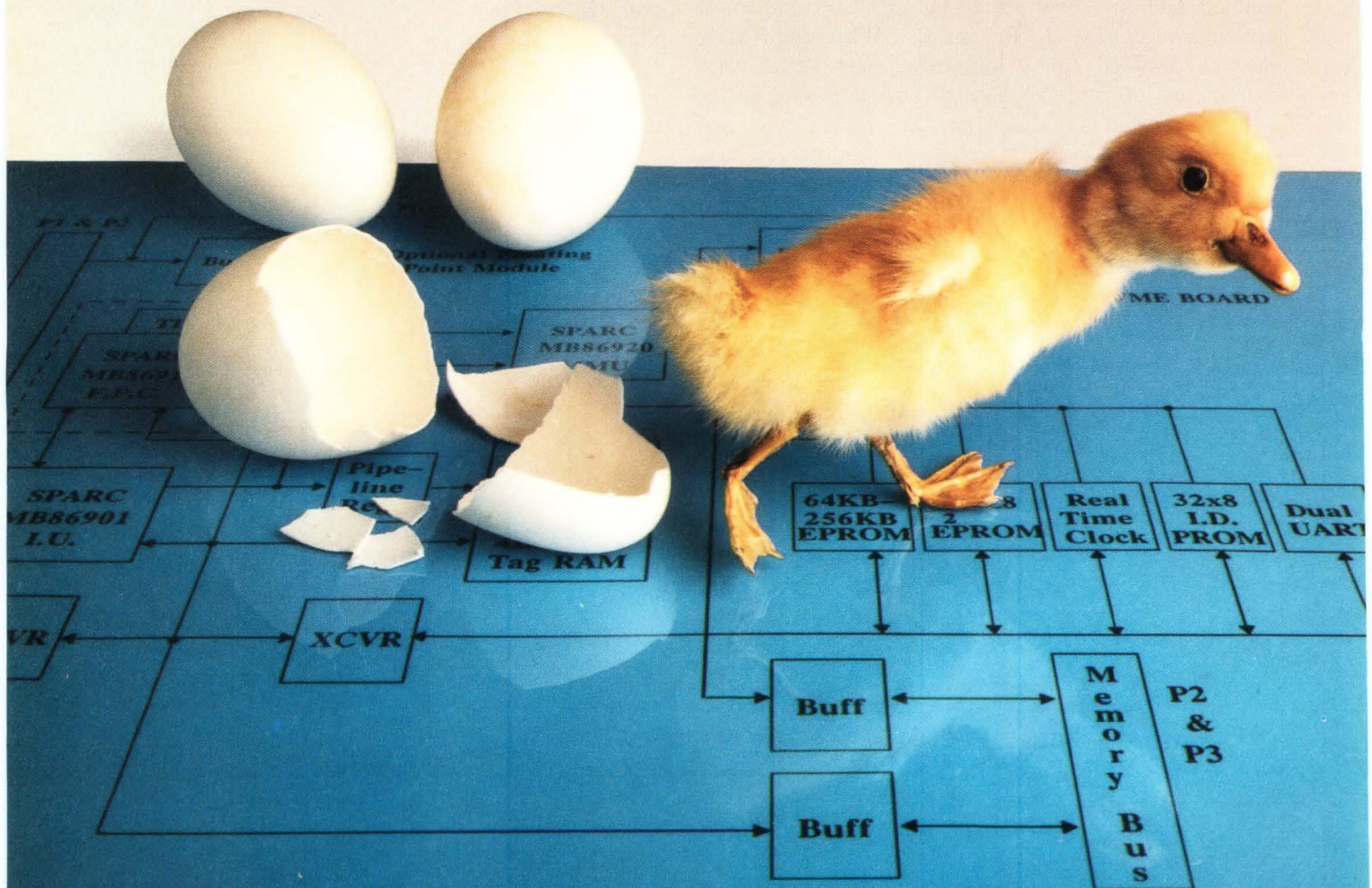Fujitsu's new RISC chip-computer development.



set speeds up your

Break out!

Get your computer to market before your competitors.

When you need to be first, nothing helps more than getting a head start. And nothing will get you started faster than these new SPARC™ devices from Fujitsu.

Not just a speedy microprocessor—but a complete high performance RISC chip-set. One that accelerates the development cycle of powerful minis, PCs and workstations. And eliminates many components plus the time it takes to integrate them. Yet, offers a high degree of design flexibility.

A complete chip-set to speed up your product development.

Fujitsu's new S-25™ chip-set includes a 25 MHz, 32-bit Integer Unit (IU) for high-speed processing. A Memory Management Unit (MMU) ideal for the UNIX® environment and tailored for SPARC processors. And a Floating Point Controller (FPC) that allows interface to the IU and supports IEEE single and double precision arithmetic.

In addition, these devices are fully supported by a

wide range of hardware and software development tools.

A proven architecture from a proven supplier.

SPARC is multi-sourced and proven over time. We first implemented it for the Sun 4/200 workstation over two years ago and have been producing it in volume ever since. Using the same Fujitsu manufacturing know-how that has made us a world leader in gate array and memory production.

The S-25 chip-set is a third-generation product designed at our Advanced Products Division in Silicon Valley. Where our engineering teams continue to advance the state-of-the-RISC-art—supported by the resources of a multi-billion dollar worldwide organization.



MB86901 (IU)

- 25 MHz
- 40 ns / cycle
- 15 MIPS

MB86911 (FPC)

- Single & double precision floating point arith.
- ANSI / IEEE 754-1985 std.
- 64-bit int. data paths

MB86920 (MMU)

- 64-entry TLB
- Fully associative
- 64-Gbyte physical address

Break outs—without breakdowns!

Enjoy the competitive advantage of getting to market first! Rely on an architecture and supplier who can get you there. On time. On spec. On budget.

When you want to be first, we're the first ones to call.
(800) 523-0034

FUJITSU

FUJITSU MICROELECTRONICS, INC.

Advanced Products Division

50 Rio Robles, Bldg. 3, San Jose, CA 95134-1804

CIRCLE NO 165

SPARC is a trademark of Sun Microsystems, Inc.
S-25 is a trademark of Fujitsu Microelectronics, Inc.
UNIX is a registered trademark of AT&T.
© Copyright 1988 Fujitsu Microelectronics, Inc.

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Simple calculator acts as low-speed counter

J N Lygouras

University of Thrace, Xanthi, Greece

By adding a handful of inexpensive components, you can transform a 4-function calculator into a low-speed counter or tachometer. Note, however, that the calculator must have a constant-calculation feature for this scheme to work.

Fig 1 illustrates the scheme. In Fig 1a, a series of 555 timers produces a string of pulses (Fig 1b), which key the calculator. When you press the reset switch, S_1 , its negative-going edge triggers the first 555 timer, IC_1 , making its output go high for about 23 msec. This high level closes electronic switch S_2 . This closure is equivalent to pressing the calculator's zero digit.

In a similar fashion, the circuit sequentially activates the plus and one keys. The negative-going output of the third 555 timer, IC_3 , triggers the fourth 555 timer, IC_4 . Triggering IC_4 enables electronic switch S_5 , which routes the input pulses to the equals key for the duration of IC_4 's time period. This sequence is equivalent to your pressing the calculator's keys as shown in Fig 2, where N is the number of counted pulses that

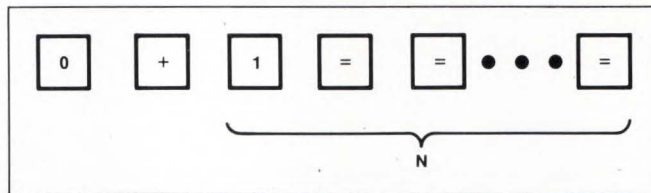


Fig 2—The circuit shown in Fig 1 mimics the key strokes shown here.

correspond to the final display on the calculator at the end of IC_4 's time period, T_C .

You can add the optional circuit to convert the counter to a tachometer. The Schmitt trigger shapes pulses from an engine's contact points. You must divide the points' signal by four because the calculator's maximum counting frequency is 20 Hz. For example, a 4-stroke, 4-cylinder engine running at 1000 rpm would generate 33.3 sparks/sec. Of course, if you divide the incoming pulse stream by four, you must increase IC_4 's counting period by a factor of four to compensate. **EDN**

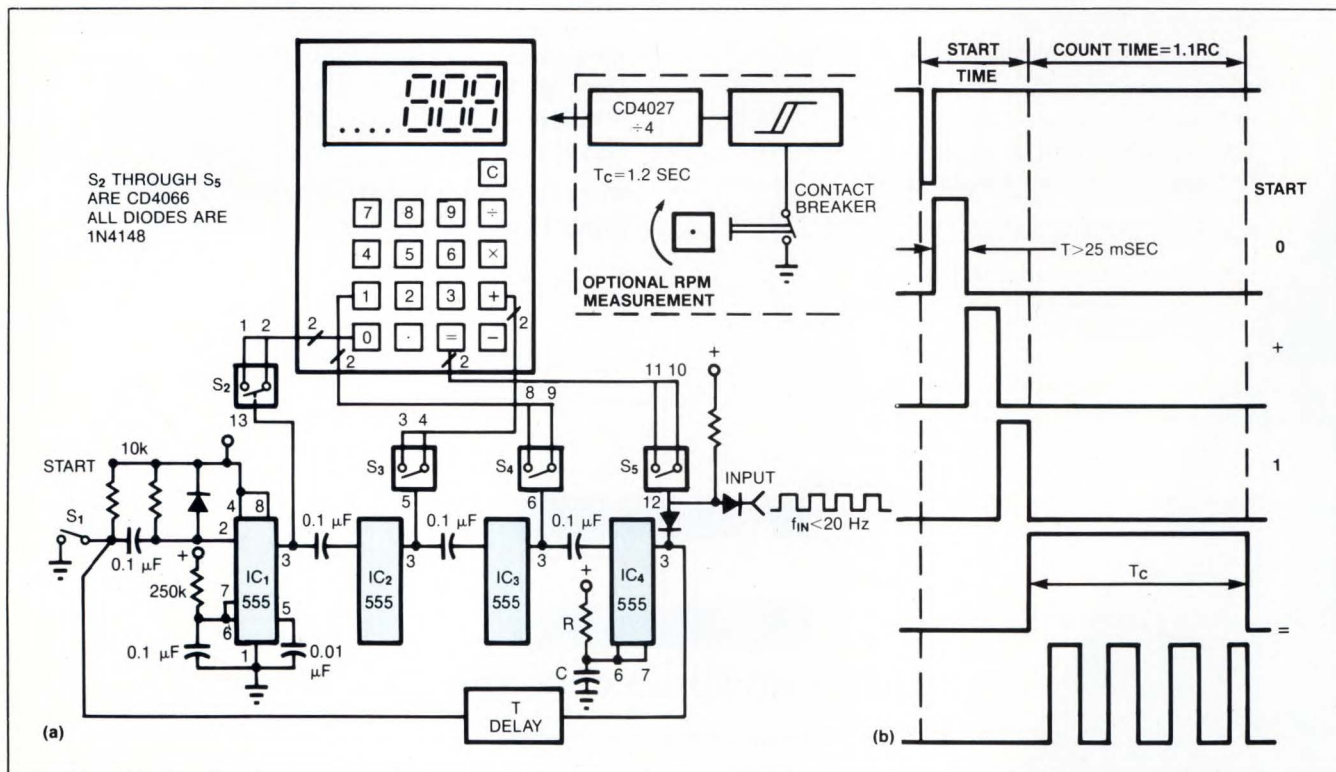


Fig 1—Electronic switches, triggered by 555 timers and an incoming pulse train, turn a simple 4-function, constant-calculation calculator into a low-speed counter or, optionally, a tachometer.

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Tachometer measures low frequencies

Ricardo Jimenez-G

Mexicali Technological Institute, Mexicali, Baja California, Mexico

The Fig 1 tachometer lets you measure heartbeats, respiratory rates, and other low-frequency events that recur at intervals of 0.33 to 40.96 sec. The circuit senses the period of f_{IN} , computes the equivalent pulses per minute, and updates the LCD accordingly. (Although the decimal readout equals $60f_{IN}$, the circuit doesn't actually produce a frequency of $60f_{IN}$.) The computation involves counting and comparison techniques and takes 0.33 sec.

To understand the circuit's operation, suppose a reset pulse arrives at pin 15 of IC₁, setting Q₁ and Q₂ low. Then, the first f_{IN} pulse drives Q₁ high, which opens the IC_{3A} gate and allows 100-Hz pulses to drive the counter IC₄. The next f_{IN} pulse drives Q₁ low and Q₂ high, which simultaneously freezes IC₄ at a count of N by turning off the 100-Hz pulses. The same f_{IN} pulse opens the gate IC_{8A}, which allows 18-kHz pulses to drive the IC₇ counter.

Each time IC₇ reaches a count equal to that of IC₄, the IC₅-IC₆ comparator produces a pulse that increments the display counter IC₁₁ and resets IC₇ via IC_{3D}. Thus, IC₇ counts at a rate of 18 kHz without interruption and resets to zero after every N counts. (N is proportional to the period of f_{IN} .) This process terminates at 6000 counts, when the BCD counters IC₉ (count of 100) and IC₁₀ (count of 60) produce a pulse at pin 11 of IC_{8D} that resets IC₁, IC₄, IC₉, and IC₁₀. The reset at pin 15 of IC₁ drives Q₀ (pin 3) high, which in turn resets the display counter and updates the display.

An f_{IN} of 1 Hz, for instance, sets IC₄ to a binary count of N=100. Consequently, IC₇ counts 60 times from 0 to 100 during the 6000-count interval, producing a readout of 60. Similarly, $f_{IN}=1.25$ Hz produces N=80 and sets the readout to $6000 \div 80 = 75$ pulses per minute. **EDN**

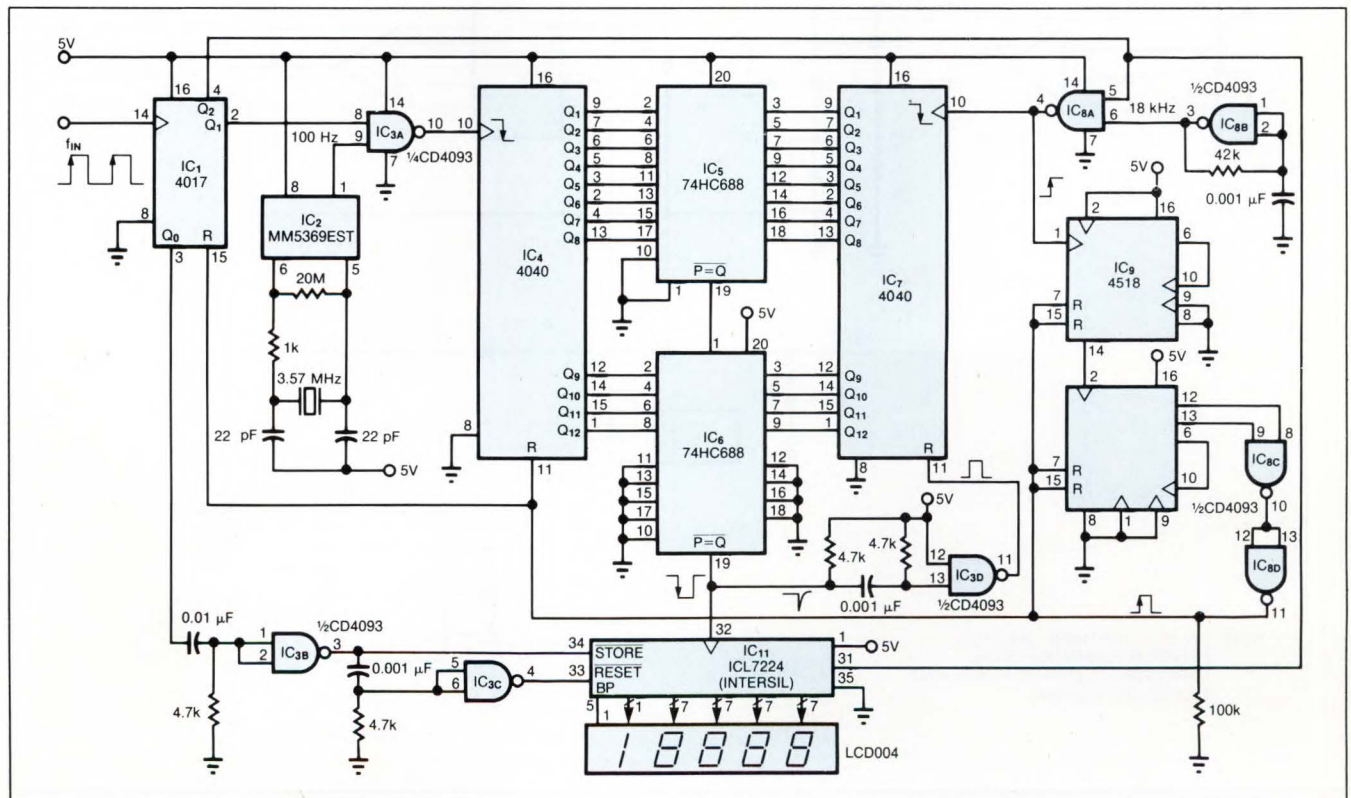


Fig 1—This tachometer circuit generates a readout, in pulses per minute, by measuring the period T of f_{IN} and solving the equation $f = 60 \div T$.

DESIGN IDEAS

EDITED BY KEN MARRIN

Power-reset circuit provides four functions

James Colotti
Eaton Corp, Farmingdale, NY

The power-reset circuit shown in **Fig 1** provides a reset signal under four conditions: during initial power-up; when the supply voltage falls below 4.5V; after a supply-voltage glitch; and after a manual reset. When you first apply power to the circuit, the output ($\overline{\text{PWRST}}$) goes low. After 500 msec, the output goes high. If the supply voltage drops below 4.5V, the output goes low and stays low until 500 msec after the supply voltage returns to 5V.

The open-collector outputs of comparators $\text{IC}_{1\text{A}}$ and $\text{IC}_{1\text{B}}$ are connected in an OR configuration. When either output is low (this condition is caused by a power-on reset or a low-power condition), that low output holds

$\text{IC}_{1\text{C}}$'s output low through D_2 . $\text{IC}_{1\text{C}}$'s low output, in turn, drives both $\text{IC}_{1\text{D}}$'s output and $\overline{\text{PWRST}}$ low.

When the outputs of both $\text{IC}_{1\text{A}}$ and $\text{IC}_{1\text{B}}$ go high—which indicates that the supply voltage has returned to 5V and that no power-on reset is in progress— $\text{IC}_{3\text{A}}$'s Q output goes high for 500 msec ($\text{IC}_{3\text{A}}$ is configured as a one-shot multivibrator). After 500 msec, the Q output goes low, $\text{IC}_{1\text{C}}$'s output goes high, and $\overline{\text{PWRST}}$ goes high.

S_1 gives you a manual-reset option. Holding S_1 closed maintains $\overline{\text{PWRST}}$ in a low state. When you release the switch, you trigger the monostable multivibrator; 500 msec later, $\overline{\text{PWRST}}$ goes high.

EDN



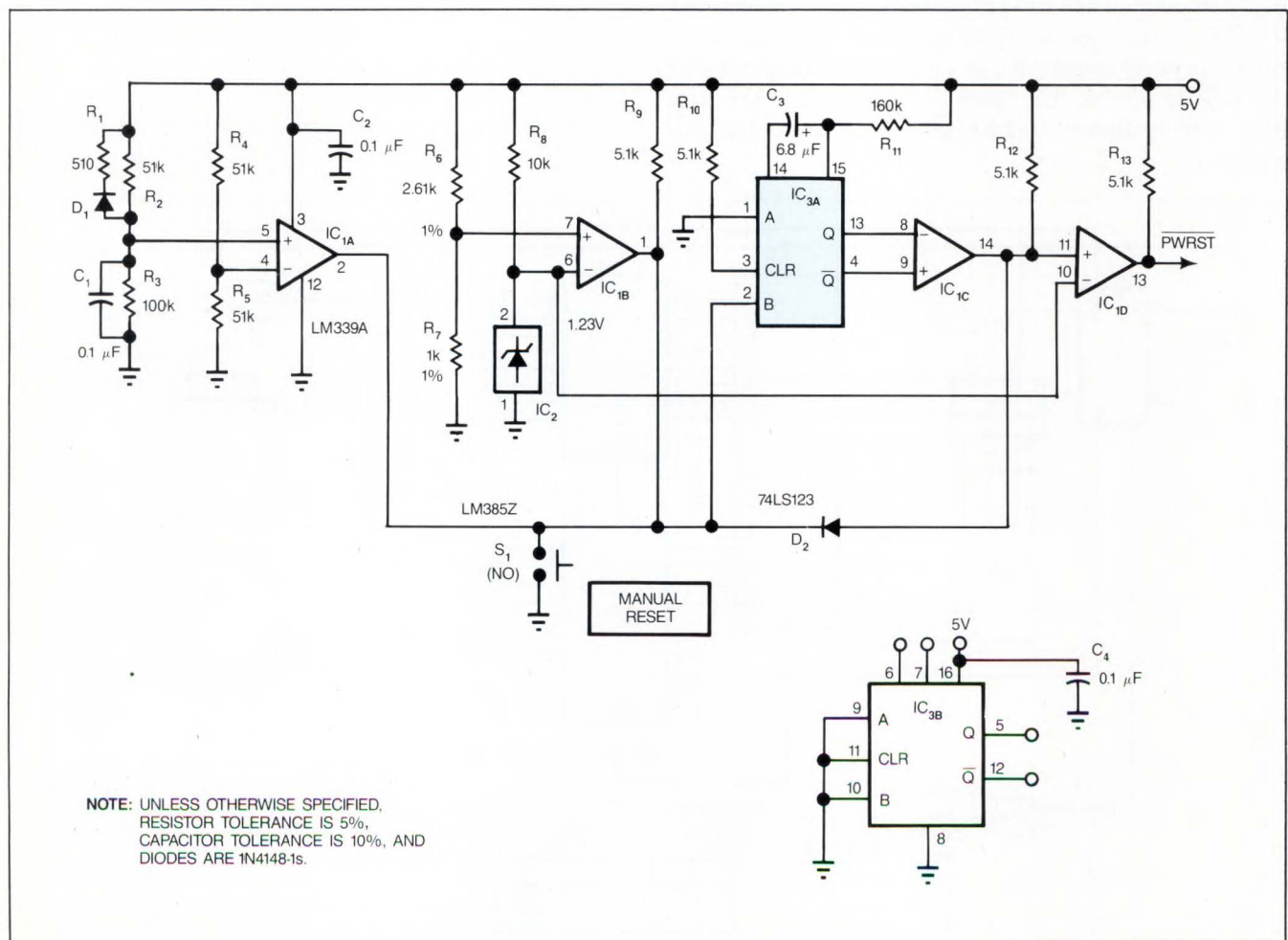


Fig 1—This power-reset circuit uses a one-shot multivibrator ($\text{IC}_{3\text{A}}$) to provide a 500-msec time delay. Once the circuit generates a power-reset signal, it will hold that signal for at least 500 msec.

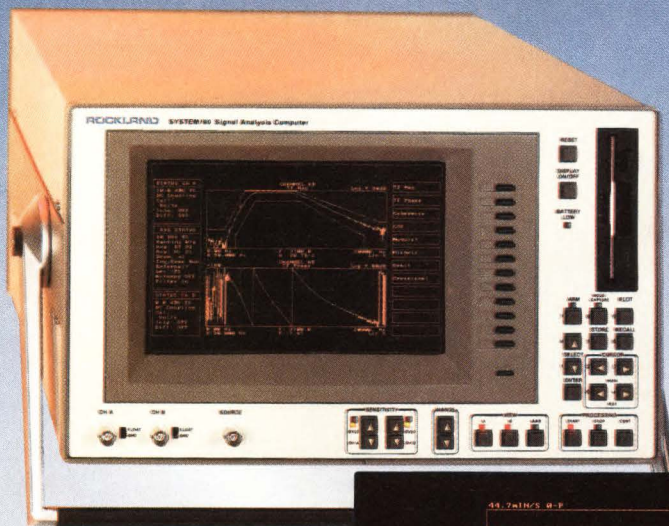

It's a 2-channel
FFT Analyzer.

It's a DOS
computer.

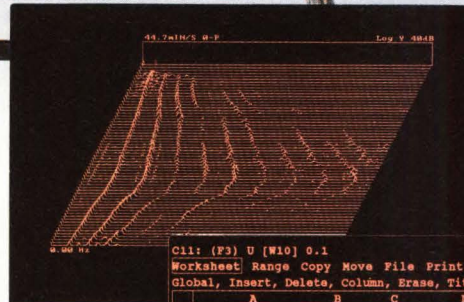


Our SYSTEM/90 Signal Analysis Workstation is both.

It's easy to take our new SYSTEM/90 Signal Analysis Workstation **anywhere** to do almost **everything**...spectrum analysis, waveform recording, even computing. SYSTEM/90 represents a new concept in instruments for the '90s...

- the **only** FFT analyzer with an imbedded IBM-compatible DOS computer...AT class in Model 9040, XT class in Model 9020 (keyboard supplied with all units)
- the **only** 2-channel FFT with optional built-in battery
- the **only** FFT offering **three** built-in media for waveform recording and data storage... 1.44 Mbyte floppy, optional non-volatile RAM to 4 Mbytes and optional removable 40 Mbyte hard disk with SCSI port to the outside world
- the **only** FFT analyzer with analog integration and input filter bypass for use as a digital oscilloscope
- high real time rate, 100 kHz range, 1/3-octave, zoom, spectral maps, correlation, histograms...and more
- easy-to-use with GO/NO GO screening profiles, unattended data logging and hands-off control
- **all** options field installable, including hard disk...no need to send the unit to the factory for upgrading

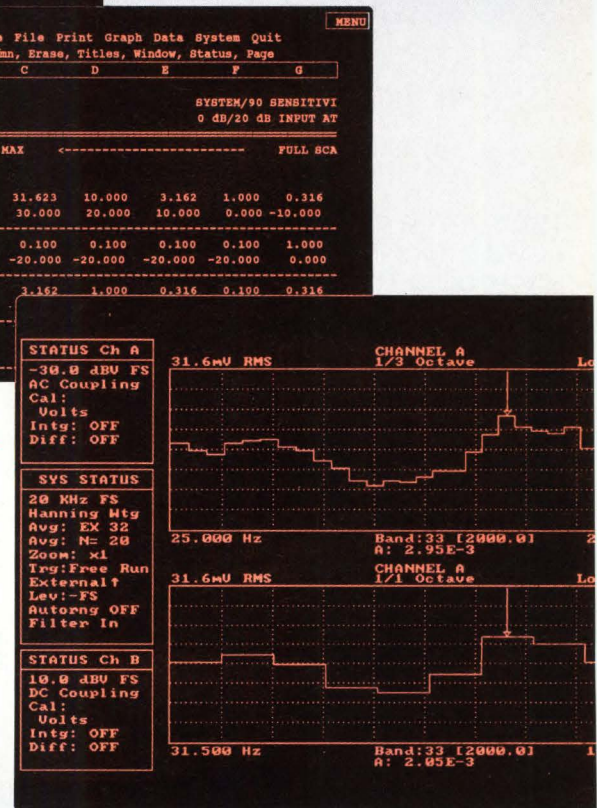Don't make your choice until you learn more about our new SYSTEM/90 Signal Analysis Workstation.




CIRCLE NO 166 FOR LITERATURE

CIRCLE NO 167 FOR DEMO

ROCKLAND

Rockland Scientific Corporation, 10 Volvo Drive, Rockleigh, NJ 07647 (201) 767-7900

THE POWER SUPPLY

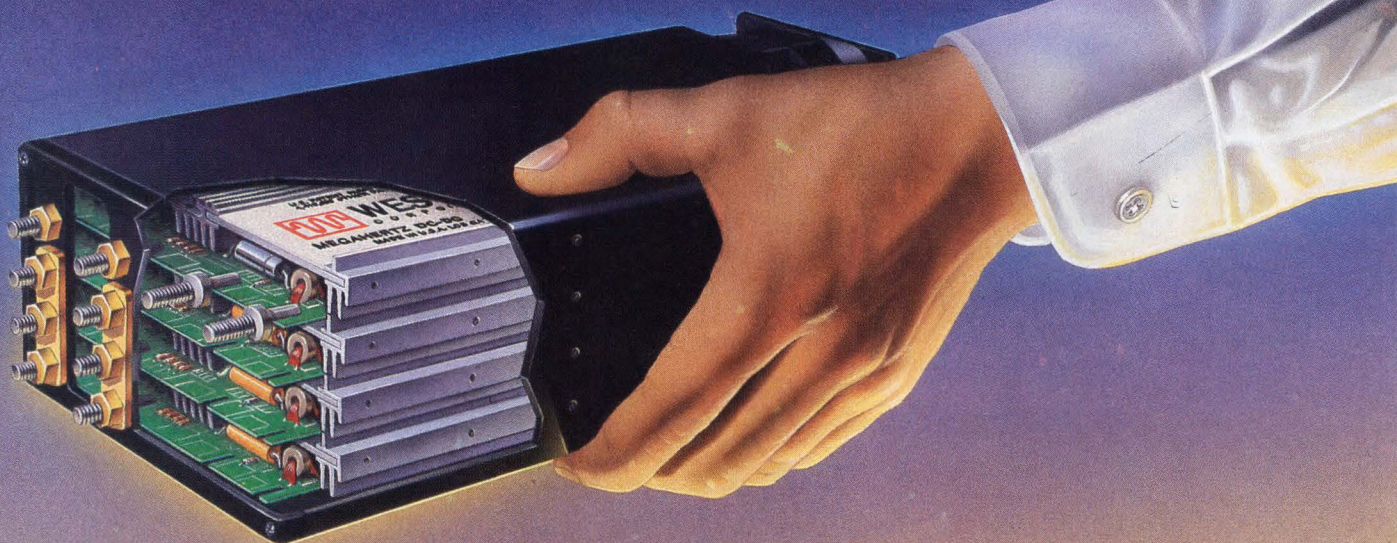

REDEFINED


THE WESTCOR STAKPAK™. NEW GENERATION 250 TO 1200 WATT SINGLE OR MULTIPLE OUTPUT OFF-LINE SWITCHER. 3.2 X 5.5 X 11.4 INCH CASE. FAN-COOLED.

Stack the odds in your favor by designing-in Westcor's 6 watt/cubic inch high power megahertz switcher. Capitalizing on patented and proven megahertz module technology and innovative thermal management techniques, the StakPak provides up to 1200 watts of power at 50°C with 1 to 8 isolated and fully regulated outputs.

For existing designs the StakPak's small size and low profile allow system enhancement without mechanical redesign. Simply replace your open frame switcher with up to 1200 watts of StakPak power or replace your "box switcher" with 2 StakPaks and realize up to twice the power without losing additional space. StakPak power factor correction provides 850 watts of output power from a standard 115 VAC wall outlet. In new designs, more space can be devoted to functionality or the system can be downsized.

The StakPak's 8 module output section can be factory configured in virtually an infinite number of voltage, current and power combinations. Special models providing between 250 to 1200 watts and outputs from 2 to 95 VDC are available.

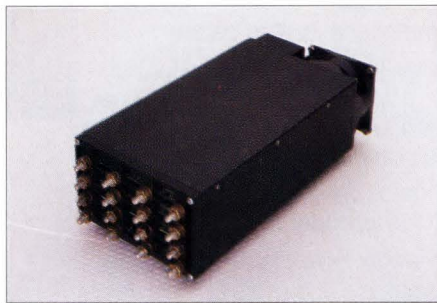Other features include outstanding electrical performance; UL, CSA, VDE safety agency approval (in process); variable speed fan option for low ambient noise environments and 3 phase or DC input options. Indeed, with unprecedented power density, versatility and new features, the StakPak redefines power packaging. Please contact Westcor for a data sheet, pricing and additional information.




STANDARD 1200 WATT STAKPAK MODELS (110/220 VAC input)

Model	Output Voltage (VDC) and Maximum Current (amperes) per Channel				
	#1	#2	#3	#4	#5
Single Output					
SP1-1801	2 @ 240				
SP1-1802	5 @ 240				
SP1-1803	12 @ 100				
SP1-1804	15 @ 80				
SP1-1805	24 @ 50				
SP1-1806	28 @ 42				
SP1-1807	48 @ 25				
Dual Output					
SP2-1801	2 @ 120	5 @ 120			
SP2-1802	5 @ 120	5 @ 120			
SP2-1803	5 @ 120	12 @ 66			
SP2-1804	12 @ 66	12 @ 66			
SP2-1805	15 @ 53	15 @ 53			
Triple Output					
SP3-1801	5 @ 180	12 @ 16	12 @ 16		
SP3-1802	5 @ 150	12 @ 33	12 @ 16		
SP3-1803	5 @ 180	15 @ 13	15 @ 13		
SP3-1804	5 @ 150	15 @ 26	15 @ 13		
Quad Output					
SP4-1801	5 @ 150	12 @ 16	12 @ 16	5 @ 30	
SP4-1802	5 @ 150	15 @ 13	15 @ 13	5 @ 30	
SP4-1803	5 @ 150	12 @ 16	12 @ 16	24 @ 8	
SP4-1804	5 @ 150	15 @ 13	15 @ 13	24 @ 8	
Five Output					
SP5-1801	5 @ 120	12 @ 16	12 @ 16	5 @ 30	24 @ 8
SP5-1802	5 @ 120	15 @ 13	15 @ 13	5 @ 30	24 @ 8

Total output power may not exceed 1200 watts for any model, single or multiple output. Lower power StakPak models are available. Please contact the factory.



WESTCOR CORPORATION • 485-100 Alberto Way • Los Gatos, CA 95032 • (408) 395-7050 • FAX (408) 395-1518

Westcor is a subsidiary of  VICOR CORPORATION

CIRCLE NO 168

EDN Design Ideas Special Issue, Vol III

DESIGN IDEAS

EDITED BY TARLTON FLEMING

Digital ICs form programmable divider

Steve Lubs

Dept of Defense, Washington, DC

The **Fig 1** circuit divides the input clock frequency by an integer between 2 and N ($N=8$ in this case). You select the integer by applying a 3-bit word at the divisor-control inputs.

IC₁ and IC₂ form an 8-bit shift register. These cascaded ICs either shift their output data to the right or load input data in parallel: When S1 (pin 10) is high, the chips load the A through D inputs (pins 3 through 6) on a positive transition of the input clock. When S1 is low, each positive clock transition causes the chips to shift their output data (which appears on Q_A through Q_D) to the right. Multiplexer IC₃ selects one of its eight inputs according to the 3-bit divisor-control input, and the multiplexer's output drives the S1 inputs of IC₁ and IC₂.

During operation, the circuit's output goes high for

one clock cycle, causing the shift register to load the input word 10000000. Succeeding clock cycles shift the input word's single 1 to the right until it enters the selected IC₃ input. The resulting output pulse loads the shift register with another 10000000, which reinitiates the cycle. Coincident with each parallel-load operation, the circuit consisting of IC₄, IC₅, and IC₆ presents a 1 to the shift register's D_{SR} input, ensuring continued operation in the event that a malfunction clears the shift register.

The circuit can operate at 50 MHz if you use high-speed devices such as ones from Fairchild's Fast Series. You can obtain larger divisors by increasing the number of shift-register stages. Adding another multiplexer, however, lowers the system clock rate. **EDN**

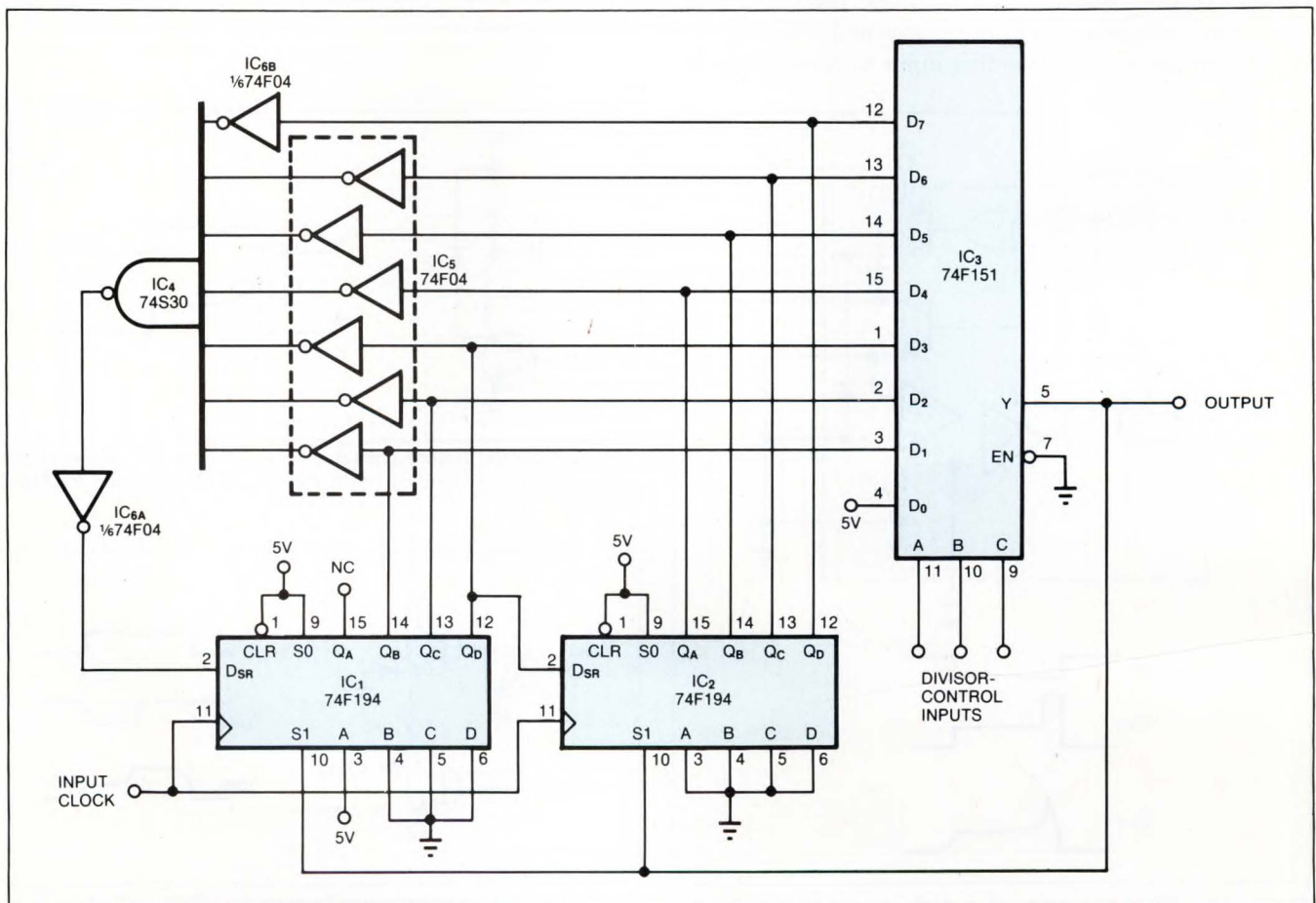


Fig 1—Two universal shift registers (IC₁ and IC₂) and a 1-of-8 data selector (IC₃) form a programmable divider; IC₁, IC₃, and IC₆ provide a backup function for the divider's operation.

DESIGN IDEAS

EDITED BY KEN MARRIN

Simple circuit supplies relay hold current

F Raymond Dewey
Sprague Electronic Co, Worcester, MA

The **Fig 1** circuit generates hold current for relays and solenoids by taking advantage of an integrated power driver's (UDN-2975W) internal short-circuit-protection circuitry. This technique provides an efficient alternative to RC timing circuits (**Fig 2**) and a simple alternative to configurations that require multiple discrete power drivers with split supplies and complicated timing sequences (**Fig 3**).

Fig 1's driver can supply as much as 5A of peak current to a relay or solenoid. A single input activates the relay. When the input goes low, both the source driver (Q_1) and the sink driver (Q_2) turn on. The positive voltage source then supplies current to the load relay. Sensing resistor R_1 monitors relay current. When the voltage across this resistor and, subsequently, the voltage at the inverting input to comparator A_1

exceed the reference voltage at the noninverting input, the comparator sets the latch. You can calculate a value for R_1 using the equation

$$R_{\text{SENSE}} = V_{\text{REF}} / (10 I_{\text{TRIP}}).$$

where V_{REF} is the reference voltage and I_{TRIP} is the current value at which the relay trips.

Once the latch is set, Q_1 turns off and the load's current and voltage drop to a value determined by supply B^+ . The sink driver remains on as long as the input stays low. You could also use a current-limiting resistor across the source driver to limit load current in the hold state. When the input goes high, the sink driver shuts off and the latch is reset. The circuit is now ready for another operation.

EDN

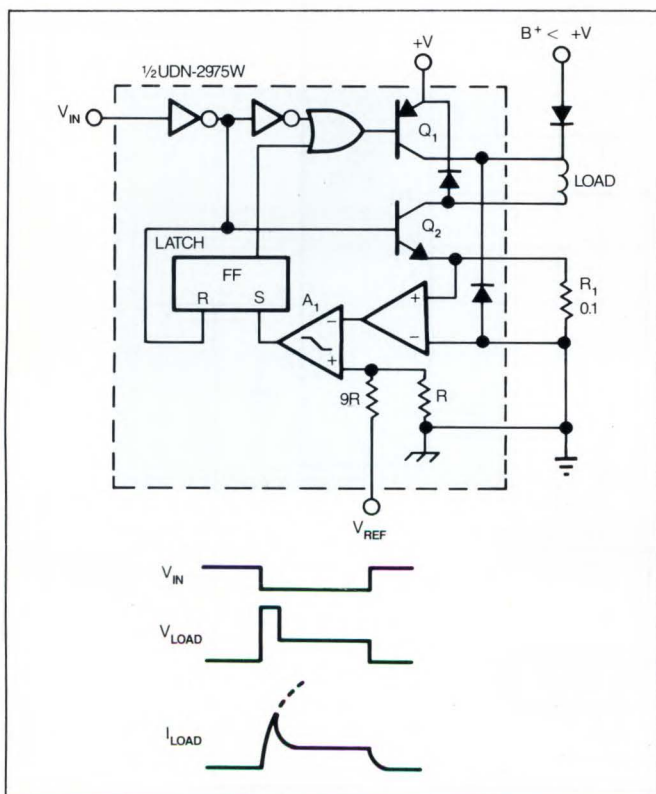


Fig 1—By taking advantage of a high-current power driver's internal short-circuit protection, you can build a simple circuit for supplying hold current to relays and solenoids.

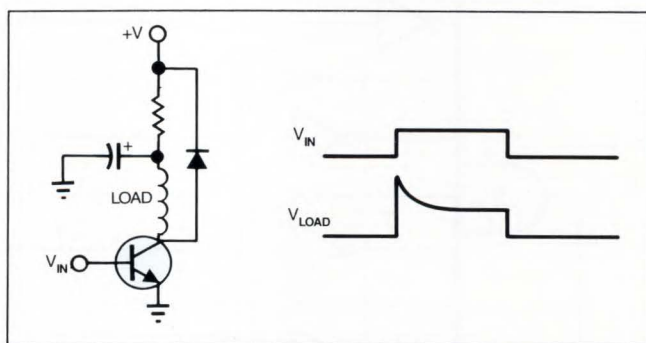


Fig 2—This RC timing circuit provides one means of generating relay and solenoid hold currents, but it's less efficient than the Fig 1 method.

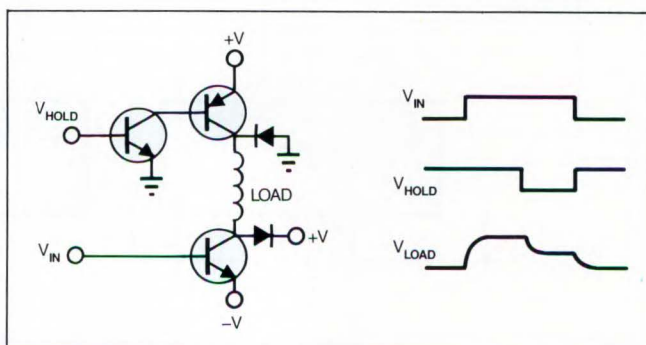


Fig 3—This hold-current control circuit for relays and solenoids is effective, but it requires split supplies and complicated timing sequences.

DESIGN IDEAS

EDITED BY ROBERT M CLARKE

Algorithm produces base-2 logarithms

Robert D Grappel,
Compdata Services Corp, Wellesley, MA

To most programmers, an algorithm that computes a logarithm is something hidden in the bowels of a compiler or math package. Typically, the computation involves floating-point operations and series expansions. Nevertheless, an algorithm exists that lets you quickly and easily calculate base-2 logarithms, even using μ Ps.

The algorithm uses the fact that a binary number can be represented as the sum of a series of powers of two in which each power is multiplied by either a zero or one coefficient. Thus, you can represent the number as a series of bits, each zero or one, with each bit's position corresponding to a power of 2. For example, the binary string 0110 represents

$$0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0.$$

(For further theory, see "Exponential and Logarithm by Sequential Squaring," *IEEE Transactions on Computers*, Vol C-33, No 5, May 1984.)

Consider a subroutine example that implements the algorithm. First, note that this example uses a scaled integer representation for the arguments for the logarithm subroutine. The assumed decimal point lies between bits 14 and 15 of a 16-bit value. Assume that the real argument value has been multiplied by 2^{14} (16,384) and is now an integer. The subroutine uses 16- and 32-bit integer operations. Its output is a scaled 16-bit fraction whose assumed decimal point is to the left of bit 16. Hence, the subroutine produces results significant to about 16 places.

Second, the example requires that the argument be between 1.0 and 2.0. This isn't a great hardship, because values outside this range can be scaled to fit, and the return value from the logarithm routine can be adjusted. Scaling base-2 values requires only shifting and adding, which isn't too difficult to accomplish. The scaling code is not shown here.

The code in Fig 1 shows how you can implement the algorithm in C. Integers are assumed to be represented in 32 bits. The array "L" stores the bits of the 16-bit logarithm.

You can also implement the algorithm on a μ P. Fig 2's code shows how simply you can write the subroutine in Motorola 68000 assembly language. Note that with

```
#define SCALE 16384 /* 14-bit scaling constant */

int x; /* the argument, whose base-2 log. is desired */
int i; /* bit counter index for L */
char L[16]; /* bits of the logarithm base-2 of x */

for (i=0; i < 16; i++)
{ /* loop through 16 bits of L */
  L[i] = 0; /* initialize bit */
  x *= x; /* square x */
  x /= SCALE; /* re-scale its value */
  if (x >= (2 * SCALE))
  {
    L[i] = 1; /* set bit in logarithm */
    x /= 2; /* ready for next position */
  }
}
```

Fig 1—Calculate base-2 logarithms to about 16 bits of precision using the algorithm implemented in this C code.

```

}
* Register usage: D0 argument (input) and logarithm base-2 (output)
*                  D1 logarithm temporary
*                  D2 bit index
*                  D3 scale factor
*
LOG0    MOVEM.L D1-D3, -(A7)    SAVE REGISTERS
        MOVEQ #0, D1           INIT. LOG. TEMP.
        MOVEQ #15, D2          INIT. BIT INDEX
        MOVEQ #14, D3          INIT. SCALE FACTOR
*
LOG1    MULL D0, D0             SQUARE ARGUMENT
        LSR.L D3, D0            RE-SCALE ARGUMENT
        CMPL.W #32768, D0       ARG < BASE-2?
        BLO.S LOG2             YES
*
        BSET D2, D1            NO, SET BIT IN LOGARITHM
        LSR.W #1, D0           READY FOR NEXT POSITION
*
LOG2    DBRA D2, LOG1          LOOP THROUGH THE 16 BITS
*
        MOVE.L D1, D0          RETURN LOGARITHM IN D0
        MOVEM.L (A7)+, D1-D3   RESTORE WORKING REGISTERS
        RTS
```

Fig 2—You can easily calculate base-2 logarithms on a μ P, as this Motorola 68000 assembly-language subroutine shows.

the scaling factor chosen, there's no danger of overflow in the multiplication step. Shifts do all the divisions. The order of bits is reversed to match Motorola's format.

You can calculate logarithms in other bases by multiplying the base-2 logarithms by the appropriate constant, which is simply the base-2 logarithm of the desired base. This multiplication requires 32 bits of precision because the constant scaled will exceed 16 bits.

EDN

Trust S-MOS. Our ASICs won't leave you out in the woods.



Instead, we'll help you along the path to higher productivity.

Through high-volume, high-yield technology, our manufacturing affiliate Seiko Epson Corp. produces millions of ASIC devices each month.

S-MOS backs up that production with a dependable design program that provides back annotation simulation and fault grades every chip to help your designs succeed.

To keep costs low, there are no CPU simulation charges.

Our full line of ASICs are migratable from gate arrays into standard cells and beyond to our Compiled Cell Custom cell-based designs.

Our ASIC solutions span from 513 to 38,550 gates with technologies down to 1.2 micron (drawn).

To save you time, we can use your existing arrays as future building blocks.

Most ASIC products are available in plastic quad flat packs, pin grid arrays, plastic leaded chip carriers, small outline packages and plastic dual-in-line packages.

So if you're looking for an ASIC program that will get you out of the woods, call us.

(408) 922-0200.



S-MOS Systems, Inc.
2460 North First Street
San Jose, CA 95131-1002

Program speeds best-fit 1%-resistor calculations

Andrew Dart
Trans-Texas Telegraph Co, Duncanville, TX

The program shown in **Fig 1a** calculates best-fit 1%-resistor values for the voltage divider shown in **Fig 1b**, and it runs 400 times faster than a similar program that appeared as a Design Idea earlier this year (see "Program calculates best-fit 1% resistors," EDN, April 18, pg 286).

The version shown in **Fig 1a** takes advantage of the fact that the 96 standard values for 1% resistors are

evenly spaced powers of the 96th root of 10. For each of the 96 values that the program calculates for R_1 , it performs only one calculation to find the value of R_2 . The program thus eliminates 95 out of 96 of the calculations that the earlier resistor-value-calculation program performed. Note that V_1 can be less than V_2 as long as V_3 's value is between V_1 and V_2 . **EDN**

```

100 REM New & Improved Version of the
110 REM One Percent Resistor Calculator Program:
120 REM 1% resistor values are based on the 96th root of 10.
130 REM Refer to EIA RS-385
140 DIM RV(99)
150 FOR X=1 TO 96
160   READ RV(X)
170 NEXT X
180 P(0)=1:P(1)=10:P(2)=100:P(3)=1000:P(4)=10000:P(5)=100000
190 CLS:REM Clear the screen
200 INPUT "Enter voltage V1";V1
210 INPUT "Enter voltage V2";V2
220 INPUT "Enter the desired voltage at V3";V3
230 IF V2>V1 THEN F1=1:X=V1:V1=V2:V2=X
240 IF V3>V1 OR V3<=V2 THEN PRINT "V1 > V3 > V2 please":GOTO 220
250 REM R is the ratio R1:R2
260 R=(V1-V3)/(V3-V2)
270 REM Be sure R is greater than 1
280 IF R<1 THEN F2=1:R=1/R
290 REM Assure 1 < Ratio < 10 by dividing by a power of ten:
300 SF=LEN(STR$(FIX(R)))-2
310 REM SF = Scale Factor
320 R=R/P(SF)
330 REM The inverse of the natural log of the 96th root of ten
340 REM is approximately 41.69227
350 Q=FIX(LOG(R)*41.69227+.5)
360 H=99
370 FOR X=1 TO 96
380   G=0
390   Y=X+Q
400   IF Y>96 THEN Y=Y-96:G=1
410   IF RV(Y)/RV(X) < H THEN H=RV(Y)/RV(X):J=RV(Y):K=RV(X)
420 NEXT X
430 IF G=1 THEN SF=SF+1
440 J=J*P(SF)
450 IF F1=1 THEN Z=J:J=K:K=Z
460 IF F2=1 THEN Z=J:J=K:K=Z
470 PRINT
480 PRINT "With ";V1;"volts at V1"
490 PRINT "and ";V2;"volts at V2"
500 PRINT "if R1 = ";J;"ohms"
510 PRINT "and R2 = ";K;"ohms"
520 PRINT "then V3 will be ";K*(V1-V2)/(J+K)+V2;" volts"
530 PRINT
540 REM 1% Resistor values:
550 DATA 1.00,1.02,1.05,1.07,1.10,1.13,1.15,1.18,1.21,1.24
560 DATA 1.27,1.30,1.33,1.37,1.40,1.43,1.47,1.50,1.54,1.58
570 DATA 1.62,1.65,1.69,1.74,1.78,1.82,1.87,1.91,1.96,2.00
580 DATA 2.05,2.10,2.15,2.21,2.26,2.32,2.37,2.43,2.49,2.55
590 DATA 2.61,2.67,2.74,2.80,2.87,2.94,3.01,3.09,3.16,3.24
600 DATA 3.32,3.40,3.48,3.57,3.65,3.74,3.83,3.92,4.02,4.12
610 DATA 4.22,4.32,4.42,4.53,4.64,4.75,4.87,4.99,5.11,5.23
620 DATA 5.36,5.49,5.62,5.76,5.90,6.04,6.19,6.34,6.49,6.65
630 DATA 6.81,6.98,7.15,7.32,7.50,7.68,7.87,8.06,8.25,8.45
640 DATA 8.66,8.87,9.09,9.31,9.53,9.76

```


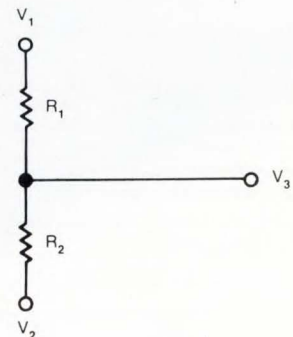


Fig 1—This program (a) calculates best-fit 1% resistors for a divider network (b) and eliminates 95 out of 96 of the calculations performed by a similar program.

E²POT™

DIGITALLY CONTROLLED POTENTIOMETERS

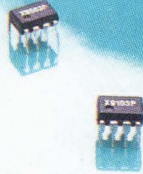


Part No.	Max. Resistance
X9103	10K Ω
X9503	50K Ω
X9104	100K Ω

E²POT is a trademark of Xicor, Inc.



SERIAL I/O

E²PROMS AND NOVAM

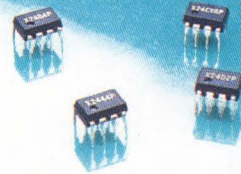


Part No.	Organization
X2402	256 x 8
X2404	512 x 8
X24C04	512 x 8
X24C16	2048 x 8
X2444	16 x 16



E²PROMs


4K, 16K, 64K, 256K

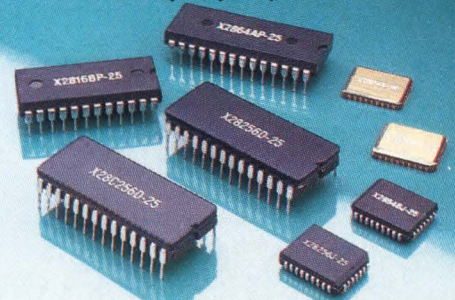

Part No.	Organization
X2804A	512 x 8
X2816B	2K x 8
X2864A	8K x 8
X2864B	8K x 8
X2864H	8K x 8
X28256	32K x 8
X28C256	32K x 8



NOVRAMs*

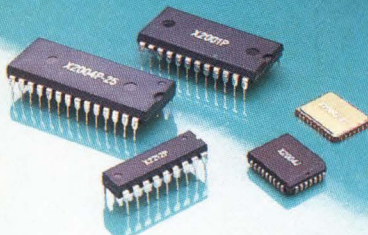

Part No.	Organization
X2201A	1K x 1
X2210	64 x 4
X2212	256 x 4
X2001	128 x 8
X2004	512 x 8

*NOVRAM is Xicor's nonvolatile static RAM device.



1 MEGABIT CMOS E²PROM.



**EARLY DESIGN-IN.
EARLIER TO MARKET.**

MIL-STD-883C
COMPLIANT
COMPONENTS

**Our CMOS E²PROM modules
get you to market ahead
of schedule.**

Chances are, your next-generation products call for more memory. And for less dependence on older, electro-mechanical devices like disks and tape drives. So you've been waiting for larger semiconductor memory to come along that offers a more reliable alternative.

Now it has. With Xicor's 1 Megabit E²PROM modules, there's no more waiting to get your next memory-intensive products off the drawing board. And out to your customers,

where they can start generating revenue sooner.

Comprised of four Xicor-made 256K CMOS E²PROMs, these modules have the future built right in. Their 32-pin dual-in-line packaging is pin compatible with our upcoming monolithic CMOS megabit parts. So you'll be able to upgrade in the near future without any redesign effort. While realizing significant cost reductions over our already price-competitive 1 Megabit modules.

Like all Xicor E²PROMs, these CMOS modules can shorten design cycles, too. They're 5V only, non-volatile devices, configured in a convenient 128K x 8 organization. Plus they include JEDEC-approved Software Data Protection, which prevents inadvertent writing to the device during power-up, power-down or any unexpected condition. This feature eliminates the need

for external hardware protection.

And for help in hitting your market window, you can count on Xicor. To date, we've shipped over 30 million 5V only E²PROM products—more than any other E² manufacturer. We back the modules with onsite technical design support. The modules are available in commercial, industrial and military temperature ranges.

So if you're moving to the megabit E²PROM level—especially for low power, portable or harsh environment applications—get an early start. Call Xicor at (408) 432-8888 today, or write: Xicor, Inc., 851 Buckeye Court, Milpitas, CA 95035.



MAKES IT MEMORABLE

SEND FOR MORE INFORMATION

In particular, I'm interested in the following Xicor E² products:

- ☐ E²POT digitally controlled potentiometers
- ☐ Serial I/O E²PROMs and NOVAM
- ☐ 4K/16K/64K E²PROMs
- ☐ 256K NVCMOS E²PROMs
- ☐ 256K CMOS E²PROMs
- ☐ NOVAMs
- ☐ 1 MEGABIT CMOS E²PROMs

☐ Please send me a FREE XICOR Data Book

☐ Please have your representative give me a call

EDN-14A

Name _____

Title _____

Company _____

Address _____

City _____ State _____ Zip _____

Telephone No. _____ Ext. _____

XICOR, INC., 851 Buckeye Court, Milpitas, CA 95035



Run Z80 software on an 8085 system

Leo M Almazan

Naval Ocean Systems Center, San Diego, CA

The Fig 1 circuit shows how to convert an 8085-based μ P system to one that runs Z80 software. The scheme involves replacing the 8085 with an NSC800 μ P. (The NSC800 is similar to the Z80 internally but has the same bus structure as the 8085). The resulting system is advantageous for those who would rather program for the Z80 than for the 8085.

The main external difference in the Z80 (NSC800) and 8085 μ P is the latter's serial-I/O lines SID and SOD;

no Z80 instructions can implement these functions. In addition, two discrepancies concern the programmer: The 8085 Trap (nonmaskable-interrupt) input causes a jump to location 24_{HEX}; the NSC800 equivalent input NMI causes a jump to location 66_{HEX}. Finally, the NSC800 control register for internal interrupts is located at 0BB_{HEX}, so that address must be free to service a mode-2 interrupt request.

EDN

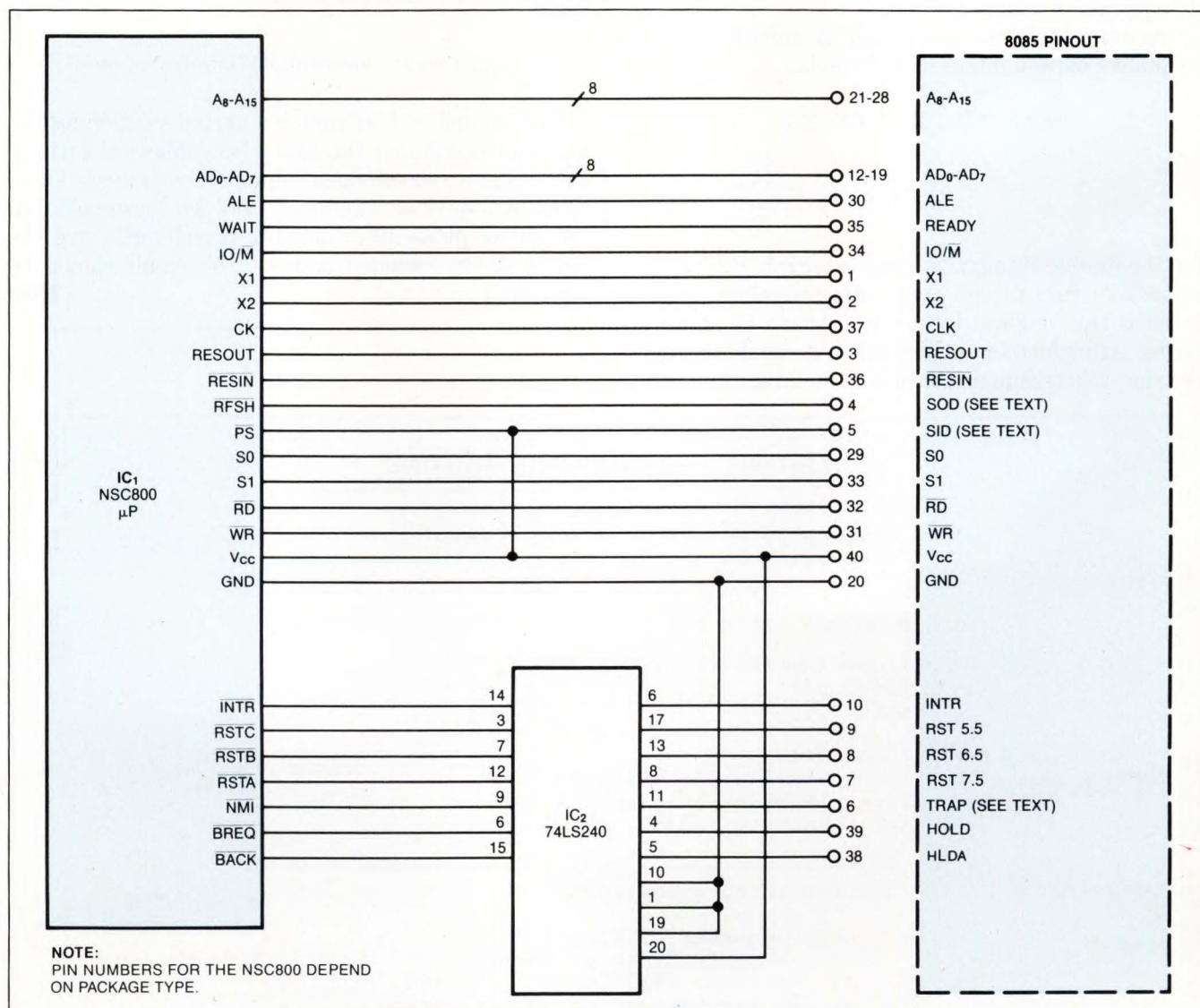


Fig 1—This circuit lets you substitute the Z80-like NSC800 for an 8085 μ P and thereby obtain a system that can develop and run Z80 software.

Simpson's rule solves double integrals

A Cameron

Defence Research Centre, Adelaide, SA,
Australia

Although one generally uses Simpson's rule to approximate single integrals, you can extend the technique for use in solving double integrals. The C language routine of **Listing 1** contains the required algorithm plus an example, demonstrating that you can apply Simpson's rule to certain complex double integrals that would normally require the application of numerical techniques. In addition, the technique applies equally well to integrals of a higher order.

You can obtain the algorithm by substituting the standard Simpson integration formula,

$$S_X(y_j) = f(x_0, y_j) + f(x_n, y_j) \\ + 4 \sum_{i=1}^{\frac{n-2}{2}} f(x_{2i-1}, y_j) + 2 \sum_{i=1}^{\frac{n-2}{2}} f(x_{2i}, y_j),$$

for the double integral's inner integral. Reapplying Simpson's rule to the outer integral allows you to express the original integral equation in algebraic terms. After further simplification, it should be apparent that this technique consists of an integration along

one axis for each interval on the orthogonal axis, followed by an application of Simpson's rule on the accumulated results along the orthogonal axis.

If $S_X(y_n)$ represents Simpson's rule applied along the x-axis as a function of the position y_n on the y-axis, then

$$\text{SIMPSON} = \frac{h_X \cdot h_Y}{9} (S_X(y_0) + S_X(y_n) + 4 \cdot S_X(y_1) \\ + 2 \cdot S_X(y_2) \dots \text{etc}),$$

where h_X and h_Y represent the increments between steps:

$$h = (\text{upper limit} - \text{lower limit}) / (\text{number of steps}).$$

The example in **Listing 1** is a partial solution for the total radiated power through a hemispherical surface. Two quarter-wavelength monopole antennas, separated by a quarter wavelength and fed by signals that are out of phase by a quarter wavelength, are the source of the radiated power. (The result should be 3.829042.)

EDN

LISTING 1—C LANGUAGE ROUTINE

```
/*-----
Simpson integration technique for
evaluating double integrals.
-----*/

#include "math.h"

float fxy[100][100],fy[100];
float pi;
main() {

float f();
float llx, lly, ulx, uly, x, y;
float hx, hy, ef, of, simpson;
int nosx, nosy, i, j;

/*-----
Simpson integration constants.

nos -> number of strips
ul  -> upper limit of integration
ll  -> lower limit of integration
h   -> incremental value per strip
-----*/
```


DESIGN IDEAS

LISTING 1—C LANGUAGE ROUTINE (Continued)

```
pi=3.1415926;
nosx=30; nosy=40;
llx=0.1e-8; lly=0.1e-8;
ulx=pi; uly=2.0*pi;
hx=(ulx-llx)/nosx;
hy=(uly-lly)/nosy;

printf (" \n\nDouble integration parameters: \n");
printf (" Step size hx and hy:  %f,%f\n",hx,hy);
printf (" Number of steps(x,y): %d,%d\n\n",nosx,nosy);

/*
Calculate all the points within the
integration region.
*/
for (j=0; j <= nosy; j++) {
    for (i=0; i <= nosx; i++) {
        x = hx*i+llx;
        y = hy*j+lly;
        fxy[i][j] = f(x,y);
    }
}

/*
Now perform a Simpson integration along
the x axis and accumulate results using
the y axis variable as an index.
*/
for (j=0; j <= nosy; j++) {
    of=fxy[1][j];
    ef=0.0;
    for (i=2; i <= nosx-2; i += 2) {
        ef += fxy[i][j];
        of += fxy[i+1][j];
    }
    fy[j]=fxy[0][j]+fxy[nosx][j]+2.0*ef+4.0*of;
}

/*
Lastly perform Simpson integration
along the y axis.
*/
of=fy[1];
ef=0.0;
for (j=2; j <= nosy-2; j += 2) {
    ef += fy[j];
    of += fy[j+1];
}
simpson = (hx*hy/9.0)*(fy[0]+fy[nosy]+2.0*ef+4.0*of);

printf("Result = %f\n\n",simpson);
}

/*
Enter the function to be integrated here.
*/
float f(x,y) float x,y; {
double xd,yd,zd,zdl;

    xd = x; yd = y;
    zd = pi*cos(xd)/2.0;
    zd = cos(zd);
    zdl = pi*(1.0-sin(xd)*cos(yd))/4.0;
    zdl = cos(zdl);
    zd = zd*zdl;
    zd = pow(zd,2.0)/sin(xd);
    return ( fabs(zd) );
}
```


Bidirectional tachometer offers low error

R L Dave

PDO, Muscat, Sultanate of Oman

The inexpensive circuit of **Fig 1** lets you sense or control shaft rotation. In addition, it provides a tachometer

output that tracks bidirectional rotation without error (except the $\pm \frac{1}{2}$ -count uncertainty common to digital circuits, that is, $\pi R/P$, where R equals the radius of the encoder disk and P equals pulses/revolution).

Photosensors A and B produce quadrature square


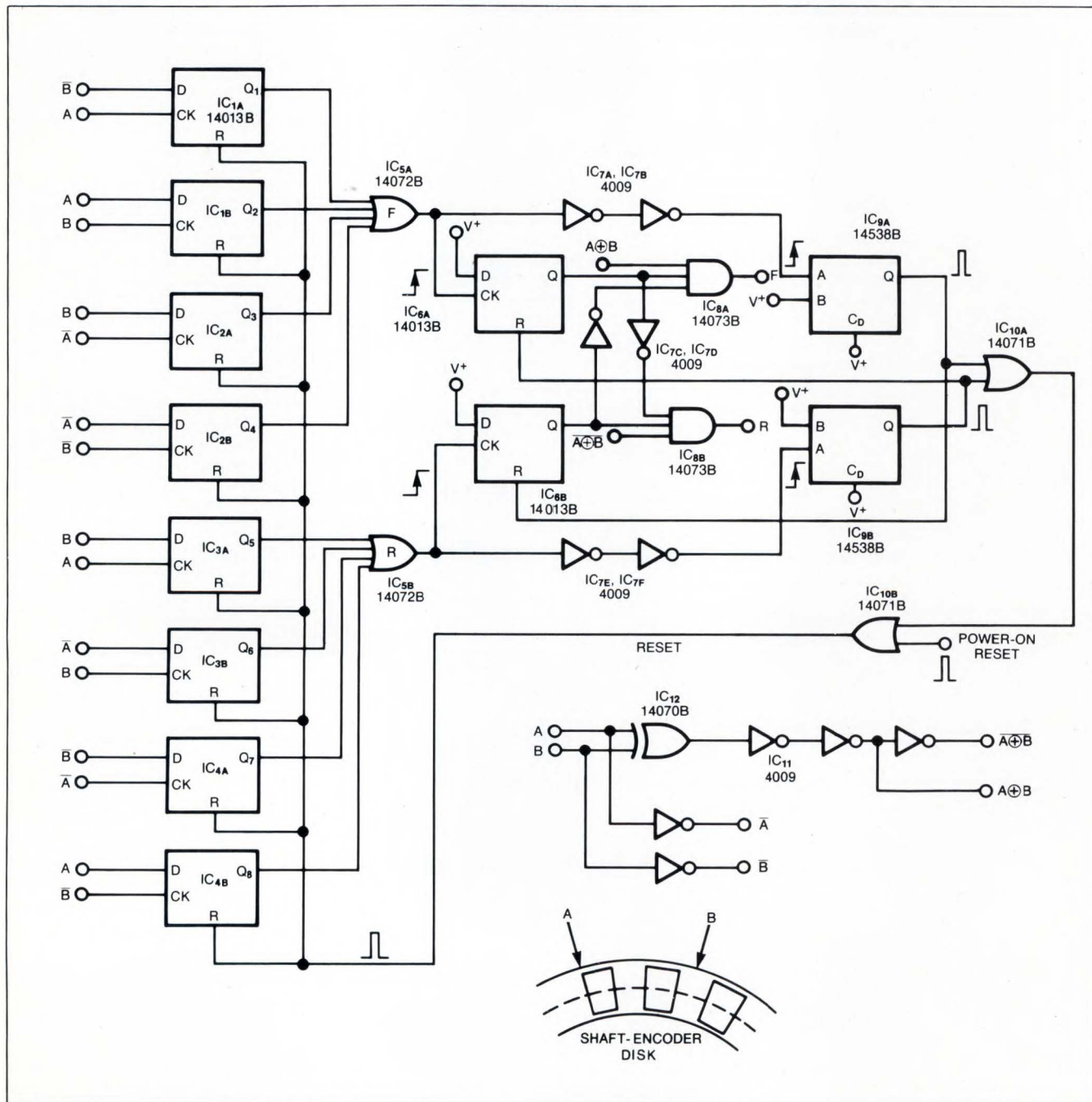


Fig 1—This circuit converts the incremental shaft encoder's photosensor outputs A and B to bidirectional tachometer outputs F (forward) and R (reverse).

Low-noise chopper.

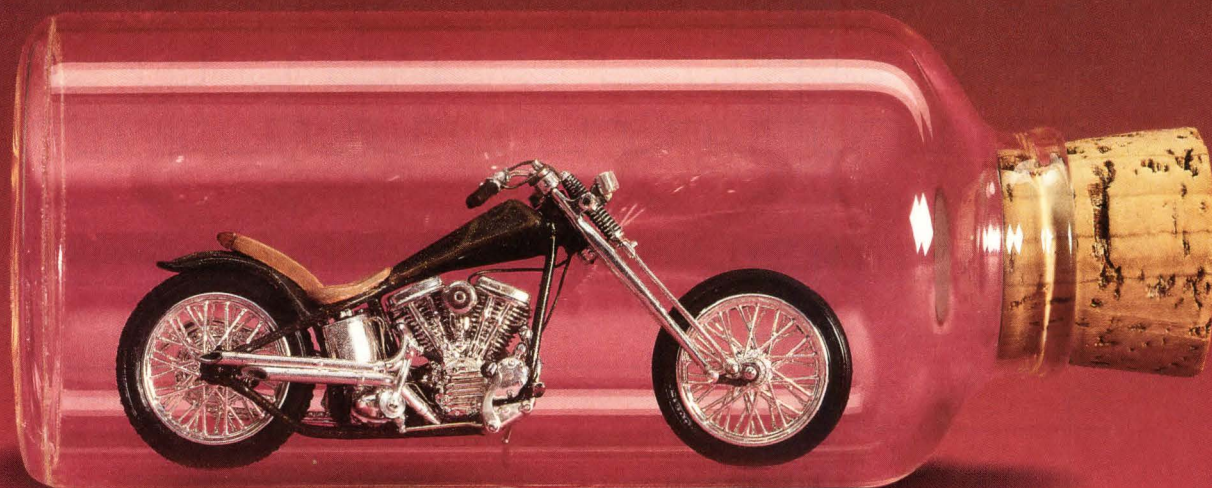

Finally, A No-Compromise Chopper Without External Caps.

At long last, Linear introduces the first chopper-stabilized op amp to include on-chip sample-and-hold capacitors and superior performance. The LTC1050.


Our no-hassle, low-cost chopper amp is as easy to use as a 741. And with two caps on board, you eliminate space-hogging demands for large value capacitors required by other choppers.

The LTC1050 offers plenty of features to leave the competition in its dust. Guaranteed maximum offset voltage of $5\mu\text{V}$. Maximum offset voltage drift of $0.05\mu\text{V}/^\circ\text{C}$ over the full military temperature range. Typical DC to 10Hz noise voltage is $1.6\mu\text{V}$ p-p (guaranteed on the "A" version). And a typical voltage gain of 160dB.

Our chopper amp features a slew rate of $4\text{V}/\mu\text{sec.}$, and a gain bandwidth product of 2.5MHz achieved with only 1mA of supply current.

Overload recovery times from

Single Supply Thermocouple Amplifier

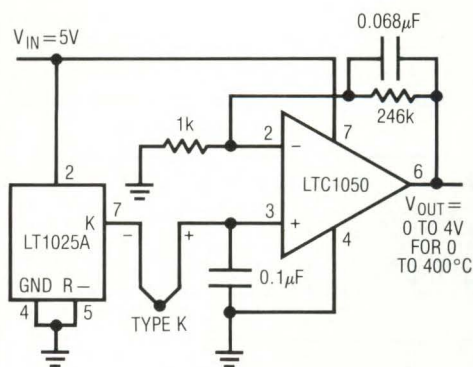

positive and negative saturation conditions are 1.5ms and 3ms, respectively (and that's about 100 times better than performance offered by chopper amps using external capacitors). Pin 5 is an optional external clock input ideal for synchronization.

Typical LTC1050 applications include: thermocouple amplifiers, electronic scales, medical instrumentation, strain gauge amplifiers, and high-resolution data acquisition systems. And our chopper plugs into the 7650 amp socket, so you can throw the capacitors away.

The LTC1050 is available in both military and commercial versions. This includes standard 8-pin plastic, SO (small surface mount), or ceramic DIP configurations. Pricing starts at \$2.25 each in quantities of 100 up (and a lot less in 10,000 piece lots).

Get your design on a fast track with our low-noise, high-performance chopper amp. For details contact Linear Technology Corporation, 1630 McCarthy Blvd., Milpitas, CA 95035. Or call 800-637-5545.



TOUGH PRODUCTS
FOR TOUGH APPLICATIONS.

CIRCLE NO 171

DESIGN IDEAS

waves (Fig 2) as the encoder disk (Fig 1) turns. Direction-sense latches IC₁ through IC₄ respond to the eight possible states of A and B, causing the OR gates IC_{5A} and IC_{5B} to identify forward (F) or reverse (R) rotation. The 3-input AND gates IC_{8A} and IC_{8B} provide tachometer pulse-count outputs proportional to the forward or reverse rpm.

IC₉ provides resets to the IC₆ latches. IC₁₀ combines

these reset pulses to provide a reset to the eight input latches for every change in the state of waveforms A and B, which ensures that the circuit is always ready to detect a change in the direction of rotation. **EDN**


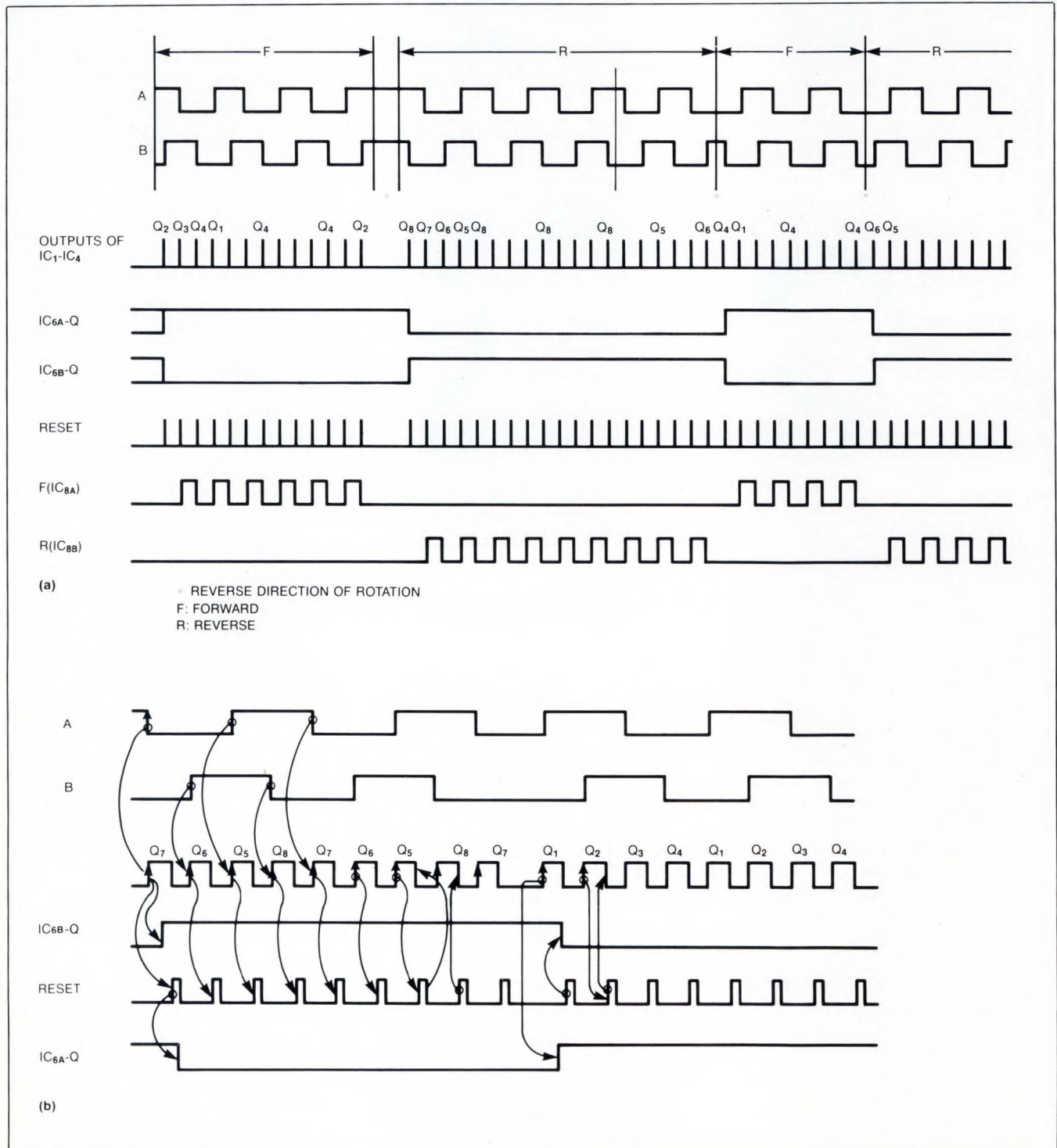


Fig 2—These waveforms (a) illustrate the operation of Fig 1. The expanded traces (b) offer greater clarity.

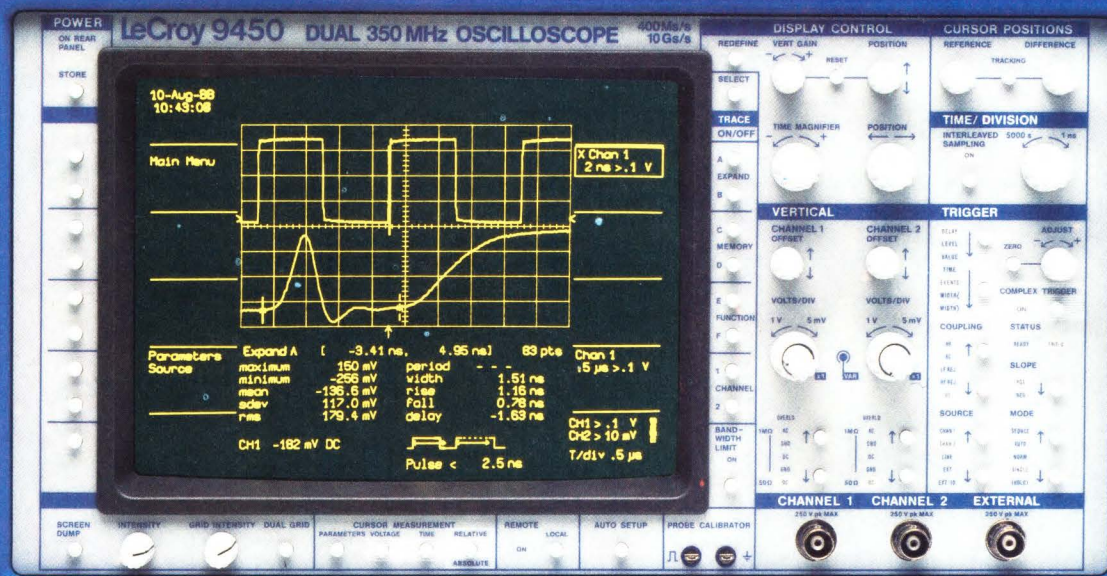SPEED, FIDELITY and... ...UNPRECEDENTED TRIGGERING



FASTGLITCH trigger mode is used to trigger on a glitch 1.51 nsec wide which occurs before the leading edge of a 500 kHz clock signal (top trace, see trigger arrow at the bottom of the graticule). Fast sampling rates, automatic pulse parameters and horizontal expansion by 250 times (lower trace) all combine to reveal the signal details.

- * 350 MHz Bandwidth, 400 Ms/s ADCs
- * 50K Non-volatile Memory per Channel
- * Glitch, Interval and Logic Trigger Modes
- * Automatic Waveform Parameters

Until now, recording very high-frequency signals with digital oscilloscopes often meant giving up measurement fidelity, due to short acquisition memories, inadequate vertical resolution, or sometimes even both. NOT ANY MORE!!

With LeCroy's new 9450 you get it all, 350 MHz bandwidth, 400 megasample/sec digitizing rates, 8-bit vertical resolution (12-bit with averaging), 50,000 words of acquisition memory per channel and... a uniquely powerful trigger system.

Glitches, drop-outs, logic patterns and states are all triggered on easily with LeCroy's new and innovative FASTGLITCH, INTERVAL and LOGIC trigger modes.

The 9450's massive memories show more pre- and post-trigger information so you can examine the cause and effect of any signal perturbation. Waveform expansion (up to 1000 times) reveals **ALL** the signal details you are looking for, and fast parameter calculations deliver the answers you need in a fraction of a second.

And... you already know how to use it. A familiar front panel, together with a push-button **AUTO SETUP** facility, lets you rapidly learn to operate this new member of the LeCroy oscilloscope family.

LeCroy Corporate Headquarters

700 Chestnut Ridge Road - Chestnut Ridge, NY 10977-6499
Tel.: 800-5-LeCroy - (914) 578 6097 / TWX: (710) 577-2832
Fax: (914) 425-8967

See us at Booth #3256

LeCroy

Innovators in Instrumentation

CIRCLE NO 172

Kentrox Industries, Portland, OR

depress the normally on start switch, the circuit deletes zero to seven full or half cycles from the line voltage applied to the load. You can create various load-voltage waveforms by appropriate settings of the 8-pole DIP switch.

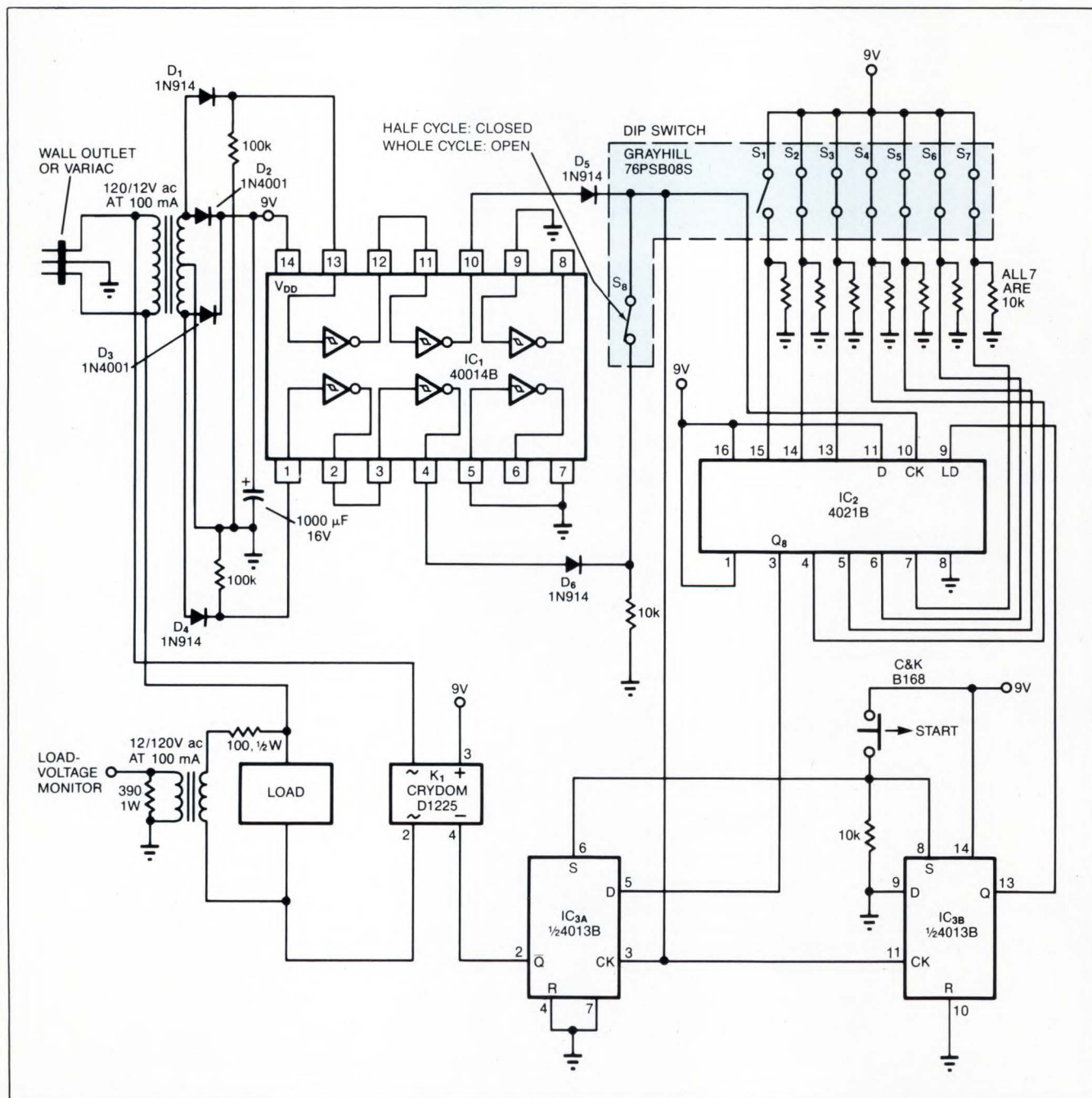



Fig 1—This circuit deletes a sequence of whole or half cycles from the line voltage applied to the load according to a 7-cycle pattern that you program using the DIP switch's sections S_1 through S_8 .



The Wrong Place To Find Out Your ICs Aren't Rad-Hard Enough.

Harris guarantees performance of its rad-hard circuits. Looking for the best protection for your systems? Come to the most specified source for military rad-hard ICs...Harris.

Our technology credentials span more than two and a half decades of programs, from Minuteman and Polaris to Trident II. Soon SDI.

The only way to stay a leader in rad-hard and hi-rel circuits is to know where technology has been, and where it's going. Our know-how shows through...from more progress in new isolation technologies like Silicon-On-Insulator to continued advances in tapping the inherent speed of GaAs.

Your job's not finished so neither is ours.

Count on us for the rad-hard military and commercial range ASICs you need to keep your systems at peak performance.

Our Rad-Hard/Hi-Rel Data Book tells the whole story of our products and processes. To order your copy, call Harris Semiconductor Custom Integrated Circuits Division.

In the U.S.: 1-800-4-HARRIS, Ext. 1905.

In Canada: 1-800-344-2444, Ext. 1905.



HARRIS
SEMICONDUCTOR SECTOR



DESIGN IDEAS


The simple full-wave rectifier (diodes D_2 and D_3) supplies about 9V to the logic ICs. Diodes D_1 and D_4 also rectify the stepped-down line voltage and apply alternate half cycles to the Schmitt-trigger inverters in IC_1 . The inverters square these half-sinusoidal waveforms, and diodes D_5 and D_6 constitute an OR gate that combines the inverter outputs for use as a clock signal to IC_2 and IC_3 .

Section S_8 of the DIP switch determines whether the circuit deletes half or full cycles. The remaining sections (S_1 through S_7) determine the number and serial position of the cycles deleted. Shift register IC_2 converts the information in these sections to a serial bit stream, which controls the solid-state relay K_1 via flip-flop IC_{3A} .


(An open switch deletes a full or half cycle by opening the relay, removing line voltage from the load during that period.)

In each scope photo of **Fig 2**, the top traces show the load voltage (which you measure at the monitor terminal,) and the bottom traces show the corresponding control voltage for the solid-state relay K_1 (which you measure at IC_{3A} , pin 2). You trigger the scope on the falling voltage (IC_3 , pins 6 and 8), which you create by activating the start button.


EDN

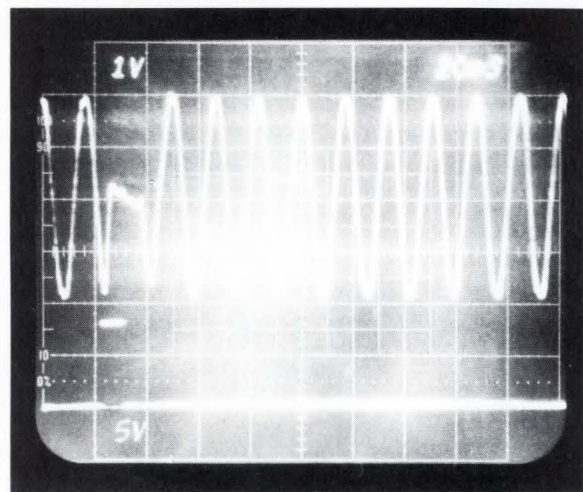


(a)

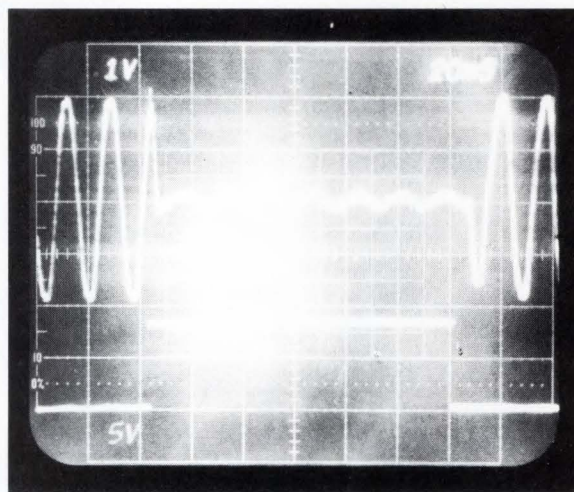

(b)

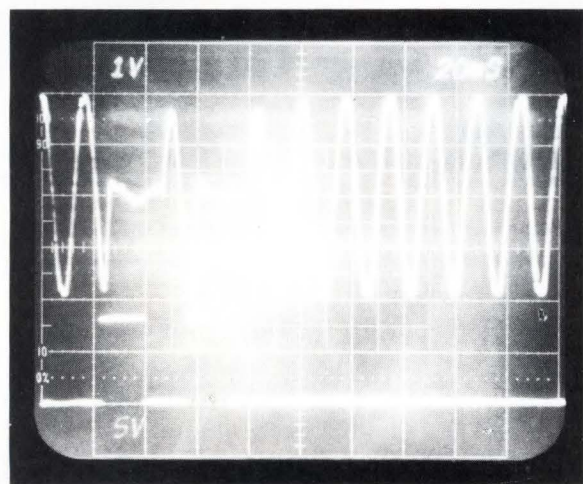

(c)

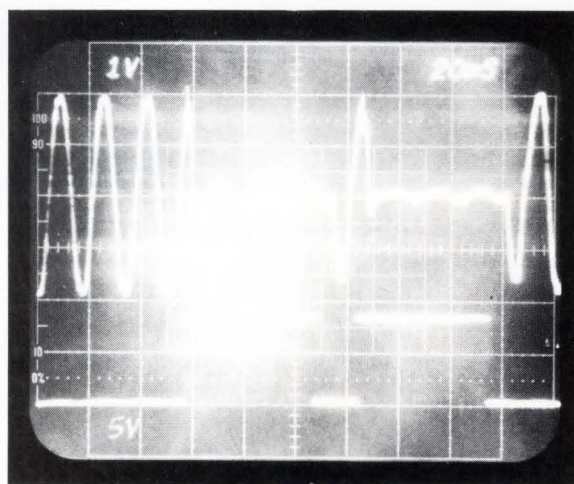

(d)

Fig 2—The top traces in these photos show the load-voltage waveforms, following activation of the start switch, for various settings of the DIP switch: With S_1 open and all others closed, one half cycle is deleted (a); with all switches open, seven full cycles are deleted (b); with either S_1 , S_2 , S_3 and S_6 open or S_1 , S_3 , and S_6 open, two alternate full cycles are deleted (c); and with all switches open except S_1 , three full cycles on either side of a single full cycle are deleted (d).

Thermistor bridge senses air flow

Larry G Smeins
Hewlett Packard Co, Loveland, CO

Using the thermistor-bridge circuit shown in **Fig 1**, you can detect system-cooling air losses caused by filter or inlet blockage or fan failure. One thermistor is mounted directly in the air flow; the other is baffled. The exposed thermistor senses the temperature in the cooling system; the baffled thermistor senses the ambient temperature in still air. As long as the thermistors are at different temperatures, the bridge stays unbalanced, and the circuit produces a logical high, indicating that the cooling system is working. If the air flow stops, the exposed thermistor will reach ambient temperature, the bridge will become balanced, and the circuit will indicate ventilation-system failure by producing a logical low.

The bridge circuit's matched thermistors are biased

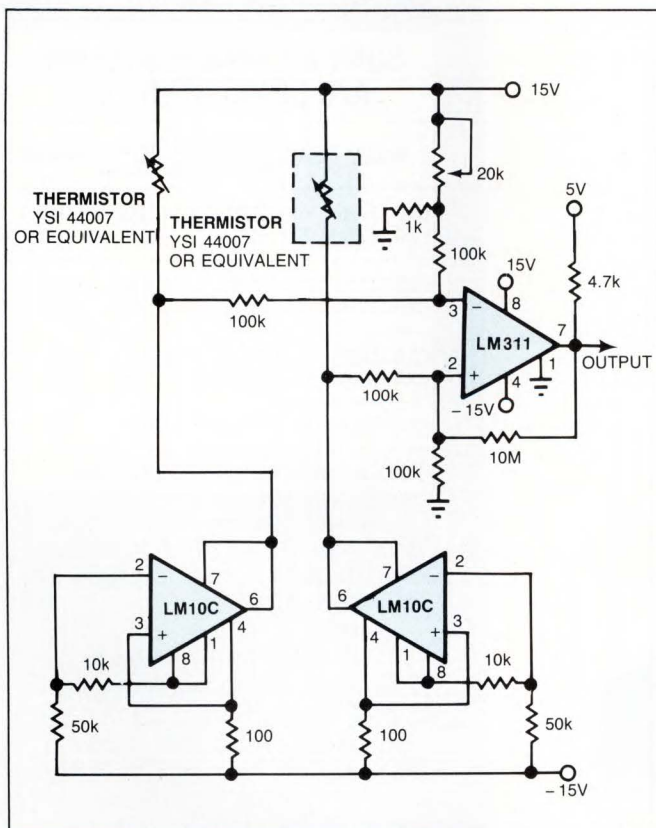


Fig 1—Using this thermistor-bridge circuit, you can detect the loss of system-cooling air caused by filter or inlet blockage or fan failure. As long as the thermistors are at different temperatures, the bridge stays unbalanced, and the circuit produces a logical high, indicating that the cooling system is working.

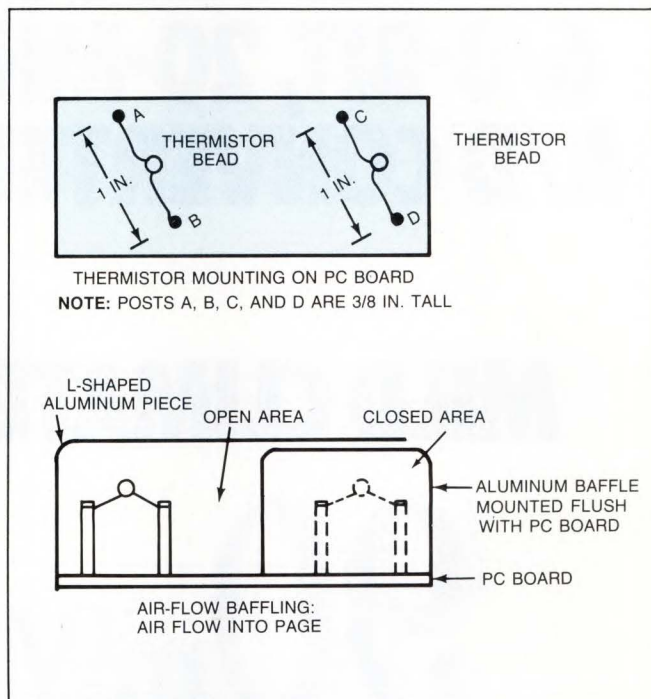


Fig 2—Mount the thermistors on a pc board and baffle one thermistor with an aluminum can mounted tightly to the board. The baffle removes one thermistor from the system-cooling air flow, keeping the thermistor at ambient temperature. The long leads maximize the thermistors' thermal isolation.

by matched-current sources. Two LM10C operational amplifiers act as constant-current sources, and an LM311 comparator senses the difference between the voltage drops across the thermistors, producing the logical high when the bridge is unbalanced and the logical low when the bridge is balanced. You use a 20-k Ω potentiometer to set the comparator's threshold; this setting determines the minimum air flow that will cause the circuit to produce a logical high. **Fig 2** shows how you can mount and baffle the thermistors. Note the thermistors' long leads; they maximize the devices' thermal isolation.

By replacing **Fig 1**'s comparator with a differential amplifier, you can build a circuit that measures the system-cooling air flow. Because only one of the thermistors is mounted in moving air, the differential amplifier's output is proportional to the air velocity. Using a given thermistor/bias combination, you can derive a calibration chart for voltage output vs air flow.

EDN

TWO REASONS TO INVEST IN SONY 6/8-BIT, 20-MHz A/D CONVERTERS.


MILD CLIMATE.

90_{mW}


power dissipation.

(70 mW, 6 bit)

REAL ESTATE.

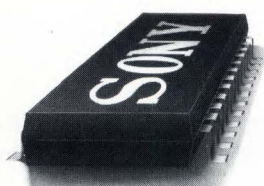

SOP package.

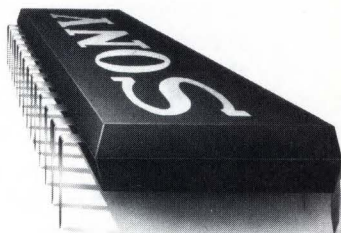

DIP package.

Looking for design advantages? You'll find them throughout Sony's newly expanded 20-MHz A/D converter line.

For starters, ultra-low power dissipation helps keep your designs cool. Via our low-power ECL-3 and CMOS processes, we offer 8-bit models with 90-mW dissipation. 6-bit models with 70-mW dissipation. Plus there's our popular CXA 1096, and all-new CXA 1296—offering 100% pin compatibility and performance of TRW's TDC 1048, yet just 25% its dissipation.

Next, miniature packages help you meet the demand for denser designs. You'll find all-new SOP (surface mount) packaging available with nearly all models, as well as standard DIP packaging.

And if you're wondering about availability and pricing, wonder no more. Sony 20-MHz A/D converters are shipping now in large quantities. At very competitive prices.

All backed by the quality, reliability and responsive service you expect from any Sony product.

SONY'S EXPANDED 20-MHz A/D CONVERTER LINE.

MODEL	BITS	TECH- NOLOGY	POWER DISSIPATION	PACKAGE
CXD 1172P	6	CMOS	70mW	DIP
CXD 1172M	6	CMOS	70mW	SOP
CXD 1175P	8	CMOS	90mW	DIP
CXD 1175M	8	CMOS	90mW	SOP
CXA 1096P	8	BIPOLAR	350mW	DIP
CXA 1096M	8	BIPOLAR	350mW	SOP
CXA 1296P*	8	BIPOLAR	350mW	DIP

*100% pin compatible with TRW's TDC 1048.

So gain the design advantage. With one of the most complete 20-MHz A/D converter selections anywhere.

Sony's.

For more information, call (714) 229-4197 today. Or write Sony Corporation of America, Component Products Division, 10833 Valley View St., Cypress, CA 90630, Attn: Semiconductor Sales. FAX (714) 229-4271.

SONY®

Sony is a registered trademark of Sony Corporation.

CIRCLE NO 174

Fortran program calculates op-amp noise

James S Taylor

James S Taylor & Associates, Fairborn, OH

Calculating the input-referred noise of an op-amp circuit isn't difficult, but making this calculation for several different op amps, over different bandwidths and for different circuit configurations, can become a chore. **Listing 1** is a Microsoft Fortran program that simplifies this task. It computes the total input-referred noise for an op-amp circuit (based on the test circuit of **Fig 1**), is flexible enough to handle a range of options, and runs on IBM PCs and compatibles.

The program prompts you for the external resistor

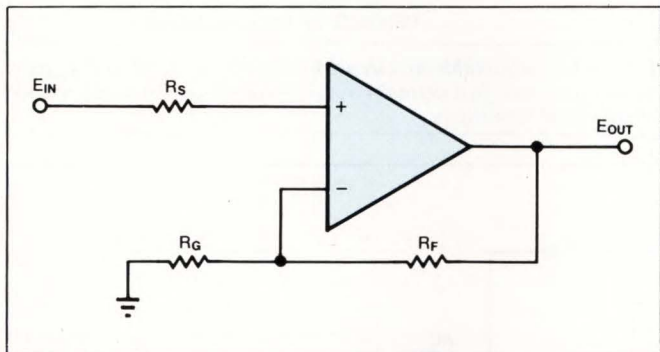


Fig 1—The program of **Listing 1** calculates the total circuit noise referred to the input of the op amp for this noninverting-gain configuration.

values and such op-amp noise parameters as noise-voltage and noise-current densities (**Listing 2**). (For those parameters, use a frequency well above the op amp's noise-corner frequency—1 kHz, for example.)

Listing 2 also includes an example of **Listing 1**'s output for the OP-27A op amp. The program presents the data inputs and the output on your CRT screen for verification before printing. Boltzmann's constant and the absolute temperature are listed in separate data statements, so you can easily modify the program to calculate the resistor's thermal noise at different temperatures.

EDN

References

1. Precision Monolithics Inc, *Application Note AN-15, Minimization of noise in operational amplifier applications*, Santa Clara, CA.
2. National Semiconductor Corp, *Application Note AN-104, Noise specs confusing?* Santa Clara, CA.
3. Signetics Corp, *Application Note AN-104, Explanation of noise*, Sunnyvale, CA.

LISTING 1—CALCULATION OF OP-AMP NOISE

```

D Line# 1      7      Microsoft FORTRAN77 V3.31 August 1985
2 C      NOISE .FOR
3 C      THE SOURCES OF NOISE IN AN OP-AMP CIRCUIT ARE:
4 C
5 C      1. THERMAL NOISE IN THE SOURCE RESISTANCE SEEN BY THE + INPUT
6 C      2. THERMAL NOISE IN THE SOURCE RESISTANCE SEEN BY THE - INPUT
7 C      3. NOISE CURRENT THROUGH THE SOURCE RESISTANCE AT THE + INPUT
8 C      4. NOISE CURRENT THROUGH THE SOURCE RESISTANCE AT THE - INPUT
9 C      5. INTERNAL OP-AMP NOISE WHICH APPEARS AS A VOLTAGE ACROSS THE
10 C      DIFFERENTIAL INPUT
11 C
12 C      REAL*4      IWN, K, LBW, NE, NI, NIN, NIP, NOISE,
13 C      &          N6, NRSP, NRSN
14 C      LOGICAL     NEW, AGAIN
15 C      CHARACTER*8 OPAMP
16 C      CHARACTER*1 ANSWER
17 C      DATA      K / 1.38E-23 /, T / 300.0 /, NEW / .TRUE. /
18 C OPEN FILES
19 C OPEN (UNIT = 1, FILE = 'CON')
20 C OPEN (UNIT = 2, FILE = 'CON')
21 C GET INPUT
22 C 1000 WRITE (1, 1) ' ', CHAR(27), 'I', '2', 'J'
23 C IF (NEW) THEN
24 C THE OP-AMP ID IS USED FOR LABELLING THE PRINTOUT
25 C WRITE (1, 2)
26 C READ (2, 3) OPAMP
    
```


AC circuit breaker has adjustable threshold

Kurt French
C F Electronics Inc, Commack, NY

Protecting sensitive electronic equipment from ac over-current conditions in the 100 to 300% range often proves to be difficult. At 125% of rated current, for example, a so-called "fast-acting" breaker probably won't trip at all (Fig 1), and a fast-acting fuse takes about 10 sec to blow. The fuse will blow in 0.02 sec at 300% of rated current, but damage can occur at that current level. The fast-acting breaker requires nearly 700% of rated current to respond in 0.02 sec.

The adjustable circuit breaker shown in Fig 2 responds in 0.02 sec under all conditions (provided you select a fast relay for K₁). For moderate overload conditions, then, it's preferable to the fuse or the fast-acting breaker. The toroid transformer (T₁) senses ac load current and produces an ac signal at the wiper

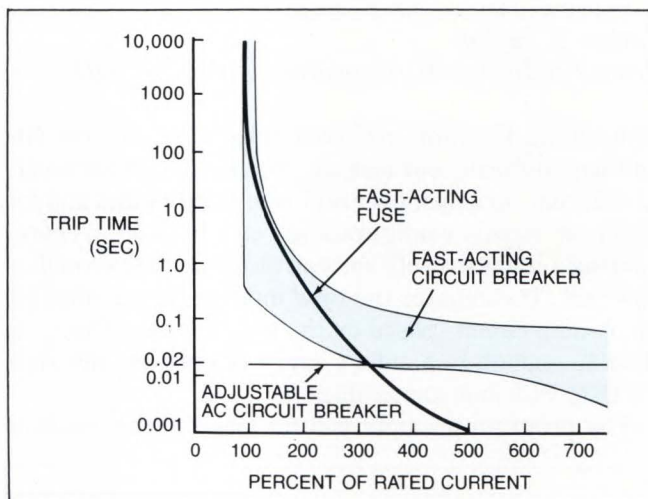


Fig 1—The adjustable ac circuit breaker shown in Fig 2 is faster than a so-called "fast-acting" circuit breaker or a fuse under moderate overload conditions.

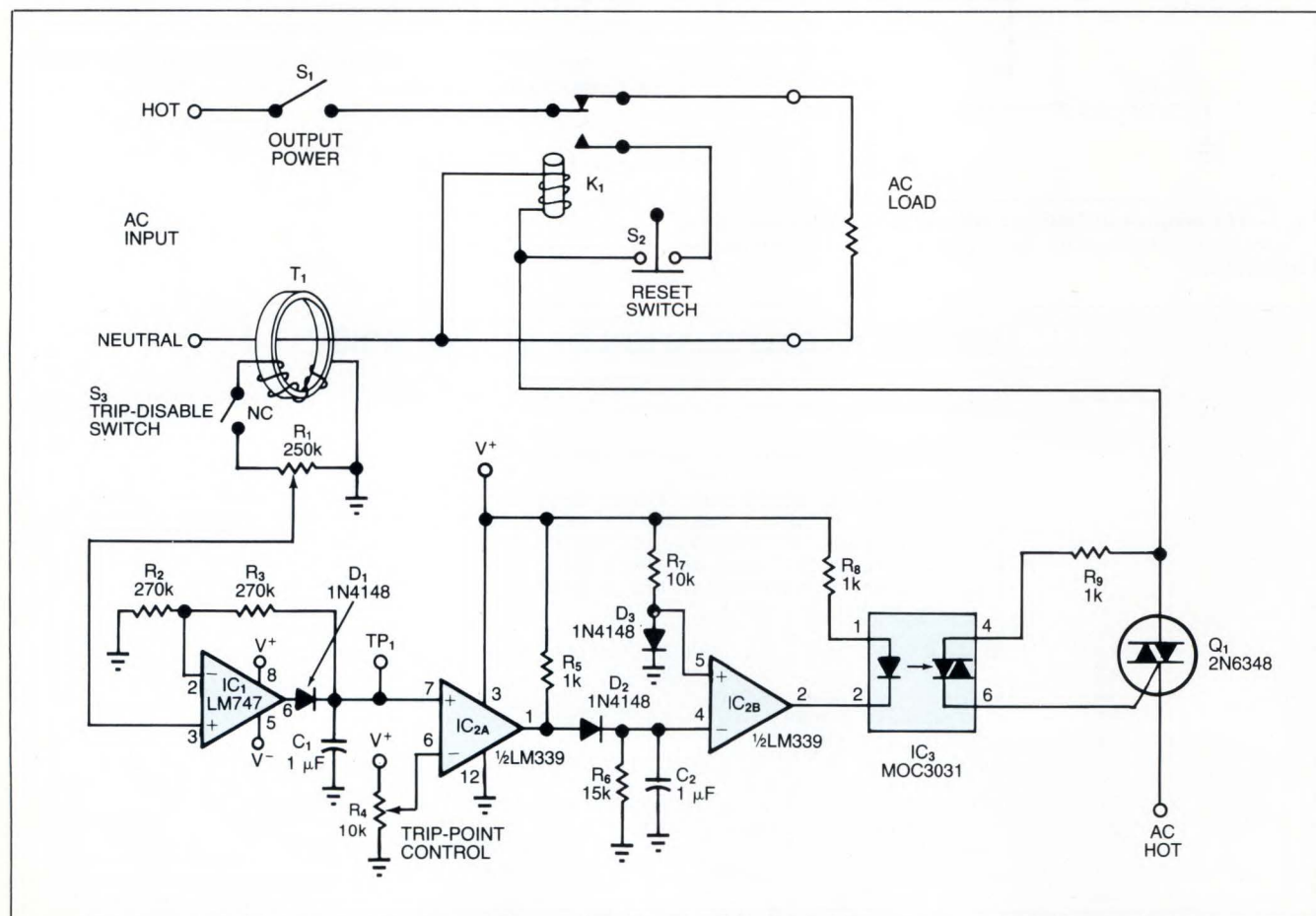


Fig 2—This ac circuit breaker features an adjustable trip point, high speed, and a fast relay controlled by an optically isolated triac. If you need additional protection for heavy overload conditions, you can connect a fast-acting fuse.

DESIGN IDEAS

of R_1 when switch S_3 is closed. Diode D_1 rectifies this signal to produce a positive voltage at the test point (TP₁). Because R_1 allows you to calibrate this voltage, the circuit accommodates a variety of current-sense transformers.

To calibrate the trip threshold, you apply the maximum expected overload and adjust R_1 until the TP_1

voltage is 0.7V below the positive saturation level for IC₁. Then you adjust R₄ for the desired trip point. To reset the circuit breaker after it has tripped, you must open S₁ or S₂.

EDN

Reconstruct missing sync pulses for VCR

James A Work Jr,
Syntex Corp, Palo Alto, CA

By using **Fig 1's** circuit, you can reconstruct the equalizing and vertical pulses that are often lost when a VCR (a Panasonic NV-8950, in this case) is in the pause or slow-motion mode. Without these pulses, the VCR's digitizer loses its sync at the top of the frame, causing horizontal distortion and instability (flag waving) at the

top of the digitized picture.

The circuit reconstructs the equalizing-pulse and vertical-sync-pulse intervals with compensating pulses. Switch S_1 selects normal-speed sync (circuit bypass) or slow-speed sync (circuit in line). **Fig 2** shows the waveforms at various points in the circuit. The comparator IC_1 picks off (via pin 7) the composite-sync information from the bottom of the composite video signal. One-shot IC_{2A} and type D flip-flop IC_3 form a pulse-


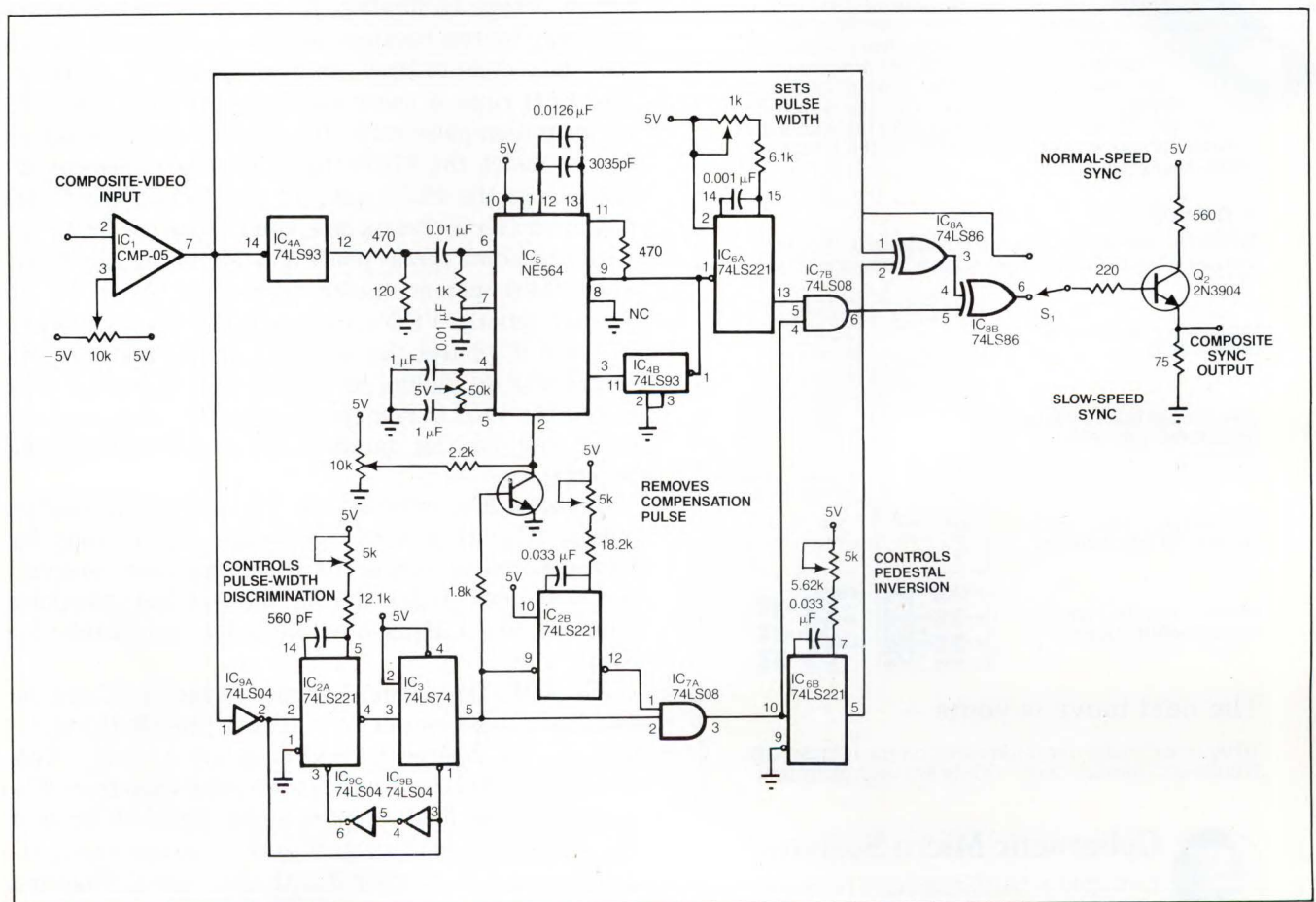


Fig 1—Your VCR won't lose sync in the pause or slow-motion modes when you use this circuit to restore the missing sync pulses.

What's Missing in this LCD Photo?

(answers below)

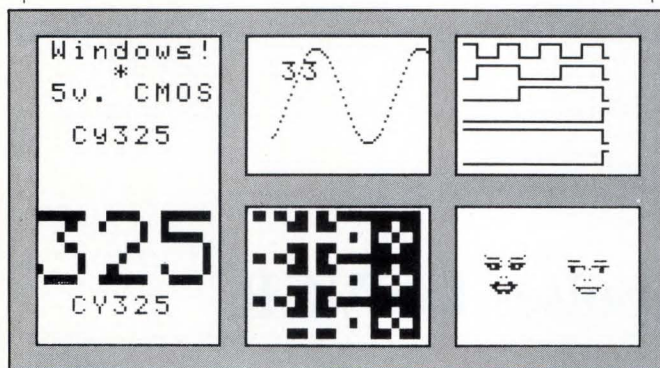

If you peeked at the answers, then you know it's Motion. In the actual LCD every one of the windows is in motion. Think for a minute how you would make six or seven unique motions *simultaneously* with the low level LCD controllers that you have seen. No way! Now think what your instrument or new system could do with dynamic text and graphics. Tests show that programmers can achieve animated presentations in only hours using the CY325.

The CY325 LCD Windows Controller Chip




lets you specify any of 250 built-in windows, or create your own with a single command; manage text and graphics with automatic cursor control; wrap or scroll text with window relative pixel plotting and clipping; read an A/D and write the waveform into the window; drive up to 6 I/O pins with logic waves, or use the 'soft-key' feature of the CY325 for menu management.


Answer:

Motion is missing in each of the windows in the photo. Text actually scrolls up in the top left window above, and:

Logic wave forms flow right to left.

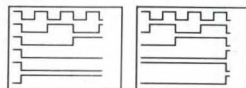

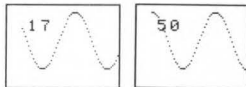Two actions here! Counter counts and sine wave advances!



Boy and girl wink, smile, and flirt in this window.



Pseudo random patterns change continuously.



The next move is yours —

Write or call today for information on the CY325 LCD Windows Controller Chip. Only \$75 each (\$20/1000).



Cybernetic Micro Systems

Box 3000 • San Gregorio, CA 94074
(415) 726-3000 • Telex: 910-350-5842

DESIGN IDEAS

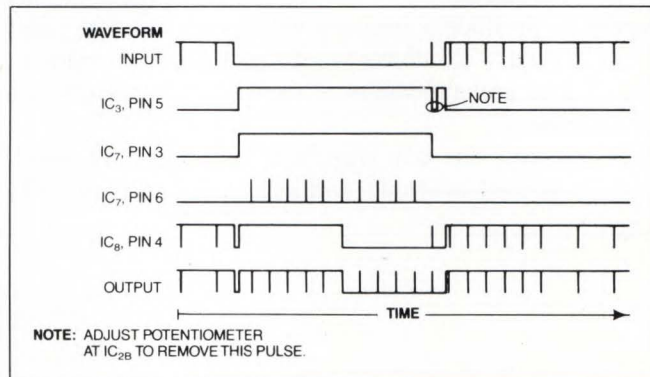


Fig 2—These waveforms show how Fig 1's circuit reconstructs the missing sync pulses.

width detector that ignores pulses longer than 6 μ sec. Because the horizontal-sync pulses are 4.77 μ sec long, the pulse-width detector (pin 5 of IC₃) changes state only when it sees the recorder's vertical-blanking pedestal. AND-gate IC_{7A} and 1-shot IC_{2B} shut off the pulse-width detector, IC₇'s pin-3 output. Another 1-shot, IC_{6B}, defines the first equalizing period before the vertical-sync-pulse interval via its output to pin 2 of XOR-gate IC_{8A}.

Phase-locked loop IC₅ generates the compensation pulses. A type JK flip-flop, IC_{4A}, divides the horizontal-sync rate by two because the PLL's VCO must have a 50% duty cycle to track its input frequency properly. The VCO runs at twice the horizontal-sync rate (the compensation-pulse rate); IC_{4B} divides the feedback by four to match the PLL's input frequency. The capacitors across the PLL's pins 12 and 13 and the 50-k Ω potentiometer across its pins 4 and 5 tune the VCO; the 1- μ F capacitors across pins 4 and 5 form the loop filter. The 10-k Ω potentiometer, connected from 5V to ground, sets the VCO's tracking range via pin 2. When IC_{2A} and IC₃ detect the vertical-blanking pedestal, IC₃ switches Q₁ on, pulling pin 2 of the PLL to ground. This causes the VCO to run open loop at the compensation-pulse rate for the duration of the vertical-blanking pedestal.

One-shot IC_{6A} provides the 4.45- μ sec compensation pulses; IC_{7B} gates these. Although RS-170 calls for 2.54- μ sec pulses during the equalizing-pulse intervals and 4.45- μ sec pulses during the vertical-sync-pulse intervals, the 4.45- μ sec pulses prove satisfactory for both.

IC_{8A} XORs the original composite-sync signal and the equalizing-pulse output from IC_{6B} to provide the envelope for the desired waveform at pin 4 of IC₈. This envelope is XORed with the gated pulse train from IC_{7B} to produce the final composite-sync signal at pin 6 of IC_{8B}. You can feed this signal to the digitizer's composite-sync input or combine it with the original video and send it to the composite video input.

EDN

Feedforward amplifier reduces distortion

Michael Ellis
Scientific Atlanta, Norcross, GA

You can employ feedforward techniques to reduce distortion in wideband RF amplifiers; the audio amplifier in **Fig 1** illustrates the feedforward principle, even though feedforward techniques offer no significant advantage in the audio-frequency range. (Both feedforward and feedback techniques reduce distortion in amplifiers, but each approach carries a distinct penalty. Feedback loops are subject to instability, whereas feedforward amplifiers are inherently stable but require an additional error amplifier.)

In **Fig 1**, the main amplifier has a gain of 10, but it introduces some distortion (D) in the amplification process. This component appears at the error ampli-

er's output ($-D$), but the signal components cancel at that amplifier's summing junction. In turn, the distortion component cancels in the output voltage divider, leaving the desired output of $-10V_{IN}$.

The feedforward technique allows amplification at RF frequencies without stability problems. In an RF amplifier, a directional coupler replaces the output 10-k Ω /10-k Ω divider. The coupler cancels the distortion while maintaining a 50 Ω (or 75 Ω) output impedance. CATV amplifiers use feedforward techniques, for example, to transmit 60 TV channels (54 to 450 MHz and higher) for 30 miles.

EDN

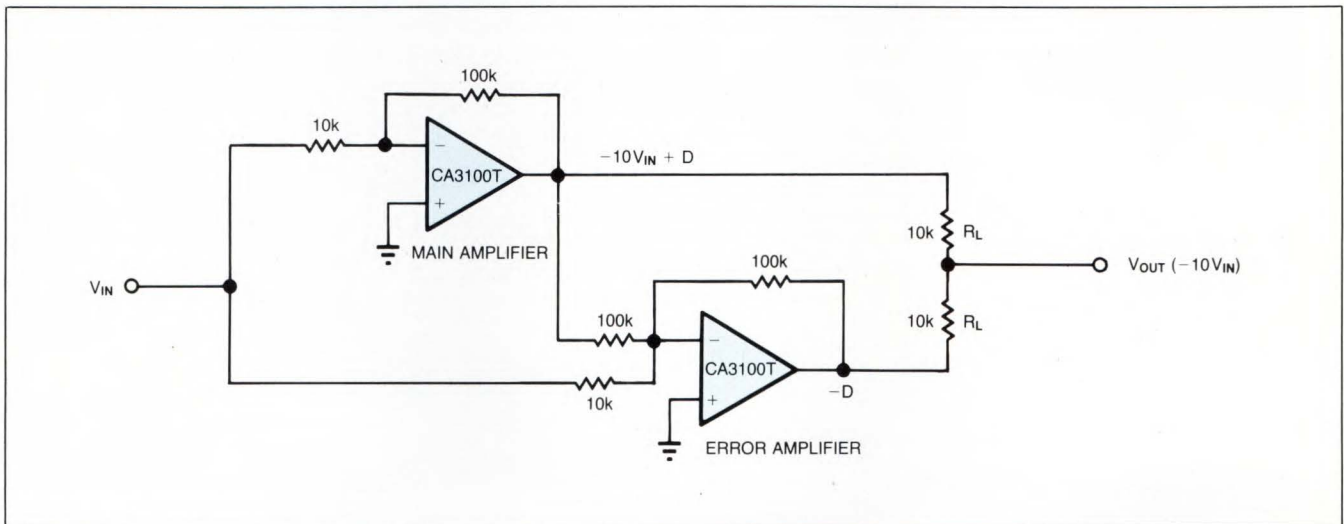


Fig 1—A feedforward error amplifier provides cancellation of the main amplifier's distortion products (D) while preserving the desired ($-10V_{IN}$) output.

Variable-gain amplifier uses matched FETs

Burton S Abrams and Daniel R Frey
Zeger-Abrams Inc, Glenside, PA


A FET can vary the gain of an amplifier by serving as a variable-resistance element, but because the FET's pinch-off voltage varies with temperature and from unit to unit, the control voltage for a particular gain is

not fixed. In **Fig 1**, though, a given control voltage $V_{CONTROL}$ produces the same channel resistance in the gain-control FET Q_{1B} for different FET pairs regardless of any variation in their parameters.

The lower circuit (IC_2) is a generalized inverting amplifier whose dc gain varies inversely with the channel resistance of Q_{1B} . The top half of the circuit

**We've discovered a way
to make a monitor
that will last for
more than eight years
between failures.**

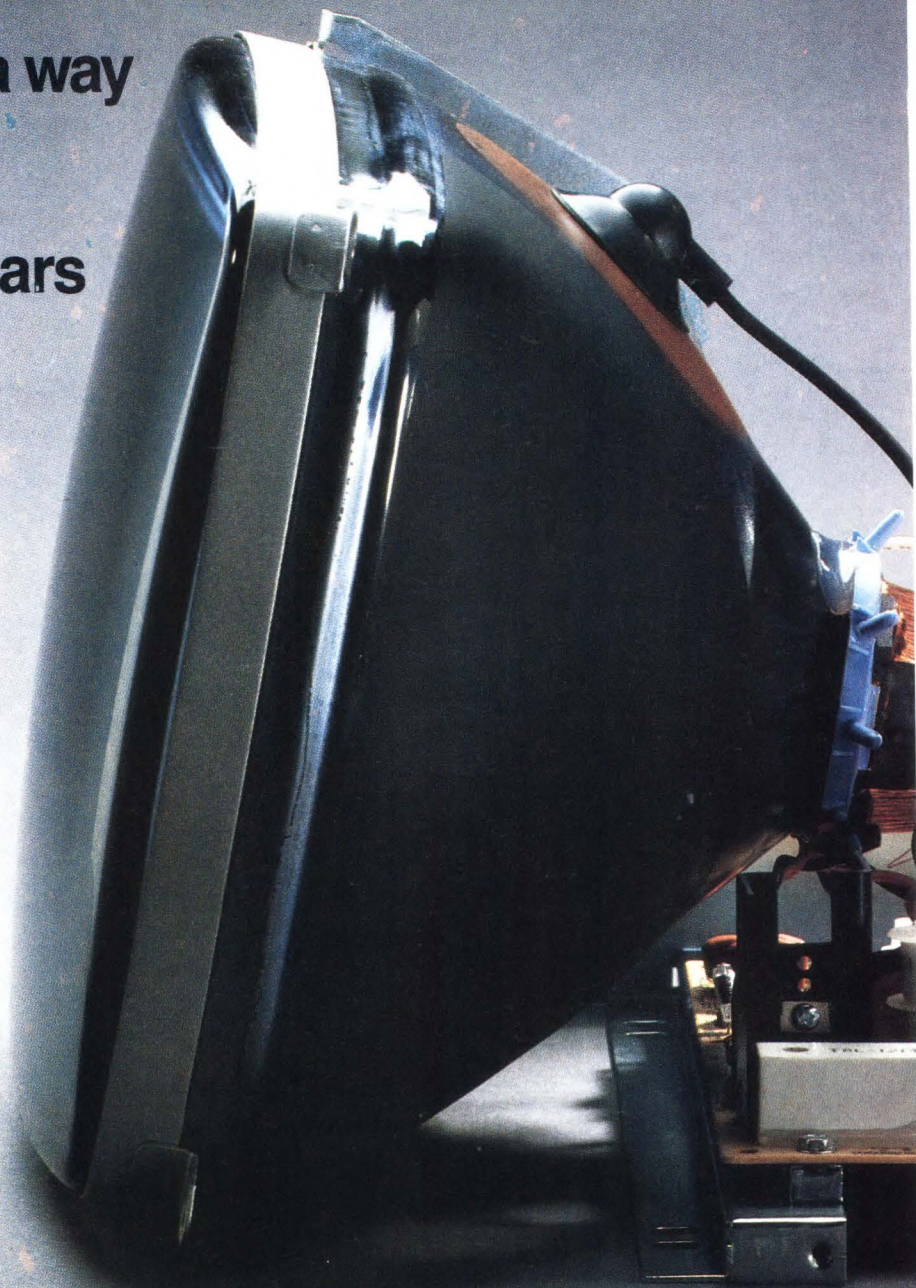**The real challenge
is to keep it busy
for that long.**



Eight years is a long time, more than 70,000 hours to be exact. In computer terms, it's several generations. And the simple truth is, it's hard to come up with a hardware application that won't be obsolete long before then. So why did we bother to create a computer monitor with a mean time between failure (MTBF) rating in excess of eight years of continual operation? Because we wanted to hold down the ultimate cost of ownership. By reducing failures in the field, we reduce service calls, warranty claims and customer complaints. Besides, we enjoyed the challenge. Now, it's your turn. For complete details on one of the most reliable lines of CRT displays the world has ever seen, call DisplayTEK, 1355 Holmes Road, Elgin, IL (312) 931-2100.



DisplayTEK

DESIGN IDEAS

(IC₁) generates a gate-to-source voltage for master FET Q_{1A} that applies to the slave FET Q_{1B} as well.

You apply the negative voltage V_{CONTROL} to set a constant current through R₁ that flows into the source of Q_{1A}. Op amp IC₁ adjusts Q_{1A}'s gate voltage to accommodate this current. Because the small positive voltage V_{BIAS} is fixed, Q_{1A}'s channel resistance must always assume the same value in response to a given value of V_{CONTROL}. And because Q_{1B} is a closely matched FET

with the same gate-source voltage, it will assume the same channel resistance as Q_{1A}.

V_{BIAS} should be much smaller than the FET's pinch-off voltage so that the FET will not operate in its saturation region. And R₁ must be large enough to avoid demanding a lower resistance than Q_{1A} can provide.

The circuit in Fig 2 includes additional refinements that compensate for other undesirable characteristics of Q_{1B}. Q_{1B}'s resistance is not only a function of gate-to-source voltage but of drain-to-source voltage as well, which varies with the input signal. The resulting output nonlinearity becomes more pronounced with an increasing signal level. In a familiar approach, the 10-kΩ resistors R₁ and R₂ mitigate this effect by applying about half the signal voltage to Q_{1B}'s gate bias voltage.

R₁ and R₂ also divide in half the gate voltage applied to Q_{1B} by the output of IC₁, so R₃ and R₄ are added to reduce Q_{1A}'s gate voltage by the same amount. Still, signal distortion is noticeable when Q_{1B}'s resistance is high. A diode-resistor network shunts Q_{1B} to compensate for this distortion at the expense of gain-control range. The circuit provides a 20-dB gain-control range for ±1V-max input signals, and it exhibits a maximum 7% output distortion—sufficient for use as an integrator within a phase-locked loop, for example. **EDN**

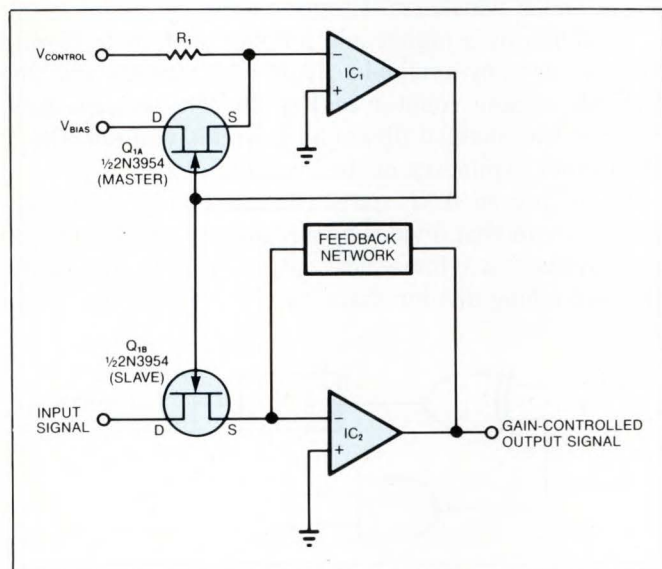


Fig 1—You use the negative voltage V_{CONTROL} to set this amplifier's gain. The matched dual-FET circuit ensures that a given gain is unaffected by the use of different FET pairs or by the effect of temperature on FET parameters.

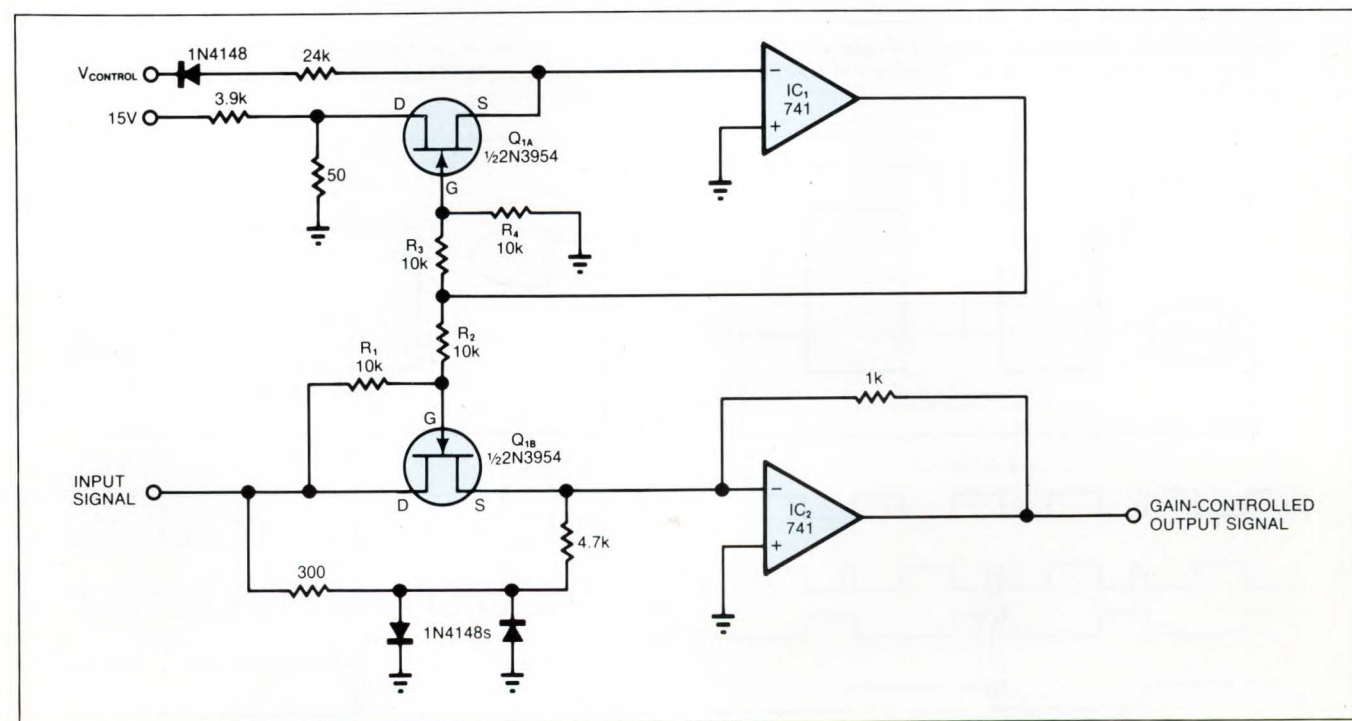


Fig 2—This circuit is similar to that of Fig 1, but it includes refinements that compensate for signal distortion caused by high FET resistance and for distortion caused by varying drain-to-source voltage.

Frequency divider generates 50% duty cycle

Andrzej Partyka
Ademco, Syosset, NY

Fig 1 is the general representation of a digital frequency divider that divides by any odd number ($M=2N-1$) and always produces an output with a symmetrical duty cycle. (The duty cycle for an ideal waveform is $t_L/(t_L+t_H)=t_L/T$, where L and H refer to the low and high portions of the waveform, and T is the period). The duty cycle of the divide-by-N circuit's output can range from $1/2N$ to $(1-1/2N)$.

Fig 2a shows the same divider circuit for the case $M=3$ (and therefore $N=2$). Because the duration of

each half period at V_{OUT} is $1\frac{1}{2}$ CLK periods, one output period equals three input periods. Note that you can simplify some applications by using the Q outputs for the A and B waveforms (in place of \bar{Q}).

To divide by a higher odd number such as 9 ($N=5$), you can use any available divide-by-5 circuit—eg, the 74XX90 decade counter in **Fig 2b**. The output duty cycle of the internal divide-by-5 circuit will not affect the output symmetry of the overall divider.

By adding an AND gate, you can build a programmable circuit that divides by any integer greater than 2 and produces a symmetrical output (**Fig 3**). The delay through a long divider chain, however, limits the maxi-

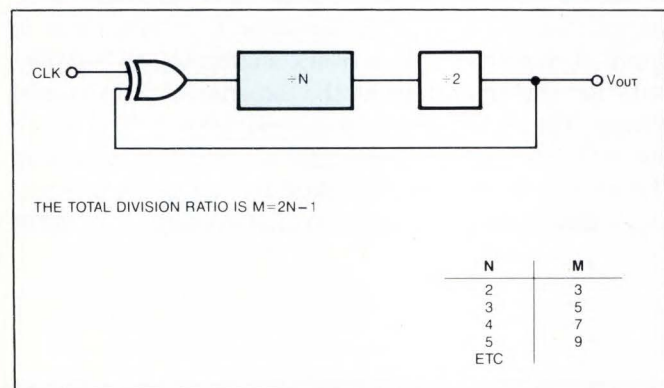


Fig 1—By choosing an appropriate value for N, you can divide the digital CLK frequency by a desired odd number and obtain a 50% output duty cycle.

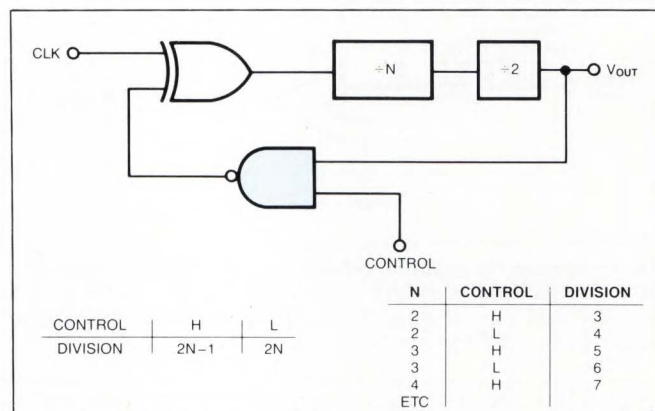


Fig 3—Adding an AND gate lets you program **Fig 1**'s circuit for even or odd division.

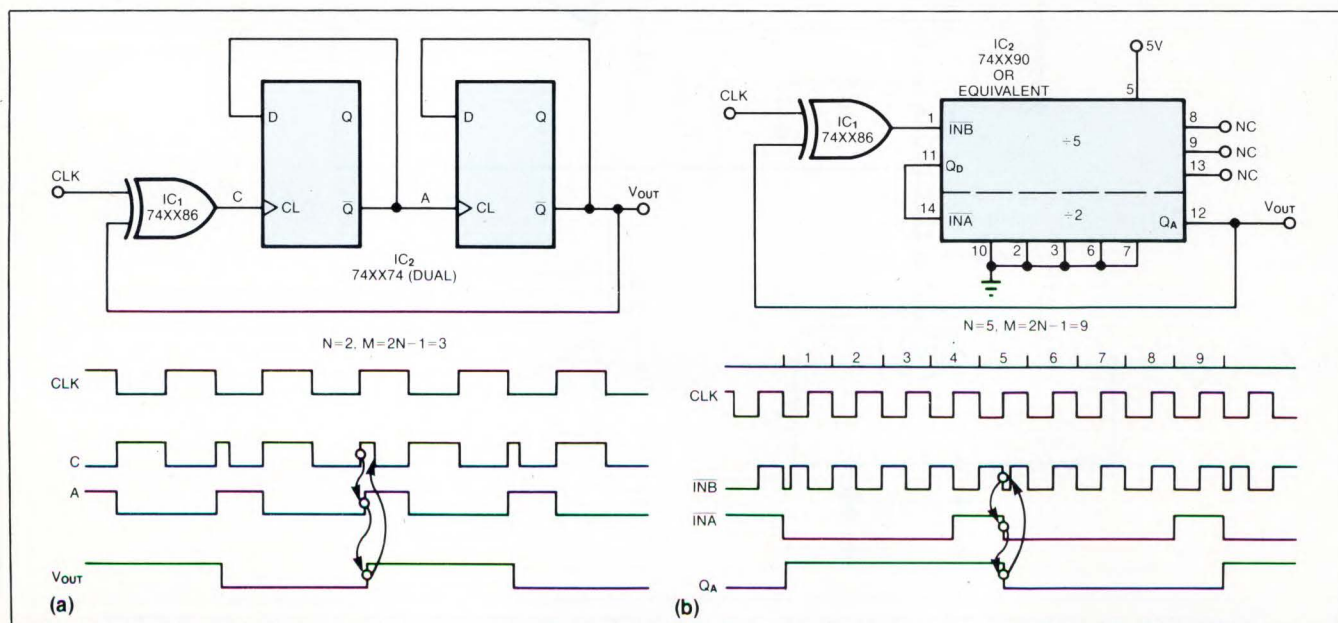


Fig 2—Here, you can see the **Fig 1** circuit's implementation of a divide-by-3 operation **(a)** and of a divide-by-9 operation **(b)**.

DESIGN IDEAS

imum CLK frequency; that is, the sum (t_{SUM}) of the propagation delays in the XOR gate, N-divider circuit, 2-divider circuit, and Control gate must be less than one-half the CLK period ($t_{\text{CLK}}/2$).

You can increase the maximum CLK frequency by adding a flip-flop (Fig 4). In this configuration, only the lower of two constraints ($t_{\text{FF}} < t_{\text{FF}}/2$ and $t_{\text{FF}} + t_{\text{SUM}} < (N - 1/2)t_{\text{CLK}}$) limits the CLK frequency. A circuit using LSTTL logic, for example, imposes a 5-MHz limit on Fig 3 and a 12.5-MHz limit on Fig 4.

EDN

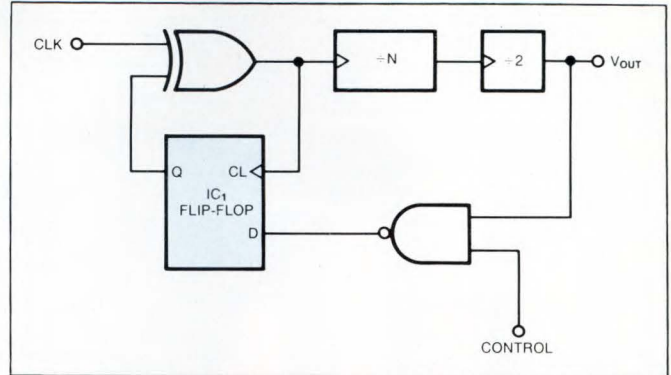


Fig 4—Adding a flip-flop (IC₁) to the Fig 3 circuit enables operation at a higher CLK frequency.

Improve voltage-controlled current source

Giovanni Stocchino,
FATME, Rome, Italy

Although you can use various methods to design voltage-controlled current sources, the design you use to eliminate one problem can easily lead to other problems. By using op amps and feedback, though, you can build a circuit that furnishes high precision, wide output-current range, high ac/dc output impedance, good temperature stability, low noise, and high input impedance.

As Fig 1 shows, you can use an emitter follower and

various circuit techniques to compensate for the inaccuracies introduced by parameters such as the transistor's base current and wiring resistance (see "Op amps compensate current source," EDN, September 15, 1983, pg 227). This approach, however, introduces the problems of lower input impedance and higher equivalent input-noise-voltage contribution from input resistors R_{IN} . Moreover, the op amp's input-offset current produces a temperature-dependent offset voltage across R_{IN} that increases the total output-current error. Finally, the error introduced by the transistor's temperature-dependent input impedance also reduces


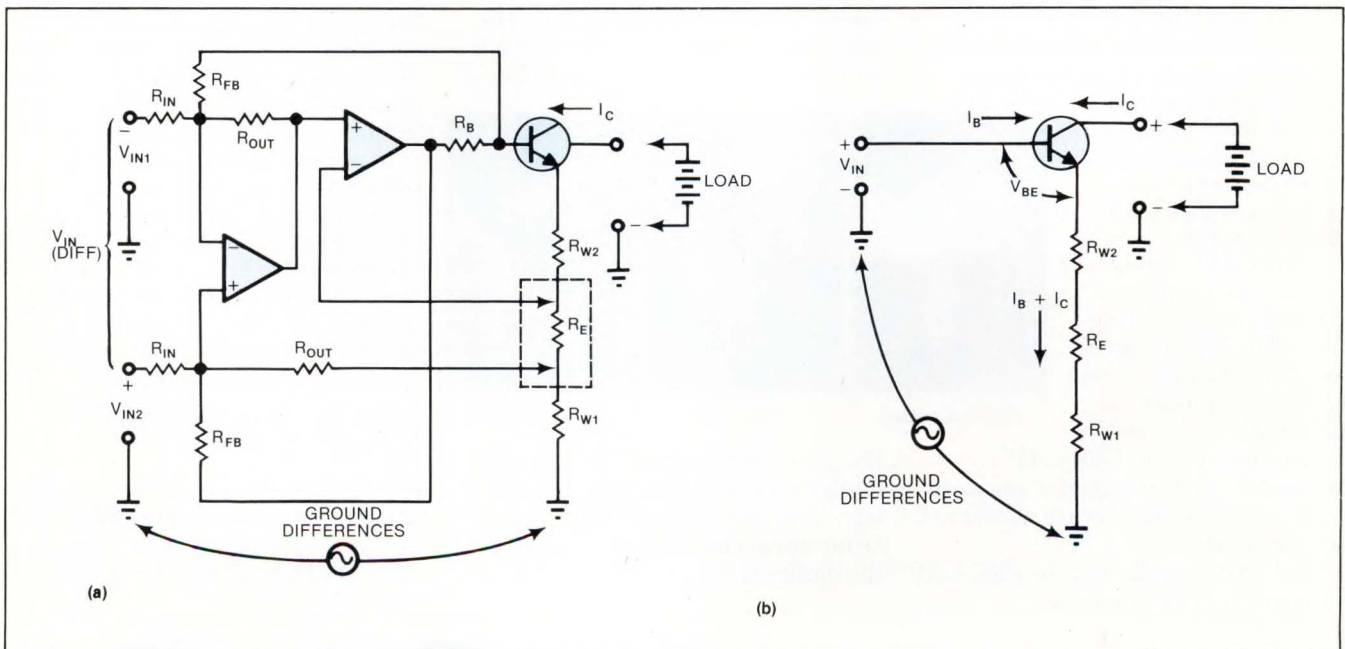


Fig 1—A circuit (a) incorporating several modifications to a basic emitter-follower current source (b) eliminates errors caused by wiring resistance, common-mode signals, and the transistor's finite base current. However, the modifications introduce offset-current and equivalent input-noise errors and give the circuit a low input impedance.

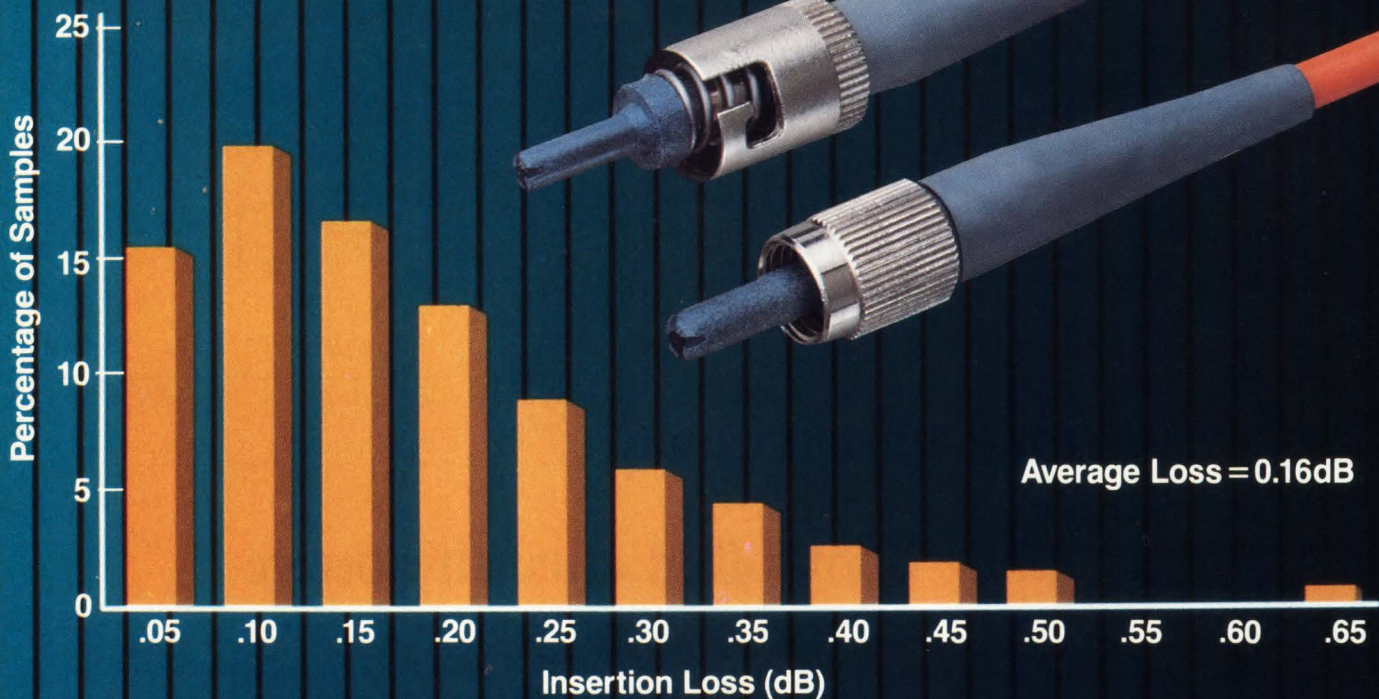

THE PRE-CAP™ CONNECTOR SYSTEM—A FIBER OPTIC CONNECTOR TECHNOLOGY THAT ANSWERS YOUR NEEDS FOR HIGH PERFORMANCE AND HIGH YIELD.

Now you can have consistent performance, high yield, and high reliability when you use our precision capillary PRE-CAP™ series fiber optic connector system. This new-technology system for glass optical fibers includes a line of the most common fiber optic connector designs—SMA and ST* types.

PRE-CAP™ series connectors combine a durable composite polymer alloy with the precision tolerance of a glass capillary to provide an extremely cost-effective connection system. PRE-CAP™ connectors provide superior alignment while matching the thermal stability of the glass fiber.

And, that's not all. With the PRE-CAP™

connector series, you get a simplified crimp and polish termination in a reduced amount of polishing time. The unique glass capillary design virtually eliminates the risk of over-polishing of

Both the SMA and ST types are highly suitable for manual or automated polishing and are adaptable on all styles of optical fiber cables. The SMA type is compatible with the 905 connector design, while the ST type features a spring-loaded bayonet lock.

In addition to connectors, the PRE-CAP™ connector series includes active and passive couplers, easy-to-use termination tooling, plus standard and custom cable assemblies. For more information or a demonstration of what PRE-CAP™ connector technology can do for you, call or write Thomas & Betts Corporation, Electronics Division, 1001 Frontier Road, Bridgewater, NJ 08807, (201) 685-1600.



Passive Couplers



Connectors



Active Couplers

the glass fiber because the fiber and capillary are uniformly polished as one. This uniform polishing means faster installation without sacrificing the quality of the connection.

*Trademark of AT&T Technologies.

To get literature immediately call:
1-800-344-4744

Thomas & Betts

DESIGN IDEAS

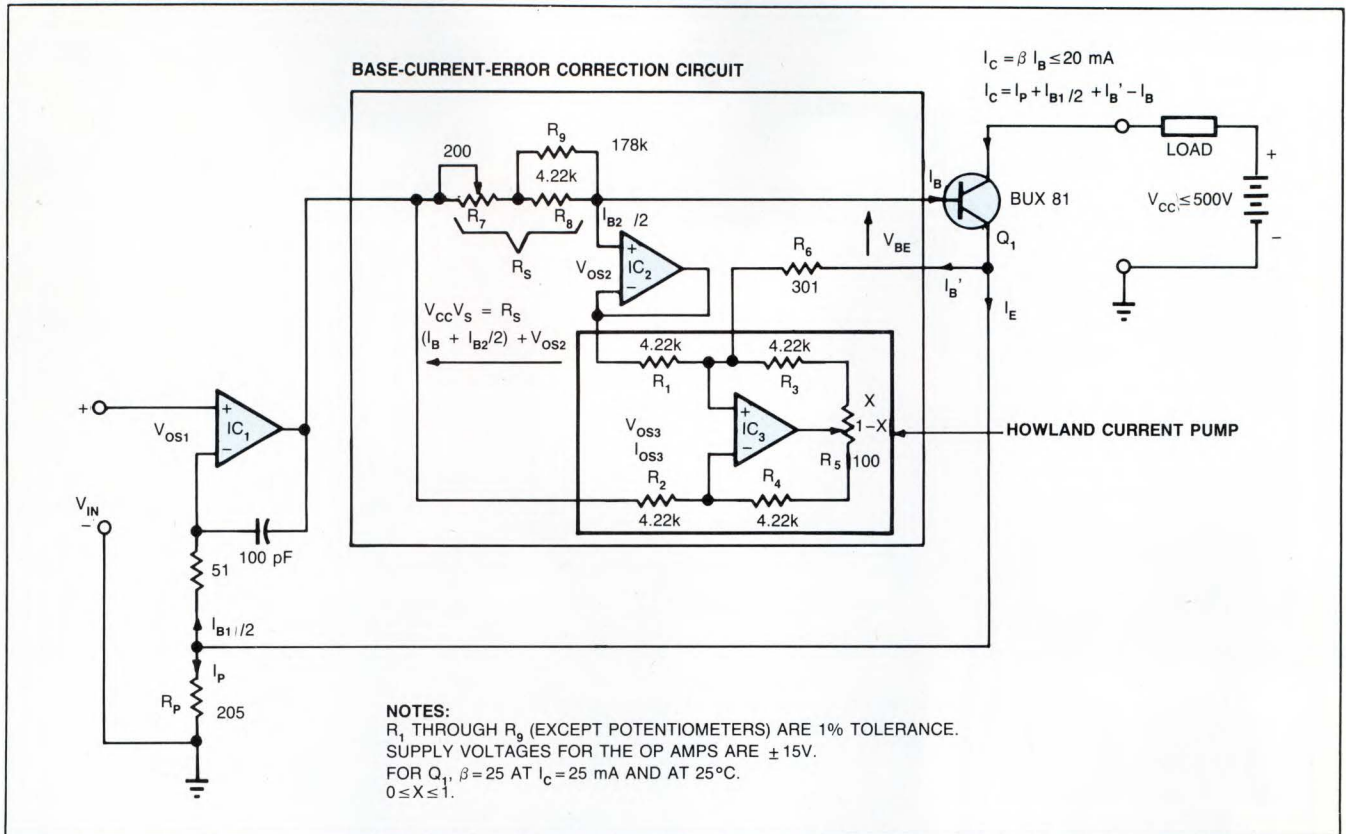


Fig 2—This improved voltage-controlled current source almost completely cancels base-current-induced error, has high input and output impedances, and features excellent compliance and a wide output range.

circuit accuracy. You can reduce this last error contribution by inserting a voltage follower between the transistor's base and feedback resistor R_{FB} .

Fig 2's voltage-controlled-current source uses a technique that almost completely cancels the error caused by the transistor's finite base current. The technique neither affects the circuit's input characteristics nor increases the error contributions from other sources. The circuit consists of the standard op-amp-plus-transistor current source (Q_1 and IC_1) plus the insertion of a base-current error-correction circuit (IC_2 and IC_3). The circuit's output current is given by the expression

$$I_C = \frac{V_{IN}}{R_P}$$

The circuit corrects the base-current error as follows. Q_1 's base current, I_B , causes a voltage drop across R_S . This drop ($I_B R_S$), through noninverting-buffer IC_2 , drives a Howland current pump consisting of IC_3 and resistors R_1 through R_6 (see "Improve circuit performance with a 1-op-amp current pump," EDN, January 20, 1983, pg 85). The Howland current pump's output,

$$I_B \approx I_{B'}$$

is then summed with the transistor's emitter current to cancel the emitter current's base-current component and thus leaves only the collector-current contribution. This process makes the voltage drop across R_P and the

feedback to IC_1 independent of base current. Thus, the circuit eliminates the base-current contribution error.

The expression for $I_{B'}$ is

$$I_B = \frac{R_S}{R_1} I_B + \frac{V}{R_S + X R_5} \left\{ \frac{R_4 + (1 - X) R_5}{R_2} - \frac{R_3 + X R_5}{R_1} \right\} \pm \epsilon \pm \gamma I_B, \quad (1)$$

where

$$V \approx \frac{R_6 R_5 I_B}{R_1} - V_{BE},$$

$$\epsilon \leq \frac{R_S}{R_1} \cdot \frac{I_{B2}}{2} + I_{OS3} + \frac{1}{R_1} (V_{OS2} + V_{OS3}),$$

$$\gamma \leq \frac{R_6}{R_1} \left(\frac{1}{A_0} + \frac{1}{CMRR} \right),$$

and

I_B = input bias current,
 I_{OS} = input offset current,
 V_{OS} = input offset voltage,
 A_0 = op amp open-loop gain,
 $CMRR$ = common-mode rejection ratio.

Because the circuit incorporates precision op amps, ϵ and γ have very low values; for example, $\epsilon \leq 50 \text{ nA}$ and $\gamma \leq 10^{-6}$.



Things Your Mother Never Told You About HV Power Supplies!

- 1.** *Your mother never told you* of the many advantages of Glassman high voltage technology over other design approaches. . .
- 2.** *Your mother never told you* that Glassman high voltage power supplies use air as the primary insulating medium in their high voltage structures. Our field-proven air insulation technique provides significant weight reduction and eliminates the unpleasant things associated with other dielectric mediums.
- 3.** *Your mother never told you* that Glassman employs the most advanced pulse-width modulated circuitry available in high voltage power supplies. Its use minimizes
- parts count and reduces complexity as compared to other designs.
- 4.** *Your mother never told you* when you need the most compact high power high voltage DC power supplies available, Glassman designs. . . manufacturers. . . and delivers them. On time, at competitive prices!
- 5.** *Your mother never told you* that Glassman has the widest range of high voltage switches available from. . . 1 watt to 15 kW, 0-1 kV to 0-600 kV, with unrivaled reliability. All backed by responsive service and a three year warranty!

And just like mother. . . Glassman gives you sound advice, loving support, and solutions to those problems that seem impossible. Don't you owe it to yourself to get all the facts on Glassman high voltage power supplies? Give us a call. The coffee's hot, the apple pie is fresh, and high voltage power supplies never were so good!

Glassman High Voltage Inc.

Route 22 (East)
Salem Industrial Park, PO Box 551
Whitehouse Station, NJ 08889
Telephone (201)534-9007
TWX 710-480-2839
FAX: (201)534-5672

CIRCLE NO 177

GLASSMAN HIGH VOLTAGE INC.



DESIGN IDEAS

For the circuit to operate properly, you must use low-temperature-coefficient resistors. Also, you have to adjust R_5 and R_7 to meet the following conditions:

$$R_S = R_1 \quad (2)$$

and

$$\frac{R_4 + (1 - X) R_5}{R_2} = \frac{R_3 + X R_5}{R_1} \quad (3)$$

When these conditions are satisfied, **Eq 1** reduces to

$$I_{B'} = I_B \pm \epsilon \pm \gamma I_B$$

and the circuit's output current is

$$I_C = I_P + \frac{I_{B1}}{2} + I_{B'} - I_B = I_P + \frac{I_{B1}}{2} \pm \epsilon \pm \gamma I_B \quad (4)$$

Bearing in mind that

$$I_B = \frac{I_C}{\beta},$$

where β is Q_1 's current gain, and that

$$I_P = \frac{(V_{IN} \pm V_{OS1})}{R_P},$$

then you can express d , the maximum deviation of the circuit's output current I_C from the ideal value

$$I_P = \frac{V_{IN}}{R_P},$$

using the expression

$$d = I_C - \frac{V_{IN}}{R_P} = \pm \left\{ \frac{\gamma}{\beta} \frac{V_{IN}}{R_P} + \frac{V_{OS1}}{R_P} + \frac{I_{B1}}{2} + \epsilon \right\} \quad (5)$$

$$= \pm 5 \times 10^{-8} \frac{V_{IN}}{R_P} \pm 90 \text{ nA}.$$

Note that this expression holds only when the conditions of **Eqs 2** and **3** are met. The prototype of this circuit has shown an accuracy better than 0.002% of full output (20 mA), with a ± 20 mA residual error. **EDN**

IC replaces mechanical-interlock switches

Charles E Murphy
Elcotel Inc, Sarasota, FL

As an alternative to mechanical-interlock switches or membrane switches with latches, **Fig 1**'s circuit debounces, latches, and displays status information for a group of eight pushbutton switches in which only one switch at a time is active. The circuit's only IC is an octal latch.

Closing any one of the switches turns on transistor Q_1 and discharges capacitor C_2 . Current through Q_1 then charges C_1 , causing a positive transition at IC_1 's CLK input (pin 11), which turns on the LED for that switch. The LED remains on until you depress another switch. Because the CLK input is edge-triggered and remains high until you release all the switches, two or more switch closures cannot register at one time unless they occur within approximately one millisecond.

Capacitor C_1 provides a delay that debounces each switch closure. Capacitor C_2 causes Q_1 to turn on briefly at power-up, which produces a pulse at IC_2 's CLK input, ensuring all LEDs are off by latching all ones at the Q outputs of IC_1 . **EDN**

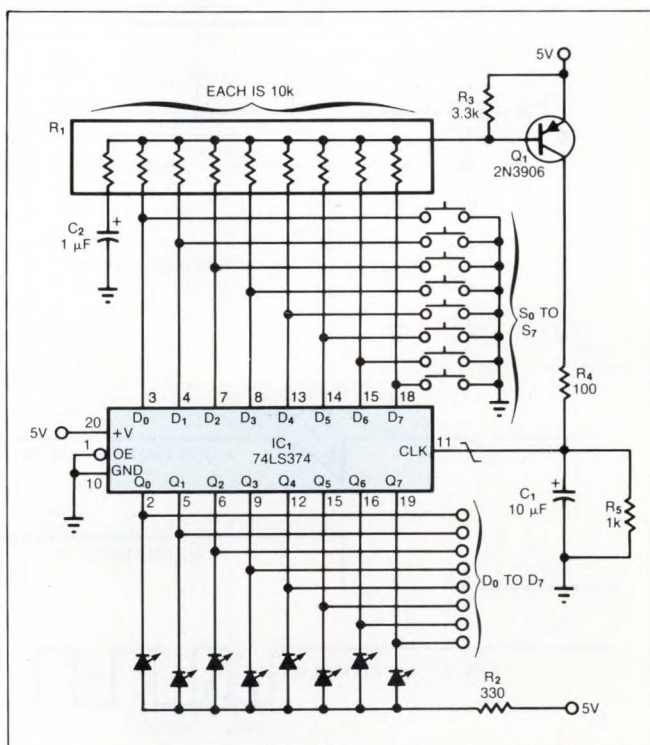


Fig 1—This single-IC circuit debounces a group of eight pushbutton switches, latches the last switch closure, and provides an LED indicator for the currently active circuit.

Burglar-alarm circuit uses one chip

Jacek Bartys

Alpha, Marco Electronics Div, Kraków, Poland

The single-chip burglar-alarm circuit shown in **Fig 1** uses a dual 556 timer, draws 10 mA of standby current, and generates a pulsing alarm signal that conserves battery energy. Once activated, the alarm will remain

on, independent of the subsequent state of any of the sensors. The sensors support both deferred and immediate-action modes. You can attach this circuit to your car's internal lighting circuitry using a single wire and a relay.

To arm this circuit, you open your car door and close switch S_A . The switch discharges capacitor C_4 and holds


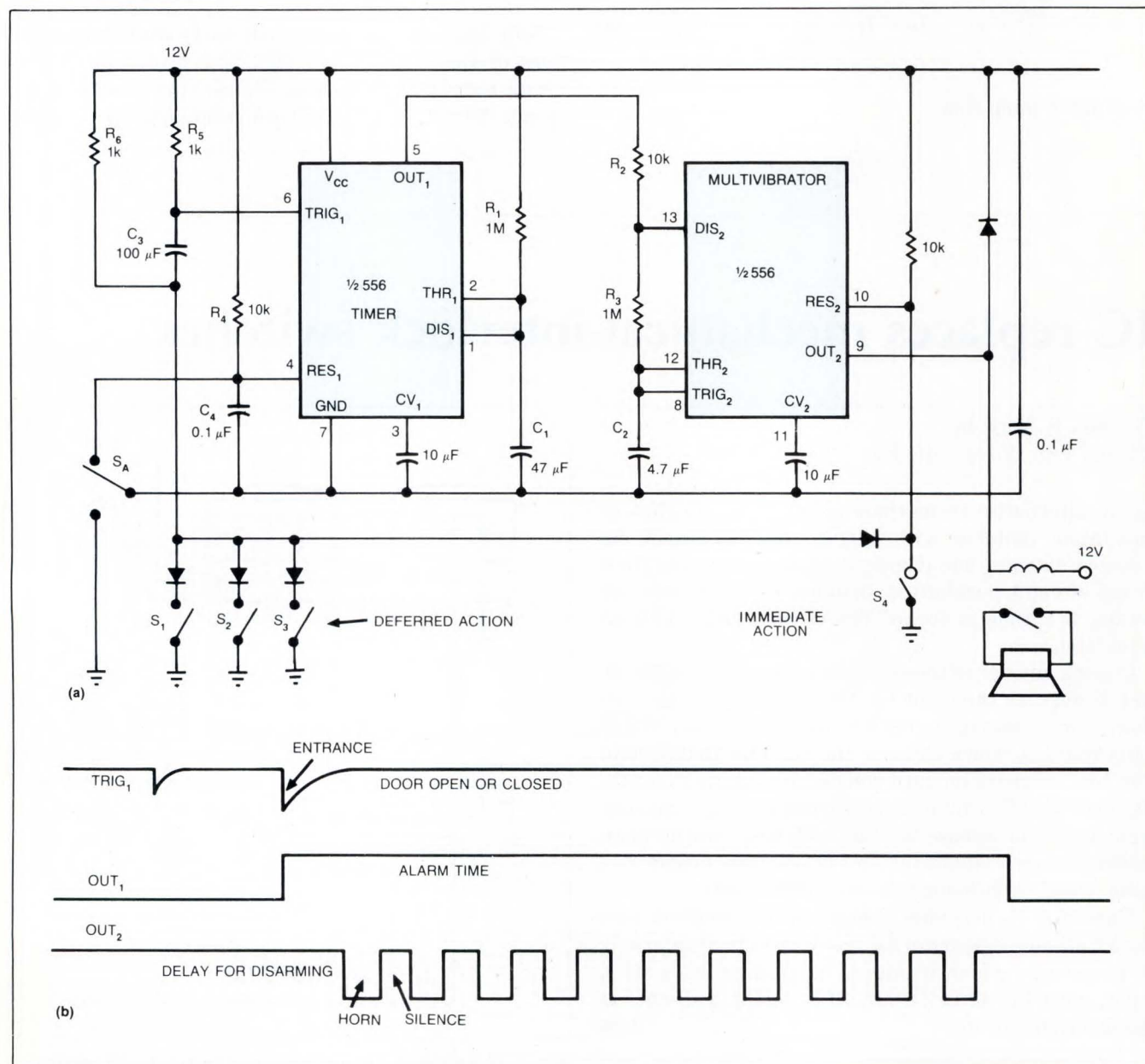


Fig 1—This burglar-alarm circuit (a) draws 10 mA of standby current and generates a pulsing alarm signal that conserves battery energy. You can connect this circuit to the lighting circuit inside your car using a single wire and a relay. The timing diagram (b) demonstrates that, while the timer's output is high, output 2 will cycle, turning the horn on and off.

SRAMs

Our New SRAMs Haul Access.

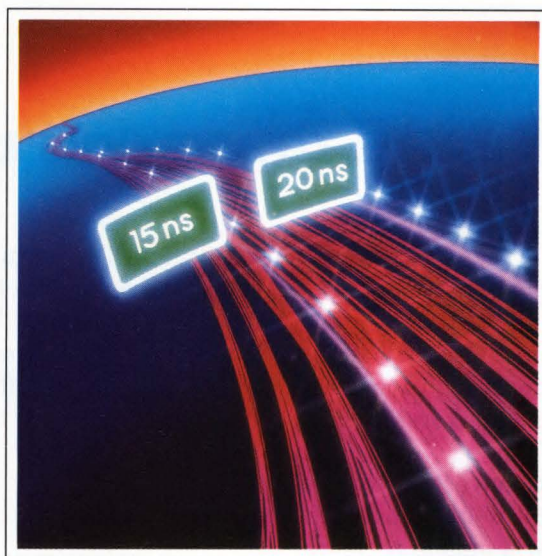

At 15 nsec, Our SRAMs Really Tear Up The Track.

If you've been wondering where to find fast SRAMs lately, we have good news for you. Now you can look to Logic Devices—the logical alternative.

Our new family of CMOS SRAMs gives you more options for high-end applications, where you have to match fast CPU speeds. They're available in speed categories from 15 to 45 nsec. So even your high-performance RISC and 32-bit micro designs can forget about wait states.


Because these parts just plain haul access. But without making

you pay a power penalty. Their advanced CMOS technology runs as low as 340 mW in active mode, and 25 mW in standby. Plus they feature proprietary Auto Powerdown™ circuitry

and 2 volt data retention, making them ideal for battery backup operation. And since these

parts are plug-compatible with industry-standard SRAMs, you have a clear upgrade path to higher performance. We've revved up production for delivery today, on all popular organizations, including 64K x 1, 16K x 4 and 8K x 8—in a variety of package types.

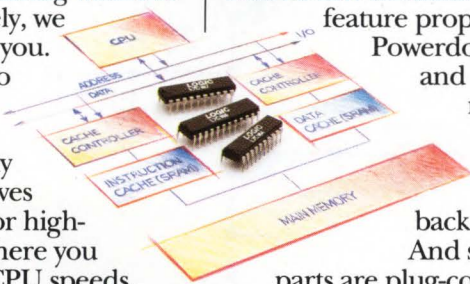For full details, call us today toll free at (800) 851-0767; in California, (800) 233-2518.



DEVICE	SPECIAL FEATURES	MAX. t_{acc} (ns)
L7C167 16Kx1*	SEP. I/O	12
L7C168 4Kx4*	COM. I/O	15
L7C170 4Kx8*	COM. I/O W/OE	15
L7C171 4Kx4*	SEP. I/O TRANSP./WRITE	15
L7C172 4Kx4*	SEP. I/O HI.IMP./WRITE	15
L6116 2Kx8*	COM. I/O W/OE	20
L7C187 64Kx1	SEP. I/O	20
L7C164 16Kx4	COM. I/O 1 CHIP ENABLE	25
L7C165 16Kx4	COM. I/O 2 CHIP ENABLES + OE	25
L7C166 16Kx4	COM. I/O 1 CHIP ENABLE + OE	25
L7C161 16Kx4	SEP. I/O TRANSP./WRITE	25
L7C162 16Kx4	SEP. I/O HI.IMP./WRITE	25
L7C163 16Kx4	SEP. I/O HI.IMP./WRITE	25
L7C165 16Kx4	COM. I/O 2 CHIP ENABLES + OE	30

* PRELIMINARY

Or write: Logic Devices, Inc., 628 East Evelyn Avenue, Sunnyvale, CA 94086; Telex 172387.

CIRCLE NO 178

LOGIC
DEVICES INCORPORATED

DESIGN IDEAS

the timer (one half of the 566 IC) in a reset state to prevent false triggering while you're arming the circuit. When you close your car door, the circuit enters a standby mode.

If the door is then reopened, the sensors apply a negative-going pulse to trigger 1. Output 1 then goes high and stays high, enabling the alarm for $1.1R_1C_1$ sec. Output 1's high state triggers the multivibrator (the other half of the 566), which begins to cycle after a delay equal to $1.1(R_2+R_3)C_2$ sec. As long as the timer's output stays high, the multivibrator will continue to cycle, turning the horn off and on at 3.3-sec intervals.

During the interval between the time that the timer's output goes high and the time that the multivibrator's output goes low, you can disarm this circuit using switch S_A . To prevent false triggering caused by switch contacts (switches 1, 2, and 3) that may bounce when you're closing the door, you should make the R_6C_3 time constant as large as possible. In addition, capacitors C_1 and C_2 should be tantalum types and should exhibit leakage of less than $1\text{ }\mu\text{A}$ at room temperature. **EDN**

Low-power RS-232C driver operates from 5V

Mark Walczak

Microcontrol Pty Ltd, Monterey, Australia

The circuit in **Fig 1** draws only 4 mA from a 5V supply while driving a standard RS-232C receiver. In contrast, a 1488 quad-driver IC draws 10 to 20 mA from each of its two supplies.

The system clock drives a dc/dc converter that produces -3.4V . Frequency can range from 0.5 to 8 MHz, but a range of 0.5 to 1 MHz will minimize power

dissipation. The circuit output withstands direct shorts to ground or to either of the supplies ($\pm 12\text{V}$ max). In place of the 74HC04 high-speed CMOS driver shown, you may want to substitute miscellaneous spare gates; one noninverting buffer, for example, can replace the two inverting types that receive the UART signal.

EDN

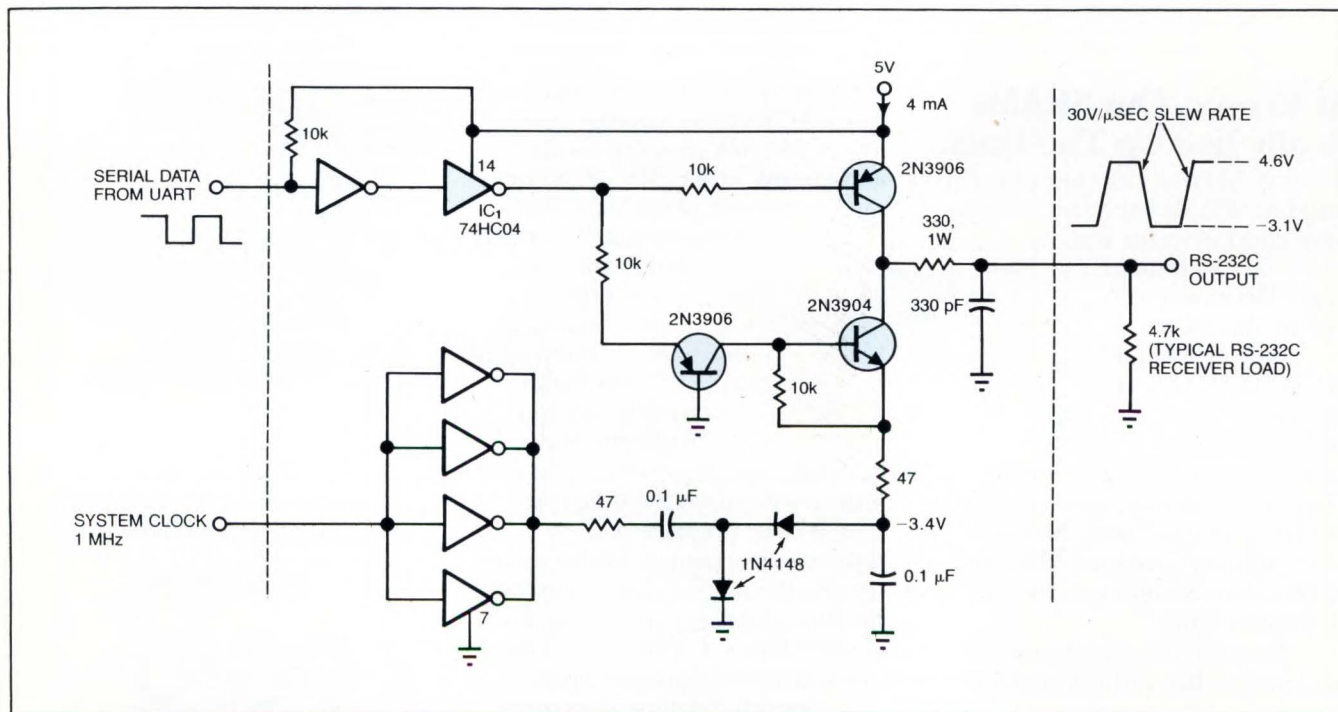


Fig 1—You can build an RS-232C driver using a CMOS IC and three transistors. Power consumption is 20 mW.

DON'T GET CAUGHT IN THE ASIC SPEED TRAP



Winning in Design Verification Demands Highest Speed And Lowest Elapsed Time. Topaz-V Gives You Both.

There's a significant difference between test rate and testing time. That difference could add hours, days or even weeks to your VLSI design verification effort. Don't be trapped by only comparing the obvious.

The Topaz-V family of VLSI Design Verification Systems redefines the meaning of speed—concentrating on how fast it can work for you and your ASIC verification requirement. Not simply how fast it can run.

These fifth generation systems incorporate the revolutionary, new virtual vector memory (V²M) architecture. It allows large vector sets to be downloaded, edited, and actively maintained on line. 'What if' analysis takes only seconds; simply change the set-up or vector and press 'start.' Time-consuming recompiles, vector re-downloading, and use of multiple vector pages are completely eliminated, slashing characterization time. Coupled with the system's 110 MHz test rate, 1.5 V/ns slew rate, 544 I/O pins, and 0.5 Gigabit per second communication interface, it will characterize your most complex device.

The Superior Solution to Prototype Testing, Failure Analysis, Quality Assurance, and Low Volume ASIC, VHSIC and VLSI Production

Specify Topaz-V. Thoughtfully engineered to satisfy your requirements for shorter test time, higher speed and greater accuracy.

Don't be caught in the ASIC speed trap. Look beyond the obvious. Redefine what speed and time really mean to you, and to your next new product's time to market.


Demand a demonstration of the Topaz-V systems; designed to meet your needs for high performance, accuracy and throughput into the decade of the Nineties. Then decide for yourself.

HILEVEL
TECHNOLOGY, INC.

At The Leading Edge of ASIC Verification

31 Technology Drive
Irvine, CA 92718
(714) 727-2100 • FAX 714-727-2101


CIRCLE NO 179

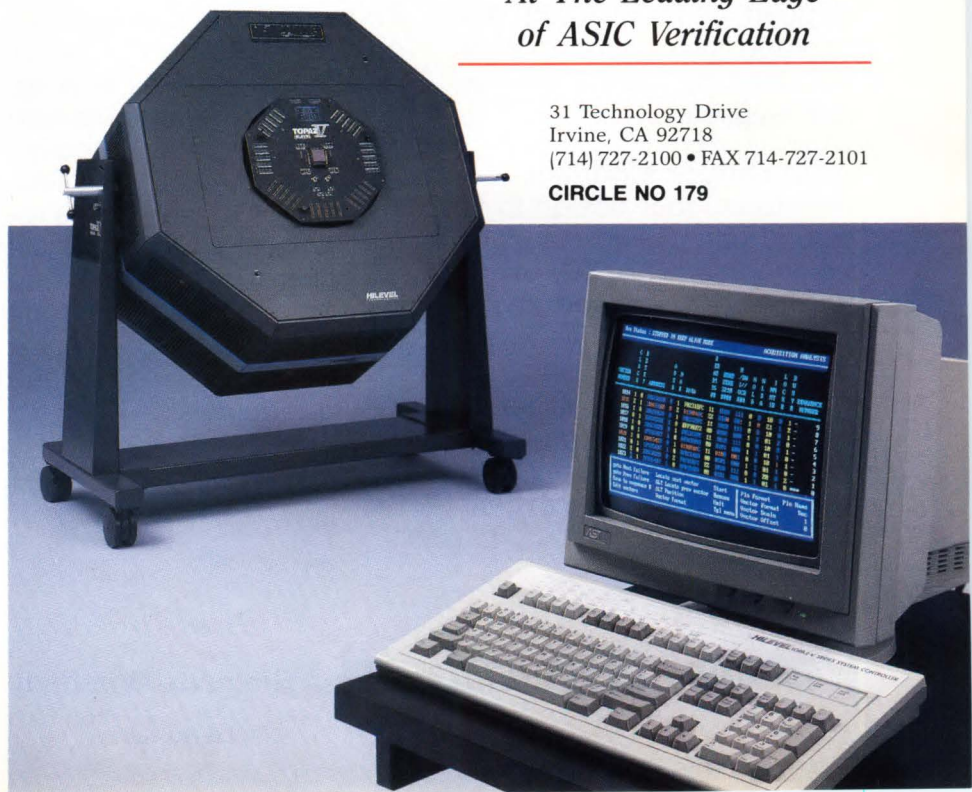

**DIAL TOLL FREE:
1-800-HILEVEL**

In California, 1-800-541-ASIC

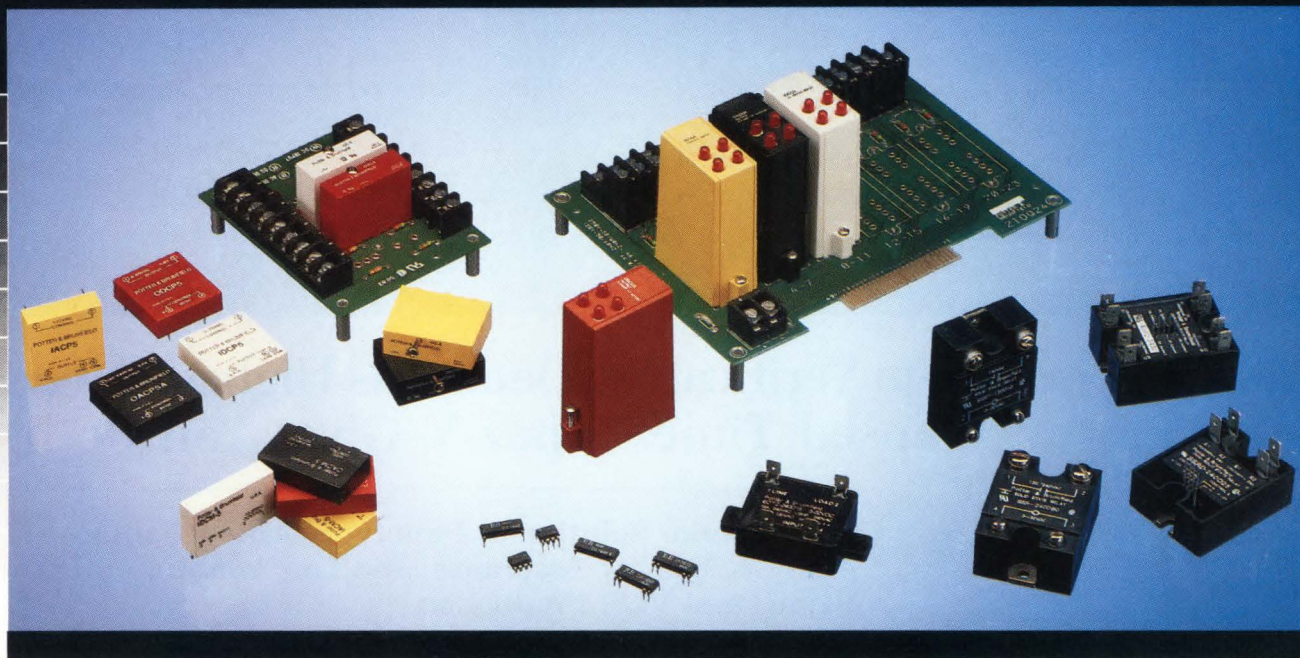Potter & Brumfield offers the solid state I/O module and relay options you need.



Expanded Offering

New product additions to Potter & Brumfield's already-broad line provide you an even greater variety of solid state products, unmatched in the industry. Now you can select solid state input/output modules and relays with the package style, performance and features just right for your application.

Input/Output Modules

Why force your design to fit around one or two standard configurations? P&B offers six different package styles for design flexibility. From plug-in quad modules to surface-mountable DIP units, our optically-isolated I/O modules provide the options and the traditional quality you expect from Potter & Brumfield.

Solid State Relays

Our new family of chassis mount relays can switch from milliamps up to 110 amps. These relays in our familiar "hockey-puck" case offer many options you might never have imagined in an SSR. Zero-voltage or random turn-on. AC or DC input. Triac or paired-SCR switches and one, two or even four outputs help open the door to your creative design. At the other end of the spectrum, DIP solid state relays put reliable P&B solid state switching of loads up to 1 amp right on your printed circuit board. And you have a choice of conventional or surface mount terminals.

Stock Availability

Most models are available from stock through our nationwide network of authorized stocking distributors, backed by our extensive factory inventory.

Find Out More

Free literature is yours for the asking. Contact us today for details on our growing line of solid state input/output modules and relays. Potter & Brumfield, A Siemens Company, 200 South Richland Creek Drive, Princeton, Indiana 47671-0001.

Call toll-free 1-800-255-2550 for the P&B authorized distributor, sales representative or regional sales office serving your area.

Potter & Brumfield A Siemens Company

Amp provides 100V common-mode range

Mark Stitt

Burr-Brown Corp, Tucson, AZ

The unity-gain amplifier of **Fig 1** can reject common-mode voltages as high as 100V. For an application that does not require galvanic isolation, this circuit is an inexpensive alternative to the conventional isolation-amplifier solution.

IC₁ is a monolithic gain-of-10 difference amplifier. By reversing normal connections to the on-chip resistor network, you place 100-k Ω resistors (instead of the 10-k Ω ones) at the amplifier's input, which attenuates the normal- and common-mode signals by a factor of 10. Then, resistors R₁, R₅, and R₆ form a T network in the feedback path that boosts the normal-mode gain to unity.

Because the addition of R₅ and R₆ degrades common-mode rejection by unbalancing the internal resistor ratios, you should restore the balance by adding about 158 Ω (R₇) in series with R₃. A fixed-value R₇ that differs by 2% from the T network's equivalent value degrades CMR by only a few dB, but note that IC₁'s CMR is already 20 dB below its specified value (100 dB min) because the amplifier is operating at a gain of 0.1 instead of 10. You can improve the CMR by using a 500 Ω potentiometer for R₇, as shown.

The differential-gain accuracy is within 2% if you use 1% resistors for R₅ and R₆. Adjusting the R₆/R₅ ratio can improve the gain accuracy, but calibration is diffi-

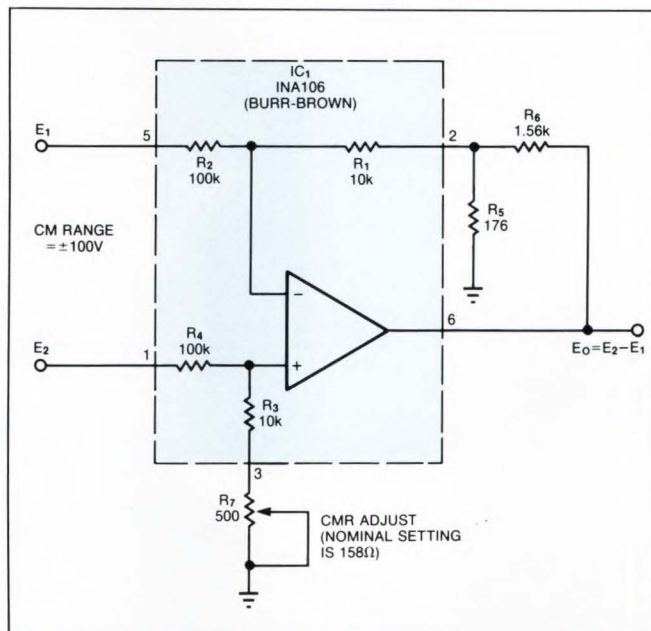


Fig 1—This amplifier offers unity gain to $E_2 - E_1$ signals while rejecting common-mode voltages as high as $\pm 100V$.

cult because the gain and CMR adjustments interact. You can eliminate this interaction and improve the gain accuracy by using the **Fig 2** circuit.

In **Fig 2**, IC₂ preserves IC₁'s CMR by buffering the R₅/R₆ network. Again, IC₁'s gain-of-0.1 connection reduces the guaranteed CMR by 20 dB—to 80 dB min. (This CMR estimate is reliable because the IC₁ ampli-


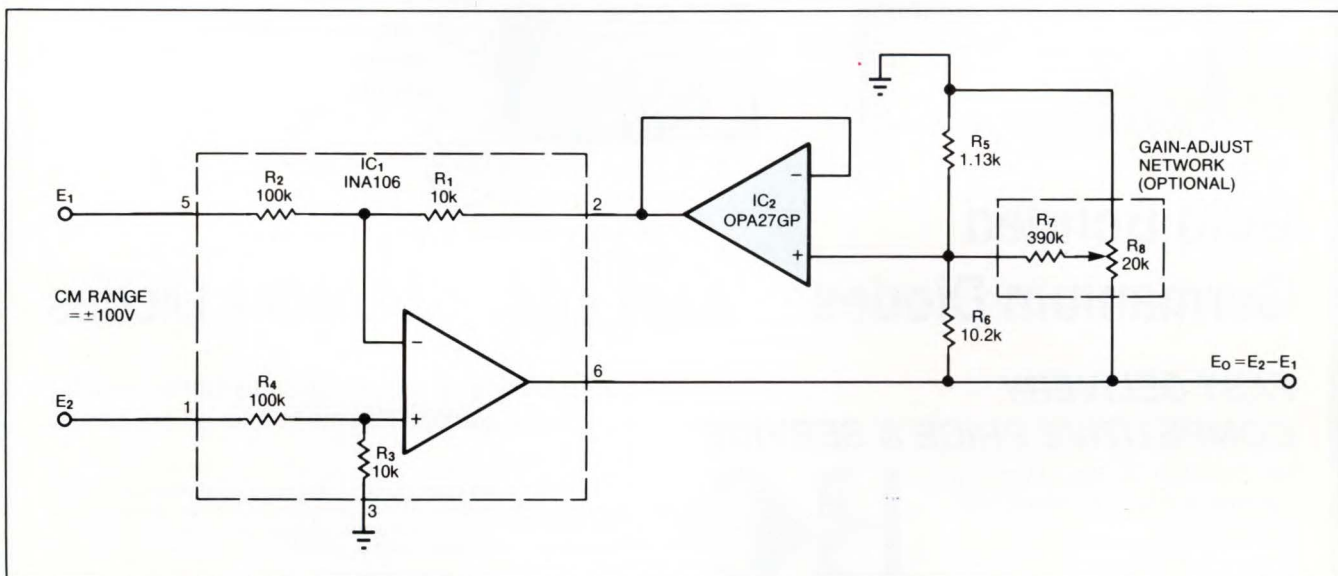


Fig 2—Adding an op amp to the **Fig 1** circuit eliminates interaction between the gain-adjust potentiometer and the CMR-adjustment pot (not shown).

VME Dream Card

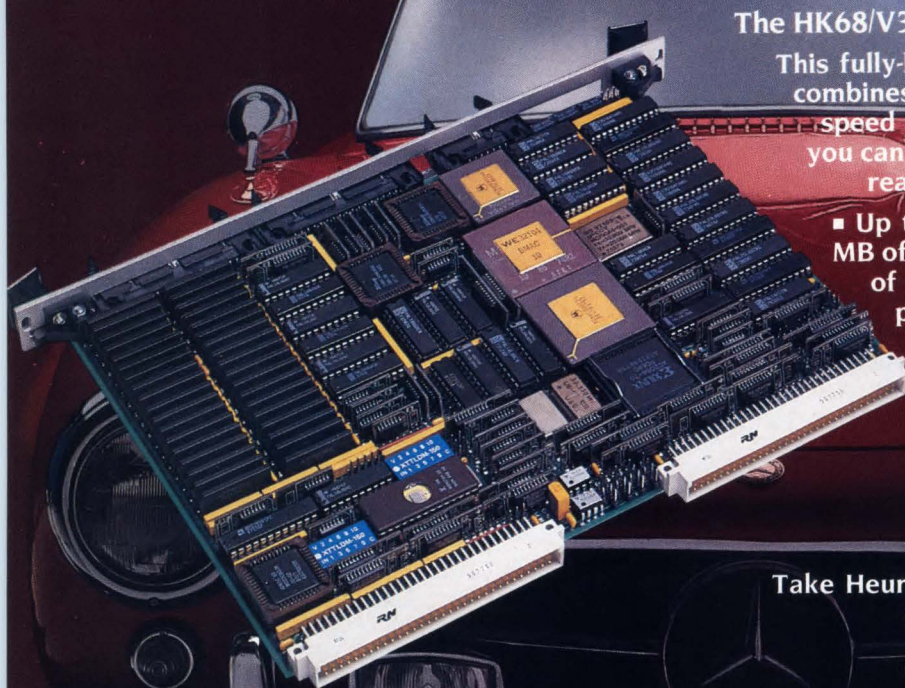

The HK68/V30 is the card you've been dreaming of.

This fully-loaded single-board VME microcomputer combines the highly sought-after qualities of high speed and advanced on-card functionality. Now you can have high-end performance for UNIX and real-time applications. Standard equipment:

- Up to 25 MHz Motorola 68030 CPU ■ 4 or 16 MB of on-board DRAM with parity ■ Up to 1 MB of EPROM ■ 2 serial I/O ports ■ Single 8-bit parallel port ■ Mailbox interrupt support.

Optional equipment includes on-board 68881/68882 FPP, SCSI interface and Time-of-Day clock with battery back-up.

HEURIKON CORP

Take Heurikon's HK68/V30 for a grand tour today.

Call toll-free: 800-356-9602 (ext. 503).


Telefax: 608-251-1076

3201 Latham Drive ■ Madison, WI 53713

CIRCLE NO 189

NO SCHOTTKYs NEEDED

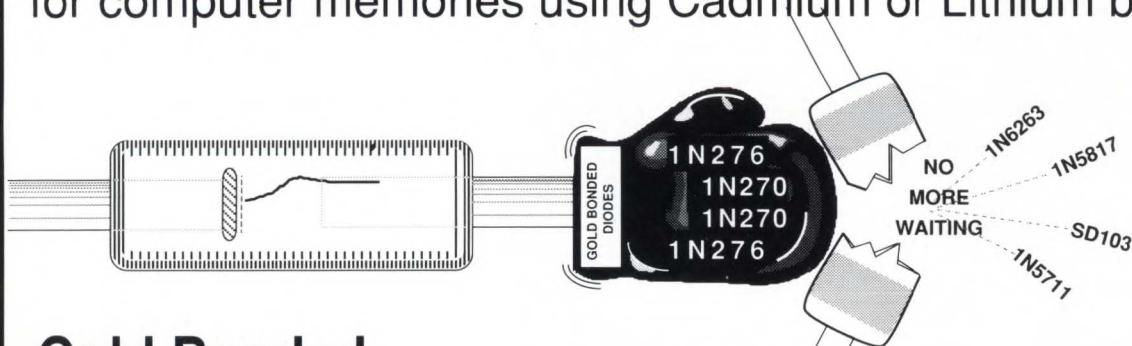for computer memories using Cadmium or Lithium batteries



**Gold Bonded
Germanium Diodes**

**CAN
REPLACE**

Schottky Diodes

FAST DELIVERY

COMPETITIVE PRICE & SERVICE

Not Sensitive To Static Discharge
Operate at Lower Current Level
Lower Noise
Higher Reliability
Lower Power Consumption



**BKC International
Electronics Inc.**

If you're looking for delivery of small-signal Schottky diodes, perhaps it's time to take off the gloves.

We manufacture over 200 different Gold Bonded Diodes with inverse current capabilities for 5 to 250 volts. All of our diodes meet the requirements of MIL-S-19500. For more information or samples, write or call BKC.

6 Lake Street, P.O. Box 1436, Lawrence, MA 01841
Telephone (508) 681-0392 • TeleFax (508) 681-9135

DESIGN IDEAS

er (distinct from its thin-film resistor network) contributes only -120 dB of CMR error. Therefore, the resistor network is responsible for most of the residual CMR error that remains after laser trimming. This trim error affects CMR by about the same amount whether operating with a gain of 10 or a gain of 0.1.)

You can improve this circuit's CMR by adding 10Ω in series with R_1 (pin 2) and adding a 20Ω potentiometer in series with R_3 (pin 3). To adjust CMR, connect the inputs and drive them with a 1-kHz square wave whose amplitude is in the range from $\pm 10\text{V}$ to $\pm 100\text{V}$. (A sine wave will introduce unwelcome CMR-vs-frequency effects.) Adjust the 20Ω pot for a minimum-amplitude signal at E_0 .

As before, $1 + R_6/R_5$ sets the gain. The tolerance on this expression plus $\pm 0.01\%$ (contributed by IC_1) deter-

mines the overall gain accuracy. You can improve gain accuracy by using higher-precision resistors or by adding the optional gain-adjust network shown (R_7 and R_8). Gain and CMR adjustments don't interact in the Fig 2 circuit.

One application for the circuit of Fig 1 or Fig 2 is in monitoring high-side load current in a regulator or power supply. By connecting the difference amplifier across a 1Ω resistor in series with the supply's output, you can interpret the difference amplifier's output as one ampere of load current per volt for supply voltages in the range from -100V to 100V .

EDN

Op amp provides a current and voltage source

Scott Wayne
Analog Devices Inc, Norwood, MA

You can obtain a controlled source of voltage ($-V_R$) and current ($V_R/2R$) by using a single op amp and four transistors (Fig 1). The current and voltage outputs track the reference voltage. Moreover, they show little variation with temperature because the circuit compensates for changes in the transistors' beta and base-emitter voltage. For best results, you should use a single-chip array for the transistors and another one for the R-value resistors.

Transistors Q_1 and Q_4 form a current mirror that generates I_0 by replicating Q_1 's collector current. To calculate V_0 , note that the currents through R_1 and R_2 are equal, so the voltage across R_2 is $V_R/2$. Similarly, the voltages across R_3 and R_4 are equal, because currents through these resistors are the same. Further, the voltage across R_4 is $V_R/2$ minus one base-emitter voltage (V_{BE}), so Q_1 's base-collector voltage is also $V_R/2 - V_{BE}$. Therefore, Q_1 's collector-emitter voltage is $V_R/2$, and $V_0 = -V_R$.

Without compensation, each transistor's V_{BE} would change about $-2.2\text{ mV}/^\circ\text{C}$, making V_0 vary with temperature. Q_2 and Q_3 prevent this variation by creating a temperature-dependent current in R_3 that moves the base voltage of Q_1 and Q_4 in a direction opposite to the change in V_{BE} .

You should choose the value of R_3 and R_4 so that the collector current of Q_2 and Q_3 will equal the collector


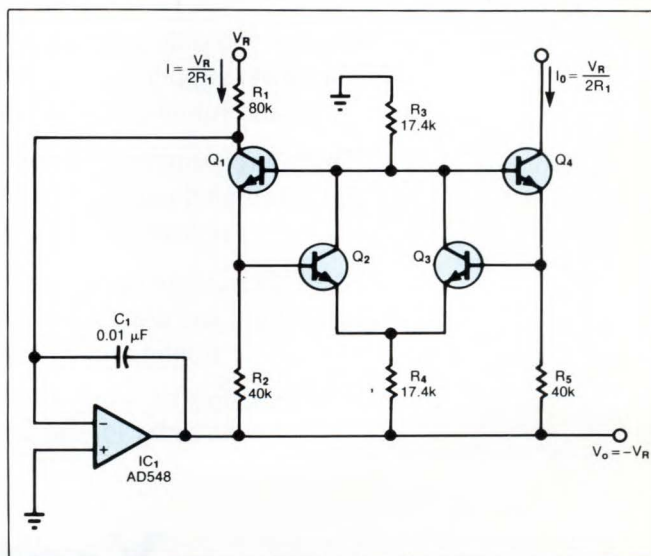


Fig 1—This single-op-amp circuit generates temperature-stable current- and voltage-source outputs that track the reference voltage (V_R).

current of Q_1 and Q_4 . The matched currents and the circuit's symmetry ensure that all betas and collector currents will remain equal as temperature varies, provided that the transistors are well matched. Capacitor C_1 reduces output noise by limiting the circuit's bandwidth.

EDN

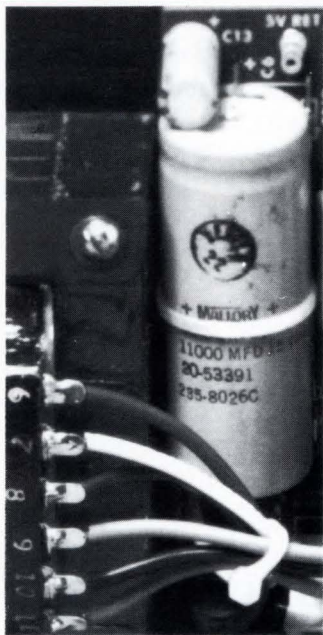

Custom Linear Power in less than 10 days and it's UL recognized.

You give us the specs... and
we deliver the power you
want... fast!

Whether you only need a few watts or hundreds of watts... our linear power supplies deliver the performance to get your system up and running fast and the reliability to keep it there.

Thirty-three standard mechanical configurations and 20,000 pre-assembled regulator combinations mean low prices and delivery in as little as 10 working days.

And because all our power supplies are built with pre-UL recognition, you don't have to worry about our power supplies holding up your system UL approval.

Get the full story on worry free linear power from Xentek. Call or write today for our free information package.


Xentek 
The Heart of Your System

760 Shadowridge Drive • Vista, CA 92083 • (619) 727-0940 • TWX: 910-322-1155 • FAX: (619) 727-8926
XENTEK — the first word in Custom Linear, Standard Linear, Custom and Standard Switchers, Extreme Isolation Transformers, Line Conditioners and Custom Military Power Conversion Equipment.

EDN PRODUCT MART

This advertising is for new and current products.

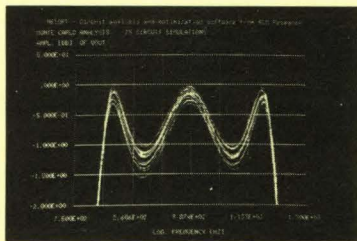Please circle Reader Service number
for additional information from manufacturers.



NETOPT / NETSIM ANALOG CIRCUIT ANALYSIS AND OPTIMIZATION SOFTWARE

NETSIM analyzes circuits in both time and frequency domains, performs Monte Carlo, tolerance/worst case analysis and extracts poles/zeros and transfer functions. • Produce yield estimates and sensitivity analysis of your analog designs • **NETOPT** includes all features of NETSIM and adds sophisticated optimization capabilities • Compensate for circuit/device parasitics, generate non-standard responses and center designs for maximum yields. • NETSIM is available for IBM PC® (\$850) and VMS®/UNIX® (\$1700.00)/NETOPT is \$1995.00 for the PC and \$3995.00 for the VMS/UNIX version.

RLM Research
P.O. Box 3630, Boulder, CO 80307-3630
(303) 499-7566

CIRCLE NO 325



JOHN BELL
ENGINEERING, INC.


CATALOG #10

Free Catalog of DIGITAL and ANALOG Interfaces for the IBM-PC, XT, AT and VME bus and Apple IIe computers. John Bell Engineering, Inc. 400 Oxford Way, Belmont, CA 94002

CIRCLE NO 328



"The Best 8051 Emulator"

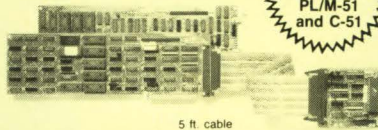

5 ft cable

8051

See EEM 88/89
Page D-1304

PC based emulators for the 8051 family

- (8051/51FA/52/31/32/44/152/451/452/535/552 + CMOS + more ...
- PC plug in boards or RS-232 box
- Pull-down menus combined with Command-Driven User Interface.
- Context sensitive help and On-Screen Editing of data
- 20 MHz real time emulation
- 128K emulation memory
- 48 bit wide, 16K deep trace buffer with loop counter
- Program Performance analyzer
- Powerful Macros with IF-ELSE, REPEAT, WHILE structures
- Source Level debug for PL/M-51 and C-51
- Symbolic debugging with in-line assembler and disassembler
- Execution time counter
- Trace can be viewed during emulation!

PRICES: 32K Emulator for 8031 \$1790; 4K Trace \$1495*

CALL OR WRITE FOR FREE DEMO DISK!

*U.S. only Ask about our demo VIDEO!

NOHAU
CORPORATION

51 E. Campbell Avenue
Campbell, CA 95008
FAX (408) 378-7869
(408) 866-1820

CIRCLE NO 326

DR. DESIGN

The **1M DRAM SuperSpec**, first of a series of books by noted computer designer Marco Thompson, reveals methods that guarantee your design will work even when different vendors' chips are used. Learn how to interpret specs, and what they really mean. This is a real hands-on working design guide you will use over and over. Eliminate the worry about flaky memory performance. Nothing in the drug store can beat this for peace of mind. Over 70 pages with 30 tables, only \$79.

FREE We'll include a free copy of the pocket-sized **XT-AT Handbook** by Choisser and Foster with each SuperSpec if you mention this ad when you order. Of course, this \$9.95 value is also available by itself. Or buy five or more for only \$5.00 each.

Annabooks

12145 Alta Carmel Ct Suite 250-262
San Diego, California 92128

(619) 271-9526 Money-back guarantee

CIRCLE NO 329

Don't Get Zapped!


High inrush current can **destroy** your sensitive VAX CPUs and peripherals in less time than it takes to flip a switch.

THE SOLUTION?

Power up with **Z-LINE TPC 115-10 MTD™** the smallest power distribution and control system available.

POWER UP WITH — — —

Z-LINE™

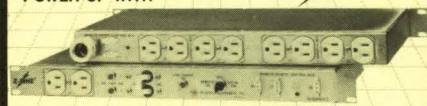

Our proprietary **Multiple Time Delay™** circuitry sequences your power-up to **protect** your systems from the spikes and surges, EMI & RFI, that **destroy** your hardware and erase your data. And our remote on/off and emergency shutdown gives the power control back to you.

All Pulizzi Engineering MTD™ controllers are compatible with DEC and UPS systems.
PRICES FROM \$436 TO \$305

DON'T WAIT UNTIL IT HAPPENS, CALL TODAY!


PULIZZI ENGINEERING INC.

3260 S. Susan Street, Santa Ana, CA 92704-6865
(714) 540-4229 FAX (714) 641-9062

CIRCLE NO 327

PAL™ /PLD SOFTWARE

Sets The Standard

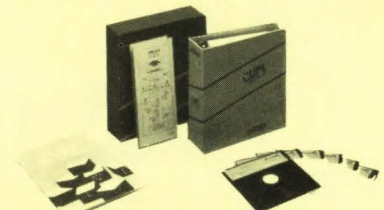


CUPL™ PLD compiler, the most powerful language for state machine logic design, now allows OrCAD™ schematic software as the front end design entry. CUPL supports all PLDs and carries the most extensive update program. Available on MS-DOS™, Apollo™, Sun™, VAX™ and most UNIX™ based platforms.

LOGICAL
DEVICES, INC.

1201 N.W. 65th Place
Ft. Lauderdale, FL 33309
305-974-0967
1-800-331-7766

CIRCLE NO 330

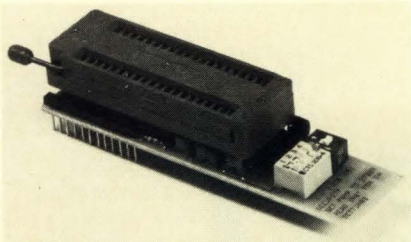To advertise in Product Mart, call Joanne Dorian, 212/463-6415



87C51 PROGRAMMER \$125

The UPA87C51 converts general purpose programmers to 8751/87C51 programmers. Select 2732A on your programmer, plug in the UPA, and you have an 8751/87C51 programmer. With the UPA87C51 you can also program the 8751 and 87C51 security bits and the 87C51 encryption array. It's very simple and VERY cost effective.


Price \$125.00 including UPS ground shipping. Adapters are also available for the 63701V0, 63705V0 and 8751 and are priced at \$65.-\$95.

Logical Systems Corp.

PO Box 6184 Syracuse NY 13217-6184 USA
(315) 478-0722 Telex 6725617 LOGS
FAX (315) 475-8460

CIRCLE NO 331

REAL WORLD I/O For PC/XT/ATs

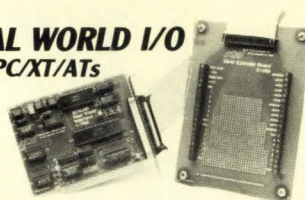


- DG24 • 24 line digital I/O; 10 MHz 8255. \$95
- AD500 • 8 channel 12-bit (plus sign) integrating A/D; prog. gains of 1, 10 & 100; 7 digital I/O lines. \$239
- AD100 • Single channel version of AD500; 10 digital I/O lines. Same programmable gains. 700 meg input Z. \$149
- AD1000 • 8 channel 12-bit A/D; 25 uS; sample & hold; 3.5 MHz timer/counters; 24 digital I/O lines. \$295
- ADA300 • 8 channel 8-bit 25 uS A/D; single D/A sample & hold; 24 digital I/O lines. \$239
- AD200 • 4 channel 12-bit 125 uS A/D; 3.5 MHz timer/counters; 24 digital I/O lines. \$239
- DA600 • Fast settling dual bipolar D/A. \$179
- PD200 • Prototype board w/ address decoder; manual. \$99

All boards include BASIC, Pascal, C, and Forth drivers. 30 day return; 1 year warranty. Call for "Real World Interfacing" application notes.

Real Time Devices, Inc.

P.O. Box 906 State College, PA 16804
(814) 234-8087

CIRCLE NO 332

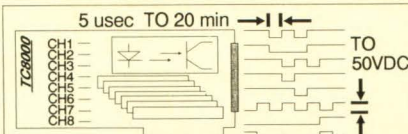


NEW PC/XT/AT INDUSTRIAL CONTROL

*** COMPLETE HARDWARE/SOFTWARE PACKAGE ***

- PHOTOCOUPLE or TTL OUTPUTS
- TRIAC OUTPUT FOR AC CONTROL
- 8 PROGRAMMABLE OUTPUTS, 256 BITS / CHANNEL
- SELECTABLE COLLECTOR/EMITTER RESISTORS
- JUMPER SELECTABLE I/O ADDRESS

SOLENOID ACTUATION
TEMPERATURE CONTROL
LIGHTING, DWELL CONTROL

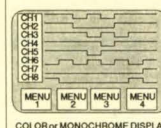LOW COST CONTROL
FACTORY AUTOMATION
TEST ENGINEERING



COLOR or MONOCHROME DISPLAY

SOFTWARE

- MENU DRIVEN SOFTWARE FOR SIMPLE WAVEFORM EDITING
- STORE/RETRIEVE WAVEFORMS
- USE STORED WAVEFORMS IN APPLICATION PROGRAMS
- SPECIAL DRIVER TO INTERFACE WITH USER APPLICATIONS

TC8000

\$595.00

Tel (714) 638-3097 Fax (714) 638-9465


NORTEK AUTOMATION

10911 Mansor Ave
Garden Grove, Ca. 92643

CIRCLE NO 333

FREE SCHEMATIC CAPTURE DEMO DISK

SCHEMA II+: Capture More Than Ever

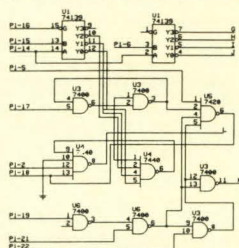

Incredible speed, ease of use and power have made SCHEMA a best-selling schematic capture program for engineering professionals the world over. Now, SCHEMA II+ sells for \$495 and supports most common IBM



PC/XT/AT/PS2 configurations.
OMATION

In Texas Call (214) 231-5167
FREE Demo Disk: 1-800-553-9119

CIRCLE NO 334




- Remote I/O
- CONTROL all your RS-232 devices from one RS-232 (COM) port
- MULTIDROP devices over several miles
- BUFFER serial data at each device in both directions
- ANY baud rate or DIFFERENT baud rates for each device
- 1-4 Units \$695.00

Connecticut microComputer, Inc.

PO Box 186
Brookfield, CT 06804
1-800-426-2872 (203) 354-9395
FAX: (203) 355-8258

CIRCLE NO 335

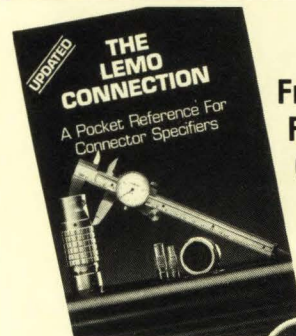

Free Catalog For Connector Specifiers

LEMO's Pocket Catalog permits connector specifiers to quickly determine which LEMO connectors meet their needs. Catalog includes tables that are organized around the main elements needed to specify connectors: number of contacts, working voltages, amps, collet ranges to accommodate cable OD, shell styles and insulating materials.

Connector families include mixed and multi contact connectors, environmentally sealed connectors, coaxial, triaxial, high voltage and plastic.


LEMO USA, INC.

P.O. Box 11488, Santa Rosa, CA 95406
phone 707/578-8811, telex 340-933, fax 707/578-0869.

CIRCLE NO 336

UNIVERSAL LOGIC PROGRAMMER

- Just \$798.00 including software, cable, manual and two updates
- Programs, reads, duplicates, tests and secures over 700 20- and 24-pin logic devices from 17 manufacturers including: Altera, AMD, AMI (Gould), Atmel, Cypress, Exel, ICL, Intel, Lattice, MMI, National, Ricoh, SGS-Thomson, Signetics, TI, and VLSI
- Updatable via floppy disk
- 23 Universal pin drivers
- Connects to any IBM compatible via parallel printer port
- Fully menu-driven software, easy to learn and quick to operate
- Supports all popular PLD development software
- Automatically tests with vectors and secures after programming
- Edits fuse maps and test vectors
- Toll-free technical support
- JEDEC file input and output
- Gold Textool ZIP IC socket
- Engr support team for fast updates
- EPROM programmers available also
- Approved by manufacturers
- On line help function
- Self calibrating
- One-year warranty
- Same day shipment
- 30-day money back guarantee

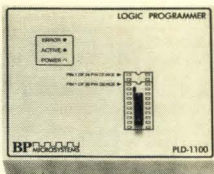

The Engineer's Programmer™

CALL FOR FREE DEMO DISK
800/225-2102

BP MICROSYSTEMS

10681 Haddington, Suite #190, Houston, TX 77043
713/461-9430 FAX 713/461-7413

CIRCLE NO 337

IEEE-488 For Personal Computers



- IBM Personal System/2™ Micro Channel™
- IBM PC, XT, AT and compatibles
- DMA transfer rates up to 1M bytes/sec
- Industry's best and most extensive software
- Free technical support and phone call
- 2-year warranty

NATIONAL INSTRUMENTS™
12109 Technology Blvd.
Austin, Texas 78727-6204

Call for
FREE Catalog
800-531-4742
512-250-9119

CIRCLE NO 338

IBM COMPATIBLE RS232/488 3 1/2" - 5 1/4" FLOPPY DATA STORAGE & TRANSFER SYSTEM



Information Transfer to/from Non IBM Compatible Systems to/from IBM & Compatibles: (Over RS-232 or 488 Interface)

- Reads & Writes MS DOS Disks
- RS-232/488 I/O
- Rugged Portable Package/battery option
- MS-DOS Driver for "Plug & Run" RS232 External Operation
- Baud Rate 100 to 38.4K Baud
- 360K/720K RAM Cartridge Option
- Price \$895 in Singles - OEM, Qty's. \$495

28 other systems with storage from 100k to 42 megabytes
ANALOG & DIGITAL PERIPHERALS, INC.

251 South Mulberry St. Troy, Ohio 45373
PO Box 499 TWX 810/450-2685
513/339-2241 FAX 513/339-0070

CIRCLE NO 339

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

EDN Design Ideas Special Issue, Vol III

EPROM PROGRAMMER

- ✓ Programs 2764 in 8 sec, 27512 in 44 sec
- ✓ Reads, copies and programs over 475 E / EPROMS from 35 mfg's including 276-27513, 27011, 68764, 68766, 2804-28256
- ✓ Automatically uses the fastest recommended algorithm as specified on the manufacturer's data sheets to ensure reliable data storage
- ✓ Connects to RS-232 on any computer, PC, XT, AT, PS/2, Mac, etc.
- ✓ Supports XMODEM/XMODEM CRC protocols & ASCII file xfers
- ✓ Optional microcontroller heads support 874x and 87C51 series
- ✓ Supports Intel, Motorola, straight hex, hex-space & binary files
- ✓ Eng'r support team for fast updates
- ✓ One-year warranty (parts & labor)
- ✓ Toll-free technical support
- ✓ 30-day money back guarantee
- ✓ 8 baud rates to 38400
- ✓ Thousands of satisfied customers attest to the EP-1's great value
- ✓ Low price, \$349. Includes IBM compatible communications program, user's manual and two free update coupons
- ✓ Checksums supported
- ✓ Gold Textool socket
- ✓ Collates 16- & 32-bit
- ✓ Same day shipment
- ✓ UV erasers from \$39.95

The Engineer's Programmer

CALL TODAY 800/225-2102


BP MICROSYSTEMS

10681 Haddington, Suite 190, Houston, TX 77043
713/461-9430 FAX 713/461-7413

CIRCLE NO 340

Analog Circuit Simulation

NEW IS_SPICE/386 On 386 PC's, \$386

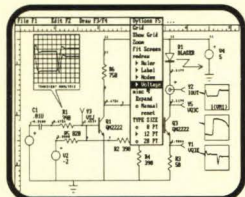

Outperforms Workstations
Increases Speed by 200 - 600%

Circuit Size nearly Unlimited
Supports 287, 387, Weitek 1167/3167

IS_SPICE runs on all 80x86 PC's for only \$95.00: Performs Complete AC, DC, and Transient Analyses.

SPICE_NET, \$295: Schematic Entry for any SPICE simulator. Automatically makes a Complete SPICE netlist. Easy to use Menu Drive program included.

PRE_SPICE, \$200: Monte Carlo Analysis, Parameter Sweeping and evaluation. Extensive Model Libraries.


Intu_Scope, \$250: A graphics Post Processor that works like a digital oscilloscope. Easy to use with the most comprehensive set of waveform operations available.

intusoft

Please Write or Call
P.O. Box 6607 (213) 833-0710
San Pedro, CA 30 Day Money
90734-6607 Back Guarantee

CIRCLE NO 343

IEEE-488 USEFUL AIDS

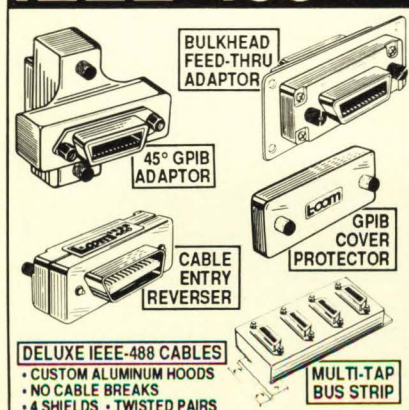


DELUXE IEEE-488 CABLES
• CUSTOM ALUMINUM HOODS
• NO CABLE BREAKS
• 4 SHIELDS • TWISTED PAIRS

MOLDED CABLES TOO, AND MORE!

Lcom 1755 Osgood St., N. Andover, MA 01845
Orders 800 343-1455 • FAX 508 689-9484
Inquiries 508 682-6936

CIRCLE NO 346

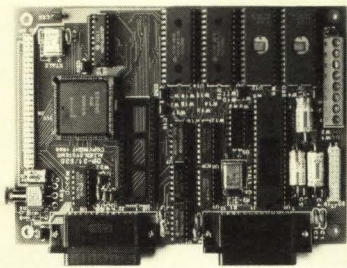
8051, 8096, 68HC11, 68008 SINGLE BOARD COMPUTERS



We feature a series of single board computers for process control applications. Available as bare boards or assembled and tested. Optional EPROM resident System Monitors and BASIC interpreters are also available.

ALLEN SYSTEMS
2151 Fairfax Road
Columbus, Ohio 43221
614-488-7122

CIRCLE NO 341

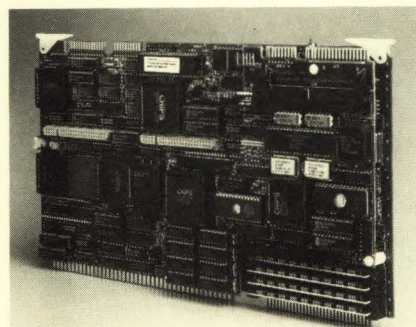

MULTIBUS™ AT-COMPATIBLE SBC

Multibus I is now IBM PC/AT™ compatible with MAT286™ our newest single board solution. MAT286 includes all of the functions of a 10 MHz AT motherboard, plus 2 serial ports, a parallel port, two SBX expansion-module interfaces, up to 512K EPROM/EEPROM/DRAM, and up to 4M of parity-checked, dual-ported DRAM. A piggy-back card, MATSYSIO, adds EGA, floppy, and SCSI interfaces. Embed all the guts of an AT, two SBX modules, and more, into two Multibus slots!

Phone (408) 253-0250 or write for more information.

Single Board Solutions, Inc.

20045 Stevens Creek Blvd, Cupertino, CA 95014
Multibus is a registered trademark of Intel Corp.
MAT286 and MATSYSIO are trademarks of Single Board Solutions, Inc.
IBM and PC/AT are trademarks of International Business Machines Corp.

CIRCLE NO 344




WIDEBAND INSTRUMENTATION RECORDER/REPRODUCERS CATALOG

Airborne, shipboard and laboratory magnetic tape and disc recording/storage/reproducing systems for military and industrial applications are described in a new comprehensive catalog. For a free copy contact:

Precision Echo, Inc.
3105 Patrick Henry Drive, Santa Clara, CA 95054
408/988-0516

"Where unique data recording/storage solutions are expected."

CIRCLE NO 347

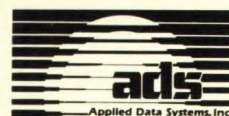

SMART CARD EXTENDER

**EASY ON \$195⁰⁰ — PC/XT
\$225⁰⁰ — AT**

A smart card extender for PC/XT/AT and compatibles

- Allows card insertion and extraction without power on/off cycles
- Saves time by eliminating DOS re-boots
- Reduces wear and tear on hard disk drives
- Extends host interface for hardware and software development and test
- A single switch controls the connection of all signals to and from the computer bus
- Patent pending



DPROM

RS232 Downloadable PROM

\$175⁰⁰ 32K x 8

\$195⁰⁰ 64K x 8

RS232



- Eprom emulator for 2716 — 27512
- Supports 8, 16, or 32 bit wide busses
- Non-Volatile memory standard
- Up to 19200 Baud
- Accepts Intel Hex and Motorola S formats
- 150ns access time standard

VectorScan 512/640 \$975⁰⁰

Graphic Controller with RS-232 Interface



- Interfaces over RS-232 ports
- Drives CGA, EGA, and Multiscan
- Resolution of 512x480 to 640x350
- 4 Bits/Pixel up to 4,096 colors
- Maintains 4 separate images
- Internal 512K byte frame buffer
- PC Version available

Applied Data Systems can customize a product to your specifications.

30 DAY NO RISK EVALUATION

APPLIED DATA SYSTEMS
409A East Preston Street
Baltimore, MD USA 21202

For more information call **800-541-2003**
Outside USA (301) 576-0335

CIRCLE NO 348

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

First, there was the vision...



Space exploration began with a vision.

The fire of imagination—fused with superior technical proficiency—leading the way to limitless possibilities. A special vision that creates the kind of breakthroughs that characterize GE Astro-Space.

Since the nation's first space communications adventure nearly 30 years ago, GE Astro-Space has been a world leader in the design and manufacture of satellites for government and commercial communications, meteorological, navigational and scientific use.

And, with over one hundred and fifty satellites currently circling the globe—and long-term projects such as the *Mars Observer*, *Space Station* and *Landsat*—we can offer Engineers the kind of rare opportunities that few are destined to realize.

If you're the visionary Engineer we're seeking, join us as we pave the way for a new generation of emerging space technology. Our mission requires the technical proficiency of Engineers with a minimum of 3 years experience in one or more of the following:

- Comm Systems MW/RF Design
- HV Power Supply Design
- Spacecraft Power Systems
- Software Design-Flt/Grd Support
- Propulsion Systems
- Antenna Mechanical Design
- TT & C/C & DH
- Launch Vehicle Integration

Our New Jersey location offers all the advantages of nearby Princeton—within easy access to New York City and Philadelphia. Additionally, selected positions are open in Valley Forge, PA. In either location, you'll experience a lifestyle that complements your career, providing opportunities for personal and professional growth.

As the largest employer of engineers and scientists in the world, GE provides competitive salaries and exceptional benefits including tuition refund and continuing education programs—so your expertise is always current and expanding.

Rush your resume to: Employee Relations, GE Astro-Space, P.O. Box 800, Princeton, New Jersey 08543-0800. An equal opportunity employer.



GE Aerospace
Astro-Space

Cross the engineering frontier.

EDN's CHARTER

EDN is written for professionals in the worldwide electronics industry who design, or manage the design of, products ranging from circuits to systems.

EDN provides accurate, detailed, and useful information about new technologies, products, design techniques, and careers.

EDN covers new and developing technologies to inform its readers of practical design matters that will be of concern to them at once or in the near future.

EDN covers new products

- that are immediately or imminently available for purchase
- that have technical data specified in enough detail to permit practical application
- for which accurate price information is available.

EDN's Magazine Edition also provides specific "how to" design information that its readers can use immediately. From time to time, EDN's technical editors undertake special "hands on" engineering projects that demonstrate EDN's commitment to readers' needs for useful design information.

EDN's News Edition also provides comprehensive analysis and news of technology, products, careers, and distribution.

275 Washington St
Newton, MA 02158
(617) 964-3030

BUSINESS/CORPORATE STAFF

Peter D Coley
VP/Publisher
Newton, MA 02158
(617) 964-3030; Telex 940573
Ora Dunbar, Assistant/Sales Coordinator

Mark J Holdreith
Advertising Sales Director
Newton, MA 02158
(617) 964-3030
Heather McElkenny, Assistant

Deborah Virtue
Business Director
Newton, MA 02158
(617) 964-3030

NEW ENGLAND
John Bartlett, Regional Manager
Chris Platt, Regional Manager
199 Wells Ave
Newton, MA 02159
(617) 964-3730

STAMFORD 06904
George Isbell, Regional Manager
8 Stamford Forum, Box 10277
(203) 328-2580

NEW YORK, NY 10011
Daniel J Rowland, Regional Manager
249 West 17th St
New York, NY 10011
(212) 463-6419

PHILADELPHIA AREA
Steve Farkas, Regional Manager
487 Devon Park Dr, Suite 206
Wayne, PA 19087
(215) 293-1212

CHICAGO AREA
Clayton Ryder, Regional Manager
Randolph D King, Regional Manager
Maris Listello, Telemarketing
Cahners Plaza
1350 E Touhy Ave, Box 5080
Des Plaines, IL 60017
(312) 635-8800

DENVER 80206
John Huff, Regional Manager
44 Cook St
(303) 388-4511

DALLAS 75243
Don Ward, Regional Manager
9330 LBJ Freeway, Suite 1060
(214) 644-3683

SAN JOSE 95128
Walt Patstone, Regional Manager
Bill Klanke, Regional Manager
Philip J Branon, Regional Manager
James W Graham, Regional Manager
3031 Tisch Way, Suite 100
(408) 243-8838

LOS ANGELES 90064
Charles J Stillman, Jr
Regional Manager
12233 W Olympic Blvd
(213) 826-5818

ORANGE COUNTY/SAN DIEGO 92715
Jim McElean, Regional Manager
18818 Teller Ave, Suite 170
Irvine, CA
(714) 851-9422

PORTLAND, OREGON 97221
Pat Dakin, Regional Manager
Walt Patstone, Regional Manager
1750 SW Skyline Blvd, Box 6
(503) 297-3382

UNITED KINGDOM/BENELUX
Jan Dawson, Regional Manager
27 Paul St
London EC2A 4JU UK
01-628 7030
Telex: 914911; FAX: 01-628 5984

SCANDINAVIA
Stuart Smith
27 Paul St
London EC2A 4JU UK
01-628 7030
Telex: 914911; FAX: 01-628 5984

FRANCE/ITALY/SPAIN
Alasdair Melville
27 Paul St
London EC2A 4JU UK
01-628 7030
Telex: 914911; FAX: 01-628 5984

WEST GERMANY/SWITZERLAND/AUSTRIA
Wolfgang Richter
Sudring 53
7240 Horb/Neckar
West Germany
49-7451-7828; Telex: 765450

EASTERN BLOC
Uwe Kretzschmar
27 Paul St
London EC2A 4JU UK
01-628 7030
Telex: 914911; FAX: 01-628 5984

FAR EAST
Ed Schrader, General Manager
18818 Teller Ave, Suite 170
Irvine, CA 92715
(714) 851-9422; Telex: 183653

HONG KONG
John Byrne & Associates Ltd
1613 Hutchison House
10 HGarcourt Road
Central Hong Kong
Tel: 5-265474
Tlx: 61708 WEDIN HX
Fax: 5-8106781

JAPAN
Kaoru Hara
Dynaco International Inc
Suite 1003, Sun-Palace Shinjuku
8-12-1 Nishishinjuku, Shinjuku-ku
Tokyo 160, Japan
Tel: (03) 366-8301
Telex: J2322609 DYNACO

KOREA
Kim Kyong-Hae, BK International
Won Chang Bldg, 3rd Floor 26-3
Yoido-dong, Youngdunpo-ku
Seoul 150, Korea
Tel: 785-6665; FAX: 784-1915
Telex: K32487 BIZKOR

**SINGAPORE/MALAYSIA/INDONESIA/THAILAND/
THE PHILIPPINES/AUSTRALIA/NEW ZEALAND**
Asia Pacific Media House PTE Ltd
Peter Cheong
100 Beach Rd
#24-03 Shaw Tower
Singapore 0718
Tel: 2915354; Telex: RS 50026 MESPLY

TAIWAN
Acteam International Marketing Corp
6F, No 43, Lane 13
Kwang Fu South Rd
Mailing Box 18-91
Taipei, Taiwan ROC
760-6209 or 760-6210
Telex: 29809; FAX: (02) 7604784

PRODUCT MART
Joanne Dorian, Manager
249 West 17th St
New York, NY 10011
(212) 463-6415

INFO CARDS
Donna Pono
Newton, MA 02158
(617) 558-4282

CAREER OPPORTUNITIES/CAREER NEWS
Roberta Renard, National Sales Manager
(201) 228-8602

Janet O Penn, Eastern Sales Manager
(201) 228-8610
103 Eisenhower Parkway
Roseland, NJ 07068

Mary Beth West, Western Sales Manager
12233 West Olympic Blvd
Los Angeles, CA 90064
(213) 826-5818

Staci Comstock, Sales Assistant
(201) 228-8608
FAX: 201-228-4622

Wendy A Casella, Advertising/Contracts Coordinator
Nan E Coulter, Advertising/Contracts Coordinator
Aileen B Turner, Advertising/Contracts Coordinator
(617) 964-3030

William Platt, Senior Vice President, Reed Publishing USA
Cahners Magazine Division
Terry McDermott, President, Cahners Publishing Co
Frank Sibley, Group Vice President, Electronics/Computers
Tom Dellamaria, VP/Production & Manufacturing

Circulation
Denver, CO: (303) 388-4511
Sherri Gronli, Group Manager
Eric Schmierer, Manager

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Joanne R Westphal, Cahners Reprint Service, Cahners Plaza, 1350 E Touhy Ave, Box 5080, Des Plaines, IL 60018. Phone (312) 635-8800.

Power-Packed Custom Fit Switchers at "Off-the-Shelf" Prices.*

4W/in.³ (and higher) power densities

* Under 50¢/W in production qty.

On-board EMI/RFI filtering to FCC/VDE

MTBF=100k+ hrs./MIL-HDK-217E

Custom capabilities span 50W-2000W


Economically & quickly tailored
to fit from proven designs

Approved to meet UL, CSA and TUV


The 225W and 265W models shown are
representative of the quality switch-mode
power supplies that we design and build to meet
your exacting specifications—at affordable pricing.

Our proven track-record in innovative power
supply technology for over 25-years attests
to this. So call us NOW for cost-conscious
quotations and responsive solutions.

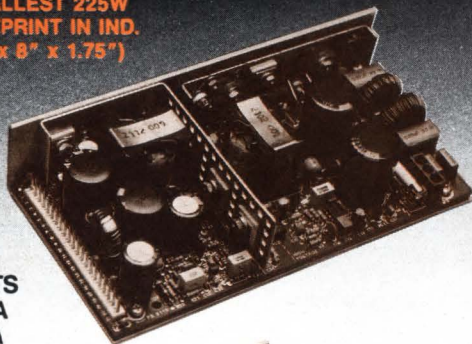**SMALLEST 225W
FOOTPRINT IN IND.
(4" x 8" x 1.75")**



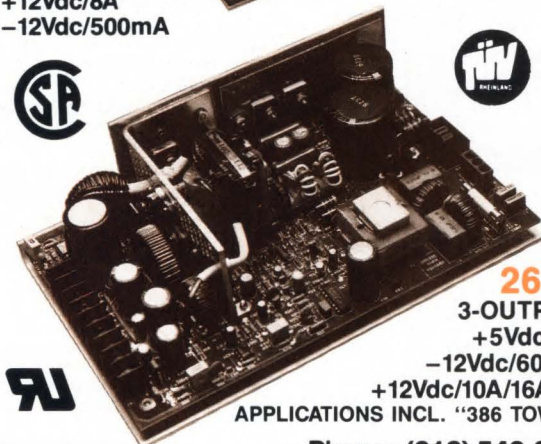225W
3-OUTPUTS
+5Vdc/25A
+12Vdc/8A
-12Vdc/500mA



265W
3-OUTPUTS
+5Vdc/28A
-12Vdc/600mA
+12Vdc/10A/16A pk.

APPLICATIONS INCL. "386 TOWER"



For a NOW response call: Phone: (213) 542-8561
FAX: (213) 371-6331



MODULAR DEVICES, INC.
4115 SPENCER STREET ■ TORRANCE, CA 90503

CIRCLE NO 182

AD INDEX

ADPI	72
Allen Systems	73
Anna Books	71
Applied Data Systems	73
BKC International	68
BP Micro Systems	72-73
Circuit Technology Inc.	4
Connecticut Micro Computer	72
Cybernetic Micro Systems	52
Dale Electronics	C1
Data I/O Corp.	C3
DisplayTEK	54
Fujitsu APD	24-25
Glassman High Voltage Inc.	60
Harris Semiconductor	45
Heuricon	68
Hilevel Technology	65
Intusoft	73
John Bell Engineering	71
John Fluke Mfg Co.	10
L-Com Inc.	73
LeCroy Corp.	43
Lemo USA	72
Linear Technology	41
Logic Devices Inc.	63
Logical Devices	71
Logical Systems	72
Modular Devices	76
National Instruments	72
Nohau	71
Nortek	72
Ohmite	6
Omaton	72
OrCad Systems Corp.	17
Potter & Brumfield	66
Precision Echo	73
Prem Magnetics Inc.	C4
Pulizzi Engineering Inc.	71
Real Time Devices	72
RLM Research	71
Rockland Scientific Corp.	29
Samsung Semiconductor	8-9
Single Board Solutions	73
S-MOS Systems Inc.	34
Sony Component	48
Sprague Electric	1
Taiyo Yuden Inc.	2
Thomas & Betts	58
Unitrode	22
Vishay	21
Wavetek	19
Westcor Corp.	30
Xentek	70
Xicor	36
Zilog	59

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

IF Reset THEN Count = 0
ELSE Count = Count + 1



LOGIC SYNTHESIS

AVAILABLE
NOW
ON THE
Sun Workstation

PALS LCAS

EPLDs

FPLAS
Gate
Arrays

LOGIC SYNTHESIS GIVES YOU MORE DESIGN CHOICES.


FutureNet® FutureDesigner™ gives you more choices than any other design entry software—choices in how you enter your design, in target technologies, and in design output. And only FutureDesigner uses logic synthesis to automatically turn your input choices into your output choices, optimizing and streamlining your design for the technology you select.

CHOOSE THE DESIGN ENTRY METHOD.

Only FutureDesigner lets you describe your design in the easiest, fastest, most natural way. You can enter some functions structurally, using DASH schematics. Others can be described behaviorally with any combination of truth tables, state diagrams, or high-level logic equations. Interactive verification and design rule checking help you catch errors up front, as you design.

CHOOSE THE TARGET TECHNOLOGY.

FutureDesigner is technology inde-

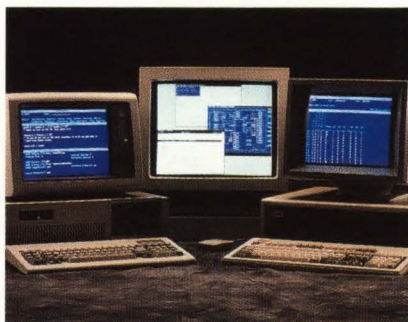

Choose the platform: FutureDesigner runs on 80386 and 80286 machines, IBM® personal computers, and the Sun-3 Series.

pendent. After you've described your design, you can choose any mix of TTLs, PLDs, LCAs, gate arrays, or other ASIC devices for implementation. It's also easy to migrate designs from one technology to another—for example, from TTL to PLD, PLD to LCA, or PLD to gate array.

CHOOSE THE OUTPUT FORMAT. With more than 100 DASH-Partners providing a broad range of comple-

mentary products and services, FutureDesigner's industry-standard format is accepted virtually everywhere. When you design with FutureDesigner, you'll have more choices in technologies, CAE systems, foundries, and service bureaus.

CHOOSE FUTUREDESIGNER WITH LOGIC SYNTHESIS.

With its unique logic synthesis capabilities, FutureDesigner reduces and factors your design, eliminating redundancy and improving efficiency. It optimizes for the particular technology you've selected, making the necessary speed/size trade-offs. Then it generates the schematics, net lists, or JEDEC files for programming PLDs. Automatically.

Call us today for more information. Find out why FutureDesigner is the design entry software of choice.


1-800-247-5700
Ext. 152

DATA I/O
Corporation

Data I/O Corporation 10525 Willows Road N.E., P.O. Box 97046, Redmond, WA 98073-9746, U.S.A. (206) 867-6899/Telex 15 2167
Data I/O Canada 6725 Airport Road, Suite 302, Mississauga, Ontario L4V 1V2 (416) 678-0761
Data I/O Europe World Trade Center, Strawinskylaan 633, 1077 XX Amsterdam, The Netherlands +31 (0)20 6622866/Telex 16616 DATIO NL
Data I/O Japan Sumitomosemer Higashishinbashi Bldg., 8F, 2-1-7, Higashi-Shinbashi, Minato-ku, Tokyo 105, Japan
(03) 432-6991/Telex 2522685 DATAIO J

©1988 Data I/O Corporation

CIRCLE NO 28

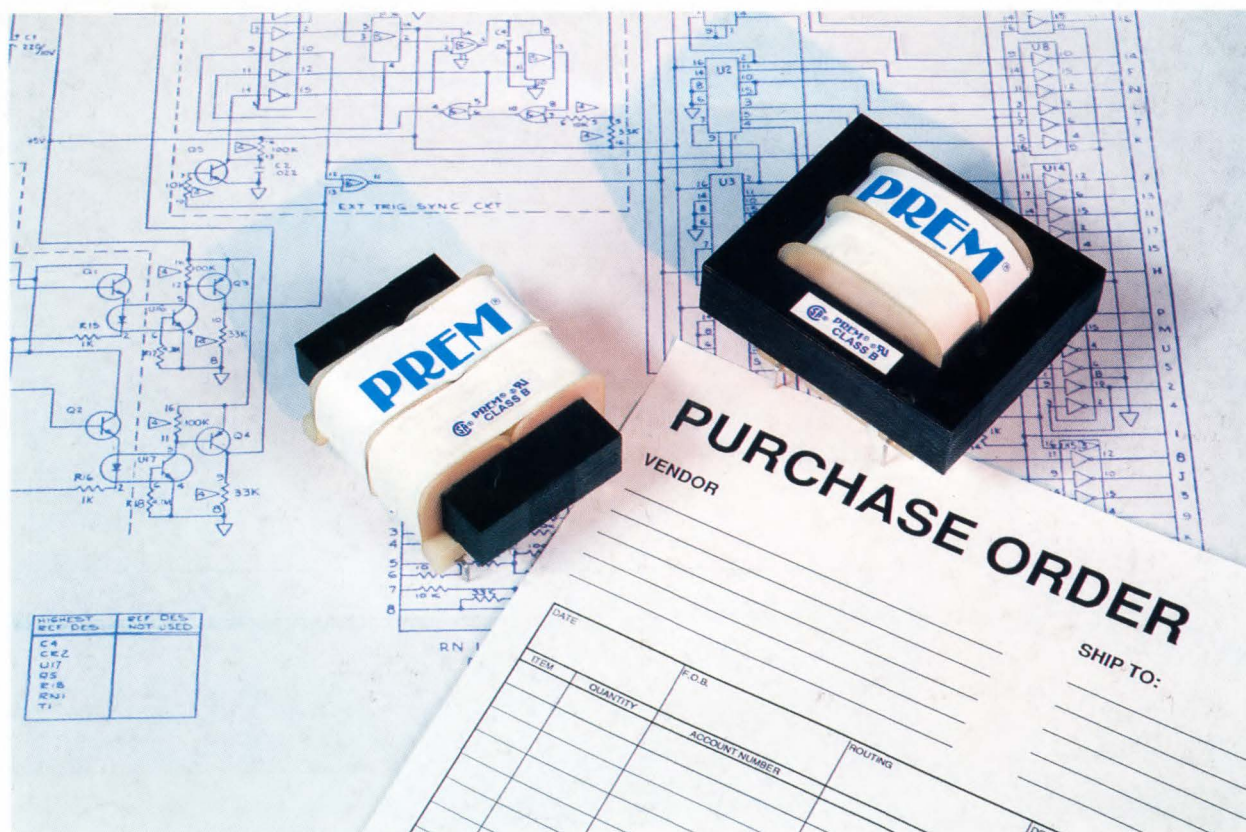

The Power Transformer on which Engineering and Purchasing Can Agree...

Purchasing

Controlling Costs...

We know part of your job is to control costs. Prem is the only transformer producer that invites you to compare. Compare Prem to Signal, Microtran, Stancor or Triad. You'll find that **PREM COSTS LESS**. And with Prem, our entire line has UL Recognition and CSA Certification at no extra cost to you. Our catalog includes cross-referenced part numbers to the above manufacturers to make comparison simple.

Deliveries Your Way...

PREMIER Service is what we call our commitment to meeting your deadlines and scheduling needs. We deliver immediately on small, in-stock quantities. And, depending on order size, we'll work with you to schedule out deliveries up to 12 months from the date of your order. Our transformers are specially packed to prevent transit damage...a worry you won't have with Prem.

Engineering

Quality...


Everybody *talks* about quality. We *do* something about it. Prem transformers are epoxy impregnated with 100% solids to withstand most aqueous and solvent printed circuit board cleaning systems. This eliminates post-wash soldering. Our units are 100% induced voltage tested for shorted turns. Pins are pre-tinned to ensure good solder contact to the pc board. Prem has received awards from leading manufacturers for our outstanding quality.

The entire Prem line of PC power transformers is CSA Certified and UL Recognized at no extra cost to you. There are no hidden charges.

Technical Assistance...

You can talk to our Technical Services Manager or any one of our experienced design engineers. They are only a phone call away if you have a question or need technical assistance. We're also willing to modify our standard PC power transformers or provide a custom design to meet your needs.

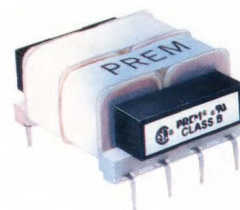For immediate technical data, see our catalog in EEM. Or call us.



PREM[®]
MAGNETICS,
INCORPORATED

3521 North Chapel Hill Road
McHenry, Illinois 60050
Tel. 815-385-2700
FAX: 815-385-8578

Where quality really counts

CIRCLE NO 29