

A CAHNERS PUBLICATION

JULY 20, 1989

# EDN<sup>®</sup>

Design Ideas  
Special Issue  
VOLUME IV


ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS



6/16/89



# Everything the SCC should have been

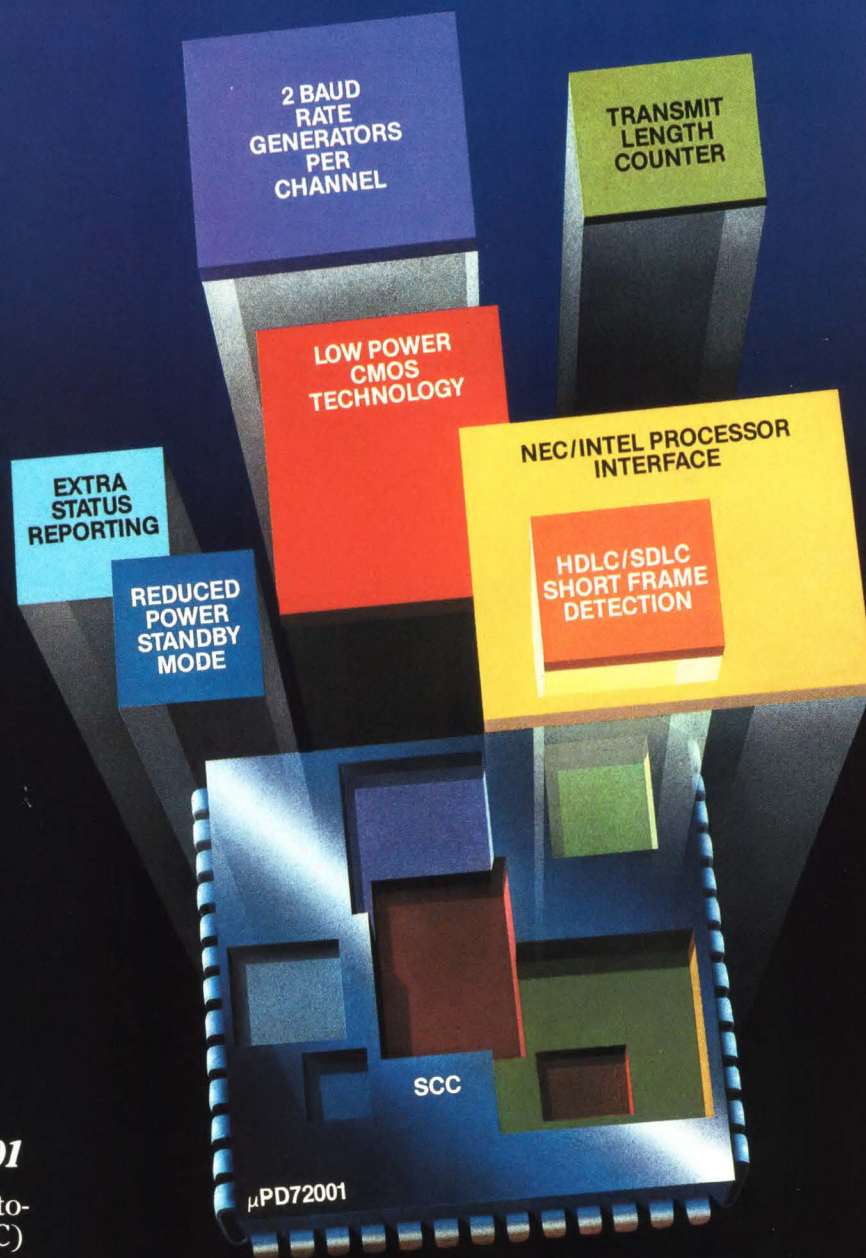

## NEC's new Chief of Protocol: the $\mu$ PD72001

NEC's  $\mu$ PD72001 Multiprotocol (SDLC/HDLC/SYNC/ASYN) Controller is a high-performance, single-chip SCC. Done right!

If you're familiar with the old 8530 architecture, you'll feel right at home with our 72001. Using our free design kit, you can make a simple conversion from your existing software and start taking advantage of all the additional performance features of the 72001.

© 1989 NEC Electronics, Inc.

For example, the 72001 has two sets of transmit length counter registers that save two interrupt service routines for each SDLC/HDLC frame transmitted.

There are many more features that you'll find extremely helpful in improving the price/performance of your next system

design. So call now or contact your local sales office for our free design kit on the Chief of Protocol: NEC's 72001. Done right!

NEC Electronics Inc.  
401 Ellis Street  
Mountain View, CA 94039-7201  
1-800-632-3531/415-965-6158

# NEC



# Oops... You Just Keyed The Transmitter Into Your Spectrum Analyzer

Costly and time consuming repairs due to accidental overload of your spectrum analyzer are now history. Rest easy...Marconi's 2382 uniquely features 50 watt front end protection. It also features full automatic self calibration, providing the industry standard for total level accuracy of  $\pm 1$  dB... including the integral tracking generator. That's right — you can count on this level of accuracy anywhere on the screen. To find out all the features of the 400 MHz and 4.2 GHz 2380 series spectrum analyzers, or to arrange for a demo, call toll-free 800 233-2955, in NJ (201) 934-9050 or write Marconi Instruments, 3 Pearl Ct., Allendale, NJ 07401.

CIRCLE NO 1

**Marconi**  
Instruments





# Pack A Punch With Vitelic's Integrated Cache RAMs.



**Double The Punch of Your High-performance 32-bit PCs and Technical Workstations.**

INTEGRATED CACHE RAMs			
Part No.	V63C328	V63C308	V63C64
Organization	8K x 16 Cache	4K x 16 Cache	8K x 8 Fast SRAM
Controller Interface	Intel 82385	CHIPS® 82C307, 82C327	All
Speed	20, 25, 33 MHz	16, 20, 25 MHz	16, 20, 25, 33 MHz
Associativity	Direct map or 2-way	2-way	Direct map, 2-way or 4-way
Size	Your choice of 16K, 32K, 64K, 128K bytes		

## A Lean, Mean Memory Machine.

Drop our cache RAM in with a cache controller for a complete cache subsystem. No more glue logic. No more matching address access times with CPU clock speeds. And, best of all, two chips replace twenty-six chips for a complete 32K byte cache subsystem.

Our integrated cache RAM frees up as much as 9 in<sup>2</sup> of valuable board space, which decreases costs associated with reliability, manufacturing and inventory. Plain and simple, this means lower costs and higher profits for you.

Our automatic power down circuitry reduces power consumption by 65%—ideal for portable applications.

## Cache and DRAMs—The Winning Combination.

Team up our cache RAMs with our DRAMs for a knock-out combination. Vitelic's smart, lightning-fast DRAMs have earned us the reputation as a worldwide leader in 70-80ns DRAMs—we ship more than 1.5 million units per month.

## CMOS—The Technology of Champions.

Vitelc's advanced CMOS process offers the triple threat of high speed, low power and high density. Vitelic's CMOS technology, coupled with innovative designs from our world-class design team, make for breakthrough cache and DRAM memory solutions.


Call us today at (800) 344-5970 or write:

Vitelc Corporation, 3910 North First Street, San Jose, CA 95134-1501 to find out how our cache RAMs and DRAMs can give your PCs and workstations the high-performance punch that will send the competition down for the count.

**VITELIC**  
The Emerging Leader  
in Specialty Memories


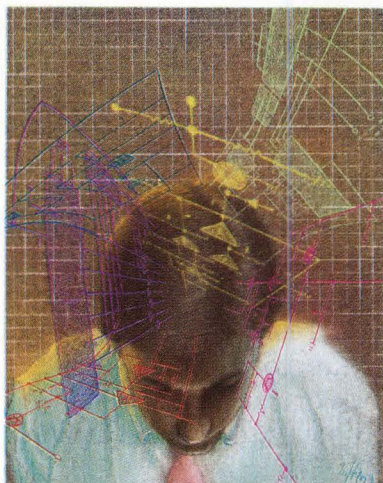
## ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS



(Illustration by Bruce Gilfoy;  
art direction by Chinsoo Chung)

### INTRODUCTION . . . . . 7

### AMPLIFIERS

One supply powers precision bridge circuit . . . . . 26

Two-way amplifier uses few parts . . . . . 32

### CONTROLLERS

Control motor speed without tachometer . . . . . 36

Solid-state switch offers fast interrupt . . . . . 12

Zero-current sensor protects relay contacts . . . . . 19

### CONVERTERS

Derive  $\pm 15V$  and 5V from a 12V battery . . . . . 13

Low-current voltage tripler is inexpensive . . . . . 16

Sampling phase detector simplifies a PLL . . . . . 16

Switching improves regulator efficiency . . . . . 26

XOR gate doubles counting frequency . . . . . 29

### GENERATORS

Power MOSFETs yield efficient power supply . . . 11

### SOFTWARE

Program calculates best-fit 1% resistors . . . . . 22

Editorial Staff . . . . . 38

Business/Corporate Staff . . . . . 47

EDN's International Advertisers Index . . . . . 48

EDN® (ISSN 0012-7515) is published 49 times a year (biweekly with 2 additional issues a month, except for February, which has 3 additional issues and July and December which have 1 additional issue) by Cahners Publishing Company, A Division of Reed Publishing USA, 275 Washington Street, Newton, MA 02158-1630. Terrence M McDermott, President; Frank Sibley, Senior Vice President/General Manager, Boston Division; Jerry D Neth, Senior Vice President/Publishing Operations; J J Walsh, Senior Vice President/Finance; Thomas J Dellamaria, Senior Vice President/Production and Manufacturing; Ralph Knupp, Vice President/Human Resources. Circulation records are maintained at Cahners Publishing Company, 44 Cook Street, Denver, CO 80206-5800. Telephone: (303) 388-4511. Second-class postage paid at Denver, CO 80206-5800 and additional mailing offices. POSTMASTER: Send address corrections to EDN® at the Denver address. EDN® copyright 1989 by Reed Publishing USA; Ronald G Segel, Chairman and Chief Executive Officer; Robert L Krakoff, President and Chief Operating Officer; William M Platt, Senior Vice President. Annual subscription rates for nonqualified people: USA, \$105/year; Canada/Mexico, \$125/year; Europe air mail, \$150/year; all other nations, \$150/year for surface mail and \$230/year for air mail. Single copies are available for \$10. Please address all subscription mail to Eric Schmierer, 44 Cook Street, Denver, CO 80206-5800.

Cahners Publishing Company, A Division of Reed Publishing USA ☐ Specialized Business Magazines for Building & Construction ☐ Manufacturing ☐ Foodservice & Lodging ☐ Electronics & Computers ☐ Interior Design ☐ Printing ☐ Publishing ☐ Industrial Research & Technology ☐ Health Care ☐ and Entertainment. Specialized Consumer Magazines: ☐ American Baby ☐ and Modern Bride.





# If our standard transformers don't meet your requirements, we'll make one that does.

Even though we make thousands of standard transformers, we realize there are times when none is quite right for the job. That's why we also offer custom design services.

MagneTek Triad engineers will work closely with you helping you find the solution to your particular transformer problem. While at the same time designing to UL, BSA, VDE, CSA, IEC and other agencies' specifications.


We design and manufacture thousands of different

custom transformers, from small switcher to large ferro-resonant models. Built to your exact specification and application need.

MagneTek Triad production capabilities include power transformers of 1 to 2,000 watts. From 45 to more than 20,000 Hz. And from printed circuit board mounted to open frame or hermetically sealed units.

And our formal quality assurance system verifies that your specifications will be consistently met or exceeded. All incoming components are tested to MIL-STD-105D. And continued inspection of wire, core, insulation and electronic components virtually eliminates imperfections.

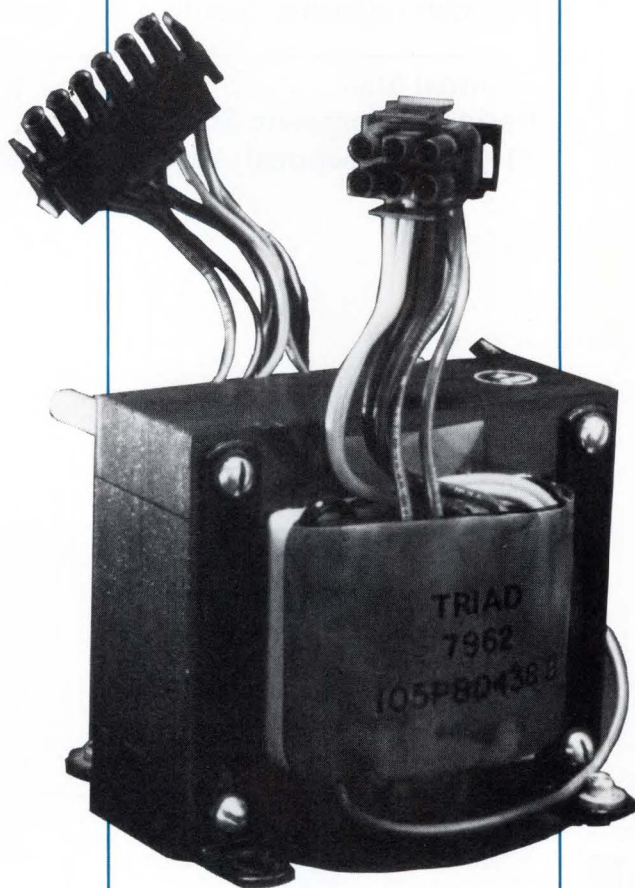For more information on **MagneTek Triad** custom transformers, call (219) 297-3111. Or write us at 1124 E. Franklin Street, Huntington, IN 46750.







## MagneTek transforms transformer problems into simple solutions.

Whether you're replacing one transformer or specifying hundreds, nobody can afford to play around. The challenge is to transform a clutter of hardware choices into one, cost-effective solution. MagneTek can help simplify the process for you.

First of all, we offer a comprehensive line of transformer products, including our Triad-

Utrad®, Better Coil®, Jefferson®, Polygon® and Ohio Transformer® brands. From tiny microcircuit coils to single- and multi-phase Powerformers®, thousands of MagneTek transformers are standard stock or catalog items at distributors nationwide.

Add to that our application engineering and service capabilities (we've rebuilt industrial and util-

ity transformers up to 200,000 kVA) and you've got a single, easy-to-tap resource for all your transformer needs. Us.



11111 Santa Monica Blvd., Los Angeles, CA 90025

800-541-9997





# OUR SMALL SOLUTION DELIVERS A MOUNTAIN OF RESULTS



## CLIMB TO THE PEAK OF PERFORMANCE WITH GRAYHILL'S MINI I/O MODULES

### With Versatility—

This space-saving series of Mini I/O Modules cuts your problems down to size! They take 4" off the length of a 16-module rack, yet retain plug compatibility. They plug in to any Grayhill mounting rack without screws, saving time and labor.

Grayhill Mini I/O Modules outperform the competitive quad pack format, providing a lower profile, superior immunity to false triggering, complete isolation, and the economic benefit of no "idle" modules. And they draw 30% less power than their big brothers.

All the mini-module advantages...combined with Grayhill "peak performance" quality.

### With Reliability—

It's Grayhill's SMT construction that gives you this superior performance. Our Mini I/O Module Quality and Reliability Report summarizes the results of our electrical noise testing, environmental testing, accelerated life testing, and physical stress testing. Ask for your copy.

### With Guaranteed Value—

Since Grayhill test results prove the unrivaled quality and reliability of these mini-modules, we are confident they will perform for the life of the product you install them in.

**If a Grayhill module ever fails, we'll send you a new one at no charge!**

### With Multiple Choices—

Conventional-size I/O modules and a choice of racks are also available, all off-the-shelf from your authorized Grayhill distributor. For custom product, a Grayhill representative is nearby to guide you through the design process.

That's a mountain of advantages in one small package...so start your climb to the top.

Call or write us for I/O Module literature and a free test sample.



**Grayhill**  
INC.  
At the Peak of Performance

561 Hillgrove Avenue, P.O. Box 10373  
LaGrange, Illinois 60525-0373 USA  
Phone: (312) 354-1040 FAX: (312) 354-2820  
Area Code 708, Effective November 11, 1989.  
TLX or TWX: 190254 GRAYHILL LAGE



# INTRODUCTION

Over the years, our readers have continually used the Information Retrieval Service cards to suggest that EDN should offer a compendium of Design Ideas. In an effort to satisfy these requests, EDN published three Design Ideas Special Issues in 1988. Reader response to these supplements was overwhelmingly positive. It was so favorable, in fact, that EDN editors decided to publish another Special Issue—this collection of more of the best Design Ideas published in EDN between 1985 and 1988.

This collection of designs reflects your needs and not the preferences of our technical editors. In fact, you and your colleagues voted for these winning ideas by circling the "bingo card" numbers that appear at the end of each Design Idea we publish. Of the circuit-design tips in this Design Issue, half garnered Best-of-Issue honors based on reader preference. The remaining Design Ideas received the second highest number of reader votes over the 1985 to 1988 time frame.

To achieve some semblance of order, we've divided the ideas into some generic categories and provided an index that lists design and circuit categories. Although the index is a handy place to look for a special circuit, we'll bet most readers will want to read the ideas one by one, just to see what circuits are available.

As you read these Design Ideas, remember that each one came from a reader who thought someone else might benefit from his or her work. So, if you find this issue helpful, thank your fellow engineers who submitted the ideas we've published over the years. And the next time you have an interesting and useful circuit, consider sharing it with other engineers by submitting it for use in EDN's regular Design Ideas section.

Besides seeing your name in print and gaining an extra \$100, you might find your idea has been selected as the issue winner. Each issue winner collects an extra \$100. Keep in mind, too, that EDN's editors also choose a grand-prize winner each year. The grand prize includes a check for \$1500. You might also see your idea published in a future EDN Design Ideas Special Issue. You'll find an entry form in the Design Ideas section in most issues of EDN.

If you enjoy this Design Ideas Special Issue and find it useful, we'd like to hear from you. If you have suggestions for improvements and changes, we'd like to hear those, too. Just send us a note or give us a call. We'd also like to thank all the readers who have submitted Design Idea entries over the years.

Enough introduction. Here are the ideas you've been clamoring for. Good reading.

**EDN**



**Tom Ormond**  
Senior Editor



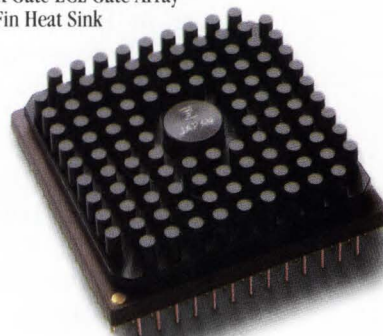
# Meet the Family.




32-bit IEEE Floating-Point General Purpose DSP  
1.2  $\mu$  CMOS 450K Transistors



100PS 10K Gate ECL Gate Array  
with Pin Fin Heat Sink



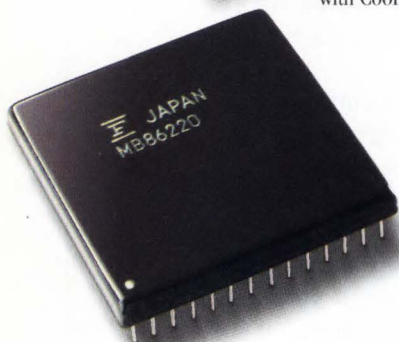12K BiCMOS Gate Array  
with Cooling Tower





24-bit Floating-Point General Purpose DSP  
1.2  $\mu$  CMOS 135-PGA




1.5  $\mu$  3000 Gate CMOS Gate Array

Ultra High Speed ECL  
(1.5 GHz typical)

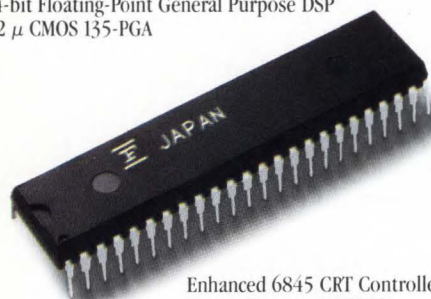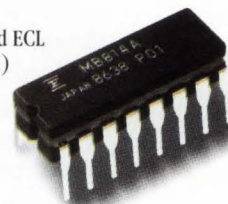


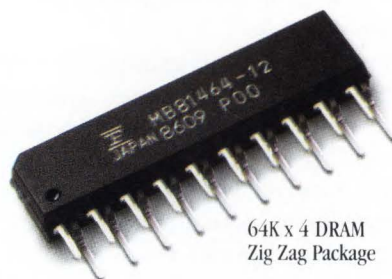Enhanced 6845 CRT Controller  
Fujitsu Part No. MB89321



64K x 4 DRAM  
Zig Zag Package

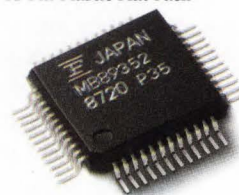SCSI Protocol Controller  
with On-Chip Drivers,  
48 Pin Plastic Flat Pack



Getting ahead is always easier when you have the support of your family. Which is precisely why the Fujitsu Microelectronics family of ASIC and standard memory products gives you all the support you need every step of the way.


Our wide selection of memory and logic products, for example, is among the most complete in the industry. Which means you can choose from every product in the book. Including static and high-speed ECL RAMs, ROMs, PROMs and EEPROMs, ultra high-speed ECL RAMs, SRAMs and DRAMs.

When it comes to ASICs, we've got everything you need to develop your own. Like powerful workstation software tools.


A broad ASIC product offering in bipolar, CMOS and BiCMOS technologies.

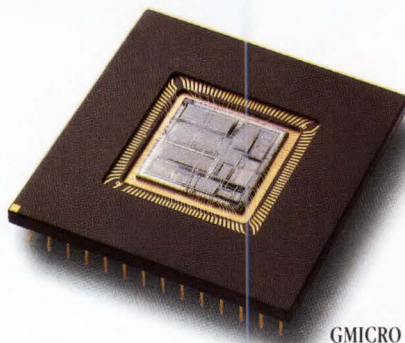And products that include high-speed ECL and BiCMOS arrays. CMOS sea-of-gates devices with over 100,000 gates. As well as standard cell capability to support up to 60,000 gates.







MB86220 DSP Emulation Processor  
for Engineering Development

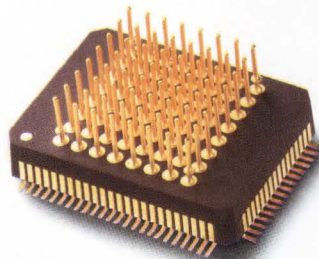

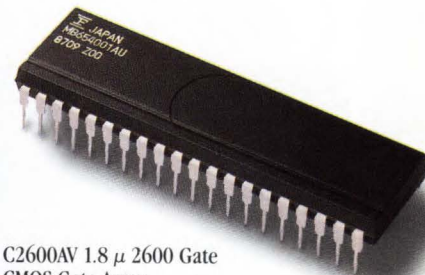GMICRO 32-bit Microprocessor  
"Super CISC"



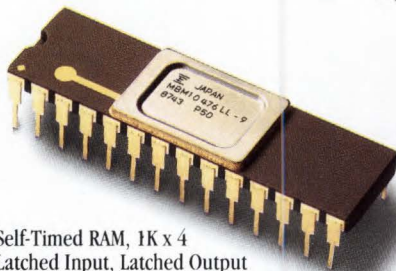C2600AV 1.8  $\mu$  2600 Gate  
CMOS Gate Array



Self-Timed RAM, 1K x 4  
Latched Input, Latched Output  
28 Pin Side-Brazed Package



24-bit Floating-Point General Purpose DSP  
1.2  $\mu$  CMOS 80 Pin Flat Package



1.5  $\mu$  12K Gate  
CMOS Gate Array  
with 152 I/O



4Mb DRAM  
300 MIL Wide, SOJ Package


High Density 1Mb, 200ns  
128K x 8 EPROM Ceramic DIP



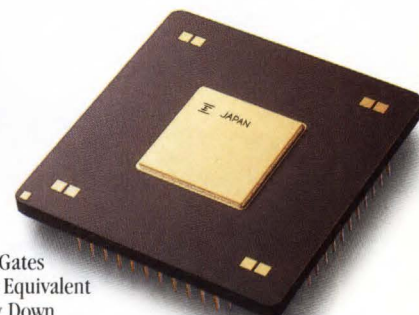1.2  $\mu$  CMOS Sea-of-Gates  
with RAM 75K Gate Equivalent  
401 Pin PGA, Cavity Down



Ultra High Speed ECL  
2-Input, D-Flip-flop  
(3.0 GHz typical)



On top of that, our microcomputer products let you choose from 4-bit micro-controllers, 8-bit to 32-bit microprocessors and SCSI controllers.

And our wide range of telecommunications products includes digital signal processors, prescalers and phase-locked loop devices.

All of which means that no matter what your needs, you've got the family behind you.

To find out more, call 1-800/642-7616. Just tell us you'd like to meet the family.



**FUJITSU MICROELECTRONICS, INC.**

Integrated Circuits Division

3545 North First Street, San Jose, CA 95134-1804. 1-800/642-7616.

Every step of the way.<sup>SM</sup>





# Things Your Mother Never Told You About HV Power Supplies!

- 1.** *Your mother never told you* of the many advantages of Glassman high voltage technology over other design approaches. . .
- 2.** *Your mother never told you* that Glassman high voltage power supplies use air as the primary insulating medium in their high voltage structures. Our field-proven air insulation technique provides significant weight reduction and eliminates the unpleasant things associated with other dielectric mediums.
- 3.** *Your mother never told you* that Glassman employs the most advanced pulse-width modulated circuitry available in high voltage power supplies. Its use minimizes parts count and reduces complexity as compared to other designs.
- 4.** *Your mother never told you* when you need the most compact high power high voltage DC power supplies available, Glassman designs. . . manufacturers. . . and delivers them. On time, at competitive prices!
- 5.** *Your mother never told you* that Glassman has the widest range of high voltage switches available from. . . 1 watt to 15 kW, 0-1 kV to 0-600 kV, with unrivaled reliability. All backed by responsive service and a three year warranty!

*And just like mother. . .* Glassman gives you sound advice, loving support, and solutions to those problems that seem impossible. Don't you owe it to yourself to get all the facts on Glassman high voltage power supplies? Give us a call. The coffee's hot, the apple pie is fresh, and high voltage power supplies never were so good!

## Glassman High Voltage Inc.

Route 22 (East)  
Salem Industrial Park, PO Box 551  
Whitehouse Station, NJ 08889  
Telephone (201)534-9007  
TWX 710-480-2839  
FAX: (201)534-5672

CIRCLE NO 7

**GLASSMAN HIGH VOLTAGE INC.**





## Power MOSFETs yield efficient power supply

Marek Gajewski  
Litton Industries, Woodland Hills, CA

Using seven power MOSFETs in various capacities, the switch-mode power supply in Fig 1 offers a 15V output and a 20A, 5V regulated output featuring 90% efficiency and low output noise. Further, the output impedance is determined primarily by coil resistance and MOSFET on-resistance; in contrast, a switcher based on duty-cycle modulation exhibits an output impedance that's higher by a factor inversely proportional to the duty cycle.

Duty-cycle modulation is used on the input side of transformer  $T_1$ , however, where transistors  $Q_1$  through  $Q_3$  and the duty-cycle modulator make up a buck-type preregulator (the regulated 5V output bucks against a 5V reference).  $Q_3$  completes a path to ground for transistors  $Q_1$  and  $Q_2$ , which then can alternately ground the ends of  $T_1$ 's primary. The primary of saturable-core transformer  $T_2$  is connected to the secondary of  $T_1$  in a free-running loop, which provides 30-kHz gate-switching signals to  $Q_1$ ,  $Q_2$ , and the output syn-

chronous-rectifier transistors  $Q_4$  and  $Q_5$ .

Transformer  $T_3$  transfers the regulated 5V output back to the input-ground-referenced preregulator circuit to provide isolation between the input and output grounds.  $T_3$ 's primary is driven by a 4041-type true/complement buffer. Unlike optoisolators, this isolation module provides a near-unity transfer function that's insensitive to temperature and production tolerances.

To prevent power dissipation due to overlapping gate-drive signals to  $Q_1$  and  $Q_2$ , diodes  $D_6$  and  $D_7$  clamp  $T_2$ 's center tap near the output ground potential (the MOSFETs require at least 3V to turn on). Loop compensation is simplified by the absence of a filter capacitor following inductor  $L_1$ , which would form a second-order pole in the regulator's transfer function. On the other hand, transformed load capacitance forms a virtual capacitor at this position, providing energy storage during the preregulator's off cycle.

EDN

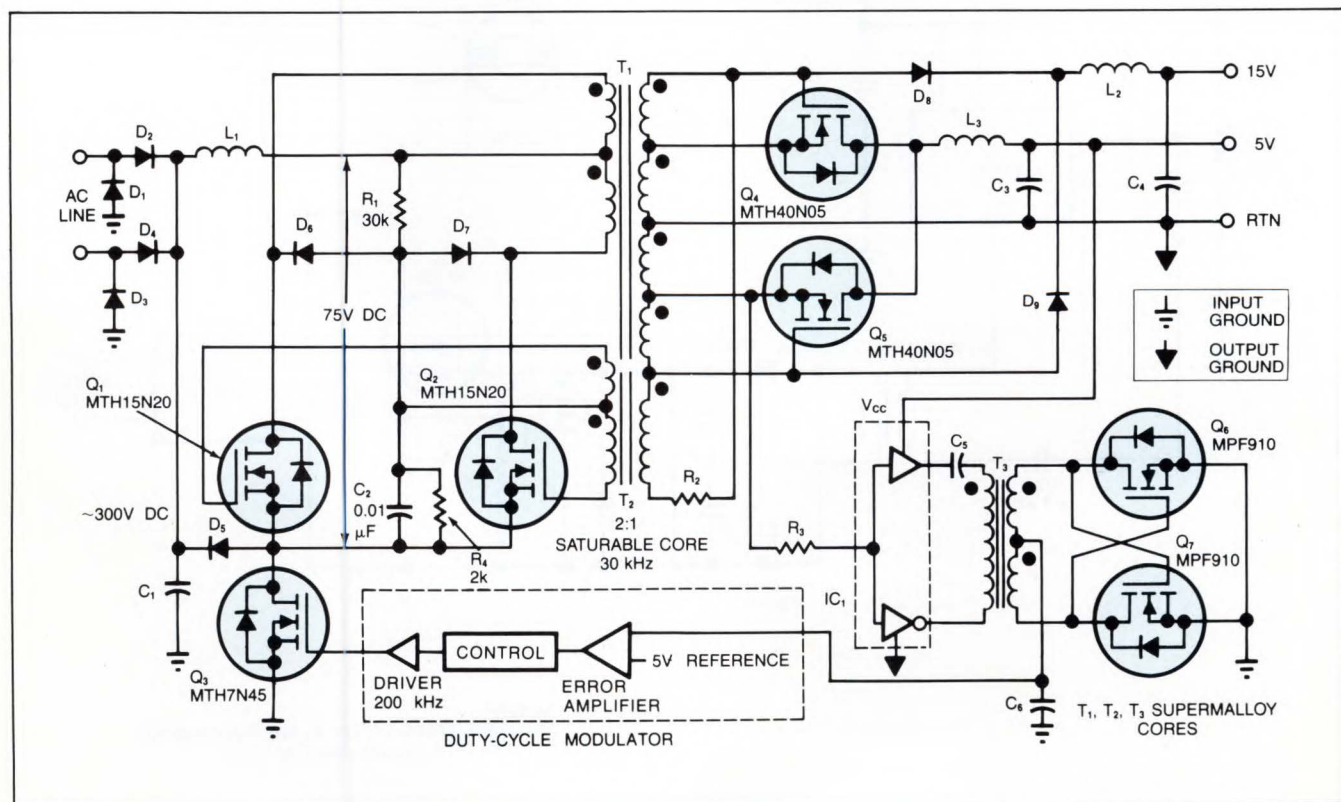


Fig 1—This switching regulator based on power MOSFETs includes a 200-kHz duty-cycle-modulated preregulator and a full-wave synchronous-rectifier output.



## Solid-state switch offers fast interrupt

Geoffrey N Drummond  
Hughes Aircraft, Torrance, CA

Based on a diode bridge and a VMOS power transistor ( $Q_1$ ), a solid-state switch (Fig 1) acts as a circuit breaker, sensing and interrupting an overcurrent condition within 2  $\mu$ sec. The circuit's isolation transformer,  $T_1$ , allows the switch to float. The components shown are capable of handling 1A rms or 8A pk. However, if your application requires the handling of more current, you can change  $R_1$ ,  $Q_1$ , and the bridge.

Compared with a thyristor, a VMOS transistor has higher saturation voltage—6 to 10V—and is less rugged—peak- to continuous-current ratio is about 4:1, vs

20:1 for a thyristor. To protect the MOSFET in the case of fault conditions, SCR  $Q_2$  exerts a crowbar action on the  $Q_1$  gate, minimizing power dissipation by forcing the transistor to turn off rapidly. The 555 timer forms an astable multivibrator that drives  $T_1$  at 150 kHz. A full-wave voltage doubler at the  $T_1$  secondary then provides 15V to the  $Q_1$  gate, which turns on the transistor and switch for normal operation.

Three overcurrent conditions will short circuit the transistor and turn off the switch. First, if resistor  $R_1$  senses excessive steady-state rms current, it will cause the switch to open at a threshold of  $R_1=0.6V/I$  rms.

Second, the circuit will accommodate time-variant currents (such as those encountered in a lamp or motor,

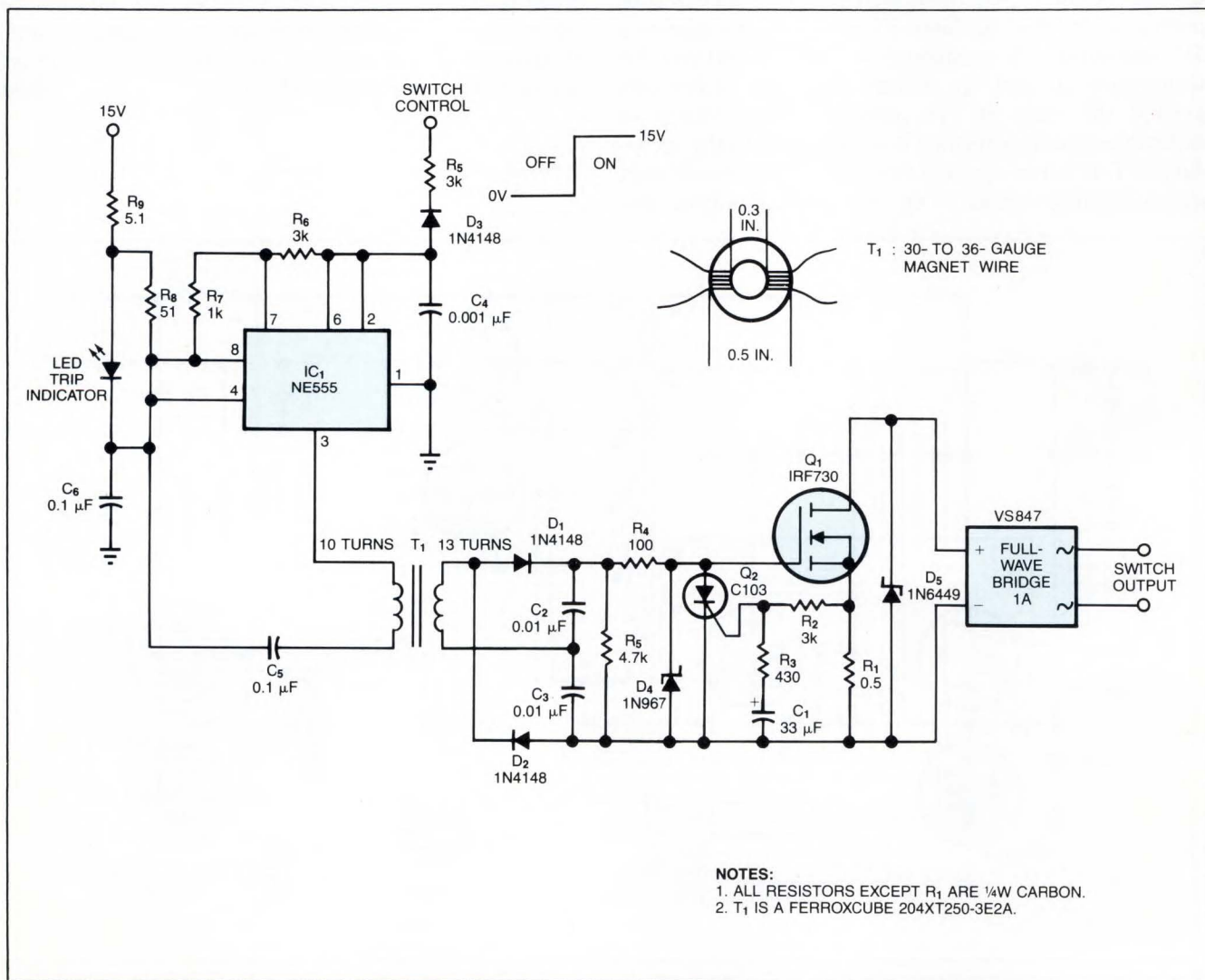


Fig 1—A floating, isolated solid-state switch interrupts fault currents in about two microseconds.



# DESIGN IDEAS

for example) in which the initial surge current is greater than the steady-state current. In this case, capacitor  $C_1$  limits the surge value by setting a limit on the ampere $\times$ second product ( $I \times t$ ) for currents between steady state and peak. This threshold is approximately


$$C_1 = I \times t \times R_1 / (0.6V \times R_2).$$

Third, you can set  $R_3$  to limit the peak current  $I_P$ , according to the relation

$$R_3 = 0.6V \times R_2 / (I_P \times R_1 - 0.6V).$$

After a delay of  $0.5 \mu\text{sec}$ , a peak current causes the switch to open completely in about two microseconds. In addition, the transient suppressor  $D_5$  limits peak voltage to 200V. Once tripped, the switch will remain off until the timer is gated off (Switch Control), or until you remove the timer's power for at least one second.

**Fig 2b** shows the results of a peak-current test (**Fig 2a**). The solid-state switch opened fully in  $2.25 \mu\text{sec}$ ; a 1A fast-blow fuse, on the other hand, passed 300A for  $10 \mu\text{sec}$  before opening, which welded the mercury relay's contacts together. **EDN**

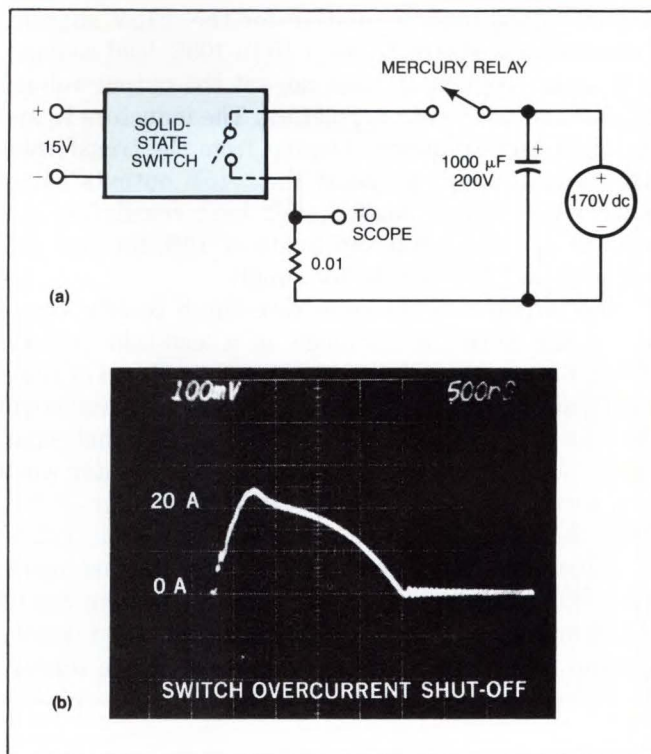

**Fig 2**—This test circuit (a) allows you to measure the delay and response time of the circuit breaker. The results are presented in b.

## Derive $\pm 15V$ and 5V from a 12V battery

Andy Jenkins

Maxim Integrated Products, Sunnyvale, CA

Parts for the triple-output dc/dc converter shown in **Fig 1** cost about \$11 in 100-piece quantities. The circuit converts the 12V output of a lead-acid battery to isolated  $\pm 15V$  supply voltages plus a nonisolated 5V supply voltage.

$IC_1$  is a switching-regulator chip normally used in step-up applications, but the transformer and circuit shown allow the device to provide a step-down function as well. The chip generates a 45-kHz signal that drives the gate of MOSFET  $Q_1$ .

$Q_1$  turns on when the gate voltage is high, causing a linear increase in  $T_1$ 's primary current, which stores energy in a magnetic field. The field starts to collapse as  $Q_1$  turns off, reversing the voltage polarity on all windings and causing the voltage on each secondary winding to increase. These secondary voltages then deliver energy to the outputs by forward-biasing the Schottky diodes  $D_1$ ,  $D_2$ , and  $D_3$ . When the 5V output rises above a desired level, feedback to the chip causes an internal error comparator to turn off the gate signal to  $Q_1$ .

The secondary-winding ratios set the output-voltage levels, and close coupling between the trifilar windings



# DESIGN IDEAS

assures good load regulation for the  $\pm 15\text{V}$  supplies (regulation is about 2% for a 10 to 100% load change). For better regulation, you can set the output voltage higher and add linear regulators. The inductors  $L_1$  and  $L_2$  block high-frequency ringing from the transformer that would otherwise boost the  $\pm 15\text{V}$  outputs out of spec when lightly loaded. For best regulation, you should provide minimum loads of 10% for the 15V supplies and 20% for the 5V supply.

The circuit can accommodate the 8 to 16V range associated with the terminals of a lead-acid battery. What's more, the protection network made up of resistor  $R_1$  and zener diode  $D_4$  allows the circuit to withstand 50V for 1 msec—a classic overvoltage test that simulates the load dump of an automobile's alternator when you turn off the ignition. For an input change of 8 to 16V, the 5V output's line regulation is typically 0.2%.

Battery current is about 600 mA for nominal operation, but current peaks in the primary winding can be 4A or more. Therefore, you should provide good-quality ground connections and short, low-impedance connec-

tions to the transformer and the MOSFET. Close decoupling using ceramic and electrolytic capacitors also reduces output noise. With proper circuit layout, the output noise is about 50 mV at the 5V output and 30 mV at the 15V outputs.

The transformer, constructed with a ferrite pot core that offers low loss and minimal magnetic leakage, has a primary inductance of about  $21\text{ }\mu\text{H}$  for the power levels shown. You must choose a core size and material that will handle the 4A peak currents without saturation. The 15V secondaries have 2.9:1 turns ratios, which provide the desired 3:1 voltage ratio after covering the rectifier losses. Actual turns are as follows: the primary,  $11\frac{1}{2}$  turns; the 15V secondaries,  $11\frac{1}{2}$  turns each; the 5V secondary, four turns. High circuit efficiency (about 75% at full load with a 12V input) eliminates any need for a heat sink on the MOSFET.

**EDN**

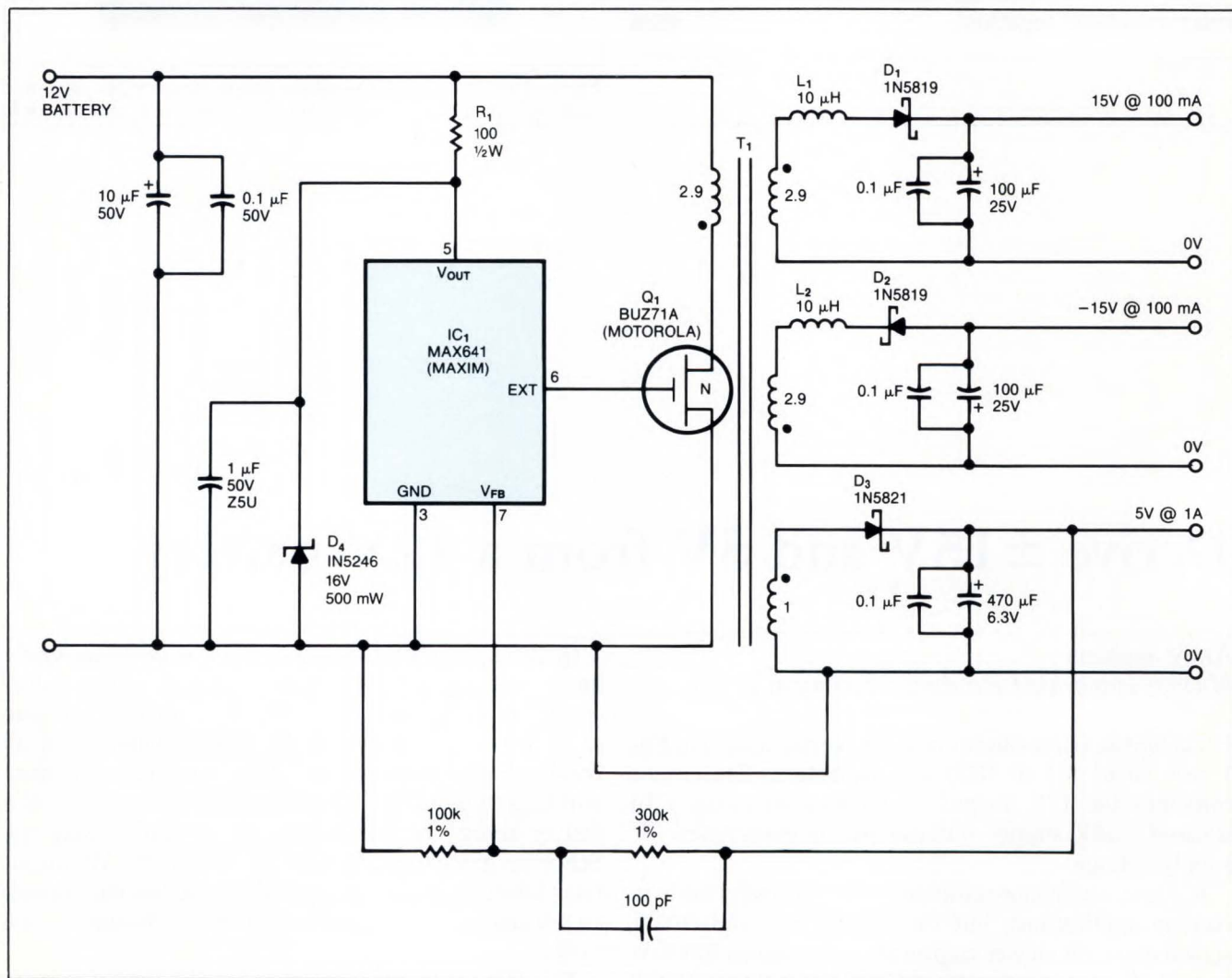


Fig 1—This triple-output dc/dc converter requires only one IC.



# Demanding Designers Need the Best

## OrCAD/SDT III

Schematic Design Tools for the PC



### Ease-of-use + Power = Productivity

In today's tough design environment, good engineering tools aren't good enough. You need the best to get the job done.

### OrCAD/SDT III offers the power

SDT III comes with the options you'd expect to pay extra for

- **Completeness:** A library of over 6100 parts that you can browse through in a breeze. Utilities to generate Bill-of-Materials, Electrical rules check, create custom library parts.
- **Compatibility:** Over thirty netlist formats, over 50 supported display adapters, over 50 printer drivers, a dozen plotter drivers. We conform to your system better than anyone.

- **Complexity:** 4000+ sheet design capacity for single designs. 200+ levels of hierarchy. Great support for small, simple designs to large, complex hierarchical systems.

- **Control:** SDT III gives you the ability to customize the work environment to make you more productive. This includes user definable macros, text/object sizes, sheet sizes, graphical object editor, even the colors on the screen.

### OrCAD/SDT III makes it easy

The lightning fast operation saves time. The intuitive, pop-up menu displays your most likely next action. This means a short learning curve and immediate productivity.

Only \$**495**

### Get our No-risk, Demo Disk

Try before you buy. Get our free demonstration disk and see for yourself the solid performance SDT III has to offer.

Once you've given our demo disk a spin, you'll know one of the reasons why OrCAD is the world's leading supplier of PC based CAE tools.

All OrCAD products come complete with one full year of technical telephone support, free product updates and access to our 24 hour BBS.



1049 S.W. Baseline Street Suite 500  
Hillsboro, Oregon 97123  
(503) 640-9488

If you would like more information about this or any other OrCAD product, contact your local OrCAD representative.



- |   |   |
|---|---|
| 1. WA, OR, MT,<br>ID, AK<br>Seltech, Inc.<br>(206)746-7970            | 9. IN, OH, KY, WV,<br>W. PA<br>Frank J. Campisano<br>(513)574-7111      |
| 2. N. CA, Reno NV<br>Elcor Associates Inc.<br>(408)980-8868           | 10. VA, TN, NC, SC<br>Tingen Technical<br>Sales<br>(919)870-6670        |
| 3. So. CA<br>A D G<br>(714)897-0319                                   | 11. FL<br>High Tech Support<br>(813)920-7564                            |
| 4. Las Vegas, UT, AZ,<br>NM, CO<br>Tusar Corporation<br>(602)998-3688 | 12. MS, AL, GA<br>Electro-Cadd<br>(404)446-7523                         |
| 5. ND, SD, MN, W. WI<br>Comstrand, Inc.<br>(612)788-9234              | 13. DE, MD, DC, E. PA,<br>NJ, NY<br>Beta Lambda, Inc.<br>(201)446-1100  |
| 6. NE, KS, IA, MO<br>Walker Engineering<br>(913)888-0089              | 14. CT, RI, MA, VT,<br>NH, ME<br>DGA Associates<br>(617)935-3001        |
| 7. TX, OK, AR, LA<br>Abcor, Inc.<br>(713)486-9251                     | 15. BC, AB, SK, MB<br>Interworld<br>Electronics, Ltd.<br>(604) 984-4171 |
| 8. MI, E. WI, IL<br>MacKellar Associates<br>(313)335-4440             | 16. ON, PQ & Maritimes<br>Electralert, LTD.<br>(416)475-6730            |

**Call today for your FREE Demo Disk!**



## Low-current voltage tripler is inexpensive

Henry Yiu  
Endevco, San Juan, CA

You can expand the low-cost (\$2.25) voltage tripler of Fig 1 by adding more stages, and you can lower the circuit's output impedance by adding more buffer inverters in parallel. To obtain a negative-voltage converter, simply reverse the diode and capacitor polarities and connect the  $V_{IN}$  terminal to ground. The circuit oscillates at approximately 350 kHz when  $R_{OSC}=1\text{ k}\Omega$  and at approximately 4 kHz when  $R_{OSC}=100\text{ k}\Omega$ . For the circuit as shown, Fig 2 charts the efficiency and the load voltage vs load current. **EDN**

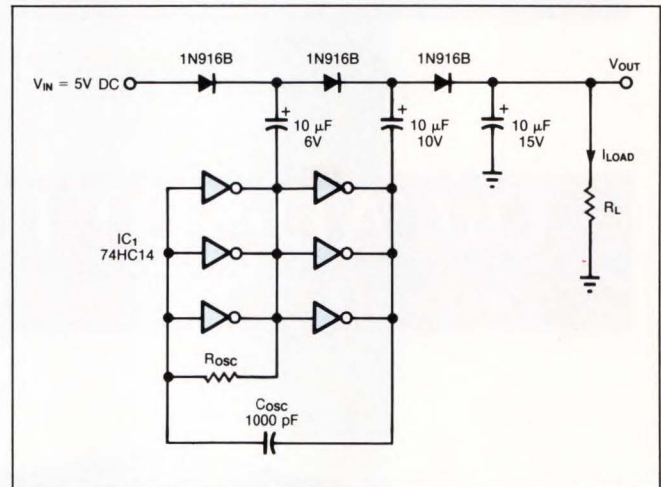


Fig 1—This circuit generates a 15V output by tripling  $V_{IN}$ .

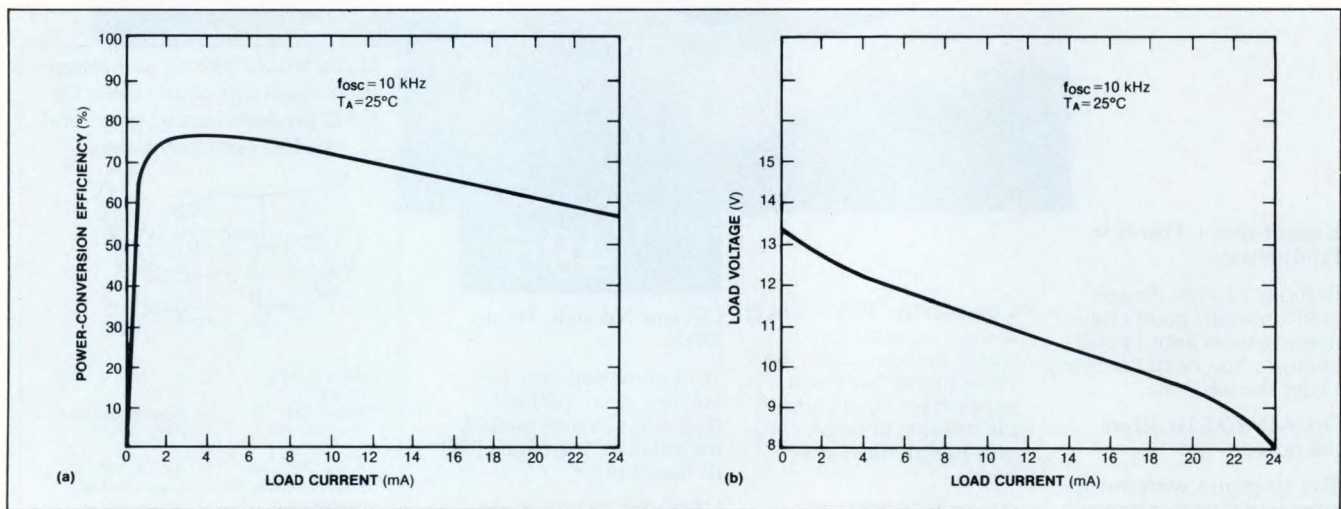


Fig 2—These curves show Fig 1's power-conversion efficiency (a) and load voltage (b) vs load current.

## Sampling phase detector simplifies a PLL

Russell Kautz  
Texas Instruments, Plano, TX

Phase-locked loops can include an analog frequency-mixing circuit (Fig 1a) or a digital divider (Fig 1b) to

accomplish synchronous down-conversion of the reference and input frequencies. An alternative, the sampling system in Fig 1c, reduces parts count and cost by a factor of eight. Moreover, the sampling approach removes frequency-conversion circuitry from the signal





# OUR POWER SUPPLY SURVIVED.



In a Navy test, a Tomahawk cruise missile exploded into a concrete building. When the dust settled, little remained but gravel and fragments of casing.

And the Abbott model C28D0.8 you see here.


Its aluminum baseplate and an adjustment cap were ripped off in the blast. But reconnected on a workbench, the

unit still provided a steady .8 amp of DC current — just as it was designed to.

Abbott Transistor Laboratories, Inc.  
2721 South La Cienega Blvd.,  
Los Angeles, CA 90034. (213) 936-8185

When reliability is imperative®

**abbott**  
MILITARY POWER SUPPLIES

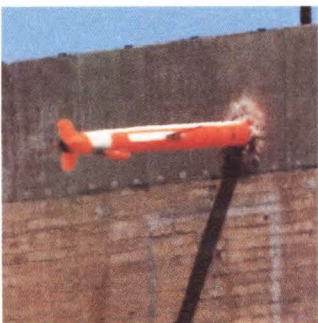





# DESIGN IDEAS

path, which provides improved short-term stability for the local oscillator, excellent temperature stability, and a thirtyfold decrease in lock-in time.

**Fig 2** demonstrates a sampling phase-detector loop that locks the output of a crystal oscillator to that of a rubidium standard. First, the zero-crossing detectors

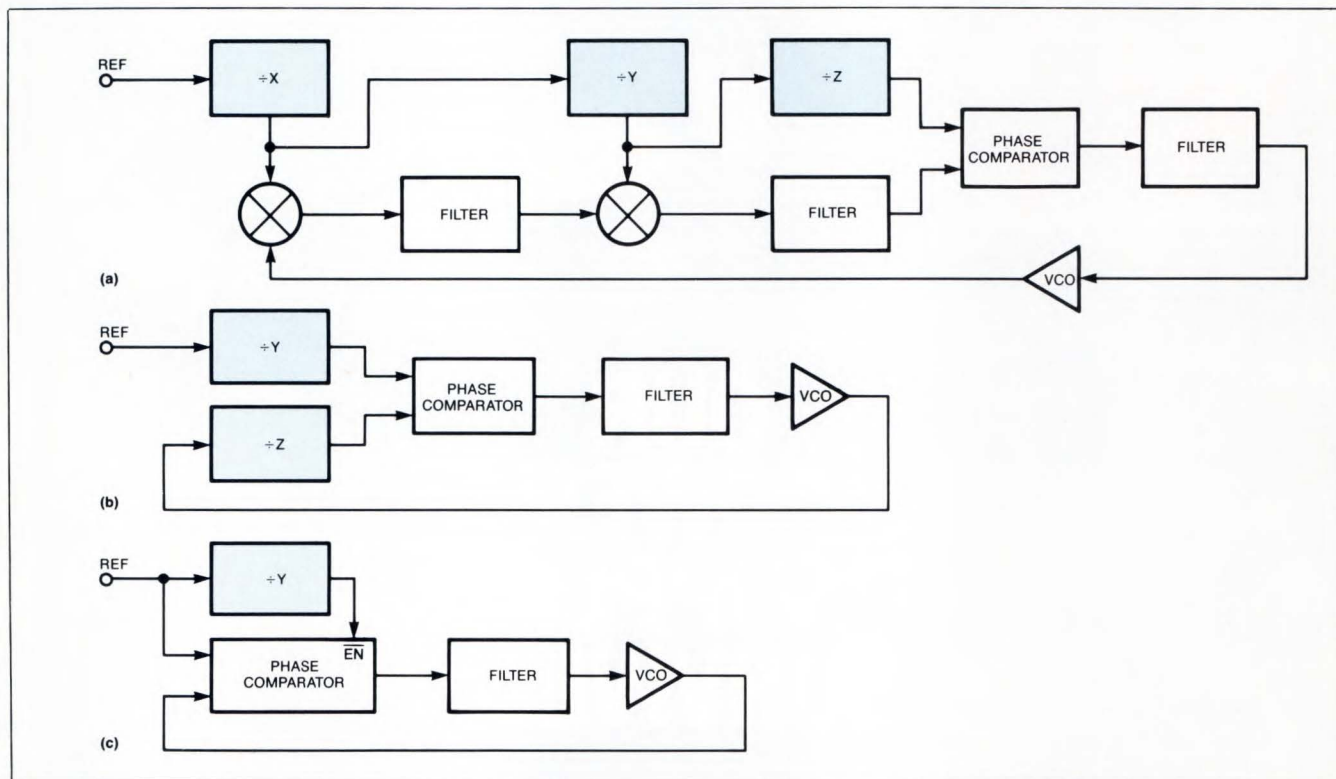

**Fig 1**—Some phase-locked loops use analog frequency-mixing techniques (a), and some divide both inputs to the phase comparator using digital dividers (b). The sampling phase comparator (c) achieves advantages by eliminating down-conversion circuitry from the signal paths.

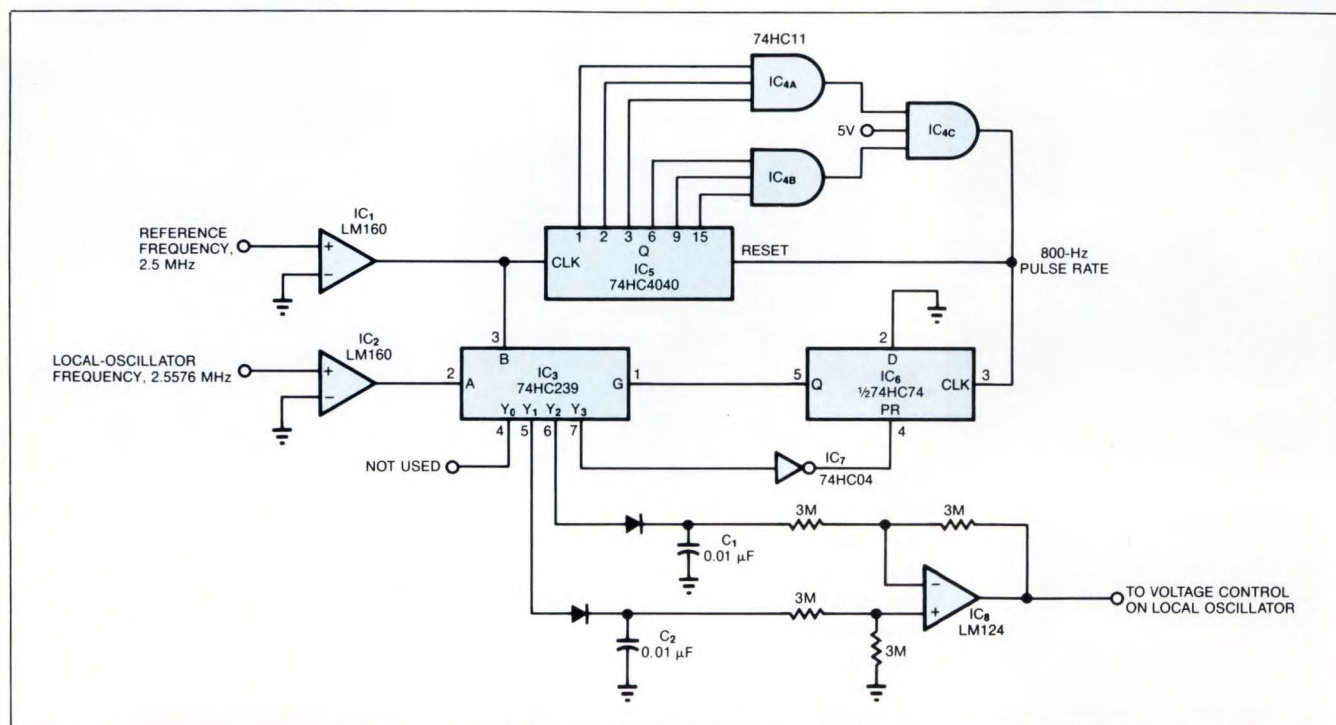

**Fig 2**—This sampling phase-locked loop generates a voltage output whose polarity and magnitude represent the local oscillator's phase error.



# DESIGN IDEAS

IC<sub>1</sub> and IC<sub>2</sub> convert the reference and local-oscillator (LO) frequencies to digital signals. The 2-to-4-line demultiplexer IC<sub>3</sub> then samples these frequencies at 800 Hz (every 1.25 msec). The reference and LO frequencies may differ, but each must be an integral multiple of the sampling rate if the system is to achieve lock.

To set the sampling period, IC<sub>4A</sub> and IC<sub>4B</sub> wait for the output 110000110101 (count of 3125) from the 12-bit counter IC<sub>5</sub>. When that output occurs, IC<sub>4C</sub> issues a brief positive pulse that resets the counter and toggles the flip-flop IC<sub>6</sub>.

Fig 3 illustrates the digital phase detection that the IC<sub>3</sub> demultiplexer performs. The presence of Y<sub>1</sub> indicates a phase lead between the LO and reference frequencies, and the duration of Y<sub>1</sub> indicates the

amount of phase lead. Similarly, Y<sub>2</sub> indicates phase lag. Y<sub>3</sub> goes high when both inputs are high, which ends the sample period by setting the flip-flop.

Note that in Fig 2 C<sub>1</sub> and C<sub>2</sub> convert the Y<sub>1</sub> and Y<sub>2</sub> pulses to voltage inputs for the differential amplifier IC<sub>8</sub>. The amplifier in turn produces a dc voltage representing polarity and magnitude of the local oscillator's phase error. When locked, the loop produces narrow Y<sub>1</sub> and Y<sub>2</sub> pulses (less than 1 nsec) of equal magnitude and duration. The amplifier rejects common-mode signals such as digital noise from the demultiplexer. **EDN**

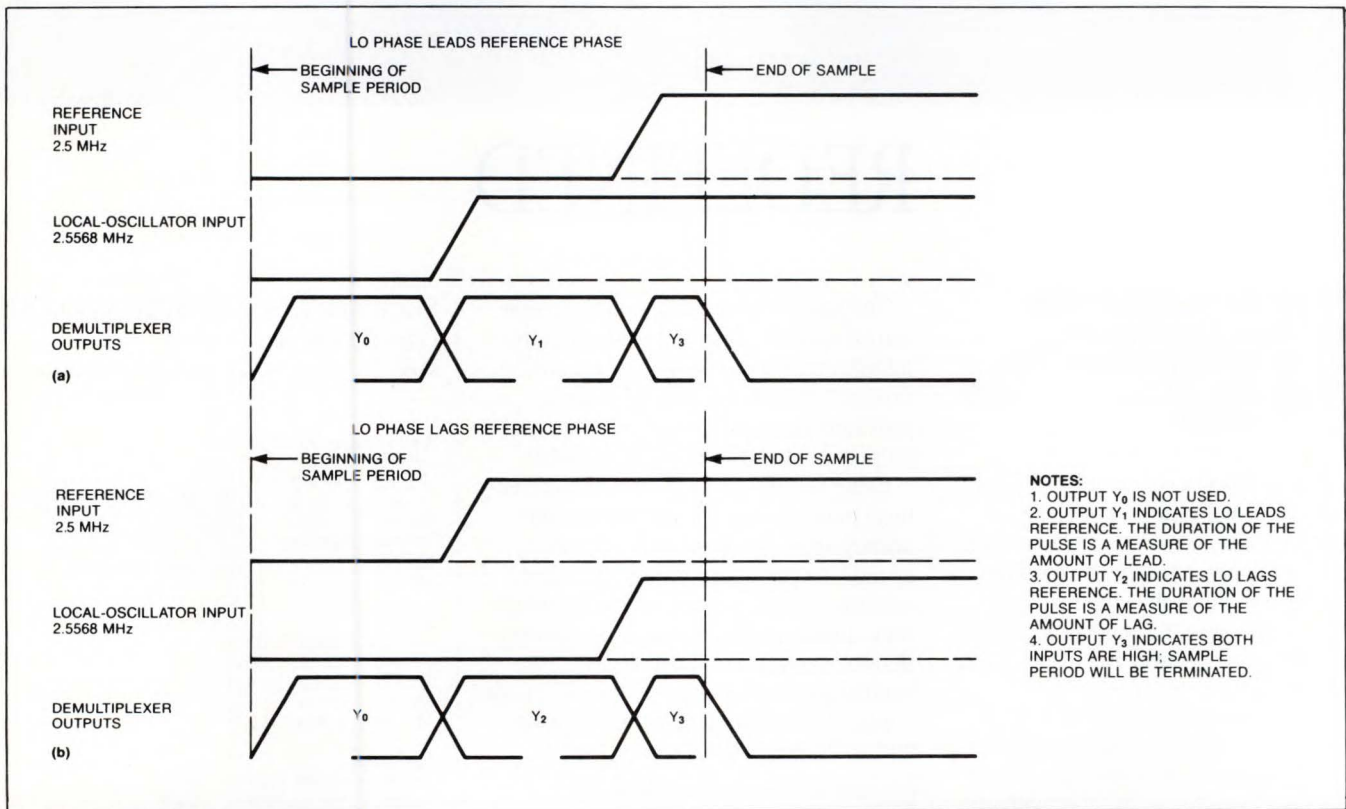


Fig 3—These waveforms depict Fig 2's operation for the cases of leading phase (a) and lagging phase (b).

## Zero-current sensor protects relay contacts


B Erik Valeur  
Electronic Instrument & Specialty Corp,  
Stoneham, MA

The Fig 1 circuit extends the life of a reed relay by allowing the relay's contacts to open only at moments of

zero current. (Destructive arcing can cause rapid contact wear if the contacts open repeatedly while conducting current.) Unlike zero-crossing circuits that predict the zero-current moment, this circuit senses that condition and responds immediately, using a fast relay (K<sub>1</sub>, 100  $\mu$ sec).



# THE POWER SUPPLY

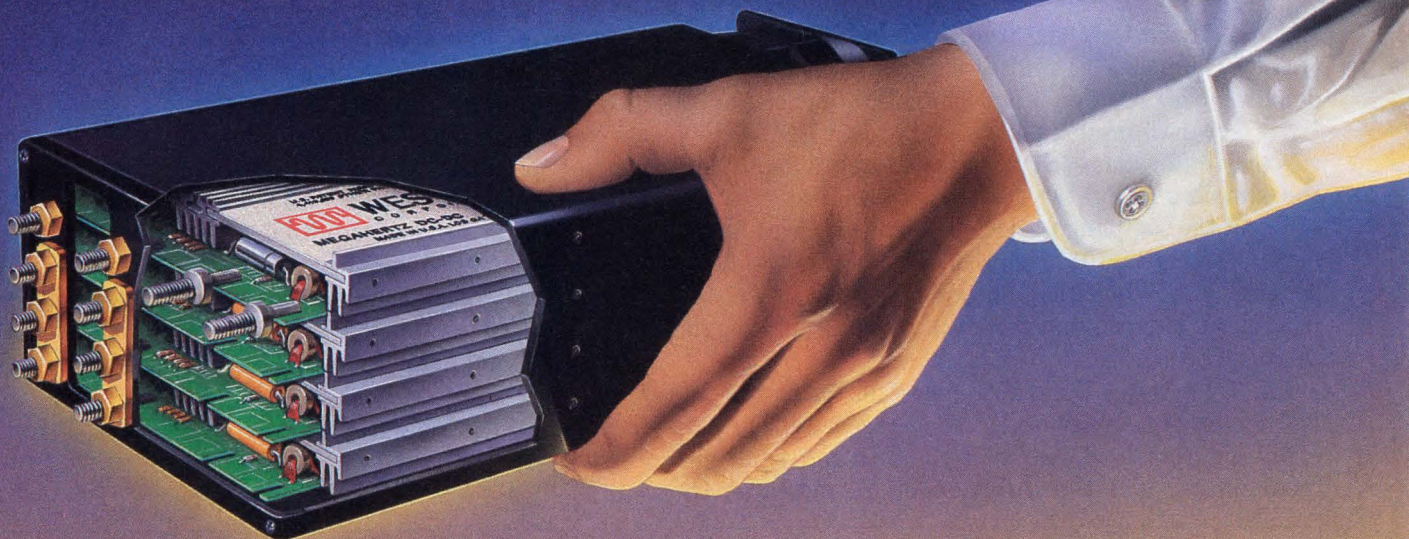

## REDEFINED


### THE WESTCOR STAKPAK™. NEW GENERATION 250 TO 1200 WATT SINGLE OR MULTIPLE OUTPUT OFF-LINE SWITCHER. 3.2 X 5.5 X 11.4 INCH CASE. FAN-COOLED.

Stack the odds in your favor by designing-in Westcor's 6 watt/cubic inch high power megahertz switcher. Capitalizing on patented and proven megahertz module technology and innovative thermal management techniques, the StakPak provides up to 1200 watts of power at 50°C with 1 to 8 isolated and fully regulated outputs.

For existing designs the StakPak's small size and low profile allow system enhancement without mechanical redesign. Simply replace your open frame switcher with up to 1200 watts of StakPak power or replace your "box switcher" with 2 StakPaks and realize up to twice the power without losing additional space. StakPak power factor correction provides 850 watts of output power from a standard 115 VAC wall outlet. In new designs, more space can be devoted to functionality or the system can be downsized.

The StakPak's 8 module output section can be factory configured in virtually an infinite number of voltage, current and power combinations. Special models providing between 250 to 1200 watts and outputs from 2 to 95 VDC are available.

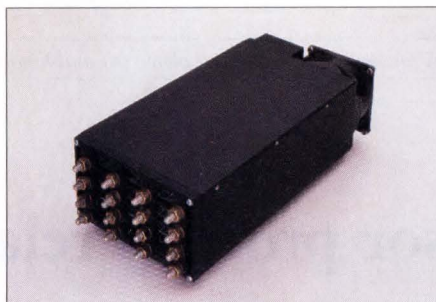Other features include outstanding electrical performance; UL, CSA, VDE safety agency approval (in process); variable speed fan option for low ambient noise environments and 3 phase or DC input options. Indeed, with unprecedented power density, versatility and new features, the StakPak redefines power packaging. Please contact Westcor for a data sheet, pricing and additional information.



### STANDARD 1200 WATT STAKPAK MODELS (110/220 VAC input)

Model Output Voltage (VDC) and Maximum Current (amperes) per Channel

	#1	#2	#3	#4	#5
<b>Single Output</b>					
SP1-1801	2 @ 240				
SP1-1802	5 @ 240				
SP1-1803	12 @ 100				
SP1-1804	15 @ 80				
SP1-1805	24 @ 50				
SP1-1806	28 @ 42				
SP1-1807	48 @ 25				

Total output power may not exceed 1200 watts for any model, single or multiple output. Lower power StakPak models are available. Please contact the factory.

<b>Dual Output</b>					
SP2-1801	2 @ 120	5 @ 120			
SP2-1802	5 @ 120	5 @ 120			
SP2-1803	5 @ 120	12 @ 66			
SP2-1804	12 @ 66	12 @ 66			
SP2-1805	15 @ 53	15 @ 53			


<b>Triple Output</b>					
SP3-1801	5 @ 180	12 @ 16	12 @ 16		
SP3-1802	5 @ 150	12 @ 33	12 @ 16		
SP3-1803	5 @ 180	15 @ 13	15 @ 13		
SP3-1804	5 @ 150	15 @ 26	15 @ 13		

<b>Quad Output</b>					
SP4-1801	5 @ 150	12 @ 16	12 @ 16	5 @ 30	
SP4-1802	5 @ 150	15 @ 13	15 @ 13	5 @ 30	
SP4-1803	5 @ 150	12 @ 16	12 @ 16	24 @ 8	
SP4-1804	5 @ 150	15 @ 13	15 @ 13	24 @ 8	


<b>Five Output</b>					
SP5-1801	5 @ 120	12 @ 16	12 @ 16	5 @ 30	24 @ 8
SP5-1802	5 @ 120	15 @ 13	15 @ 13	5 @ 30	24 @ 8



WESTCOR CORPORATION • 485-100 Alberto Way • Los Gatos, CA 95032 • (408) 395-7050 • FAX (408) 395-1518

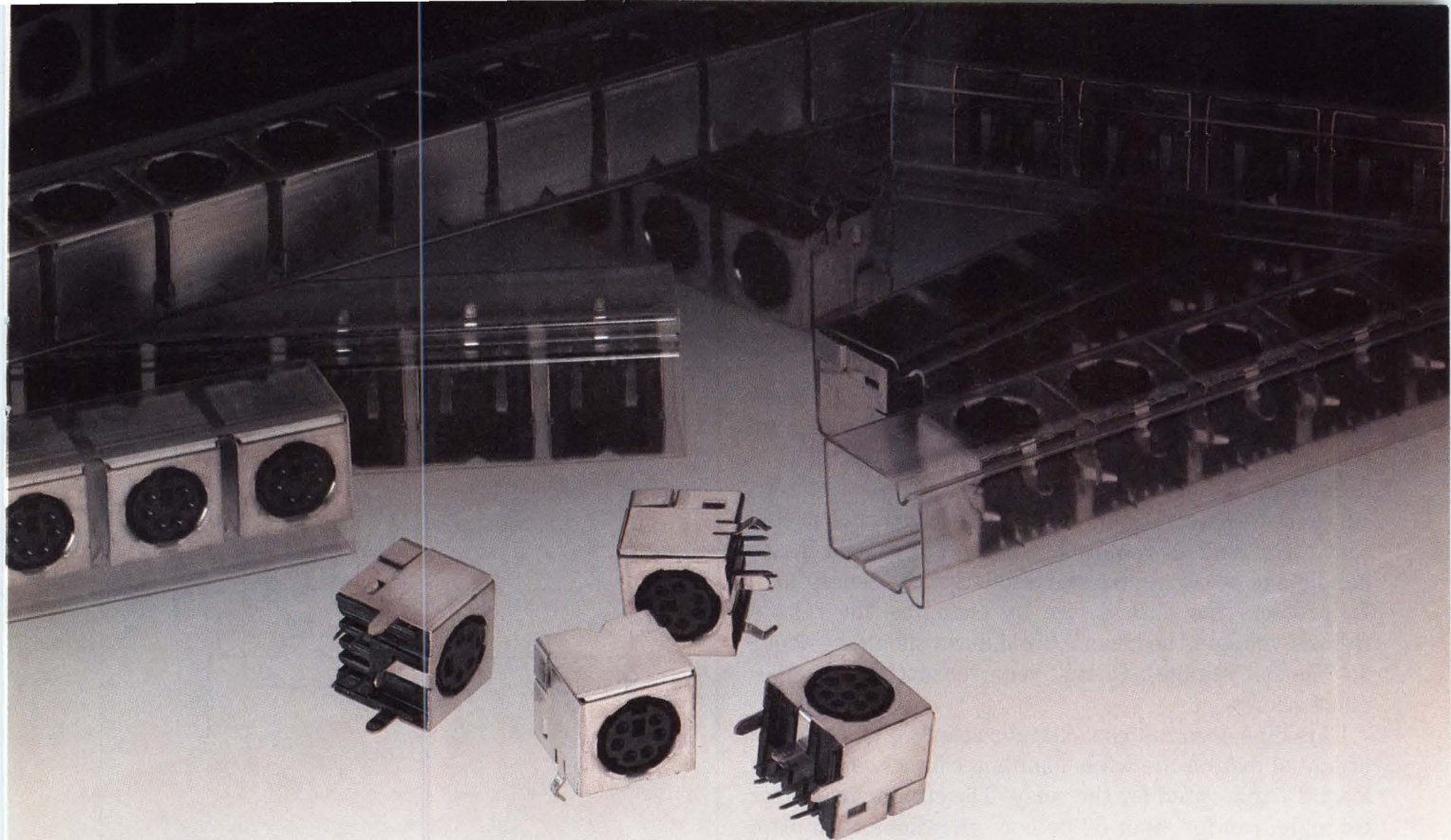Westcor is a subsidiary of  VICOR CORPORATION





# Many minis. Mini wait.

AMP shielded miniature circular DIN receptacles are available in production quantities. Right now.

With all the features and options you need. And a mini-leadtime of four weeks ARO.

The one-piece shield (in tin-plated copper alloy) uses cantilever beam contacts to provide an uncomplicated low-impedance path from plug shield to pcb ground. An optional hold-down feature secures connector to board during processing.


Available in 3 through 8 positions, these right-angle pcb-mount receptacles feature precision-formed,

*Automateable: surface for vacuum pickup, gripper locating datum.*

*Shielded mating face.*

*Polarization & keying.*

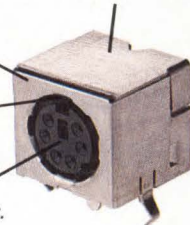*High-temp housing for reflow processes.*



gold-plated contacts for long life and max reliability, and tin-plated tails for easy soldering. They mate with standard or latching cable connectors, and have built-in polarization and keying.

Design highlights: no stubbing, positive contact retention prevents backout, and the envelope is a cube only 1/2" to a side. Plus: 94V-0 rated housing material (tolerates high-temp solder reflow procedures), positioning datum and surface area for vacuum pickup, and packaging for robotic applications.

**Call 1-800-522-6752 for product information and the name of your nearby AMP Authorized Distributor. AMP Incorporated, Harrisburg, PA 17105-3608.**

## **AMP** Interconnecting ideas




## DESIGN IDEAS

The on/off switch  $S_1$  controls the application of  $V_{\text{SUPPLY}}$  to the load by controlling  $K_1$ . Load current biases one of the diode pairs on, which in turn activates one of two LEDs in the optocoupler. This action turns on the phototransistor, ensuring that the relay remains closed while load current is flowing regardless of the state of  $S_1$ .

Conventional 60-Hz ac current, however, goes through zero twice per cycle, about every 8 msec. At that time the phototransistor turns off, and (if you have opened S<sub>1</sub>) K<sub>1</sub> opens, at or near the moment of zero current. Resistor R<sub>1</sub> limits the LED current if necessary. (No limit is required in this circuit, which can handle one or two amperes.) Similarly, the zener diode D<sub>1</sub> protects the opto device by clamping the relay's flyback voltage (the zener's breakdown should be about 4× the coil voltage). D<sub>1</sub> isn't required with the components shown.

This type of circuit can extend a relay's life by several orders of magnitude while handling contact currents at least  $2\times$  that rated for the relay. The circuit shown, for example, ran for 40 or 50 million operations with little evidence of wear and no signs of contact breakdown.

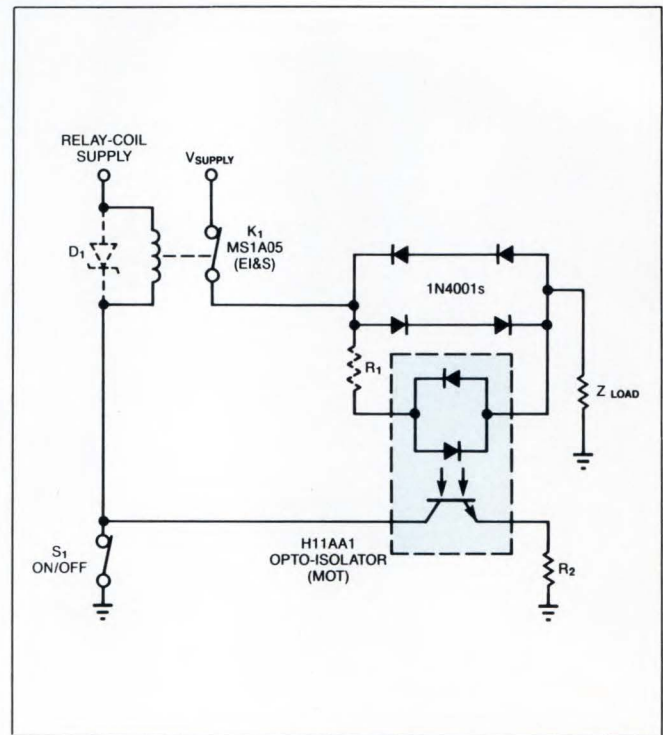**EDN**

**Fig 1—You control this power circuit by operating the  $S_1$  switch; the diodes and the optoisolator prevent a response in the relay except when the relay contacts' current is near zero.**

## Program calculates best-fit 1% resistors

Mick Murray  
*Lab-Line Instruments, Franklin Park, IL*

When designing a voltage divider to establish a critical reference voltage in circuits such as comparators and offset-voltage sources, engineers commonly use a non-optimum trial-and-error approach for choosing an acceptable combination of resistors. The Basic program shown in **Fig 1a** calculates the best possible combination of 1% resistors for the voltage-divider circuit in **Fig 1b**. It takes about 11 minutes to run on the Intel MDS-230 computer.

The program prompts you for the most positive

string voltage ( $V_1$ ), the most negative string voltage ( $V_2$ ), and the voltage that you want the divider to generate ( $V_3$ ). Once you've entered these values, the program calculates  $R_1$  and  $R_2$  using a table of standard, precision, 1% resistance values (96 values per decade). The program can handle resistor ratios as large as 1000:1.  $V_1$ ,  $V_2$ , and  $V_3$  may be any combination of positive and negative voltages.

To determine the best possible resistor values, the program calculates the voltage divider's output for every combination of the 96 resistor values stored in its table. As the program tests each resistor combination, it stores the best combination that it has found to that



# DESIGN IDEAS

point. Each time the program finds a better combination, it stores that combination and prints it out on the screen. The program also displays its progress on the screen.

When the program is finished, it displays values for  $R_1$  and  $R_2$  and the actual voltage that  $R_1$  and  $R_2$  generate when used in the circuit's configuration. You

can scale these values to meet your impedance needs. Line 1180 sounds a bell to let you know that the program is finished.

**EDN**

```
(a) 10 REM *****
20 REM
30 REM      1% PRECISION RESISTOR FINDING PROGRAM
40 REM      COPYRIGHT 1984 MICK MURRAY
50 REM      LAB-LINE INSTRUMENTS INC.
60 REM
70 REM *****
80 REM
90 FOR T=1 TO 24:PRINT:NEXT
100 PRINT"*****"
110 PRINT:PRINT"      1% PRECISION RESISTOR FINDING PROGRAM"
120 PRINT:PRINT"*****"
130 PRINT:PRINT
140 PRINT"THIS PROGRAM WILL FIND THE TWO CLOSEST VALUES OF"
150 PRINT"THE 96 STANDARD 1% RESISTOR DECADE, TO GENERATE"
160 PRINT"A SPECIFIED VOLTAGE ('V3') DETERMINED BY THE "
170 PRINT"GIVEN STRING VOLTAGES ('V1'&'V2'). IT WILL ASK"
180 PRINT"YOU FOR THE STRING VOLTAGES, AND WHAT THE"
190 PRINT"GENERATED (V3) VOLTAGE THAT YOU WISH TO OBTAIN"
200 PRINT"IS. IN ALL CASES, V1 SHOULD BE GIVEN AS THE MOST"
210 PRINT"POSITIVE, V2 THE MOST NEGATIVE, AND V3 ANYWHERE"
220 PRINT"BETWEEN THE TWO."
230 PRINT"      R1 & R2 WILL CONTINUALLY BE DISPLAYED "
240 PRINT"DURING THE COURSE OF COMPUTATION, AS THE"
250 PRINT"TWO CLOSEST VALUES FOUND UP TO THAT TIME."
260 PRINT"      R1 IS THE RESISTOR TIED TO THE MOST POSITIVE VOLTAGE,"
270 PRINT"AND R2 IS THE RESISTOR TIED TO THE MOST NEGATIVE VOLTAGE."
280 PRINT:PRINT:PRINT
290 INPUT"TYPE <RETURN> TO CONTINUE...";BG$
300 FOR J=1 TO 5:PRINT:NEXT J
310 DIM D(96)
320 DIM F(96)
330 INPUT"INPUT V1 (MOST POSITIVE STRING VOLTAGE): ";V1
340 INPUT"INPUT V2 (MOST NEGATIVE STRING VOLTAGE): ";V2
350 IF V2>=V1 THEN 1290
360 INPUT"INPUT V3 (DESIRED GENERATED VOLTAGE): ";V3
370 IF V3<=V2 OR V3>=V1 THEN 1310
380 X=((V1-V2)-V3+V2)/(V3-V2)
390 PRINT "RATIO FOR COMPUTATION =";X
400 REM 'T' IS 1 IF R1>R2;T=2 IF R1<R2
410 IF X<1 THEN 440
420 T=1
430 GOTO 450
440 T=2
450 REM T=1 IF R1>R2 : T=2 IF R2>R1
460 FOR I=1 TO 96
470 READ D(I)
480 NEXT I
490 RESTORE
500 FOR I=1 TO 96
510 READ F(I)
520 NEXT I
530 R1=1
540 R2=1
550 IF X>1 THEN 580
560 A1=1
570 GOTO 590
580 A1=X
590 FOR I=1 TO 96
600 IF Y=0 THEN 690
610 FOR W=1 TO 5:PRINT:NEXT W
620 PRINT Y "OUT OF 96 COMPUTATIONS DONE: BEST SO FAR ARE:"
630 M$="*****"
640 PRINT M$
650 PRINT "R1=" R1", & R2=" R2
```

**Fig 1—Choosing the best possible resistor combination for a voltage divider (b) is a tedious trial-and-error process. A Basic program (a) helps alleviate this tedium by automatically choosing these values for you.**




# DESIGN IDEAS

```

660 PRINT "RATIO OF R1/R2=" R1/R2 ":: DESIRED RATIO IS "X"."
670 PRINT M$
680 PRINT TAB(30);"PLEASE HOLD..."
690 Y=Y+1
700 FOR M=1 TO 96
710 IF T=1 THEN 740
720 Z=F(M)
730 GOTO 750
740 Z=D(I)
750 IF X>9.760002 THEN 780
760 IF X<.102459 THEN 780
770 GOTO 870
780 IF X>97.6 THEN 820
790 IF X<.0102459 THEN 820
800 Z=10*Z
810 GOTO 870
820 IF X>976 THEN 860
830 IF X<1.02459E-03 THEN 860
840 Z=100*Z
850 GOTO 870
860 Z=1000*Z
870 IF T=1 THEN 900
880 A2=D(I)/Z
890 GOTO 910
900 A2=Z/F(M)
910 A3=ABS (A2-X)
920 IF A3 A1 THEN 1000
930 A1=A3
940 IF T=1 THEN 980
950 R1=D(I)
960 R2=Z
970 GOTO 1000
980 R1=Z
990 R2=F(M)
1000 NEXT M
1010 NEXT I
1020 PRINT "DESIRED R1/R2 RATIO WAS ";X
1030 PRINT"THE BEST THAT I CAN DO FOR YOU WITH"
1040 PRINT"THE STANDARD 96 1% RESISTER VALUES"
1050 PRINT"ARE:"
1060 PRINT "R1= ";R1" OHMS"
1070 PRINT "R2= ";R2" OHMS"
1080 PRINT "RATIO OF R1/R2 = ";R1/R2
1090 PRINT "FOR V1="V1" VOLTS; V2="V2" VOLTS; &V3="V3" VOLTS."
1100 PRINT"*****"
1110 PRINT"*****"
1120 PRINT"***** USE R1="R1" OHMS, & R2="R2" OHMS! *****"
1130 PRINT"*****"
1140 PRINT"*****"
1150 PRINT"RESULTS IF R1=" R1 ", AND IF R2=" R2 "IS:"
1160 PRINT"V3 WILL BE: "(((V1-V2)*R2)/(R1+R2))+V2 "VOLTS!!"
1170 PRINT"
1171 REM SOUND ROUTINE: FINISHED CALCULATIONS
1179 PRINT"CALCULATIONS COMPLETED. "
1180 PRINT CHR$(7);:FOR T=1TO1000:NEXT:TOTO1180
1190 END
1200 DATA 1.00,1.02,1.05,1.07,1.10,1.13,1.15,1.18,1.21,1.24
1210 DATA 1.27,1.30,1.33,1.37,1.40,1.43,1.47,1.50,1.54,1.58
1220 DATA 1.62,1.65,1.69,1.74,1.78,1.82,1.87,1.91,1.96,2.00
1230 DATA 2.05,2.10,2.15,2.21,2.26,2.32,2.37,2.43,2.49,2.55
1240 DATA 2.61,2.67,2.74,2.80,2.87,2.94,3.01,3.09,3.16,3.24,3.32
1250 DATA 3.40,3.48,3.57,3.65,3.74,3.83,3.92,4.02,4.12,4.22,4.32,4.42
1260 DATA 4.53,4.64,4.75,4.87,4.99,5.11,5.23,5.36,5.49,5.62,5.76,5.9
1270 DATA 6.04,6.19,6.34,6.49,6.65,6.81,6.98,7.15,7.32,7.5,7.68,7.87
1280 DATA 8.06,8.25,8.45,8.66,8.87,9.09,9.31,9.53,9.76
1290 PRINT:PRINT"V1 MUST BE THE MOST POSITIVE VOLTAGE, AND"
1300 PRINT"V2 MUST BE THE MOST NEGATIVE VOLTAGE! PLEASE RE-INPUT:":PRINT:GOTO 33C
1310 PRINT:PRINT"V3 IS THE DESIRED GENERATED VOLTAGE DETERMINED BY R1 AND R2,"
1320 PRINT"AND MUST LIE BETWEEN V1 AND V2!"
1330 PRINT" PLEASE RE-ENTER DESIRED V3 VOLTAGE:":PRINT:GOTO 360

```

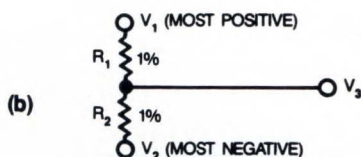



# To Brighten-up Your Display Innovations


...turn onto itron VFD super-smart modules.

- ☐ HIGH VISIBILITY    ☐ LOW POWER
- ☐ SURFACE-MOUNT TECHNOLOGY
- ☐ LONG-TERM RELIABILITY
- ☐ 5Vdc POWER SUPPLY OPERATION

*Noritake*  
WORLDWIDE FOR  
*itron*<sup>®</sup>

VACUUM FLUORESCENT  
DISPLAYS    ☐ MODULES

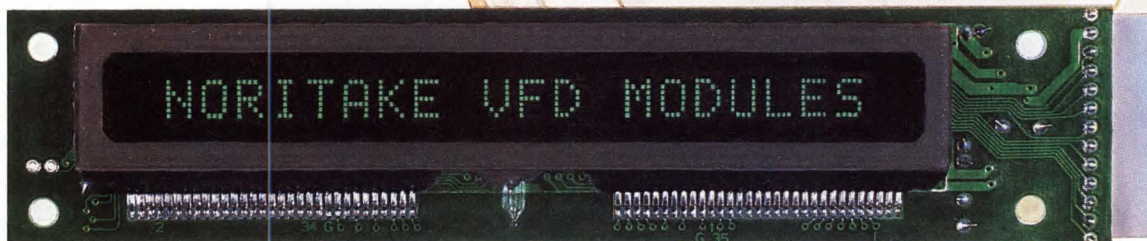Patented and manufactured by  
ISE ELECTRONICS CORP.



Model CU205SCPB

## DOT CHARACTER DISPLAY MODULES

CHARACTER FORMAT	MODEL NUMBER	NUMBER OF CHARACTERS	CHARACTER HEIGHT (MM)	INPUT (SERIAL/ PARALLEL)	BI-DIRECT BUS
5 x 7 DOT MATRIX	CU165SCPB-S	1 x 16	5.0	S/P	
	CU169SCPB-L	1 x 16	9.0	P	X
	CU205SCPB-S	1 x 20	5.0	S/P	
	CU209SCPB-L	1 x 20	9.2	P	X
	CU2015SCPB-L	1 x 20	15.1	P	X
5 x 7 DOT MATRIX PLUS CURSOR	CU406SCPB-S	1 x 40	5.0	P	X
	CU20026SCPB-S	2 x 20	5.1	P	X
	CU40026SCPB-S	2 x 40	5.0	P	X
	CU40046SCPB-S	4 x 40	5.0	S/P	X
	CU40066SCPB-S	6 x 40	5.0	S/P	X
	CU40086SCPB-S	8 x 40	5.0	P	X

The models shown are typical examples of the broad selection available for immediate delivery. Contact our nearest Sales Office or Representative to help select the right Noritake VFD for your application as well as for details on costs, custom designs, etc.

## NORITAKE SALES OFFICES

NORITAKE CO., INC. ☐ Electronics Division

LA: 23820 Hawthorne Blvd. ☐ Suite 100 ☐ Torrance, CA 90505  
Phone: (213) 373-6704 ☐ FAX: (213) 772-3918

CHICAGO: 415 E. Golf Rd. ☐ Suite 109 ☐ Arlington Hts., IL 60005  
Phone: (312) 439-9020 ☐ FAX: (312) 593-2285

BOSTON: 263 Winn Street ☐ Suite 1D ☐ Burlington, MA 01803  
Phone: (617) 270-0360 ☐ FAX: (617) 273-2892 ☐ TLX: 4973468

DALLAS: 2454 Trade Mart ☐ Dallas, TX 75207  
Phone: (214) 742-9389 ☐ FAX: (214) 747-5065

NORITAKE EUROPA GmbH ☐ Electronics Division

EUROPE: Frankfurter Strasse 97-99, D-6096 Raunheim, F.R. Germany  
Phone: 06142-43095/96/97 ☐ FAX: 06142-22799 ☐ TLX: 4182982dnd


NORITAKE CO., LTD. ☐ Electronics Division

JAPAN: 1-36 Noritake Shinmachi, 3 Chome, Nishi-Ku, Nagoya  
Phone: (052) 562-0336 ☐ FAX: (052) 581-1679 (Gill) ☐ TLX: 59738

## DOT MATRIX DISPLAY MODULES

DOT MATRIX FORMAT (DOTS/LINE x NO. OF LINES)	MODEL NUMBER	NO. OF LINES AND CHARACTERS/LINE (5 x 7 DOT CONFIGURATION)	GRAPHICS CAPABILITY
192 x 16 (3072 DOTS TOTAL)	GU192X16	2 x 32	YES
256 x 16 (4096 DOTS TOTAL)	GU256X16	2 x 42	YES
256 x 64 (16,384 DOTS TOTAL)	GU256X64	8 x 42	YES

Model GU192X16

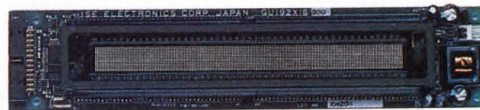

## REPRESENTATIVES

WA, OR: (503) 684-1671 ☐ Components West, Inc.

No. CA, NV: (415) 961-1422 ☐ Westech Sales

So. CA: SD (619) 292-1771 / OC (714) 891-4621 ☐ ELSCO

TX, OK, AR, LA: (214) 386-4888 ☐ Norcom, Inc.

CO, UT: (303) 794-4684 ☐ MRC

OH, WV, W. PA, KY: (216) 461-6161 ☐ Arthur H. Baier

No. IL, So. WI: (312) 439-9810 ☐ Coombs Associates, Inc.

AL, GA, MS, TN: (205) 533-1730 ☐ Interep Associates

IN: (317) 844-4842 ☐ Fred A. Dorsey & Associates, Inc.

No. WI, MN, No. IA, ND, SD: (612) 536-9512 ☐ Tech. Components

N.E.: (508) 788-0316 ☐ International Mktg. Group

PA, MD, DE: (215) 233-0333 ☐ C.H. Newson & Associates

FL, PUERTO RICO: (407) 831-8233 ☐ Semtronic Asso., Inc.

NY, NJ: (201) 376-3324 ☐ F.F. Sylvester Associates

VA: (804) 740-0063 ☐ Glasscock Associates

NC, SC: (919) 782-8100 ☐ C-Tech Sales Co.

CANADA: (416) 671-8111 ☐ Gidden Morton Associates



## One supply powers precision bridge circuit


Jerry Graeme  
Burr-Brown Corp, Tucson, AZ

Precise amplification and a high common-mode rejection ratio make an instrumentation amplifier well suited to the task of monitoring the output of a resistive transducer bridge. For systems with only one power supply, **Fig 1** shows how you can connect the bridge, the instrumentation amp, and an op amp to provide a buffered reference for the instrumentation amp's output.

For linear operation, the amplifier inputs (and outputs) must come within no more than several volts of either ground or  $V^+$ . Accordingly, the bridge properly biases both amplifier inputs, and the instrumentation amp's high CMRR ensures little error from this large offset.

The OPA111AM buffers the reference node of the bridge and applies that voltage to the instrumentation amp's REF terminal. (Most instrumentation amplifiers include a REF terminal, which may be biased to offset the output.) You measure between the amplifier outputs to exclude the fixed output offset.

The op amp output can serve as a reference common for all connections following the instrumentation amp—this output provides low impedance over a frequency range well beyond that of the bridge signal. To handle higher-frequency currents, connect capacitance between the op amp output and ground; if necessary,

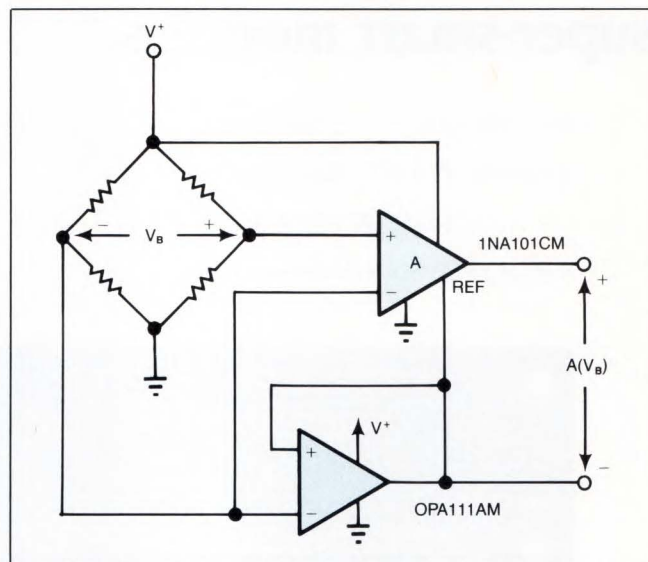

**Fig 1**—Use one power supply to excite the bridge and to develop a buffered output signal in this precision circuit.

decouple this capacitance with a small resistor within the op amp's feedback loop.

The error introduced by the additional op amp is small. The input bias current  $I_B$  of the op amp creates a bridge error of  $I_B \times R/2$ , where  $R$  is the resistance of one leg of the bridge. Input offset voltage has no effect on the output voltage; it adds to the output offset with respect to ground, which is excluded from the measurement.

EDN

## Switching improves regulator efficiency

Fran Hoffart  
National Semiconductor Corp, Santa Clara, CA


By using **Fig 1**'s circuit to lower the input voltage to a series-pass regulator when its output voltage is adjusted to a low value, you can minimize the voltage drop across the regulator. This decreases the regulator's dissipation and improves its efficiency.

The problem of large voltage drops across regulators occurs in linear power supplies whose output voltages are adjustable over a wide range. Low-voltage settings can impose high power-dissipation requirements on series-pass regulators; you'd have to attach large heat sinks to keep the regulator from overloading. Also,

many regulators have foldback-current-limiting circuits, which decrease the amount of current the regulator can deliver as the difference between the input and output voltages increases.

As one solution, when the regulator's output voltage is adjusted to a low value, you lower its input voltage by manually switching between secondary taps on a power transformer. Alternatively, you can switch from a full-wave center-tap rectifier circuit to a full-wave bridge rectifier circuit when you need higher output voltages. This method also uses the transformer more efficiently than the tap-switching method, allowing higher load currents in the full-wave center-tap circuit. **Fig 2** shows how to use an spdt switch or relay to select



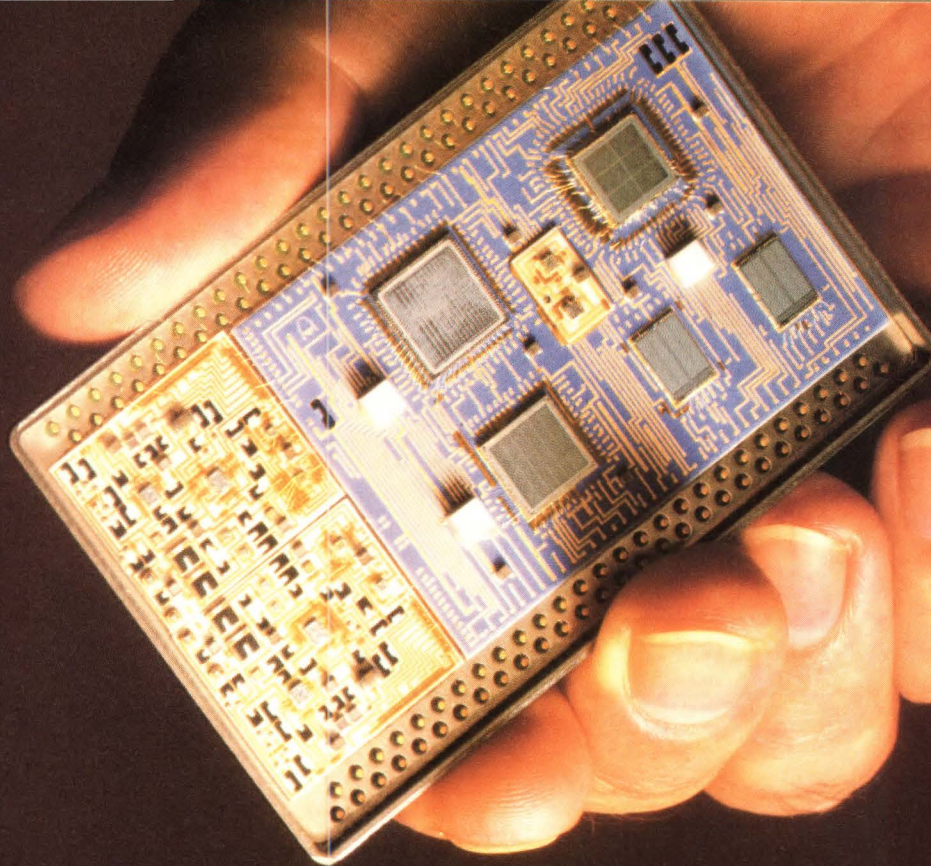

# Reintroducing the most powerful, flexible and unique MIL-STD-1553 interface currently available. And reintroducing today's Aeroflex.

This is the package so many MIL-STD-1553 design engineers are talking about – the Aeroflex ARX Universal Bus Interface Unit (UBIU).

SEAFAC tested and approved to MIL-STD-1553 A & B requirements, this rugged 2x3.1" device offers low power consumption, ease of application, a considerably shortened design cycle and increased reliability. All in a device that combines the functions it takes three competitive hybrids to perform.

Available in production quantities in +5V and  $\pm 12V$  or +5V and  $\pm 15V$  versions, the Aeroflex UBIU is the most complete Bus interface yet available. The addition of just two coupling transformers is all it takes to fully interface an 8 or 16 Bit subsystem to a dual redundant MIL-STD-1553 Data Bus.

Its on-board transceivers are well matched to the Encoder-Decoder's logic to yield optimum parametric performance as it's observed on the Bus, eliminating sensitivities to board layout parasitics and other mismatches due to lot variations or incompatibility between components from different manufacturers.

Each Aeroflex UBIU is fully tested for performance to specifications over the full operating case temperature range. Full compliance of the UBIU to specified parameters is assured and is repeatable at all times, eliminating the hassle of sporadic problems.

Aeroflex has one of the most complete lines of 1553 transceivers available anywhere, including an array of new single 5V supply units.

And Aeroflex offers a family of 12V and 15V single and dual channel transceivers that include hard to find variable output devices – right off-the-shelf.

Certified by DESC in accordance with MIL-STD-1772, Aeroflex' Microelectronics Division is long one of America's leading manufacturers of high-reliability custom and 1553 Data Bus microcircuits for military, aerospace communication, industrial and health related applications. For more information write Aeroflex Laboratories, Inc., Microelectronics Division, 35 South Service Rd., Plainview, NY 11803. Or call 516-694-6700. Outside New York call 1-800-THE-1553. Our FAX number is 516-694-6771. Get to know today's Aeroflex now.




**Custom Hybrid and MIL-STD-1553 Microcircuits**

**MIL-STD-1772 Certified**

**CIRCLE NO 12**



# DESIGN IDEAS

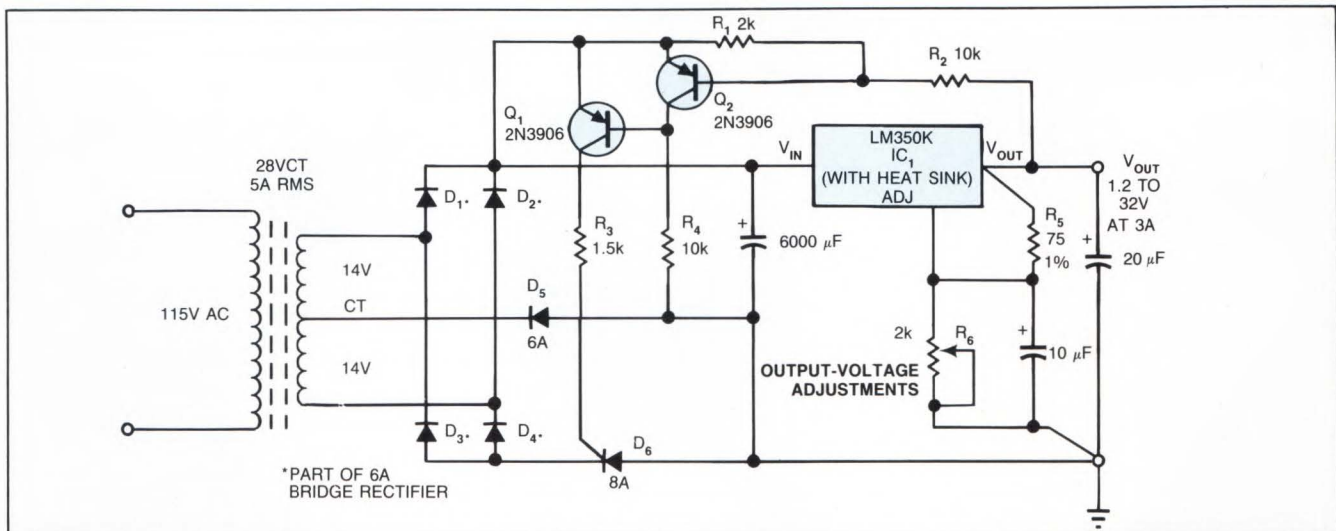


**Fig 1—Electronically switching from a full-wave bridge to a full-wave center-tap circuit in this series-pass regulator lowers the voltage across a rectifier, reduces its dissipation, and eliminates the need for a large heat sink.**

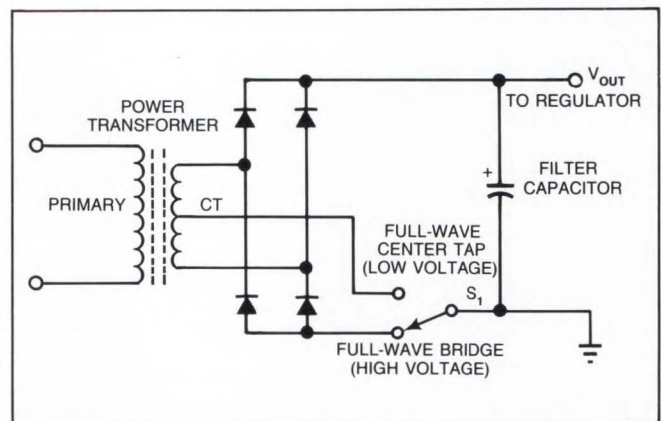
one of the rectifier circuits; the output voltage of the full-wave bridge circuit is twice that of the full-wave center-tap circuit.

Fig 1's circuit switches between rectifier circuits automatically and in proportion to the output-voltage setting and the load. Fig 3 shows the circuit's performance for three output-voltage settings and each setting's respective input voltage. As the output voltage increases, so does the input voltage. This effect greatly decreases power dissipation in the regulator and lets the regulator supply more current to the load.

In detail, the operation proceeds as follows. SCR  $D_6$  switches between the two rectifier configurations. When  $D_6$  is off, the circuit functions as a full-wave center-tap rectifier using diodes  $D_1$ ,  $D_2$ , and  $D_5$ . It applies 17V plus any ripple to the regulator's input. The



**Fig 2—This manual-switching circuit shows how lifting one point above ground changes a full-wave bridge to a full-wave center-tap rectifier circuit.**

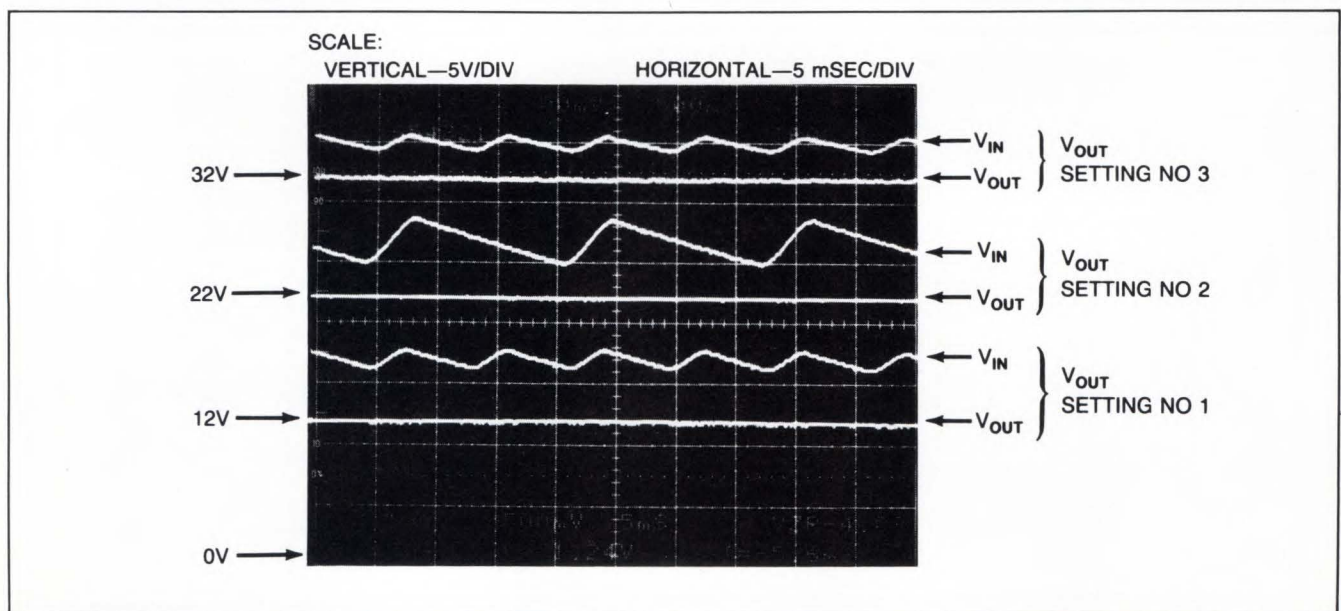

**Fig 3—Three different regulator settings generate these waveforms, which characterize the performance of Fig 1's regulator circuit.**



# DESIGN IDEAS

voltage across the regulator's input and output supplies base drive to  $Q_2$ . As long as this voltage is high enough (approximately 3V) to keep  $Q_2$  on,  $Q_1$  and SCR  $D_6$  remain off. (When  $Q_2$  is on, it removes the drive from  $Q_1$ , thereby turning it off and preventing the SCR from being switched on.)

When you increase the regulator's output voltage, the voltage across the regulator drops below 3V and  $Q_2$  turns off. This action turns  $Q_1$  on, supplying gate drive to the SCR and changing the rectifier circuit from a full-wave center tap to a full-wave bridge using diodes  $D_1$ ,  $D_2$ ,  $D_3$ , and  $D_4$ . The voltage at the regulator's input increases on a cycle-by-cycle basis, depending on the load current needed.

If you're using a light load, the circuit may switch rectifiers every 10 or 20 cycles, depending on demand

(Fig 3). With heavier loads, the circuit will switch more often. For high output voltages, the SCR is on every cycle and the input voltage is at its 35V maximum.

When you build this circuit, keep a few points in mind: In the intermediate voltage settings, the SCR doesn't conduct every cycle, and the peak diode currents are higher than they would be if the diodes conducted every cycle. Thus you'll have to choose diodes with a current rating that's two or more times higher than would normally be required. Also, when choosing a transformer, remember that you get less output current from the transformer when using a full-wave bridge, so specify the current rating accordingly.

EDN

## XOR gate doubles counting frequency

Andrew Gorajek  
Adelaide Microelectronics Centre, Technology  
Park, The Levels, South Australia

Suitable for noisy industrial environments and requiring no passive components, the frequency doubler in Fig 1 inserts an XOR gate into the first stage of a digital counter. The circuit works with virtually any counter and XOR gate. An XOR gate, in series with the counter's clock input, works as a digitally controlled inverter. The gate gets its control signal from the counter's first-stage output,  $Q_0$ .

After resetting, output  $Q_0$  is low and the MC14070B XOR gate,  $IC_1$ , acts as a noninverting buffer. Because the MC14518 counter,  $IC_2$ , counts on the rising edges of the clock signals, the first positive-going transition of the input signal makes  $IC_2$ 's  $Q_0$  output go high (Fig 1b), which makes  $IC_1$  an inverter. The next negative-going transition of the input signal appears to the counter's clock input as a positive-going transition and changes  $Q_0$  to low. Further transitions of the input signal will cause this sequence to repeat. The resulting clock signal has twice the frequency of the input and consists of short pulses whose width is the sum of the propagation delays introduced by the counter and the XOR gate ( $t_{P1}$  and  $t_{P2}$ ).

EDN


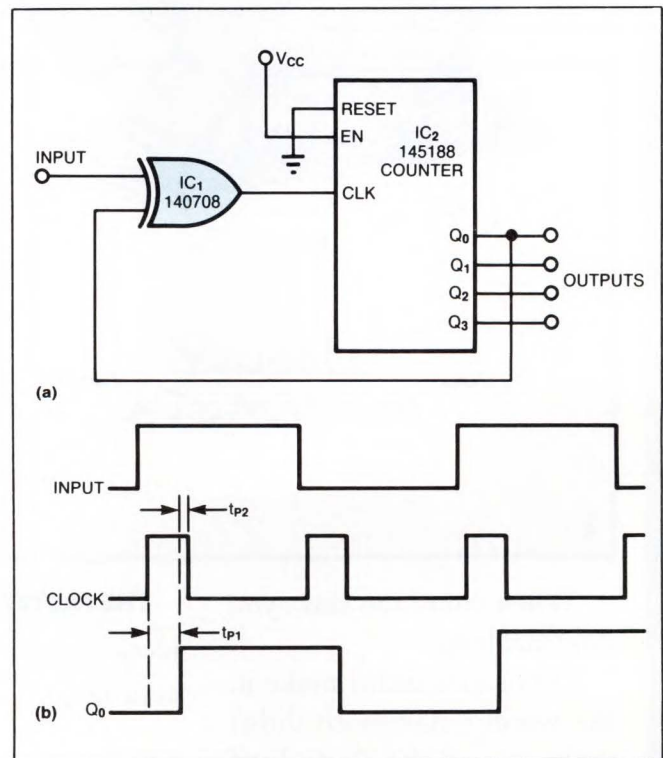


Fig 1—An XOR gate in series with a counter's clock input effectively doubles the input-clock rate. The XOR gate transforms the input signal into a series of short pulses whose width is the sum of the gate's and the counter's propagation delays. Feeding back the counter's  $Q_0$  output to the XOR gate makes the gate a controlled inverter. Inverting the negative-going input transitions allows the counter to count both positive- and negative-going edges.

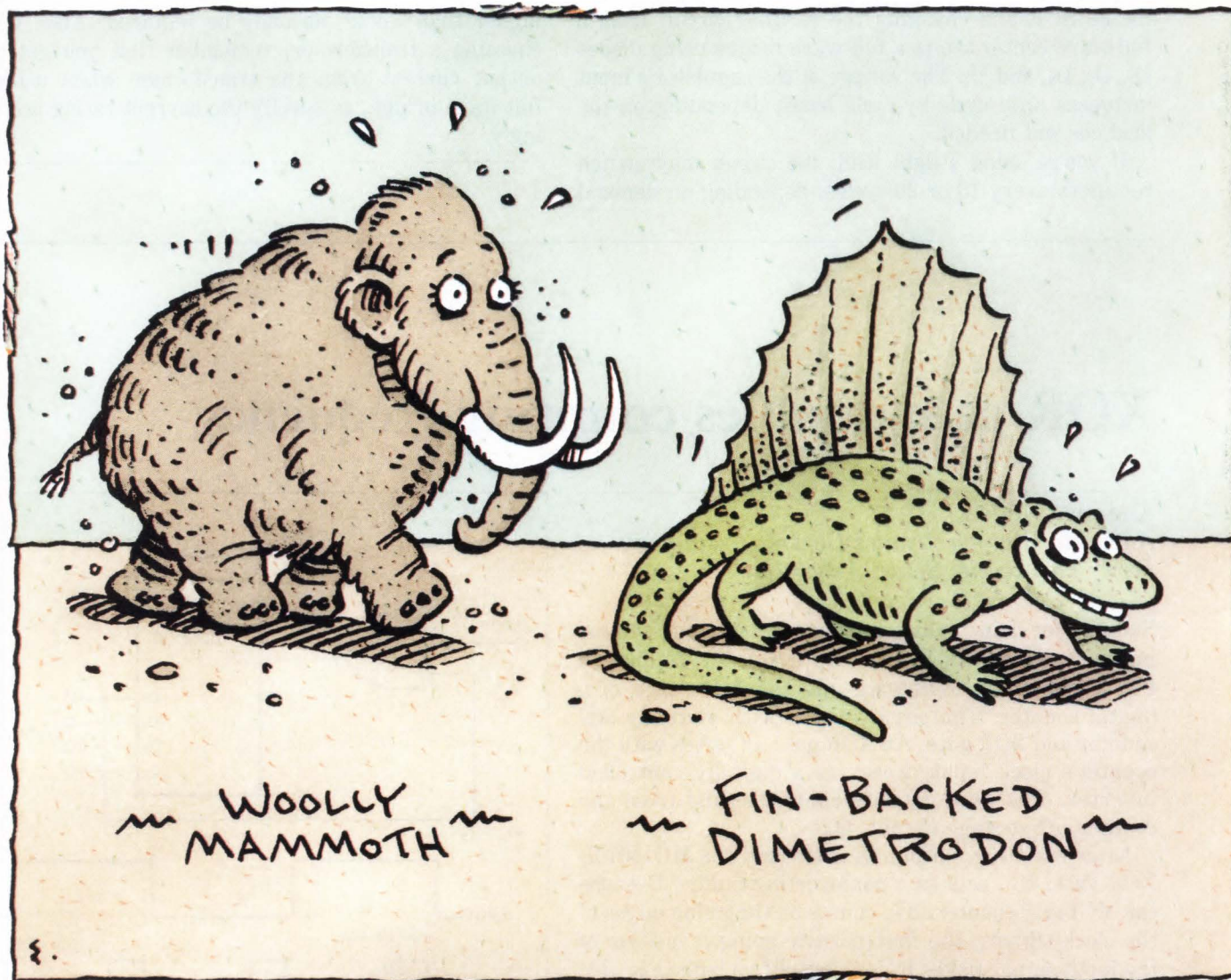

# A SLOW FIF



When you're too slow, you don't last long.

Dinosaurs didn't make it, the woolly mammoth didn't make it, and the dodo bird didn't make it.

Up until now, for high-performance applications FIFOs haven't made it either. Because

## THE FASTEST FIFOs MADE.

Part Type	Org.	Speeds	Packages
KM75C01A	512x9	20, 25, 35, 50,	28-pin DIP
		80 ns	32-pin PLCC
KM75C02A	1Kx9	20, 25, 35, 50,	28-pin DIP
		80 ns	32-pin PLCC

they haven't been fast enough to do the job.


Samsung's Fantastic FIFOs™

change that. In speeds now up to 20 ns, they're the fastest ever made.

Which means that in areas like parallel processing, where designers have had to use fast static RAMs because FIFOs were too slow, you can now get the speed you need in a FIFO.



# O, IS NO FIFO.

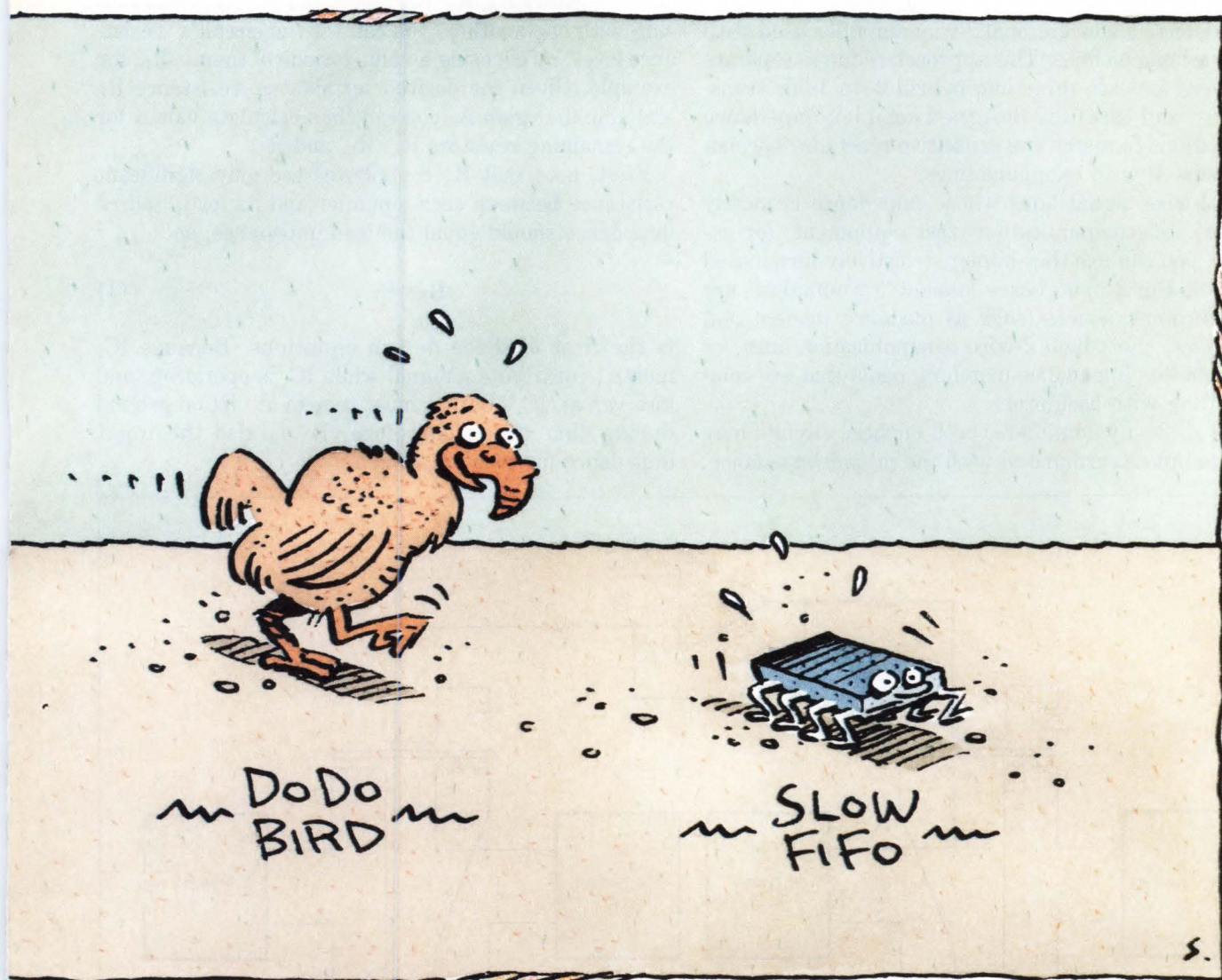

Our Fantastic FIFOs are in the x9 organization, they're in CMOS, and we now have them in both DIP and PLCC surface-mount packaging.

Equally good news: in areas where you need a *lot* of FIFOs, like large networks and even mini-supercomputers, you can

now get the *pricing* you need.

All in all, Samsung's Fantastic FIFOs, once and for all, fulfill the *promise* of FIFOs.

Because a slow FIFO is no FIFO, and these parts make *that* problem go away.

For pricing and data sheets on the fastest FIFOs in the

world, call 1-800-669-5400 or 408-434-5400 now. Or write to FIFO Marketing, Samsung Semiconductor, 3725 No. First Street, San Jose, CA 95134.



**SAMSUNG**  
Semiconductor

© Samsung Semiconductor, Inc., 1989. Samsung NOW and Fantastic FIFOs are trademarks of Samsung Semiconductor, Inc.



## Two-way amplifier uses few parts

Rudy Stefenel  
Luma Telecom, Santa Clara, CA

**Fig 1** depicts a conventional 2-way amplifier used with 2-wire telephone lines. This approach requires separate amplifiers for each direction, hybrid 2- to 4-line transformers, and carefully designed complex-impedance terminations to match the capacitive reactance normally associated with telephone lines.

For 2-wire signal lines whose impedance is mostly resistive (telecommunications test equipment, for example), you can use the simpler, resistively terminated circuit of **Fig 2**. The boxes labeled "termination" are two telecomm devices (such as modems, modem test equipment, short-haul 2-wire communication lines, or minimum-loss impedance-matching pads) that are communicating with each other.


Like all 2-way amplifiers, both of these circuits may oscillate unless terminated with the proper impedance.

Moreover, higher audio gain imposes greater accuracy constraints on the terminating impedance values. Because resistors  $R_A$ ,  $R_B$ ,  $R_C$ , and  $R_D$  have a fixed relationship with one another, you can set the circuit's "resistance level" by choosing a value for one of them— $R_D$ , for example. Given the desired termination resistance  $R_L$  and amplifier gain  $A$ , you can then calculate values for the remaining resistors  $R_A$ ,  $R_B$ , and  $R_C$ .

First, note that  $R_A$  contributes the only significant resistance between each amplifier and its load. Source impedance should equal the load impedance, so

$$R_A = R_L \quad (1)$$


is the first of three design equations. Because  $IC_2$  mustn't contribute a signal while  $IC_1$  is operating (and vice versa),  $IC_2$ 's output must remain at virtual ground during that time. Therefore,  $R_A$  is also the input impedance for each amplifier.

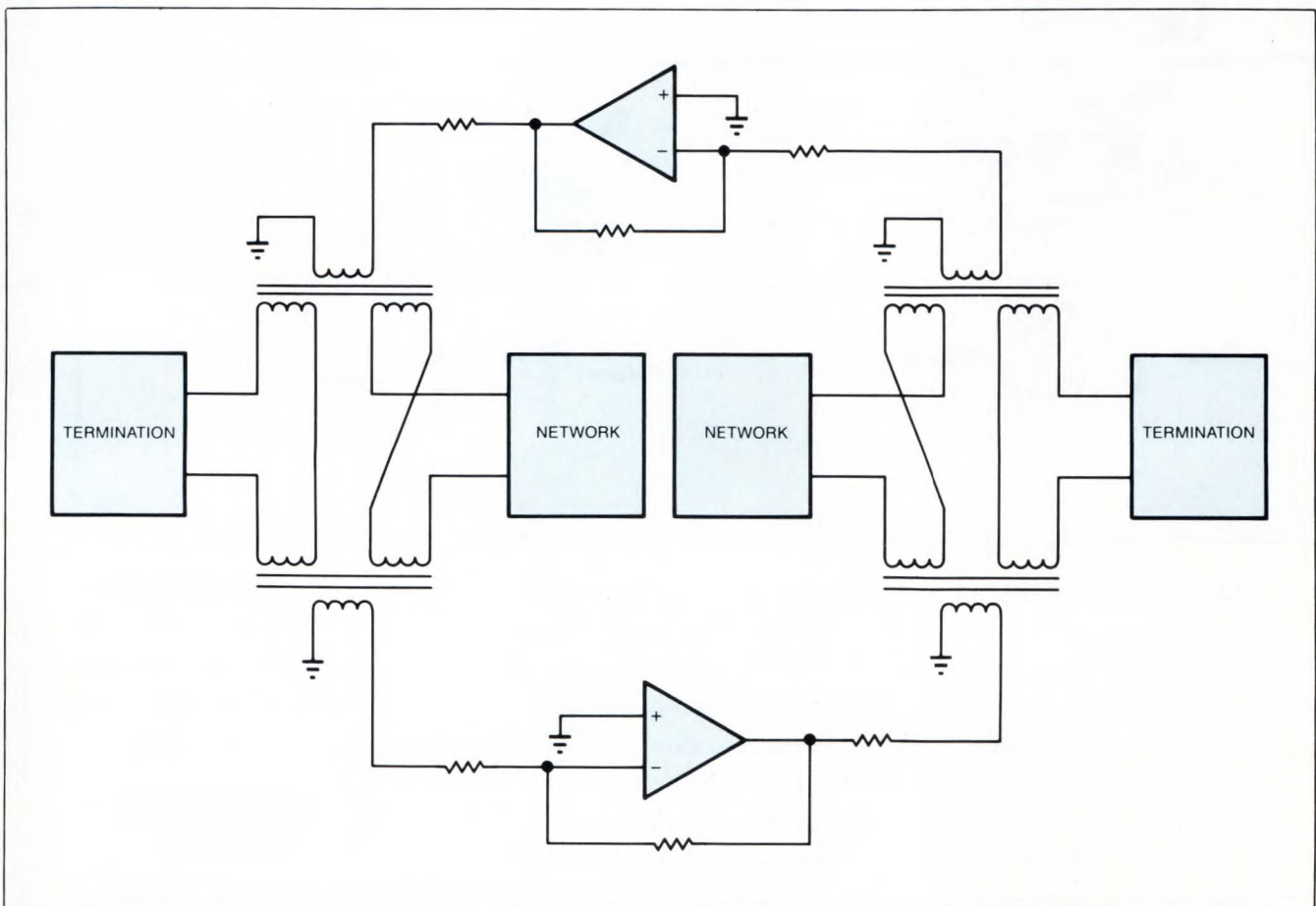

**Fig 1**—This schematic shows a typical 2-way amplifier used with telephone lines.



# Small Space Bus Interface.

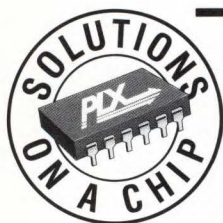

Clip this coupon and you could save 4 square inches of board space, or more, on your VME, VSB or Micro Channel bus interface.

Save precious board space. Start using PLX high-drive bus interface ICs.

Just one 24-pin PLX IC does the job of 6 ICs: a PAL, plus high current drivers, Schmitt trigger buffers, delay lines, and registers.

Take advantage of our sample offer for two free ICs and discover how compact and efficient a bus interface can be.

PLX: I accept your offer, please send me a free sample of the two units checked below. (Offer expires 12/31/89)

- |  |  |
|--|--|
| <input type="checkbox"/> VME1220 Master Controller | <input type="checkbox"/> VME4000 Interrupt Handler |
| <input type="checkbox"/> VME2000 Slave Controller  | <input type="checkbox"/> VSB1200 Master Controller |
| <input type="checkbox"/> VME3000 Interrupter       | <input type="checkbox"/> VSB2000 Slave Controller  |
|  | <input type="checkbox"/> MCA1200 MC Bus Master     |

( )  
BUSINESS PHONE

NAME

COMPANY

ADDRESS

Attach coupon to business card or letterhead and mail to:  
PLX Technology, 625 Clyde Ave., Mountain View, CA  
94043. Phone 1-800-759-3735.



PLX is a trademark of PLX Technologies, Inc. Other brands or product names are trademarks of their respective holders.



# DESIGN IDEAS

Next, the gain from IC<sub>1</sub>'s noninverting input to its output is the given gain A:

$$\frac{R_D + \frac{R_C R_B}{R_C + R_B}}{\frac{R_C R_B}{R_C + R_B}}, \quad A = \frac{1}{2} \left[ \frac{R_D + \frac{R_C R_B}{R_C + R_B}}{\frac{R_C R_B}{R_C + R_B}} \right] \quad (2)$$

and the gain from IC<sub>1</sub>'s output to R<sub>L</sub> is ½ because R<sub>A</sub>=R<sub>L</sub> (Eq 1). The product of these gains must equal

To ensure that no signal is emitted from IC<sub>2</sub> when only the lefthand signal source is active, IC<sub>2</sub>'s differen-

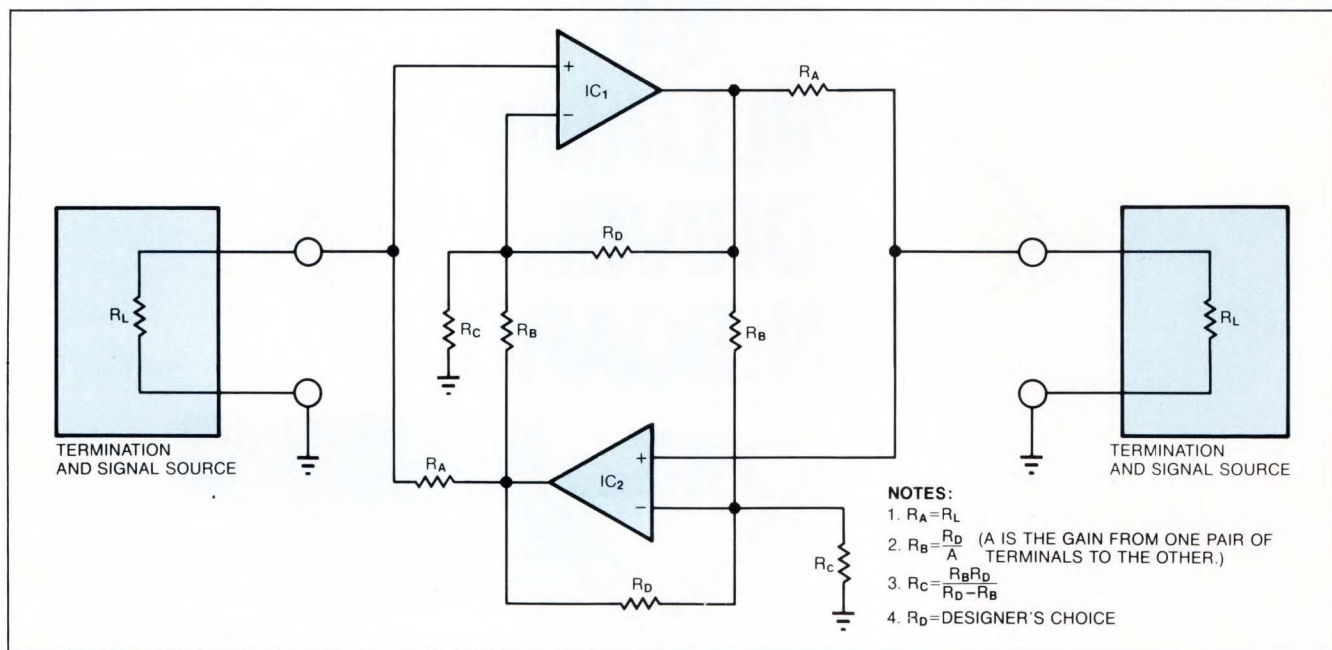


Fig 2—This simpler 2-way amplifier is suitable for lines whose impedance is primarily resistive.

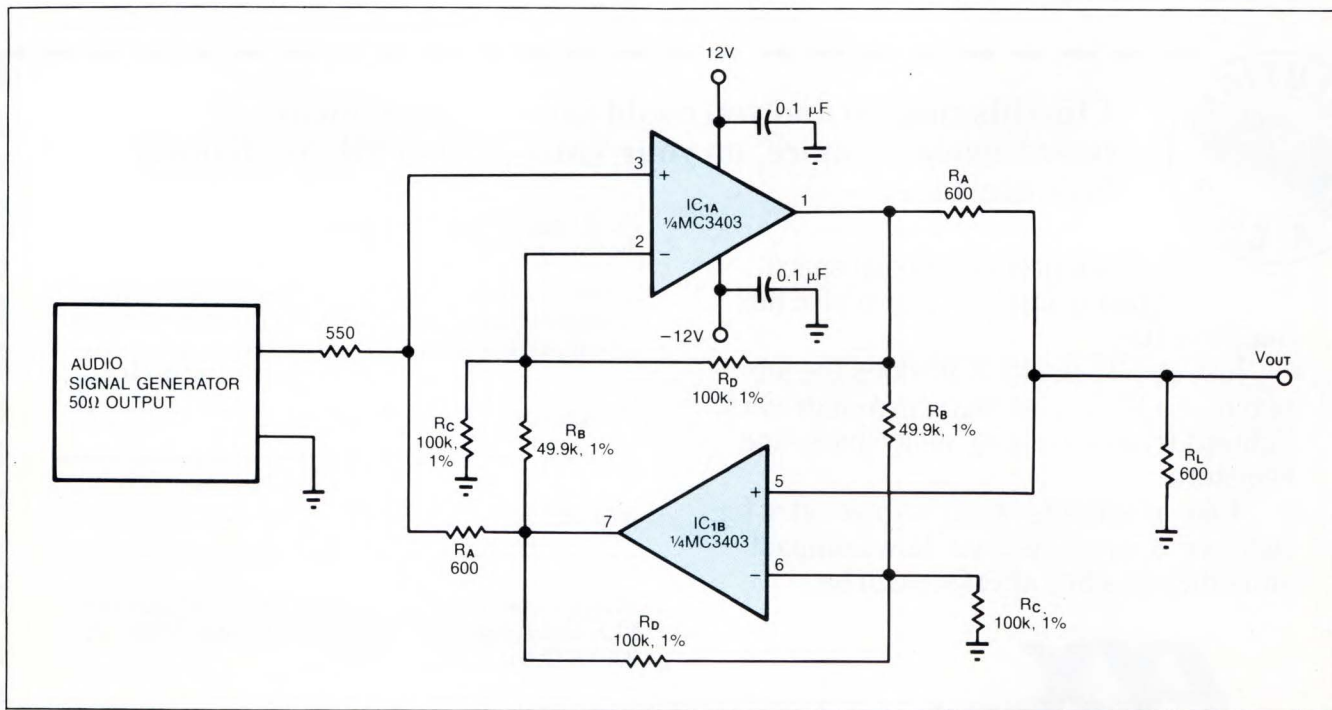


Fig 3—Based on the circuit of Fig 2, this 2-way amplifier provides a gain of 2 between 600Ω terminations.



# Our FCT Doesn't Bounce So High.

The results are in. VTC's new, improved Advanced CMOS Logic (ACL) has been fully qualified. Every part. Every package type.

And our ground bounce is *significantly* less than that reported for competitive FCT products. Which means reduced noise and better performance for your system.

VTC's ACL product line — including both ACT and FCT — is manufactured in our new, world-class, state-of-the-art 6" CMOS wafer fab. For higher quality and reliability, with lower costs.

Both our FCT and ACT are compliant to MIL-STD-883C Class B . . . 79 parts total. Commercial grade, too — ideal for bus applications, with up to 64mA drive.

Packages include CERDIP, LCC, PDIP, and SOIC. And, VTC's ACL is available through distributors worldwide.

So call today. We won't send you a lot of noise . . . just our ACL qualification data, some ground-bounce data, and a short-form product catalog.

VTC Incorporated, 2401 East 86th Street, Bloomington, MN 55425 USA. Fax 612/851-5199. Telex 857113. (In Minnesota, call 612/851-5200.)

**CALL 1-800-VTC-CMOS**

## VTC's ACL Products: FCT and ACT

240	533	640	823A	827A	843A	861A
244	534	645	824A	828A	844A	862A
245	573	821A	825A	841A	845A	863A
373	574	822A	826A	842A	846A	864A
374						

Plus 21 additional ACT parts.



**VTC Incorporated**  
Performance, Pure & Simple™



# DESIGN IDEAS

tial input must be zero. This is so if IC<sub>2</sub>'s inputs are equal, which implies equal voltage dividers:

$$\frac{\frac{R_C R_D}{R_C + R_D}}{R_B + \frac{R_C R_D}{R_C + R_D}} = \frac{R_L}{R_A + R_L} = \frac{1}{2}$$

Simplifying this equation yields

$$\frac{R_C R_D}{R_B R_C + R_B R_D + R_C R_D} = \frac{1}{2} \quad (3)$$

You can solve **Eqs 2 and 3** simultaneously for the remaining unknowns  $R_B$  and  $R_C$ . First, simplify **Eq 2**:

$$A = \frac{1}{2} \left( \frac{R_D R_C + R_D R_B + R_C R_B}{R_C R_B} \right) \quad (4)$$

Next, rearrange **Eq 3** as

$$R_B R_C + R_B R_D = R_C R_D, \quad (5)$$

and substitute into **Eq 4**:

$$A = \frac{1}{2} \left( \frac{R_D R_C + R_C R_D}{R_C R_B} \right) = \frac{R_D}{R_B}$$

Therefore,

$$R_B = \frac{R_D}{A}$$

is the second design equation.

For the last design equation, solve **Eq 5** for  $R_C$ :

$$R_C = \frac{R_B R_D}{R_D - R_B}$$

**Fig 3** shows an example of a circuit using 600Ω resistive loads and a gain of 2. The signal at IC<sub>1B</sub>'s output measures only 2 to 3% of the signal-generator output. **EDN**

## Control motor speed without tachometer

David Wolze

KLA Instruments, Santa Clara, CA

The circuit shown in **Fig 1** provides bidirectional speed regulation for small motors and requires no tachometer. The voltage that summing amplifier IC<sub>1A</sub> applies to the motor's windings equals


$$\left( V_C + R_1 \left( \frac{R_3}{R_{2A} + R_{2B}} \right) \right) I_M \left( \frac{R_6}{R_5} \right),$$

where  $V_C$  is the command voltage and  $I_M$  is the motor current.

If you set the motor's winding resistance and brush resistance ( $R_M$ ) equal to

$$R_1 \left( \frac{R_3}{R_{2A} + R_{2B}} \right),$$

the command voltage will be proportional to the motor winding's counter EMF.  $C_1$  provides compensation. You should set  $R_1$ 's value so that it equals 5 to 10% of  $R_M$ 's

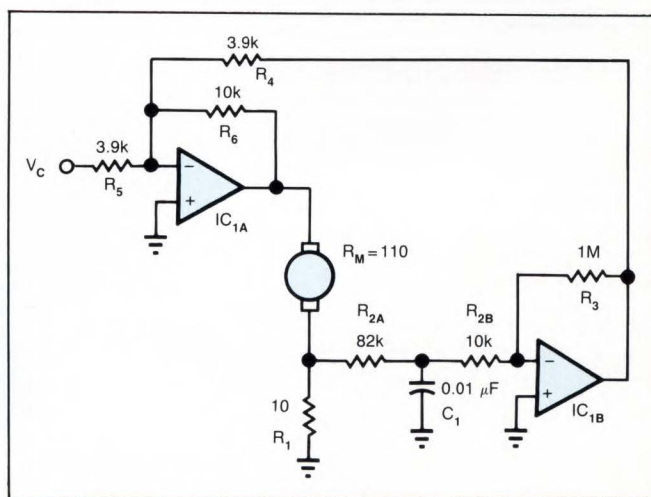

**Fig 1—This dc servo-motor circuit** provides bidirectional motor-speed control without requiring a tachometer.

value. You can generally find  $R_M$ 's value in a motor's spec sheet. **EDN**



# High performance filters off the shelf.



## An exciting new series of accurate 8th order filters.


Take your pick. We have the performance low pass filter you want.

### By the bin.

The LTC1064 makes a switched-capacitor filter competitive with the performance of active rc filters for the first time. Four independent high performance second order filter sections are in a single 24-pin DIP allowing an eighth order filter. This new filter has outstanding speed, with cutoff frequencies as high as 100kHz, as well as broad dynamic range, low noise, clock tunability, frequency and "Q" accuracy.

The LTC1064 uses external resistors to configure the filter. We make designs even easier with options that put these programming resistors on the chip. The result is a symphony of features: smaller package size, 14-pin DIP, increased speed, low noise, and guaranteed

Gain vs Frequency

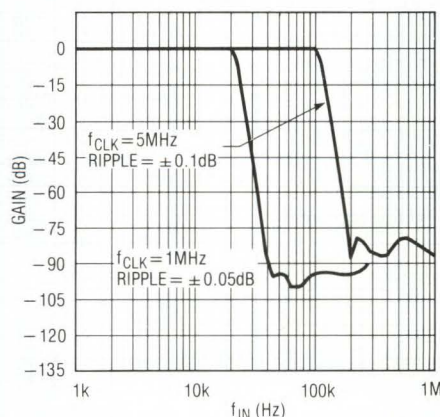

performance. Check out the classic of your choice: Cauer. Butterworth. Bessel. They're available now right off the shelf.

For volume applications, you can specify custom internal thin-film resistor arrays for your filter.

Typical applications for the LTC filters include: sonar/radar, ultrasound, telecom, process control, power supply monitoring, cellular telephones, satellite transceivers, and anti-aliasing filters for data acquisition.

In quantities of 100, the price for commercial versions of the LTC1064CN is \$8.40. The LTC1064-1, LTC1064-2, LTC1064-3 and LTC1064-4 are \$11.25 each. For additional details on military version pricing, sample availability and technical data sheets, contact: Linear Technology Corporation, 1630 McCarthy Blvd., Milpitas, CA 95035. Or call 800/637-5545.



TOUGH PRODUCTS  
FOR TOUGH APPLICATIONS.

CIRCLE NO 16



## Design Entry Blank

**\$100 Cash Award for all entries selected by editors. An additional \$100 Cash Award for the winning design of each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.**

To: Design Ideas Editor, EDN Magazine  
Cahners Publishing Co  
275 Washington St, Newton, MA 02158

I hereby submit my Design Ideas entry.

Name \_\_\_\_\_

Title \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Division (if any) \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Design Title \_\_\_\_\_

Home Address \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Social Security Number \_\_\_\_\_

(Must accompany all Design Ideas submitted by US authors)

**Entry blank must accompany all entries.** Design entered must be submitted exclusively to EDN, must not be patented, and must have no patent pending. Design must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed \_\_\_\_\_

Date \_\_\_\_\_

**Your vote determines this issue's winner.** All designs published win \$100 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize. **Vote now**, by circling the appropriate number on the reader inquiry card.

VP/Publisher  
Peter D Coley

Editor/Editorial Director  
Jonathan Titus

Managing Editor  
John S Haystead

Assistant Managing Editor  
Joan Morrow

Special Projects  
Gary Legg

Home Office Editorial Staff  
275 Washington St, Newton, MA 02158  
(617) 964-3030

Tom Ormond, *Senior Editor*  
Joanne De Oliveira, *Associate Editor*  
John A Gallant, *Associate Editor*  
Michael C Markowitz, *Associate Editor*  
Dave Pryce, *Associate Editor*  
James P Scanlan, *Associate Editor*  
Julie Anne Schofield, *Associate Editor*  
Charles Small, *Associate Editor*  
Dan Strassberg, *Associate Editor*  
Anne Watson Swager, *Associate Editor*  
Chris Terry, *Associate Editor*  
Kathleen M Vejvoda, *Associate Editor*  
Helen McElwee, *Senior Copy Editor*  
Susan L Infantine, *Senior Production Editor*  
Christine McElvenny, *Production Editor*  
Brian Tobey, *Production Editor*

Editorial Field Offices  
Margery S Conner, *Regional Editor*  
Atascadero, CA: (805) 461-9549

Doug Conner, *Regional Editor*  
Atascadero, CA: (805) 461-9669

Steven H Leibson, *Regional Editor*  
Boulder, CO: (303) 494-2233

J D Mosley, *Regional Editor*  
Arlington, TX: (817) 465-4961

Richard A Quinell, *Regional Editor*  
San Jose, CA: (408) 296-0868

Maury Wright, *Regional Editor*  
San Diego, CA: (619) 748-6785

### Contributing Editors

Robert Pease, Bob Peterson,  
Don Powers, Bill Travis

### Editorial Services

Kathy Leonard, *Editorial Coordinator*  
Nancy Weiland, Helen Benedict

### Art Staff

Ken Racicot, *Senior Art Director*  
Chinsoo Chung, *Associate Art Director*  
Cathy Filipski, *Staff Artist*  
Martha Crowell, *Staff Artist*

### Production/Manufacturing Staff

Andrew A Jantz, *Production Supervisor*  
Danielle M Biviano, *Production Manager*  
Deborah Hodin, *Production Assistant*  
Sandy Wucinich, *Production Assistant*  
Diane Malone, *Composition*

### Director of Art Department

Joan Kelly  
Norman Graf, *Associate*

### VP/Production/Manufacturing

Wayne Hulitzky

### Director of Production/Manufacturing

John R Sanders

### Business Director

Deborah Virtue

### Marketing Communications

Anne Foley, *Promotion Manager*  
Sara Morris, *Marketing Services Administrator*  
Gordon Keegan, *Promotion Specialist*



# Your Imagination— Your Only Limitation...

## Pixie™—Programmable Graphic LCD Switch Module (Icon-in-a-Switch) and Intelligent Controller




Actual Size

interface.

At last you can finally use your imagination and communicate with just keyswitches. Since the arrival of computers everyone has been awaiting a simple man-machine

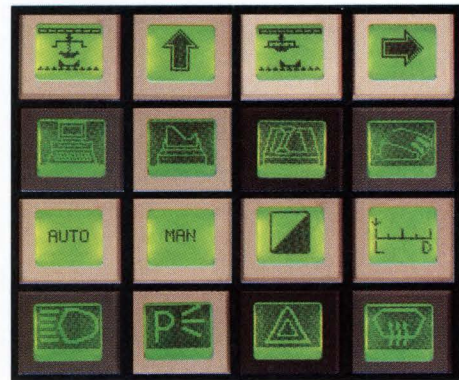The introduction of the Pixie Graphic LCD Switch and Controller provide a unique and creative solution to this man-machine interface problem.



1/2 Actual Size

The Pixie integrates a low-power 864 pixel graphic LCD, utilizing super-twist technology, with LED backlighting conditions and a custom IC driver into a keycap of a contact switch providing a user-friendly method for machine control and display applications. Controller cards are available with many designed-in options that enable you to integrate the Pixie with your individual system. There are limitless applications, from vending machines to industrial process control.

**Graphics Control**

**IEE  
Intelligent  
Controller**

**RS-232**

**RS-422**

**500mA Switch Closure**

So, use your imagination. Call or write for a comprehensive data package and evaluation kit information and ask about our PIXIEtalk software.



Circle 18 Reference Material

INDUSTRIAL ELECTRONIC ENGINEERS, INC.  
Component Products Division  
7740 Lemona Ave., Van Nuys, CA 91409-9234  
FAX: (818) 376-1075 (G2/G3) • Telex: 6831955 IEEINTL  
Tel.: (818) 787-0311, Ext. 377

Circle 17 Immediate Application



# VISHAY Electronic Components Group Will Satisfy All Your Resistor Needs

## ANGSTROHM

### Power Rheostats

MIL-R-22 Approved

Resistance Range from  $0.5\Omega$  to  $10k\Omega$

Resistance Tolerance  $\pm 10\%$ , others available

Power Rating 12.5, 25, 50, 100, 150 & 300 watts  
( $300^\circ\text{C}$  rise in free air)

Types MP06, MP10, MP15, MP25, MP30, MP40.

### Precision Metal Film

MIL-R-10509 & MIL-R-55182 Approved

Over 1.234 billion unit failure rate hours to MIL-R-55182 without a single failure.

Hermetically Sealed Styles RNR/RNN/RNC,  
Characteristics C & E, Established Reliability.

Resistors, Networks, Specials.

CIRCLE 85

## DALE

### Precision & Commercial Components Military Trimmers - Techno Division

MIL-R-22097, MIL-R-27208,

MIL-R-39015 & MIL-R-39035 Approved

Surface Mounted Components, Wirewound, Metal Oxide & Carbon Film Resistors, Thick & Thin Film Chip Resistors, Resistor & Resistor/Capacitor Networks, Commercial Trimmers, Thermistors, Inductive Components, Transformers, Clock Oscillators, Connectors, Plasma Display, Touch Panels.

CIRCLE 86

## ELLIOTT/JORDAN

### Precision Wirewound

Temperature Sensing and Compensating,  
Hermetically-Sealed, Special TCR,  
Four Terminal, Low Reactance.

Resistors, Printed Circuit, Axial & Radial  
Leaded, 4 Terminal Molded, Silicone  
Molded/Coated, Ultra-Miniature,  
Surface Mount.

CIRCLE 87

## OHMTEK

### Thin Film

MIL-R-55342 Approved, Char. E, K Chips

TCR to  $5\text{ppm}/^\circ\text{C}$

Tracking to  $1\text{ppm}/^\circ\text{C}$

Ratio Tolerances to 0.005%

Resistance Range  $50\Omega$  to  $10M\Omega$

Precision Custom & Standard Networks  
SIPs, DIPs, LCCs, Flatpacks, Small Outline  
Custom Arrays, Silicon & Alumina Chips for  
Hybrids, Microwave Substrates.

CIRCLE 88

## ULTRONIX

### Precision & Power Wirewound

MIL-R-26, MIL-R-93, MIL-R-18546,  
MIL-R-39005 (RBR), MIL-R-39007, MIL-R-39009,  
MIL-R-55182 & MIL-R-83401 Approved

Established Reliability, Temperature Sensing,  
Ultra-high Stability, Hermetically Sealed.

Resistors, Printed Circuit, Axial &  
Radial Leaded, 4 Terminal Molded,  
Silicone Molded/Coated, Ultra-Miniature,  
Surface Mount.

CIRCLE 89

## VISHAY

### Precision Bulk Metal Foil

MIL-R-122, MIL-R-22097,

MIL-R-55182/9 & MIL-R-83401 Approved

TCR to  $0.1\text{ppm}/^\circ\text{C}$

TCR Tracking to  $0.2\text{ppm}/^\circ\text{C}$

Absolute Initial Resistance to 0.001%

Resistance Ratio Stability to 0.001%

Load Life Stability to 0.0025%

Shelf Life Stability to 0.0005%

Thermal EMF to  $0.03\text{V}/^\circ\text{C}$


Resistors, Trimmers, Networks, Chips,  
Surface Mount, Specials.

CIRCLE 90
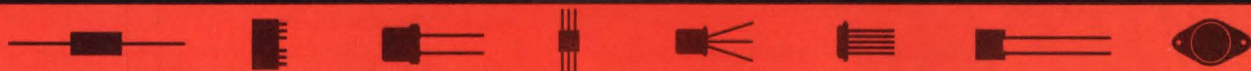
## VISHAY Electronic Components Group

...a VISHAY Company

63 Lincoln Hwy. ♦ Malvern, PA 19355 ♦ (215) 644-1300 ♦ FAX (215) 296-0657 ♦ Sales FAX (215) 640-9081





# EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number  
for additional information from manufacturers.

## Don't Get Zapped!

High inrush current can **destroy** your sensitive VAX CPUs and peripherals in **less time than it takes to flip a switch.**

### THE SOLUTION?

Power up with **Z-LINE TPC 115-10 MTD™**, the **smallest** power distribution and control system available.

POWER UP WITH ———

**Z-LINE™**

Our proprietary **Multiple Time Delay™** circuitry sequences your power-up to **protect** your systems from the spikes and surges, EMI & RFI, that **destroy your hardware and erase your data.** And our remote on/off and emergency shutdown gives the **power control back to you.**

All Pulizzi Engineering MTD™ controllers are compatible with DEC and UPS systems.

PRICES FROM \$436 TO \$305

**DON'T WAIT UNTIL IT HAPPENS, CALL TODAY!**


**PULIZZI ENGINEERING INC.**

3260 S. Susan Street, Santa Ana, CA 92704-6865  
(714) 540-4229 FAX (714) 641-9062

CIRCLE NO 325

## 68HC11

PC-based emulator for 68HC11

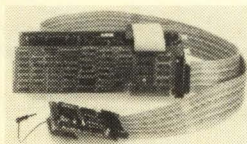

- PC plug-in or RS-232 box.
- 48 bit wide 16K deep trace. All functions usable without disturbing emulation. Time stamping. Two level trigger.
- Pull-down menus with full window support, combined with command-driven User Interface.
- Up to 3.3MHz real time emulation.
- Symbolic and C Source Level Debugging, including in-line assembler and disassembler.
- No intrusions to the 68HC11's resources.

PRICES: 64K Emulator and pod \$2590,\*  
4K Trace \$1995\*

CALL OR WRITE FOR FREE DEMO DISK!


**NOHAU**  
CORPORATION

51 E. Campbell Avenue  
Campbell, CA 95008  
FAX (408) 378-7869  
(408) 866-1820

\*US only

CIRCLE NO 326

## LEADLESS CHIP TO WIRE WRAP ADAPTERS

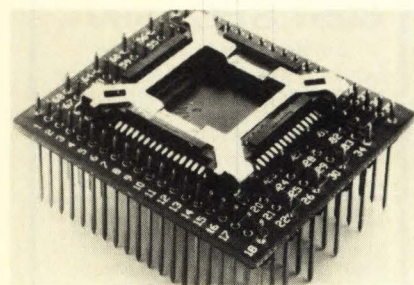


Save prototyping time, LCC, PCC, PGA, and PQFP socket adapters provide the designer with a labeled test point for each pin and are available for 20 thru 100 pin chips. WW pin rows are on .3" centers. Unit pricing for the 52 pin version is \$41.00 delivered from stock.

### ANTONA CORPORATION

1643 1/2 Westwood Blvd., L.A., CA 90024  
(213) 473-8995 FAX # (213) 473-7112

CIRCLE NO 327

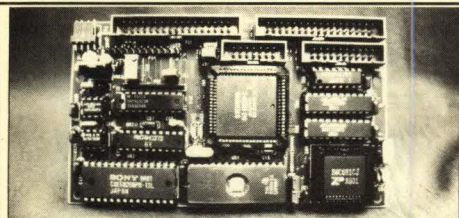

## 3" X 5" Single Board Computer Based on 80C535

- 8051 type architecture
- CMOS (95 ma @ 8 V typical)
- 32K RAM/32K or 64K EPROM
- 40 Digital I/O Lines
- Two RS232 Serial Ports
- One RS485 Port
- 8-bit A/D w/8 multiplexed inputs
- 5X4 Keypad Encoder
- Power Supervisory Circuits
- Four 16-bit timer/counters
- Expansion Bus
- On board +5 V regulation
- C Source Utilities on 5.25" Disk
- Optional Real Time Clock

GPC11 Price: \$275 qty 1 - OEM pricing available.

### TRI-L DATA SYSTEMS, INC.

524 Cooke Street, 2nd Floor  
Honolulu, Hawaii, USA 96813-5236  
Tel. No. (808) 545-3415/FAX (808) 545-3607

CIRCLE NO 328

## PAL™ /PLD SOFTWARE

Sets The Standard



CUPL™ PLD compiler, the most powerful language for state machine logic design, now allows front end design entry with popular schematic capture packages such as OrCAD, P-CAD, Schema or Hi-Wire. CUPL supports all PLDs and carries the most extensive update program. Available on MS-DOS™, Apollo™, Sun™ VAX™ and most UNIX™ based platforms.

**LOGICAL**  
DEVICES, INC.


1201 N.W. 65th Place  
Ft. Lauderdale, FL 33309  
305-491-7404

1-800-331-7766

CIRCLE NO 329

## Analog Circuit Simulation

IsSpice/286 Breaks the DOS Barrier

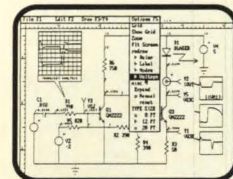

Run Unlimited  
Size Simulations  
on Your PC

IsSpice/286 \$210, a complete Spice program that runs on 80286 based PC's in extended memory. Circuit size is only limited by the amount of extended memory. Simulates over 700 components per megabyte of RAM. IsSpice/386 \$386, The fastest PC based Spice program 1000 components per megabyte of extended RAM. IsSpice \$95, Runs on any PC . AC, DC, and Transient.

Special Graphics Turn Your PC into a Workstation

SpiceNet \$295, Schematic editor for any Spice simulator. Generates a complete Spice netlist.

IntuScope \$250, Graphics post processor that performs all the functions of a digital oscilloscope.

PreSpice \$200, Extensive model libraries, Monte Carlo analysis and parameters sweeping.

**intusoft**


P.O. Box 6607 (213) 833-0710  
San Pedro, CA 30 Day Money  
90734-6607 Back Guarantee

CIRCLE NO 330

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## REAL WORLD I/O For PC/XT/ATs

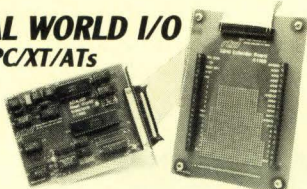

- DG24** • 24 line digital I/O; 10 MHz 8255. **\$95**
- AD500** • 8 channel 12-bit (plus sign) integrating A/D; prog. gains of 1, 10 & 100; 7 digital I/O lines. **\$239**
- AD100** • Single channel version of AD500; 10 digital I/O lines. Same programmable gains. 700 meg input Z. **\$149**
- AD1000** • 8 channel 12-bit A/D; 25 uS; sample & hold; 3.5 MHz timer/counters; 24 digital I/O lines. **\$295**
- ADA300** • 8 channel 8-bit 25 uS A/D; single D/A sample & hold; 24 digital I/O lines. **\$239**
- AD200** • 4 channel 12-bit 125 uS A/D; 3.5 MHz timer/counters; 24 digital I/O lines. **\$239**
- DA600** • Fast settling dual bipolar D/A. **\$179**
- PD200** • Prototype board w/ address decoder; manual **\$99**

All boards include BASIC, Pascal, C, and Fort drivers. 30 day return; 1 year warranty. Call for "Real World Interfacing" application notes.

### Real Time Devices, Inc.

P.O. Box 906 State College, PA 16804  
(814) 234-8087

CIRCLE NO 331


## Jameco Electronics JE680 Universal IC Programmer

Programs PROMs, EPROMs, EEPROMs, PALs, GALs, RALs, EPLDs and PEELs
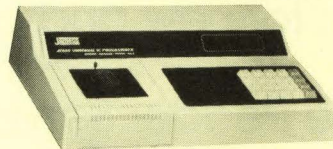
### JE680 Features:

- Stand-alone or computer controlled modes w/ MS-DOS menu-driven software (included)
- Parallel and RS232C interface ports
- Auto-Sense™ of IC insertion
- Supports/translates between 18 data formats
- Full functional test on logic devices
- Over 400 IC definitions in ROM - no personality modules needed
- JEDEC standard supported, accepting input from virtually all major software packages
- One-Year Warranty

Listing of over 400 programmable devices and 74-page catalog available upon request!




JE680 Universal IC Programmer .....\$1799.95

Jameco Electronics • 1355 Shoreway Road, Belmont CA 94002  
• Phone (415) 592-8097 • FAX (415) 592-2503

CIRCLE NO 332
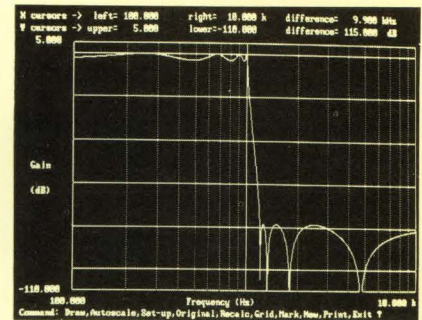
## New AFDPLUS Advanced Active Filter Design Software



- Fully Interactive
  - On Screen Design & Evaluation
  - On Screen Editing
  - Menu Driven
  - Automated Installation
  - Schematic Display & Print
- Introductory price \$850.00 (price effective through 08/15/89)  
Call for your **FREE DEMO DISK** (303)-499-7566 or to order AFDPLUS send check or purchase order to

RLM Research

P.O. Box 3630  
Boulder CO 80307-3630



CIRCLE NO 333

## 8051 SBC \$99<sup>oem</sup>

Single Board Computer

FEATURES: 8031, RAM and ROM Sockets, 8 bit I/O, RS 232 port, optional UART, and Expansion Bus. Size: 3.5" x 6.0", +5Vdc only. OPTIONS: 8032, CMOS, 18 MHz, NV Memory, Monitor Firmware and High Level Languages. Development Board.....\$199

## 8031 ICE \$199

Our emulator provides most of the features of an 8031 In-Circuit-Emulator at a significantly lower price. It assists in integration, debug and test phases of development. Commands include: disassembly, trace, breakpoints, alter register/memory, and load Intel Hex file.


8051 Simulator Program.....\$99  
IBM PC/XT/AT Software simulation of 8051 µC.



HiTech Equipment Corporation  
9400 Activity Road  
San Diego, CA 92126  
(619) 566-1892

CIRCLE NO 334

## IEEE-488<sup>USEFUL</sup> AIDS

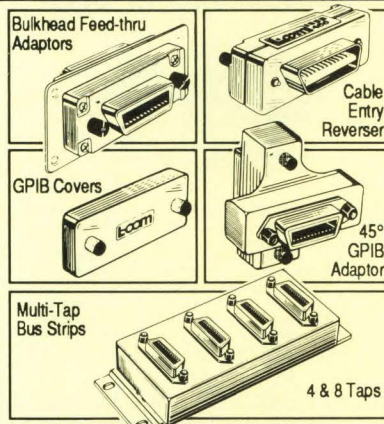


DELUXE and MOLDED IEEE-488 Cables too!



1755 Osgood St., N. Andover, MA 01845  
Inquiries 508 682-6936 FAX 508 689-9484  
Toll Free Ordering 800 343-1455

CIRCLE NO 335
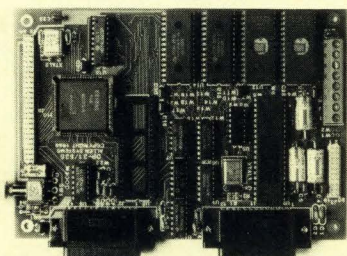
## 8051, 8096, 68HC11, 68008 SINGLE BOARD COMPUTERS




We feature a series of single board computers for process control applications. Available as bare boards or assembled and tested. Optional EPROM resident System Monitors and BASIC interpreters are also available.

ALLEN SYSTEMS  
2346 Brandon Road  
Columbus, Ohio 43221  
614-488-7122

CIRCLE NO 337

## FIX/PGA/LCC/TEST ADAPTOR

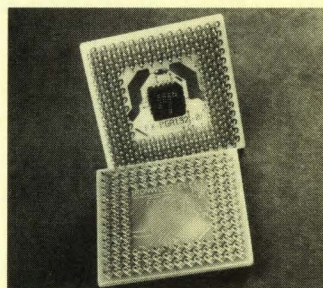


### MANY NEW PARTS

VLSI prototype adaptors allow prototyping of devices from 24 pin (VRAM ZIP), Shrink DIP, to 256 pin SPARC, PLCC, LCC, SLAMPAK, and FLATPAK. Annotated test adaptors for 680X0, 80X86. Stacking memory modules for up to 16 MBYTE DRAM SIMMS. FIX-80386 to fix errata 21 problem in 386 PC's (causes lockup). All gold Machined pins/most wirewrap panel patterns. Customs - quick turnaround.

IRONWOOD ELECTRONICS, INC.

P.O. BOX 21-151  
ST. PAUL, MN 55121  
(612) 431-7025

CIRCLE NO 338

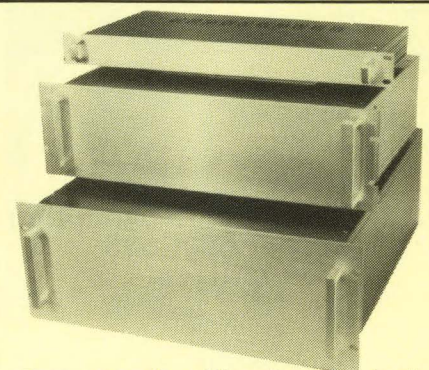

These top-quality 19" rack-mount chassis are made of heavy gauge aluminum and/or steel. The front brushed aluminum panel is anodized in black or clear. Dimensions are 1 to 6 rack unit height by 8", 10", 12", 14" and 20" depth. Most orders will be shipped within 24 hours. Custom made enclosures are available upon request.



16 NORTH THIRD STREET  
HARRISON, NJ 07029  
TEL: (201) 484-1115 FAX: (201) 484-0530

CIRCLE NO 339

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

EDN Design Ideas Special Issue, Vol IV



## IEEE-488

488 (GP-IB, HP-IB) control for your PC/XT/AT

Control instruments, plotters, and printers.  
Supports BASIC, C, FORTRAN, and Pascal.  
Fast and easy to use. High-speed DMA.  
Software library included so you spend less time programming.  
Thousands sold. Risk free guarantee.  
Hardware and software - \$395.

Product literature 1-800-234-4CEC  
Technical assistance 617-273-1818



Capital Equipment Corp.  
Burlington, MA. 01803



CIRCLE NO 340

## BIOS SOURCE CODE


The **The AT BiosKit** is a book with diskettes containing source code in C, plus utility programs to help you create a Bios. Now you can have a Bios with documentation for your own applications: modify boot-up, eliminate the keyboard, install security features, etc. Only \$199 complete. The **XT BiosKit** is only \$99, or get both BiosKits for \$279. The **Intel Wildcard Supplement** for the XT BiosKit is \$49.

### — XT-AT HANDBOOK —

The **XT-AT Handbook** is full of hardware and software information in a shirt pocket size book. Over 70 pages covering 38 subjects, including connectors, I/O maps, controller programming, DOS and DEBUG commands, board dimensions, character codes, hard disk drive types, and much more. Only \$9.95 each qty 1-4, five or more, \$5 each.
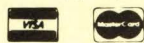
### Annabooks

12145 Alta Carmel Ct Suite 250-262  
San Diego, California 92128  
(619) 271-9526



CIRCLE NO 343

## C for the 8051 Compare:

**Benchmark Results** — Sample program: Eratosthenes sieve Program from BYTE (1/83), expanded with I/O and interrupt handling.

	Archimedes		FRANKLIN	
	ICC51 v2.20A	MCC51 v1.2	C51 v2.1	
Compilation time	12 sec ✓	18 sec	17 sec	
Linkage time	29 sec	9 sec	6 sec	✓
Execution time	11.45 sec	9.00 sec	0.88 sec	✓
Total code size	5318 bytes	3798	1726	✓
Sieve module size	736	1021	541	✓

Call now for your free DEMO disk.




**FRANKLIN**  
SOFTWARE, INC.

888 Saratoga Ave. #2 • San Jose, CA 95129  
(408) 296-8051 • FAX (408) 296-8061

CIRCLE NO 346
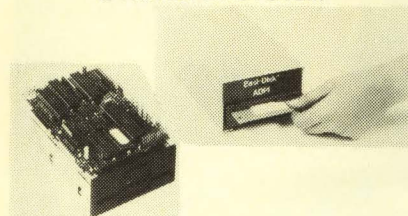
## IBM COMPATIBLE RS232C/488 3 1/2 x 5 1/4" FLOPPY DATA STORAGE & TRANSFER SYSTEM



Information Transfer to/from Non IBM Compatible Systems to/from IBM & Compatibles (Over RS-232 or 488 Interface).

- Reads & Writes MS DOS Disks
- RS-232C/488 I/O
- Rugged Portable Package/battery option
- MS DOS Driver for "Plug & Run" RS-232 External Operation
- Baud Rate 110 to 38.4K Baud
- 360K/720K RAM Cartridge Option
- Price \$895 in Singles-OEM Qty's. \$495.

28 other systems with storage from 100K to 42 megabytes.



**ANALOG & DIGITAL PERIPHERALS, INC.**  
251 South Mulberry St., Troy, Ohio 45373  
P.O. Box 499 TWX 810/450-2685  
513/339-2241 FAX 513/339-0070

CIRCLE NO 341



### MIL-STD-1553 Interface Board For IBM-PC/XT/AT or Compatibles

Dual redundant bus controller, remote terminal and monitor with powerful easy-to-use software. From only \$2095


Call now for data on MIL-STD-1553 and ARINC 429 for PC/XT/AT, VME and VXI

**Ballard Technology**

1216 N.W. 75th St.,  
Seattle, WA 98117  
(206) 782-8704

CIRCLE NO 344
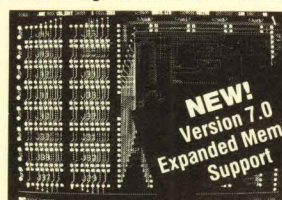
### Schematic Capture, to PCB Layout Vertical Design Workstation - \$695.00



**NEW!**  
Version 7.0  
Expanded Memory  
Support


Other Companies talk about Sophistication, but we deliver it. Our full featured CAD software sets industry standard in performance and flexibility with features such as:

- User definable Menus, macros and user interface
  - User definable grid, pad and trace sizes (1 mil increments)
  - DRC with Back annotation, Optimized Rat's Nest
  - Comprehensive SMT Support
  - Superior Analog design (Irregular filled polygons etc)
  - Very large boards > 500 equivalent IC's
- Compare our CAD software specification with those so-called sophisticated systems, and if you are that interested, we are that good. Prices start as little as \$695.00. Optimal Autorouter, GERBER interface
- 30 day money back guarantee
  - Full function Evaluation kit with full user manual \$75.00 (Creditable towards purchase of regular system)

### Interactive CAD Systems

2352 Rambo Court, Santa Clara, CA 95054  
(408) 970-0852

CIRCLE NO 347

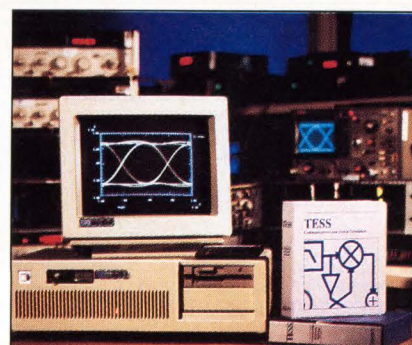

### Communications Block Diagram Simulator for PCs


- TESS™ simulates modems, radios, & other systems
- Built-in FFT spectrum analyzer, plus over 50 models: filters, mixer, VCO, logic & PAL's, BERT and test eqmt
- Capture schematics graphically with OrCAD® & PCAD®
- Add your own models to TESS easily using MODGEN
- Call for 3-disk demo kit • TESS is not copy protected

TESS Simulator \$495  
MODGEN™ Model/Generator \$245  
OrCAD/SDT III® Part Library \$145  
P-CAD® Part Library \$225

TESOFT PO BOX 305  
Roswell GA 30077-0305  
404-751-9785 FAX 404-664-5817  
VISA, MasterCard, PO's accepted

CIRCLE NO 342

## INCANDESCENT (IT IS)?

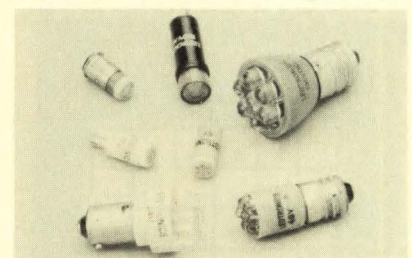

### OUR BASED LED'S *a sure cure!*

Directly Replaces lamp #327/387, 714, 6839, 7387, 755, 47, 85, 1835, 24E, 120MB, 120 PSB & Hundreds More. 10 to 20 yrs. Life at Fraction of Power. No Shock/Vibration Failures. Multichips, Clusters, BiPolar, BiColors. Choice of 7 Colors.



Put More  
LIFE in  
Your LIGHT

**LEDTRONICS, INC.** TEL: 213-676-7996

FAX: 213-676-0108 TLX: 494-5454

4009 Pacific Coast Hwy., Torrance, CA 90505

CIRCLE NO 345

## ULTIBOARD COMPUTER AIDED PCB DESIGN



### The ULTIMate PCB layout package featuring:

- Full SMT support
- 32 layer support with blind and buried vias
- Curved traces
- Real-Time Design Rule Check
- Powerful placement aids
- Trace Shove and Reroute-While-Move
- Autoroute by window, component, or net
- Backannotation to OrCAD, DASH, Schema, ViewLogic



USA/Canada: Norcross GA, USA • Tel: (800) 242-0125/Fax: (800) 242-0125  
Europe: Nantwich, Cheshire, UK • Tel: 0151 215 4442/Fax: 43545

ASK FOR YOUR FREE DEMO DISK


CIRCLE NO 348

To advertise in Product Mart, call Joanne Dorian, 212/463-6415



## E/EPROM & MICRO PROGRAMMER

**\$895**

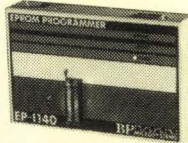

- EP-II40 includes: software, cable, user's manual, 2 free software update coupons, toll-free technical support, one-year warranty & a unconditional 30-day money back guarantee
- Programs 24-, 28-, 32- & 40-pin E/EPROMs
- Supports 874X & 875X series microcontrollers
- Connects to a standard parallel port
- Hardware to support future parts to 8 Megabit
- Software updates on floppy disk
- 32-pin model, EP-II32, available for \$695

**The Engineer's Programmer™**

**CALL TODAY 800-225-2102**

**BP MICROSYSTEMS**

10681 Haddington, #190, Houston, TX 77043  
713/461-9430 FAX 713/461-7413

CIRCLE NO 349

## \$249. TERMINAL




- Featuring**
- Standard RS-232 Serial Asynchronous ASCII Communications
  - 48 Character LCD Display (2 Lines of 24 Each)
  - 24 Key Membrane Keyboard with embossed graphics
  - Ten key numeric array plus 8 programmable function keys
  - Optional RS-422 multidrop protocol mode
  - Keyboard selectable SET-UP features—baud rates, parity, etc.
  - Size (5.625" W x 6.9" D x 1.75" H), Weight 1.25 lbs.
  - 5 x 7 Dot Matrix font with underline cursor
  - Displays 96 Character ASCII Set (upper and lower case)
  - Optional Bar Code Wand (shown)

**COMPUTERWISE, INC.**

302 N. Winchester • Olathe, KS 66062 • 800-255-3739 • FAX (913) 829-0810

CIRCLE NO 752

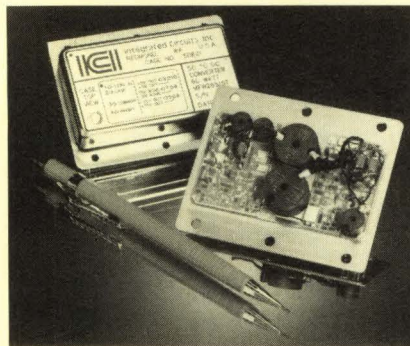

## MINIATURE 70 WATT DC-DC CONVERTER

ICI announces the addition of the MFW series of 50-70 watt DC-DC converters to its line of HI-REL devices. Up to 88% efficient, these converters are available in 5, 12, 15 V single, dual & triple output configurations. For MIL & other HI-REL applications, 125°C T<sub>C</sub> is possible with derated power output. Additional environment screening is available.

Interpoint, 10301 Willows RD., Redmond, WA, 98052,  
800/822-8782

CIRCLE NO 350

**SPECIAL OFFER**

**PHOTOPLOT  
AUTOROUTE**

**SCHEMA PCB**

PCB, PLOT & DRILL  
Regularly **\$2,025**  
until August 31st  
all three **\$1,495.**  
You save **\$530!**


Mainframe PCB layout features for  
your PC... + **FREE**, ongoing, 1-800  
support... + our 30 Day Money Back  
Guarantee!



**FREE DEMO KIT**  
1-800-553-9119

**OMATION**

CIRCLE NO 753

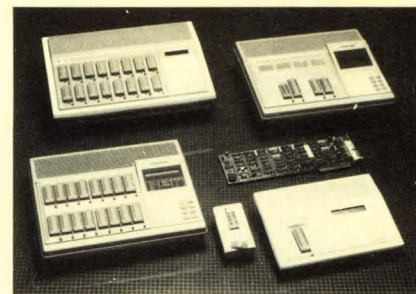

**PROMAC**

Programming Instruments

- Stand-Alone or PC-Based
- Engineering / Development
- Production / Field Service
- E/EE PROM / PAL / EPLD / Bipolar
- Single-Chip Microcomputers
- Simulator / Erasers / Surface-Mount



**adams-macdonald**  
ENTERPRISES INC.

800 Airport Road Telex 882141  
Monterey, California 93940 Fax (408) 373-3622  
Tel (408) 373-3627 800-777-1202

CIRCLE NO 751

## Development Tools

PseudoSam Cross-assemblers \$50.00

PseudoMax Cross-simulators \$100.00

PseudoSid Cross-disassemblers \$100.00

PseudoPack Developer's Package \$200.00 (\$50.00 Savings)

### POWERFUL

- PseudoCode supports an extensive line of professional cross-development tools. Tools that speed development of microprocessor based products. Fast, sophisticated macro assemblers to generate your program code. Versatile simulators that allow testing and debugging of the program even before the hardware exists. Easy to use disassemblers to help recover lost source programs.

### AFFORDABLE

- Until now, powerful tools like these have been priced from 5 to 10 times our price. Putting these time saving tools out of reach of all but large corporate engineering departments.

### BROAD RANGE OF SUPPORT

- PseudoCode currently has products for the following microprocessor families (with more in development):

Intel 8048	RCA 1802.05	Intel 8051	Intel 8096
Motorola 6800	Motorola 6801	Motorola 68HC11	Motorola 6805
Hitachi 6301	MOS Tech 6502	WDC 65C02	NSC 800
Rockwell 65C02	Intel 8080.85	Zilog Z80	
Hitachi HD64180	Motorola 68000.8	Motorola 68010	

- For more information call, write or use the reader service number below.
- To place an order, call or write:

PseudoCode  
P.O. Box 1423  
Newport News, VA 23601-0423  
(804) 595-3703

CIRCLE NO 754

**ADVERTISE  
IN  
PRODUCT  
MART  
AT  
LOW COST**

**Fill out this form to advertise in Product Mart.**

EDN072089

**ISSUE(S) REQUESTED** \_\_\_\_\_

<b>RATE:</b>	<b>1x</b>	<b>4x</b>	<b>7x</b>	<b>13x</b>	<b>19x</b>	<b>26x</b>	<b>39x</b>	<b>52x</b>
(Please circle)	\$855	825	805	725	705	695	685	665

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Telephone \_\_\_\_\_

Signature \_\_\_\_\_

AD ENCLOSED ☐

AD TO FOLLOW ☐


Mail to: EDN / 275 Washington Street / Newton, MA 02158-1630

**EDN PRODUCT MART appears in every issue — 26x a year!**

To advertise in Product Mart, call Joanne Dorian, 212/463-6415


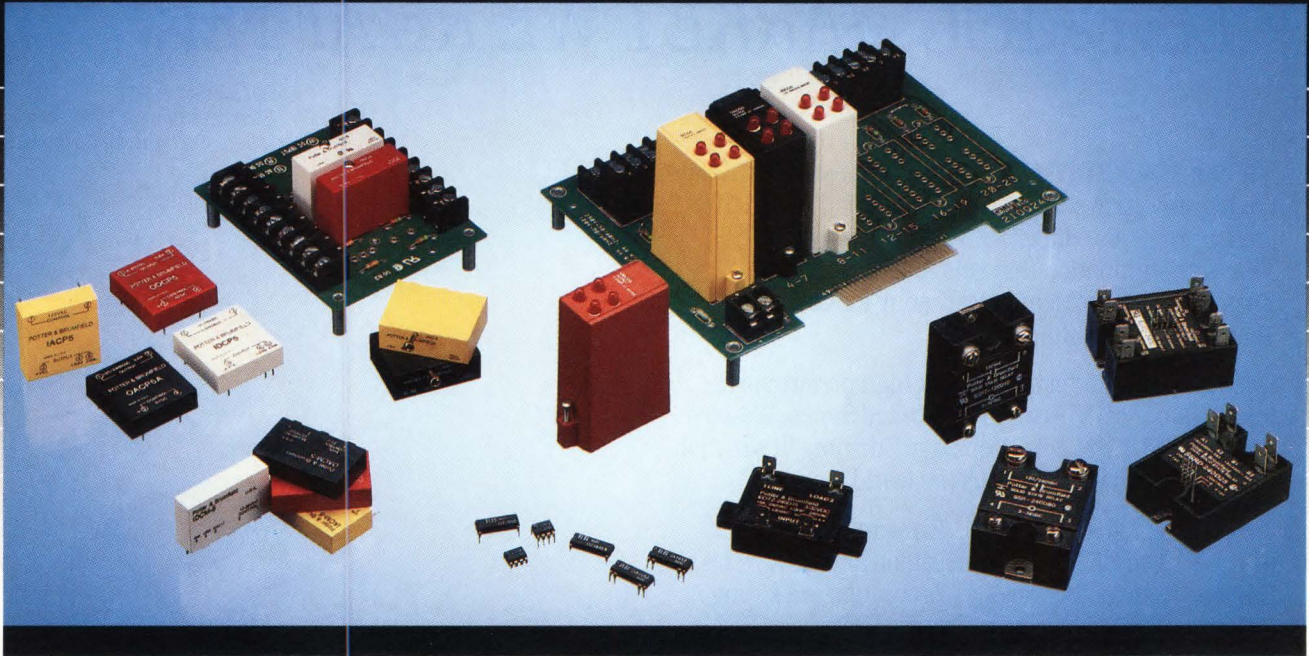
# Potter & Brumfield offers the solid state I/O module and relay options you need.



## Expanded Offering

New product additions to Potter & Brumfield's already-broad line provide you an even greater variety of solid state products, unmatched in the industry. Now you can select solid state input/output modules and relays with the package style, performance and features just right for your application.

## Input/Output Modules

Why force your design to fit around one or two standard configurations? P&B offers six different package styles for design flexibility. From plug-in quad modules to surface-mountable DIP units, our optically-isolated I/O modules provide the options and the traditional quality you expect from Potter & Brumfield.

## Solid State Relays

Our new family of chassis mount relays can switch from milliamps up to 110 amps. These relays in our familiar "hockey-puck" case offer many options you might never have imagined in an SSR. Zero-voltage or random turn-on. AC or DC input. Triac or paired-SCR switches and one, two or even four outputs help open the door to your creative design. At the other end of the spectrum, DIP solid state relays put reliable P&B solid state switching of loads up to 1 amp right on your printed circuit board. And you have a choice of conventional or surface mount terminals.

## Stock Availability

Most models are available from stock through our nationwide network of authorized stocking distributors, backed by our extensive factory inventory.

## Find Out More

Free literature is yours for the asking. Contact us today for details on our growing line of solid state input/output modules and relays. Potter & Brumfield, A Siemens Company, 200 South Richland Creek Drive, Princeton, Indiana 47671-0001.

**Call toll-free 1-800-255-2550 for the P&B authorized distributor, sales representative or regional sales office serving your area.**

# Potter & Brumfield

A Siemens Company

8806



# "EDN'S MAGAZINE AND NEWS EDITIONS ADDRESS THE WORLDWIDE LINEAR IC MARKET WE'RE AFTER."

Bill Ehram  
Vice President of Marketing  
Linear Technology Corporation

**"When I buy EDN's Magazine and News Editions,** I'm buying a powerful worldwide circulation and the most prestigious editorial environments available. That's a combination that gets results," says Bill Ehram, Vice President of Marketing for Linear Technology Corporation.

Ehram knows industry sales for high-performance linear ICs are split between the United States, Western Europe, and the Pacific Rim. Says Ehram, "It's my job to choose media that mirrors the world markets."

For complete global coverage, Ehram places his advertising in EDN Magazine Edition and EDN News Edition. "Linear Technology Corporation is a strong supporter of EDN Magazine Edition. We rely on EDN's targeted coverage of the U.S. and Western Europe. When EDN News Edition added Pacific Rim circulation in December 1987, we added it to our media schedule."


For Bill Ehram, "EDN's Magazine and News Editions form the cornerstone for Linear Technology Corporation's media plan now and in the future."



Advertising in EDN Magazine and News Editions works for Linear Technology Corporation. It can work for you.

**EDN**

**Where Advertising Works**

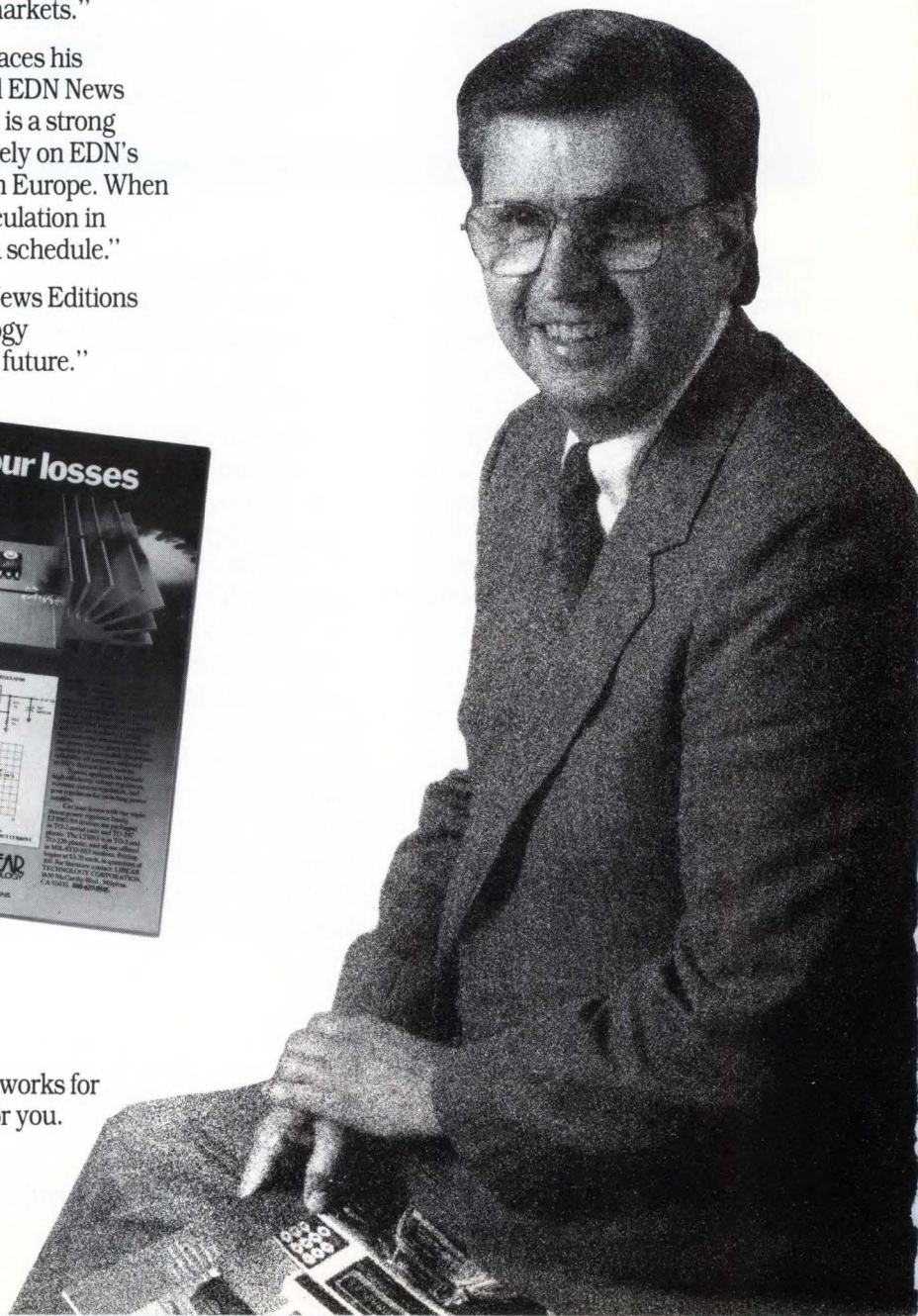



# BUSINESS/CORPORATE STAFF

**Peter D Coley**  
VP/Publisher  
Newton, MA 02158  
(617) 964-3030; Telex 940573  
Ora Dunbar, Assistant/Sales Coordinator

**Mark J Holdreith**  
Advertising Sales Director  
Newton, MA 02158  
(617) 964-3030  
Heather McElkenny, Assistant

**Deborah Virtue**  
Business Director  
Newton, MA 02158  
(617) 964-3030

**NEW ENGLAND**  
Chris Platt, Regional Manager  
Clint Baker, Regional Manager  
199 Wells Ave  
Newton, MA 02159  
(617) 964-3730

**STAMFORD 06904**  
George Isbell, Regional Manager  
8 Stamford Forum, Box 10277  
(203) 328-2580

**NEW YORK, NY 10011**  
Daniel J Rowland, Regional Manager  
249 West 17th St  
(212) 463-6419

**PHILADELPHIA AREA**  
Steve Farkas, Regional Manager  
487 Devon Park Dr, Suite 206  
Wayne, PA 19087  
(215) 293-1212

**CHICAGO AREA**  
Greg Anastos, Regional Manager  
Jack Johnson, Regional Manager  
Holli Gronset, Telemarketing  
Cahners Plaza  
1350 E Touhy Ave, Box 5080  
Des Plaines, IL 60017  
(312) 635-8800

**DENVER 80206**  
John Huff, Regional Manager  
44 Cook St  
(303) 388-4511

**DALLAS 75243**  
Don Ward, Regional Manager  
9330 LBJ Freeway, Suite 1060  
(214) 644-3683

**SAN JOSE 95128**  
Walt Patstone, Regional Manager  
Bill Klanke, Regional Manager  
Philip J Branon, Regional Manager  
James W Graham, Regional Manager  
3031 Tisch Way, Suite 100  
(408) 243-8838

**LOS ANGELES 90064**  
Charles J Stillman, Jr  
Regional Manager  
12233 W Olympic Blvd  
(213) 826-5818

**ORANGE COUNTY/SAN DIEGO 92715**  
Jim McErlan, Regional Manager  
18818 Teller Ave, Suite 170  
Irvine, CA  
(714) 851-9422

**PORTLAND, OREGON 97221**  
Pat Dakin, Regional Manager  
Walt Patstone, Regional Manager  
1750 SW Skyline Blvd, Box 6  
(503) 297-3382

**UNITED KINGDOM/BENELUX**  
Jan Dawson, Regional Manager  
27 Paul St  
London EC2A 4JU UK  
44 01-628 7030  
Telex: 914911; FAX: 01-628 5984

**SCANDINAVIA**  
Stuart Smith  
27 Paul St  
London EC2A 4JU UK  
01-628 7030  
Telex: 914911; FAX: 01-628 5984

**FRANCE/ITALY/SPAIN**  
Alasdair Melville  
27 Paul St  
London EC2A 4JU UK  
01-628 7030  
Telex: 914911; FAX: 01-628 5984

**WEST GERMANY/SWITZERLAND/AUSTRIA**  
Wolfgang Richter  
Sudring 53  
7240 Horb/Neckar  
West Germany  
49-7451-7828; Telex: 765450

**EASTERN BLOC**  
Uwe Kretschmar  
27 Paul St  
London EC2A 4JU UK  
01-628 7030  
Telex: 914911; FAX: 01-628 5984

**FAR EAST**  
Ed Schrader, General Manager  
18818 Teller Ave, Suite 170  
Irvine, CA 92715  
(714) 851-9422; Telex: 183653

**HONG KONG**  
John Byrne & Associates Ltd  
1613 Hutchison House  
10 HGarcourt Road  
Central Hong Kong  
Tel: 5-265474  
Tlx: 61708 WEDIN HX  
Fax: 5-8106781

**JAPAN**  
Kaoru Hara  
Dynaco International Inc  
Suite 1003, Sun-Palace Shinjuku  
8-12-1 Nishishinjuku, Shinjuku-ku  
Tokyo 160, Japan  
Tel: (03) 366-8301  
Telex: J2322609 DYNACO

**KOREA**  
Kim Kyong-Hae, BK International  
Won Chang Bldg, 3rd Floor 26-3  
Yoido-dong, Youngdungpo-ku  
Seoul 150, Korea  
Tel: 785-6665; FAX: 784-1915  
Telex: K32487 BIZKOR

**SINGAPORE/MALAYSIA/INDONESIA/THAILAND/  
THE PHILIPPINES/AUSTRALIA/NEW ZEALAND**  
Asia Pacific Media House PTE Ltd  
Peter Cheong  
100 Beach Rd  
#24-03 Shaw Tower  
Singapore 0718  
Tel: 2915354; Telex: RS 50026 MESPLY

**TAIWAN**  
Acteam International Marketing Corp  
6F, No 43, Lane 13  
Kwang Fu South Rd  
Mailing Box 18-91  
Taipei, Taiwan ROC  
760-6209 or 760-6210  
Telex: 29809; FAX: (02) 7604784

**PRODUCT MART**  
Joanne Dorian, Manager  
249 West 17th St  
New York, NY 10011  
(212) 463-6415

**INFO CARDS**  
Donna Pono  
Newton, MA 02158  
(617) 558-4282

**CAREER OPPORTUNITIES/CAREER NEWS**  
Roberta Renard, National Sales Manager  
103 Eisenhower Parkway  
Roseland, NJ 07068  
(201) 228-8602

Janet O Penn, Eastern Sales Manager  
103 Eisenhower Parkway  
Roseland, NJ 07068  
(201) 228-8610

Paula Compton, Western Sales Manager  
18818 Teller Ave, Suite 170  
Irvine, CA 92715  
(714) 851-9422

Diane Philipbar, Sales Assistant  
103 Eisenhower Parkway  
Roseland, NJ 07068  
(201) 228-8608

Wendy A Casella, Advertising/Contracts Coordinator  
Nan E Coulter, Advertising/Contracts Coordinator  
Aileen B Turner, Advertising/Contracts Coordinator  
(617) 964-3030

**William Platt, Senior Vice President, Reed Publishing USA**  
**Cahners Magazine Division**  
Terry McDermott, President, Cahners Publishing Co  
Frank Sibley, Senior Vice President/General Manager,  
Boston Division  
Tom Dellamaria, VP/Production & Manufacturing

**Circulation**  
Denver, CO: (303) 388-4511  
Eric Schmierer, Group Manager

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Joanne R Westphal, Cahners Reprint Service, Cahners Plaza, 1350 E Touhy Ave, Box 5080, Des Plaines, IL 60018. Phone (312) 635-8800.

# EDN's CHARTER

**EDN** is written for professionals in the worldwide electronics industry who design, or manage the design of, products ranging from circuits to systems.

**EDN** provides accurate, detailed, and useful information about new technologies, products, design techniques, and careers.

**EDN** covers new and developing technologies to inform its readers of practical design matters that will be of concern to them at once or in the near future.

**EDN** covers new products

- that are immediately or imminently available for purchase
- that have technical data specified in enough detail to permit practical application
- for which accurate price information is available.

**EDN's** Magazine Edition also provides specific "how to" design information that its readers can use immediately. From time to time, EDN's technical editors undertake special "hands on" engineering projects that demonstrate EDN's commitment to readers' needs for useful design information.

**EDN's** News Edition also provides comprehensive analysis and news of technology, products, careers, and distribution.

## EDN

275 Washington St  
Newton, MA 02158  
(617) 964-3030



# Logic. Pure and Simple.

The MODEL 860 programmer. The logical choice for logic device programming.

A complete range of logic device support at an affordable price. Stand-alone operation. Setting user-friendly trends. Portable and lightweight. On-line customer support.


- Programs:
  - PAL, GAL, IFL, E/EEPLD, PEEL and ZPAL devices
  - 20, 24, 28 and 40 pin DIP devices without adapter
- 64K byte standard RAM (256K optional)
- Blows device security fuse
- JEDEC and HEX formats
- Test vector and preload capabilities
- RS-232C serial port
- Options:
  - PLCC adapter
  - LOGILINK™ software for remote operation

Call DIGELEC for our full range of programmers.  
**Logic. The DIGELEC Way.**

**digelec** PROM & LOGIC PROGRAMMERS

CIRCLE NO 22

\$2795\*

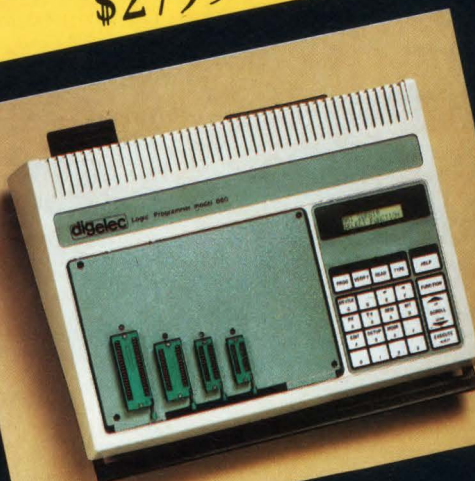

\*U.S. domestic price.

USA HQ: 22736 Vanowen St., West Hills, CA 91307. Tel: (818) 887-3755.

Outside California Tel: (800) 367-8750

Europe HQ: Gaissacherstrasse 18, D-8000 Munich 70. Tel: (089) 776 098.

## ADVERTISERS INDEX

Abbott Transistor Laboratories . . . . .	17	Logical Devices Inc . . . . .	41
Adams-Macdonald Corp . . . . .	44	Marconi Instruments . . . . .	1
ADPI . . . . .	43	Magnetek . . . . .	4-5
Allen Systems . . . . .	42	NEC Electronics Inc . . . . .	C2
AMP . . . . .	20-21	Nohau Corp . . . . .	41
Ango Electronics Corp . . . . .	42	Noritake Inc/Electronics Div . . . . .	25
Annabooks . . . . .	43	Omaton Inc . . . . .	44
Antona Corp . . . . .	41	OrCAD Systems Corp . . . . .	15
ARX . . . . .	27	PLX Technology . . . . .	33
Ballard Technology . . . . .	43	Potter & Brumfield . . . . .	45
BP Microsystems . . . . .	44	Prem Magnetics Inc . . . . .	C4
Capital Equipment Corp . . . . .	43	PseudoCode . . . . .	44
Computerwise Inc . . . . .	44	Pulizzi Engineering . . . . .	41
Digelec Inc . . . . .	48	Real Time Devices . . . . .	42
Franklin Software Inc . . . . .	43	RLM Research . . . . .	42
Fujitsu Microelectronics Inc . . . . .	8-9	Samsung Semiconductor . . . . .	30-31
Glassman High Voltage Inc . . . . .	10	Tesoft . . . . .	43
Grayhill Inc . . . . .	6	Thomas and Betts Corp . . . . .	C3
HiTech Equipment Corp . . . . .	42	Tri-L Data Systems Inc . . . . .	41
Interactive CAD Systems . . . . .	43	Ultimate Technology . . . . .	43
IEE . . . . .	39	Vishay Resistive Group . . . . .	40
Interpoint . . . . .	44	Vitellic Semiconductor . . . . .	2
Intusoft . . . . .	41	VTC Inc . . . . .	35
Ironwood Electronics Inc . . . . .	42	Westcor . . . . .	46
Jameco Electronics . . . . .	42		
L-Com Inc . . . . .	42		
Ledtronics . . . . .	43		
Linear Technology Corp . . . . .	37		

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

### Be An Author!

When you write for EDN, you earn professional recognition. And you earn \$75 per published magazine page.

EDN publishes how-to design application information that is read by more than 137,300 electronics engineers and engineering managers worldwide. That's an audience that could belong to you.

If you have an appropriate article idea, send your proposal and outline to: John Haystead, 275 Washington Street, Newton, MA 02158-1630.


For a FREE EDN Writer's Guide—which includes tips on how to write for EDN and other technical publications—please circle number 800 on the Information Retrieval Service Card.

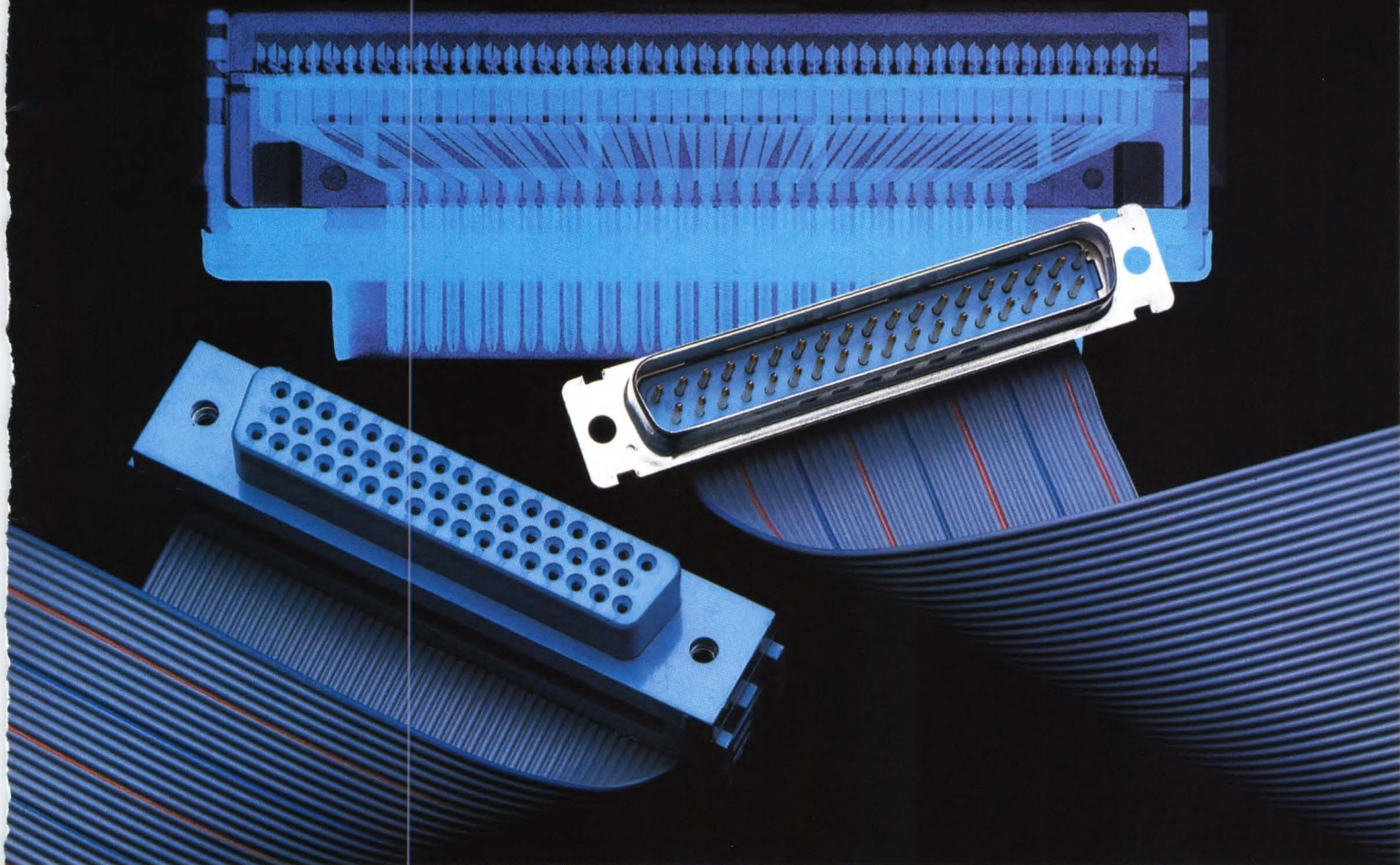**EDN**

First in Readership among Design Engineers and Engineering Managers in Electronics.



X-ray: ANSLEY® 50-pin "D" Connector with patented spread pitch design.



## A revealing look at the broadest line of IDC connectors available.

We show an X-ray of one of our IDC connectors to emphasize that it's what's beneath the surface that makes the difference in IDC connector performance. To make your best choice among IDC connector systems, take a close look at our line.

### The broadest line in the industry.

- "D" connectors, headers, female sockets, ribbon, card edge, male, DIP plug, plus a full line of flat and round-to-flat cables.

### A real system with real system benefits.

- Cable, connectors and tooling (hand or automatic) are designed and built to work as a system — this is your assurance of reliability.

### Designed for performance, built for productivity.

- We extrude our cable to maintain precise conductor to conductor spacing.
- Our beryllium copper contacts assure long-term stress retention in the critical crimp zone — preventing relaxation and the potential for intermittance.

- ANSLEY® pioneered the **one-piece connector** design. It's still the standard of the industry.
- Self-aligning **cable guides** in the connector assure positive termination every time — the key to high-yield, low-scrap production.

### The company behind the product.

A close look at our company will reveal our strong financial position, our commitment to the future, and our ability to support you worldwide. Write for our Annual Report — it's like an X-ray of our company.

To take a close look at our complete ANSLEY® IDC Connector line, and for the location of our nearest stocking distributor, call **1-800-344-4744.**


Thomas & Betts Corporation, Electronics Division,  
1001 Frontier Road, Bridgewater, NJ 08807 201-685-1600

## **Thomas & Betts**

Thomas & Betts facilities in Australia: Wyong North N.S.W., 43 53 2300; Canada: Ontario, 416-858-1010; France: Rungis Cedex, 1-46 87 23 85; Hong Kong: Kowloon, (852) 3-7391286; Italy: Milan, 02-61 20 451; Japan: Tokyo, 3 791 6411; Mexico: Naucalpan, 905 393 85 10; Singapore: 747 0244; Spain: Barcelona, 03-3 00 22 52; Sweden: Upplands Vasby, 07 60-8 81 10; Taiwan: Taipei, 2 713 0509; United Kingdom: Dunstable 0582-608101; West Germany: Egelsbach, 0 61 03-40-40.

CIRCLE NO 23



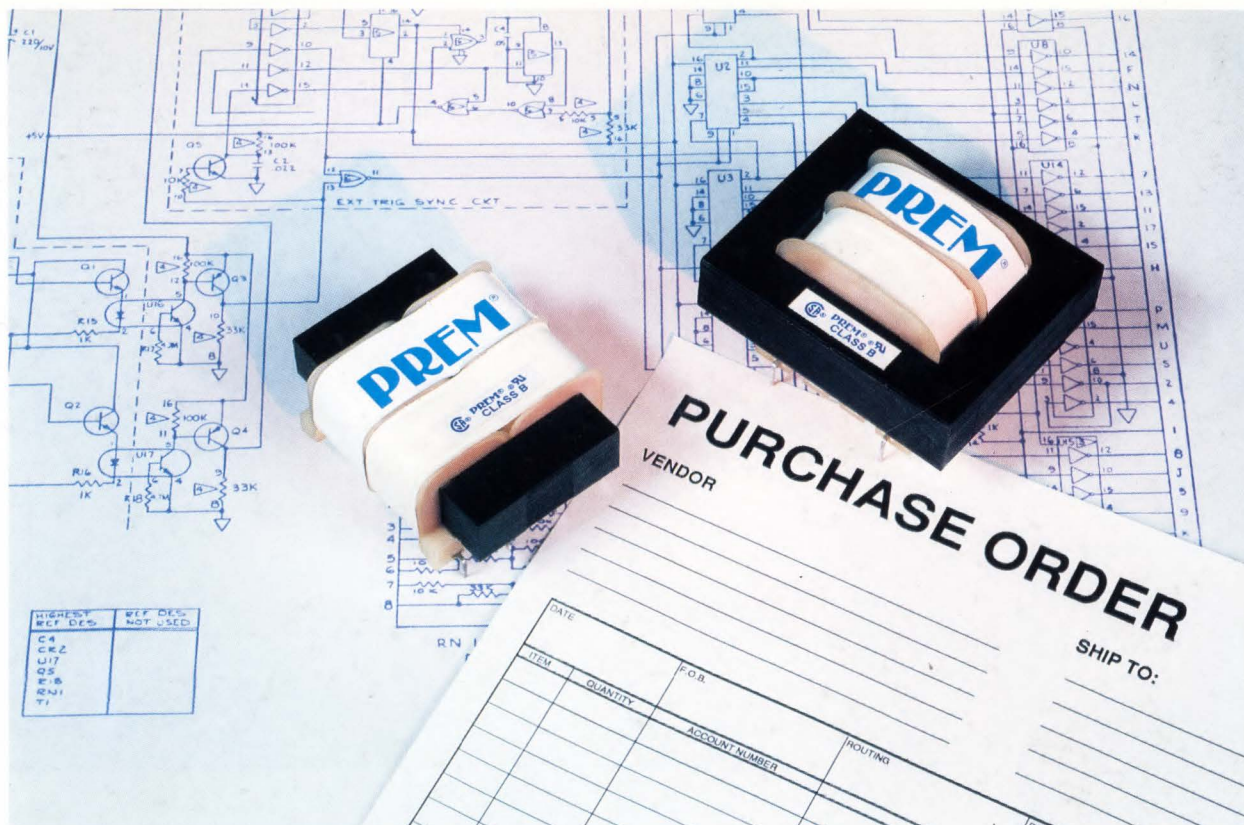

## The Power Transformer on which Engineering and Purchasing Can Agree...

### Purchasing

#### Controlling Costs...

We know part of your job is to control costs. Prem is the only transformer producer that invites you to compare. Compare Prem to Signal, Microtran, Stancor or Triad. You'll find that **PREM COSTS LESS**. And with Prem, our entire line has UL Recognition and CSA Certification at no extra cost to you. Our catalog includes cross-referenced part numbers to the above manufacturers to make comparison simple.

#### Deliveries Your Way...

**PREMIER** Service is what we call our commitment to meeting your deadlines and scheduling needs. We deliver immediately on small, in-stock quantities. And, depending on order size, we'll work with you to schedule out deliveries up to 12 months from the date of your order. Our transformers are specially packed to prevent transit damage...a worry you won't have with Prem.

### Engineering

#### Quality...


Everybody *talks* about quality. We *do* something about it. Prem transformers are epoxy impregnated with 100% solids to withstand most aqueous and solvent printed circuit board cleaning systems. This eliminates post-wash soldering. Our units are 100% induced voltage tested for shorted turns. Pins are pre-tinned to ensure good solder contact to the pc board. Prem has received awards from leading manufacturers for our outstanding quality.

The entire Prem line of PC power transformers is CSA Certified and UL Recognized at no extra cost to you. There are no hidden charges.
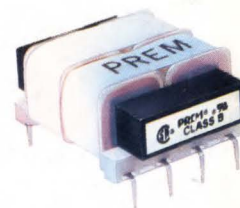
#### Technical Assistance...

You can talk to our Technical Services Manager or any one of our experienced design engineers. They are only a phone call away if you have a question or need technical assistance. We're also willing to modify our standard PC power transformers or provide a custom design to meet your needs.

For immediate technical data, see our catalog in EEM. Or call us.



# PREM<sup>®</sup>

**MAGNETICS,  
INCORPORATED**

3521 North Chapel Hill Road  
McHenry, Illinois 60050  
Tel. 815-385-2700  
FAX: 815-385-8578

Where quality really counts