


Automatic Electric's Plant
NORTHLAKE, ILLINOIS

basic circuits


RELAYS • SWITCHES • CONTROL SYSTEMS

AUTOMATIC ELECTRIC

NORTHLAKE, ILLINOIS

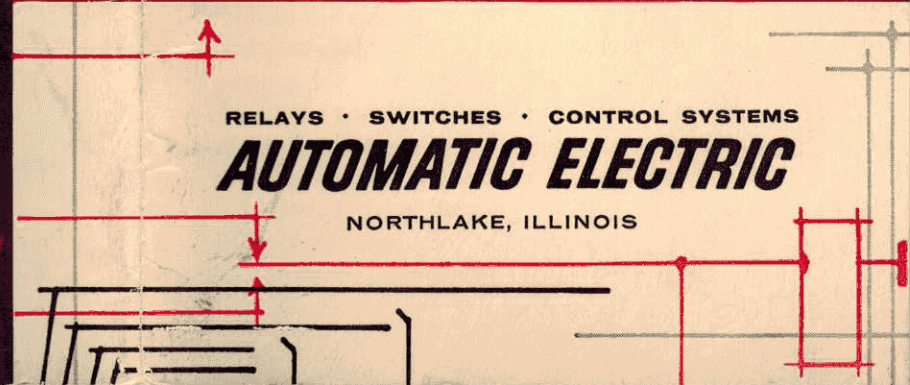

**AE
CAN
DO**

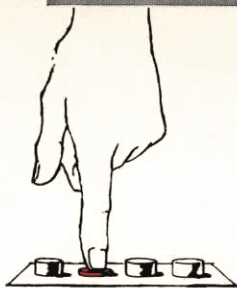

**MAKING IDEAS WORK
AUTOMATICALLY**

basic circuits

FOREWORD

Certain basic relay combinations and characteristics achieve specific circuit results in telephony. These basic circuits have become the building blocks of automatic telephone switching. Adaptable to other automated tasks, they are finding new and increasing use in industry every day. This book depicts a few such basic circuits.

We recommend that the information in this book be used only as a guide to determine the availability of a circuit and its components. Remember, even the best and most time proven circuit may fail because of the wrong choice of equipment. For this reason we make no attempt to define specific electrical parameters or component values.

Automatic Electric pioneered automatic telephone switching more than 60 years ago. Along with our growth in telephony, we have designed and furnished relays and switches for many industrial applications, making us uniquely qualified to advise our customers.

Our service extends to the expert engineering and manufacture of entire control systems. Call on our experienced staff engineers and salesmen to help you with control circuitry, engineering details, and component selection. If you prefer, address requests for such guidance to the home office: Automatic Electric Company, Director, Control Equipment Sales, Northlake, Illinois.

table of contents

**AE
CAN
DO**



	Page		Page
RELAY TRANSFER TREES			
Basic four-relay transfer tree. Fig. 1.....	6	Slow operate and release by series resistor and shunt condenser. Fig. 7.....	9
Rearrangement of basic four-relay transfer tree. Fig. 2.....	7	Slow operate by switched condenser shunt and series resistor. Fig. 8.....	9
RELAY COIL SYMBOLS		RELAY LOCKING CIRCUITS	
Quick-acting coils. Fig. 3.....	8	Locking on operating winding. Fig. 9 (a).....	10
Slow-acting coils. Fig. 3.....	8	Locking on auxiliary winding. Fig. 9 (b).....	10
Slow-releasing coils. Fig. 3.....	8	FORCED RELEASE OF RELAY	
Slow-operating coils. Fig. 3.....	8	Double-wound relay. Fig. 10.....	10
RELAY COIL TERMINAL CONNECTIONS		Shunt release of single-wound relay. Fig. 11.....	10
Single-wound coils. Fig. 3.....	8	REMOTE TWO-WIRE TO THREE-WIRE IMPULSE CONTROL	
Double-wound concentric coils. Fig. 3.....	8	Remote impulse control including reset over two wires (A B function). Fig. 12.....	11
Double-wound two-section coils. Fig. 3.....	8	Remote switching of groups of impulses (A B C function). Fig. 13.....	11
Single-wound slugged coils. Fig. 3.....	8	INFORMATION TRANSFER AS A FUNCTION OF IMPULSE TRAINS	
Single-wound sleeved coils. Fig. 3.....	8	Simple counting chain, two relays per step. Fig. 14..	12
Single-wound sleeved and slugged coils. Fig. 3....	8	Endless counting chain, two relays per step. Fig. 15.....	13
SLOW-OPERATING AND SLOW-RELEASING CIRCUITS			
Slow release by non-inductive shunt. Fig. 4.....	9		
Slow release by shorted heel-end winding. Fig. 5..	9		
Slow operate by shorted armature-end winding. Fig. 6.....	9		

TABLE OF CONTENTS cont'd.

**AE
CAN
DO**



	Page		Page
Count up, count down chain, two relays per step. Fig. 16.....	14	Pulse inversion circuit for "direct drive" of rotary stepping switch. Fig. 28.....	20
Bi-directional counting chain, add and subtract input, two relays per step. Fig. 17.....	15	Self-interrupted searching for absence of potential. Fig. 29.....	21
PULSE GENERATORS		Self-interrupted searching for presence of potential. Fig. 30.....	21
Low speed capacitive generator. Fig. 18.....	16	Self-interrupted stepping, shunt stopping. Fig. 31..	22
Medium speed slugged relay generator. Fig. 19....	16	Self-stepping, relay interrupted. Fig. 32.....	22
High speed relay generator. Fig. 20.....	16	Lock pulsing. Fig. 33.....	23
PULSE STRETCHING		Wiper disconnect circuit during stepping. Fig. 34..	23
Single-wound coil with non-inductive shunt. Fig. 21.	17	LOCAL SEQUENTIAL STEPPING SWITCH CONTROL WITHOUT RELAYS. Fig. 35.....	24
Two single-wound relays. Fig. 22.....	17	PREDETERMINED ROTARY SWITCH COUNTER	
RELAYS WITH CAM-OPERATED CON- TACTS (SERIES OCS)		Decimal count and carry. Fig. 36 (a).....	25
Pulse driven with reset function. Fig. 23.....	18	Predetermined count chain circuits. Fig. 36 (b)....	26
Mechanically latched on-off function. Fig. 24.....	18	Count complete function output and reset circuit. Fig. 36 (c).....	27
A. C. RECTIFIER CIRCUITS		SEQUENTIAL STEPPING, Fig. 37.....	28
Cat. No. PA-97 rectifier. Fig. 25.....	19	SYNCHRONIZED STEPPING, Fig. 38.....	29
Cat. No. PA-98 rectifier. Fig. 26.....	19	Typical count, connect, recycle circuit. Fig. 39.	30, 31
ROTARY SWITCH CIRCUITS			
Current limiting resistor for long pulse duration. Fig. 27.....	20		

IDENTITY OF RELAYS OPERATED TO SECURE FUNCTION ON OUTPUT LEADS INDICATED

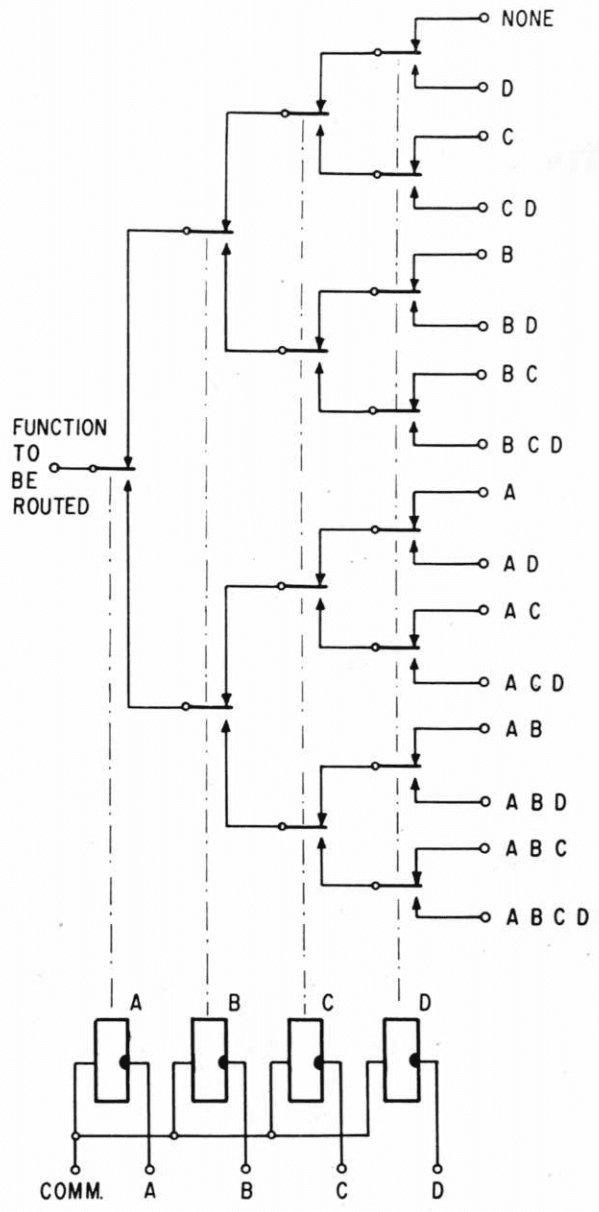


Fig. 1. Basic four-relay transfer tree. Single input is connected to any chosen output.

IDENTITY OF RELAYS OPERATED TO SECURE FUNCTION ON OUTPUT LEADS INDICATED


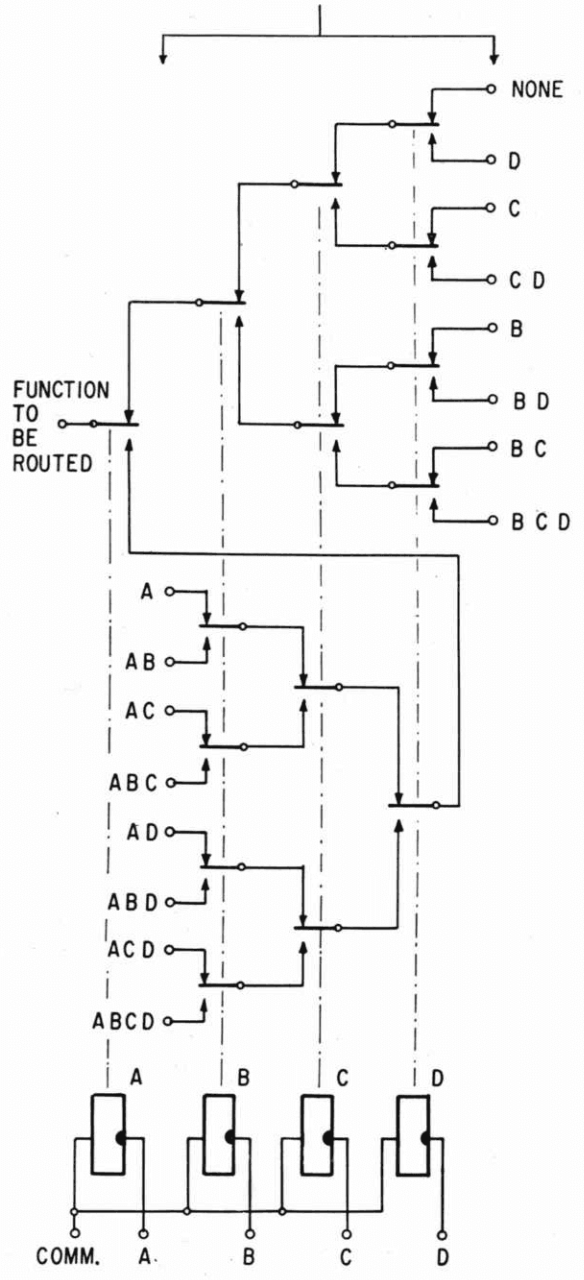


Fig. 2. Rearrangement of transfer tree to equalize contacts.

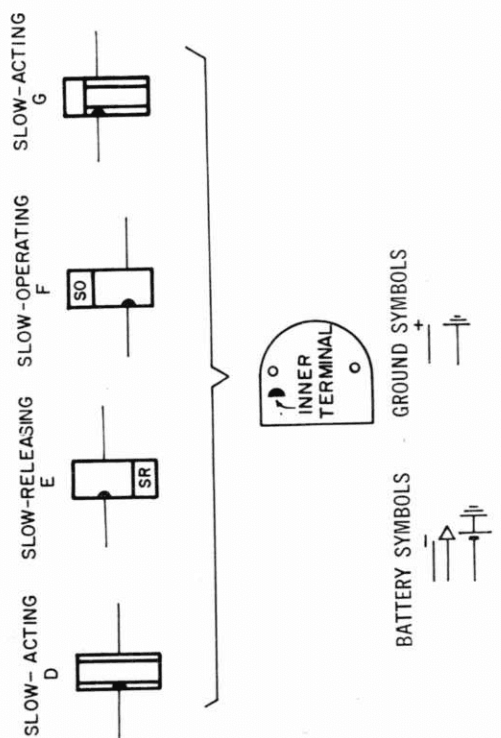

1-1 = INSIDE WDG. 1-1 = ARM. END WDG.
 2-2 = OUTSIDE WDG. 2-2 = HEEL END WDG.

Fig. 3. Relay coil symbols and coil connections.

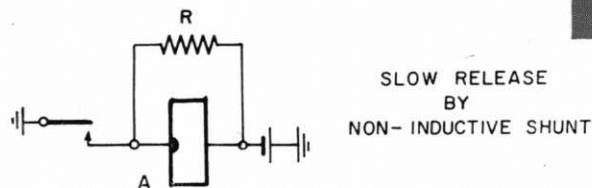


Fig. 4.

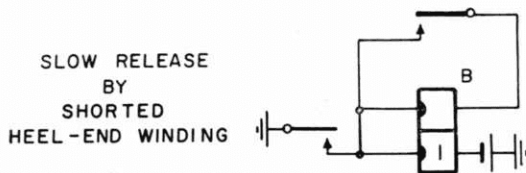


Fig. 5.

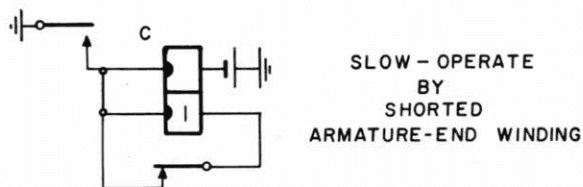


Fig. 6.

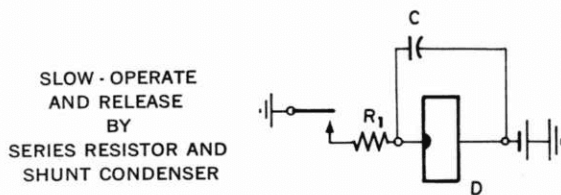


Fig. 7.

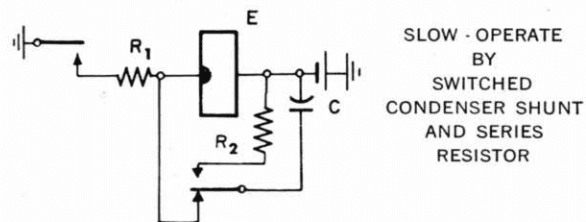


Fig. 8.

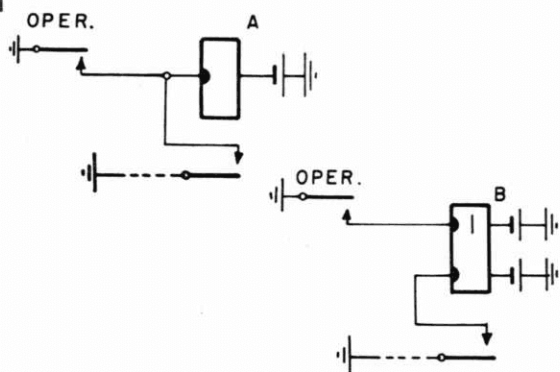


Fig. 9. (a) Locking on operating winding.
(b) Locking on auxiliary winding.

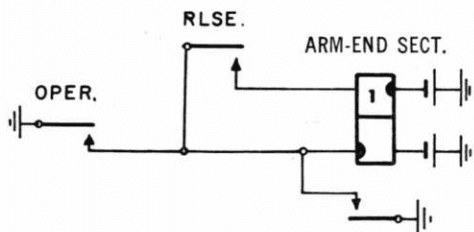


Fig. 10. Forced release of double-wound relay.

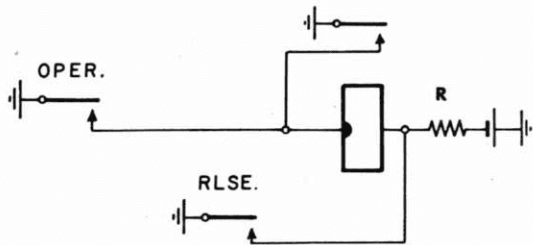


Fig. 11. Shunt release of single-wound relay.

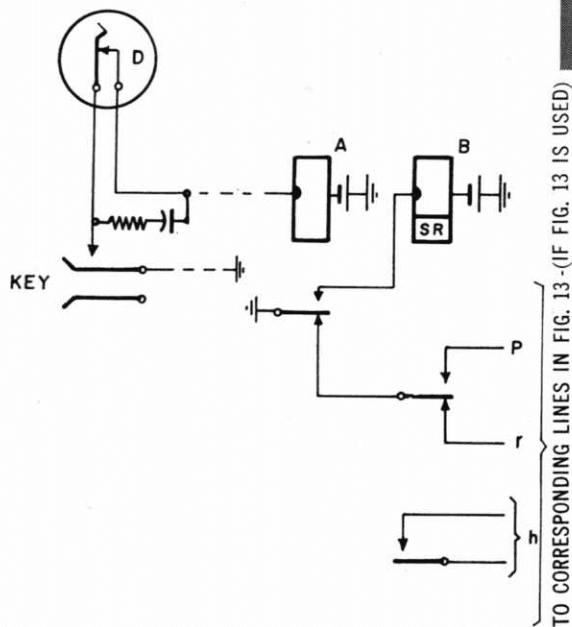


Fig. 12. Remote impulse control including reset over two wires (A B function).

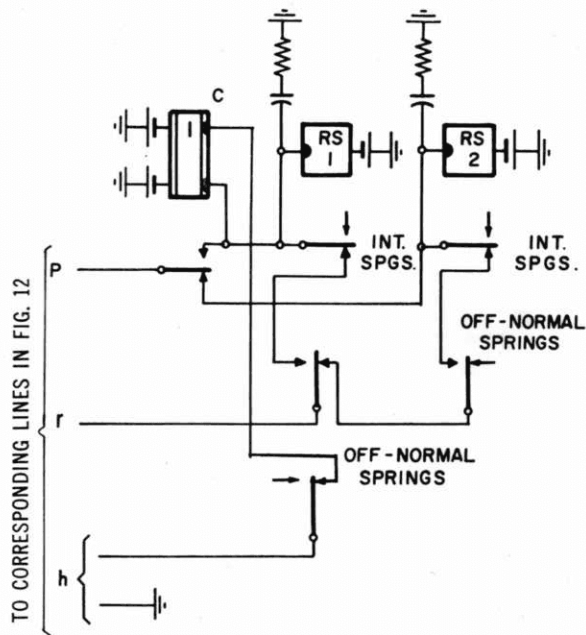


Fig. 13. Remote switching of groups of impulses (A B C function).

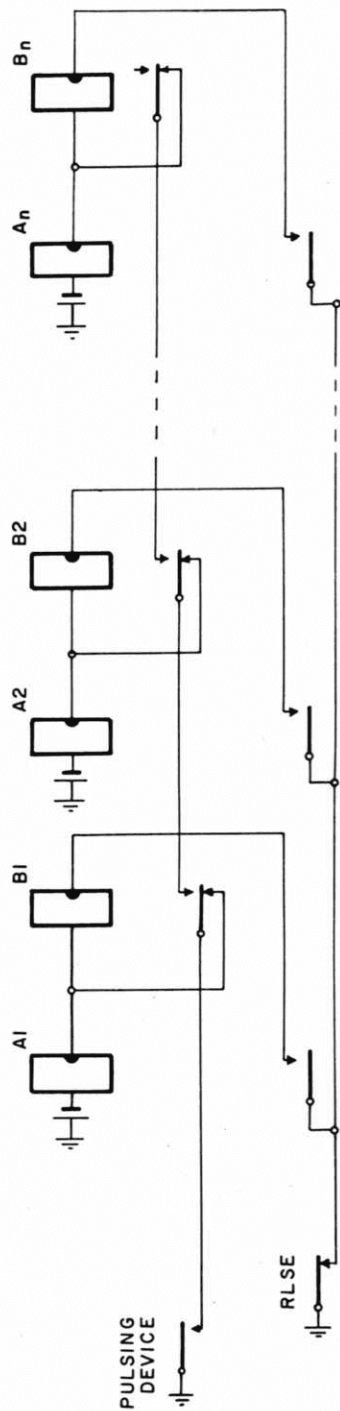


Fig. 14. Simple counting chain, two relays per step.

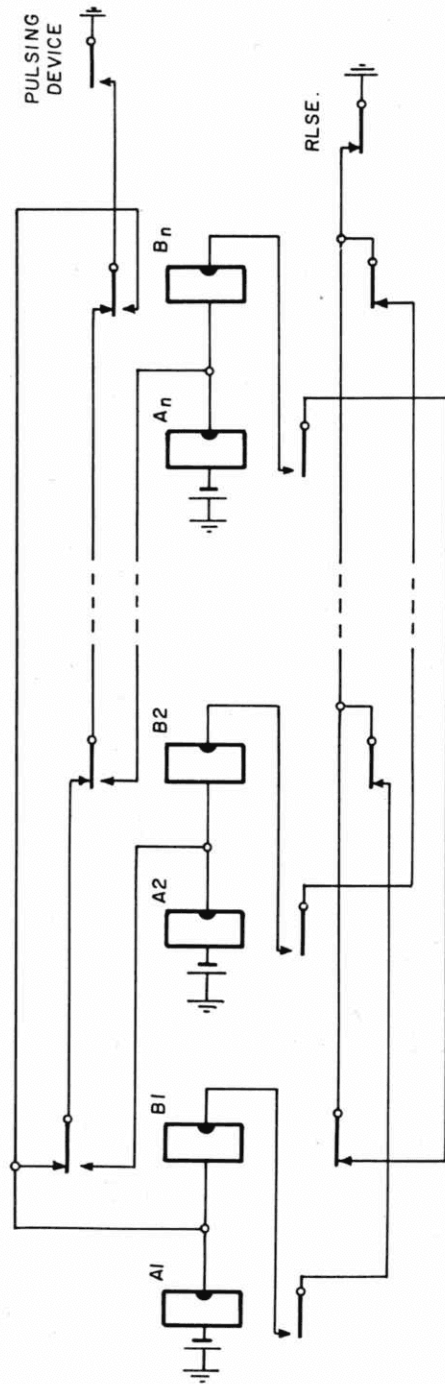


Fig. 15. Endless counting chain, two relays per step.

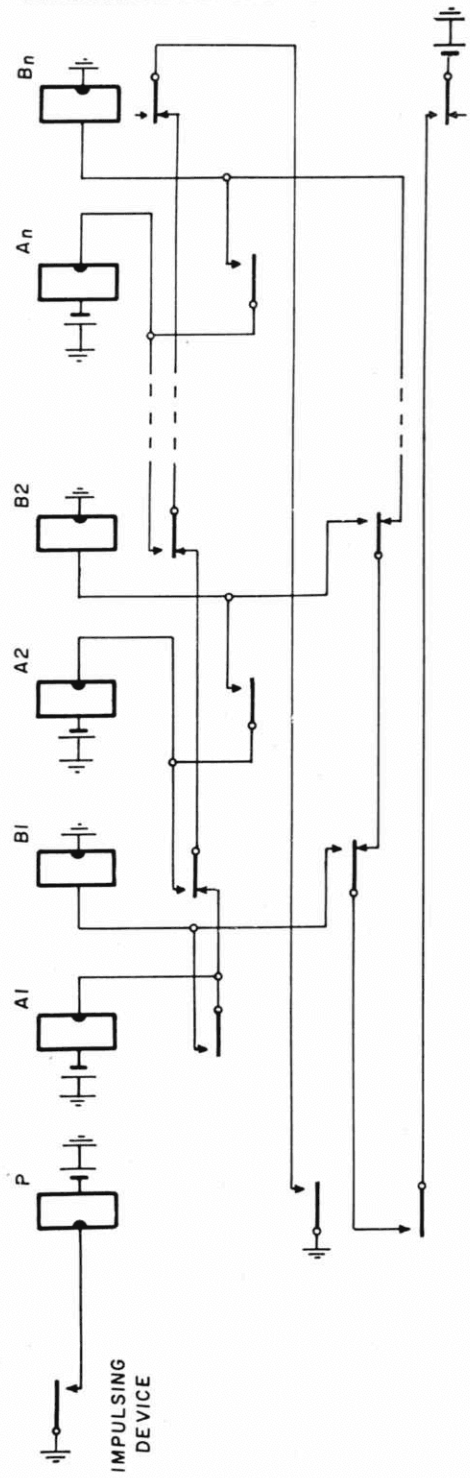


Fig. 16. Count up, count down chain, two relays per step.

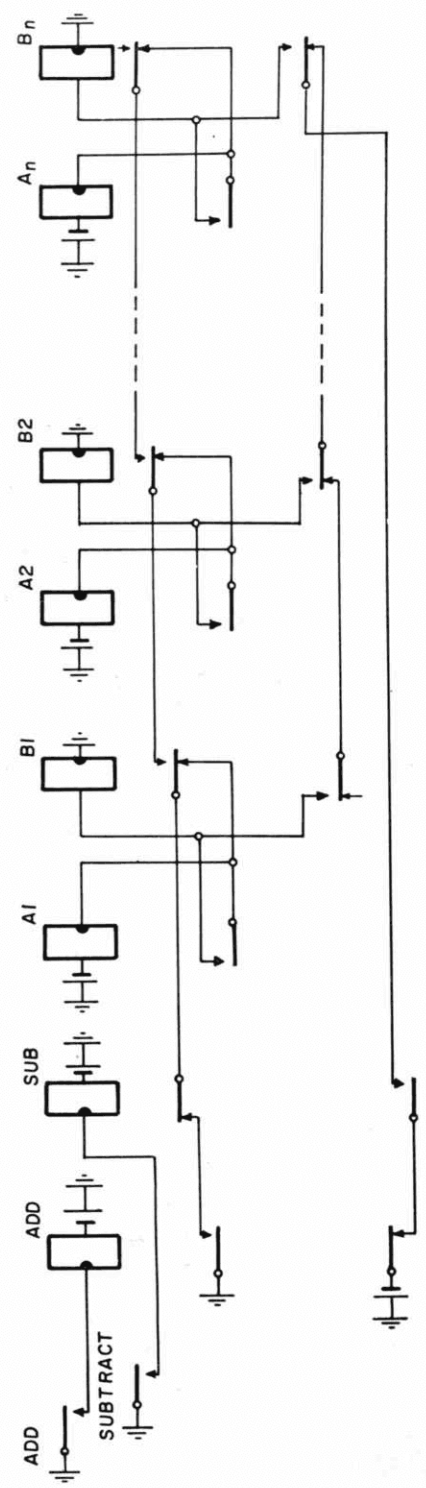


Fig. 17. Bi-directional counting chain, add and subtract input, two relays per step.

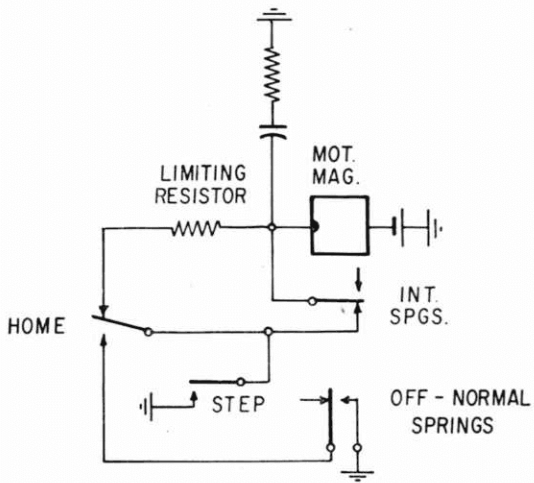


Fig. 27. Current limiting resistor for long pulse duration, to avoid overheating coil.

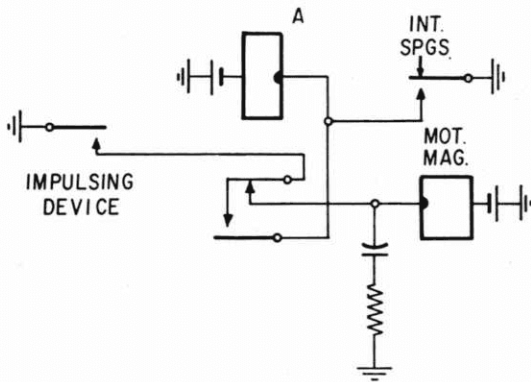


Fig. 28. Pulse inversion circuit for rotary switch "direct drive", to step switch on pulse closure.

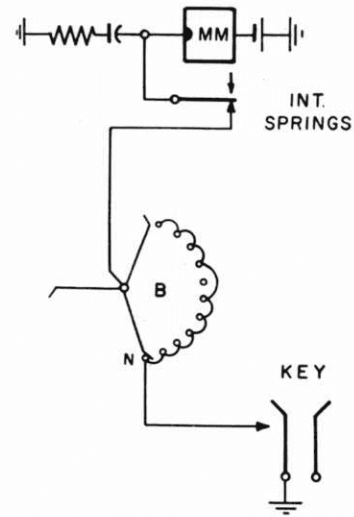


Fig. 29. Self-interrupted searching, to stop on absence of potential.

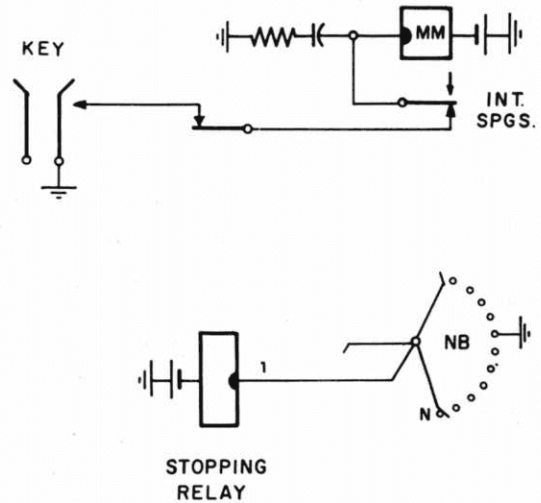


Fig. 30. Self-interrupted searching, to stop on presence of potential.

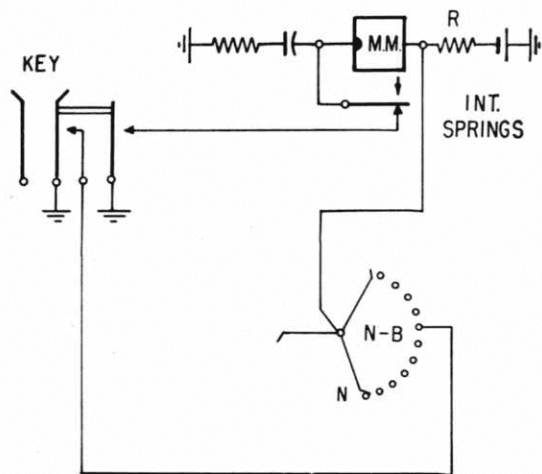


Fig. 31. Self-interrupted stepping, shunt stopping.

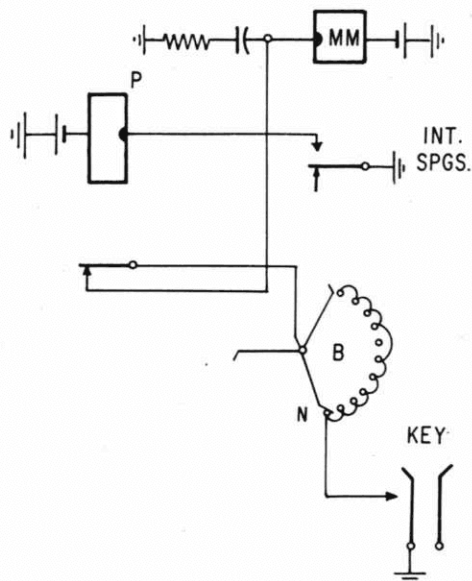


Fig. 32. Self-stepping, relay interrupted.

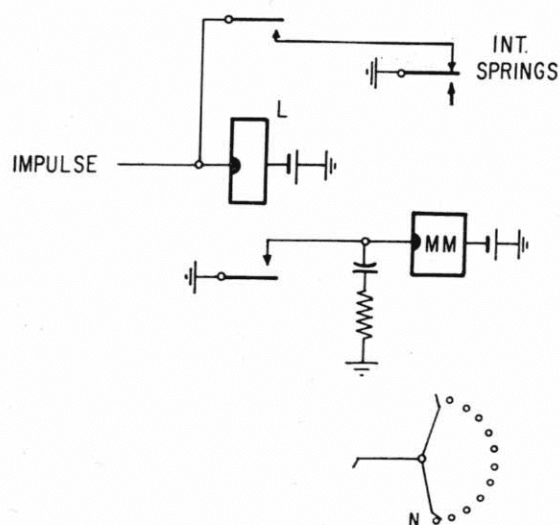


Fig. 33. Lock pulsing to insure stepping on inadequate or irregular-shaped pulse.

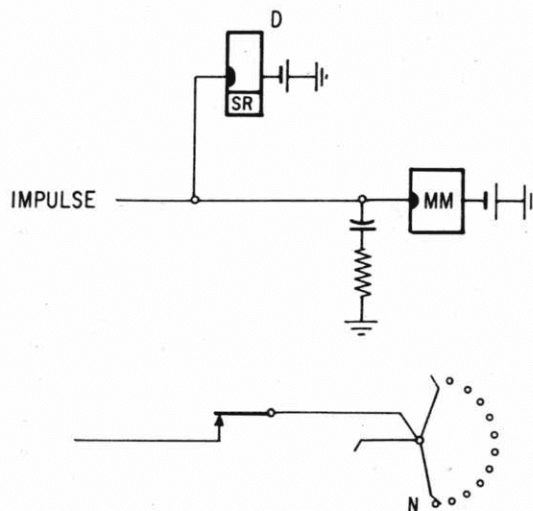


Fig. 34. Wiper disconnect circuit during stepping, to avoid energizing circuits wiped over.

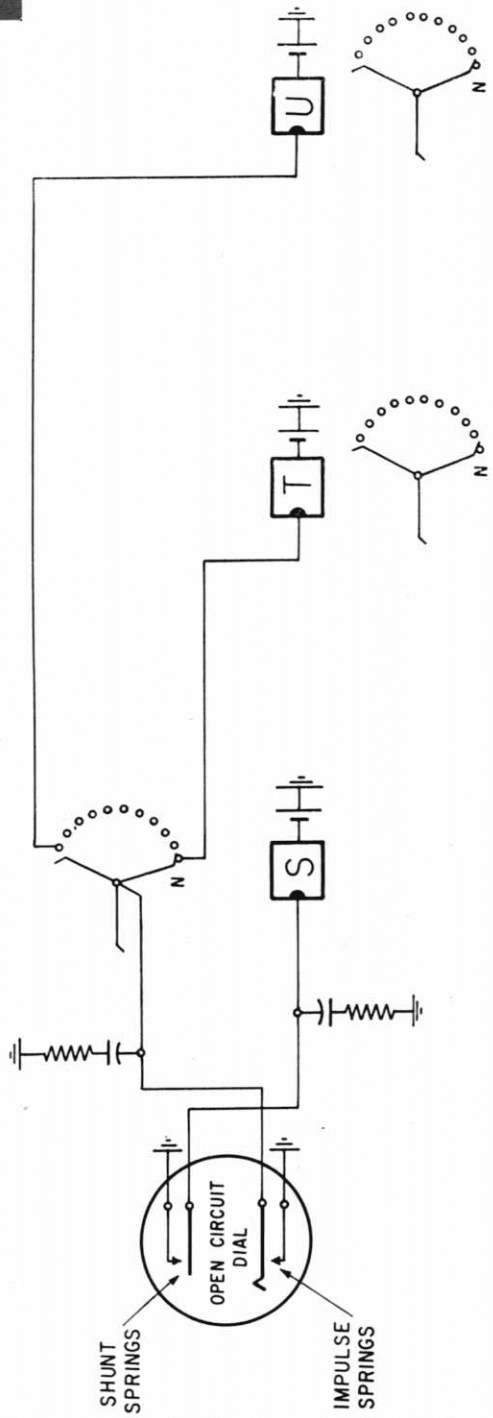


Fig. 35. Local sequential stepping switch control without relays. (See Fig. 12 and 13 for remote operation.)

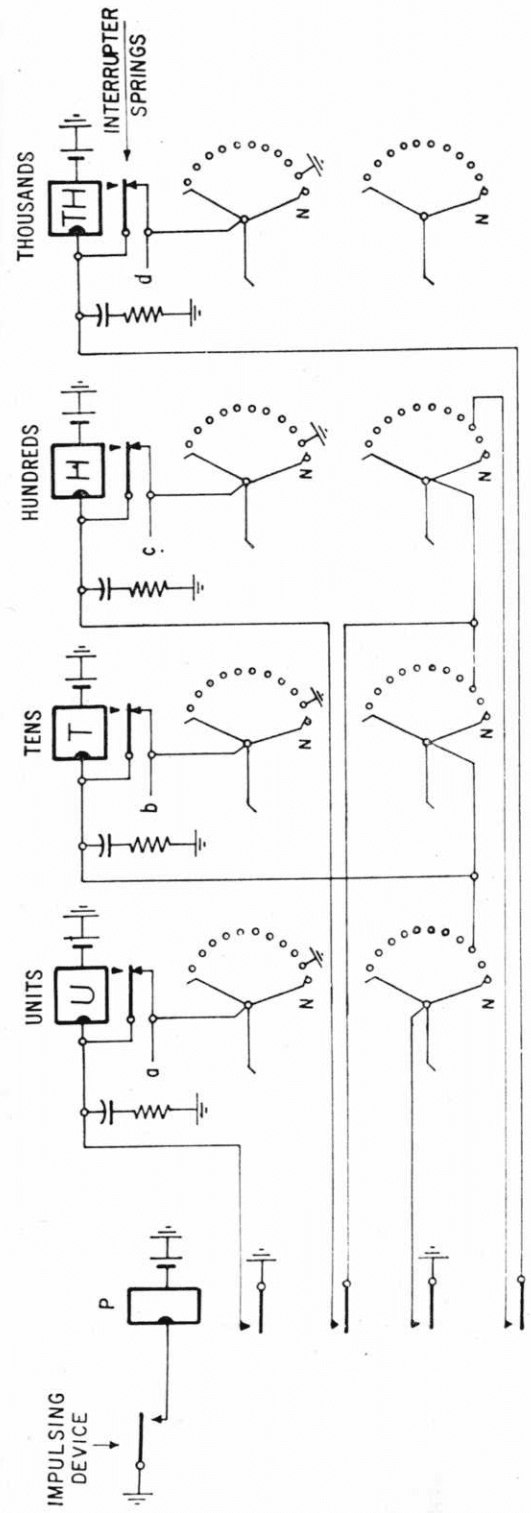


Fig. 36A. Decimal count and carry.

PREDETERMINED COUNTER

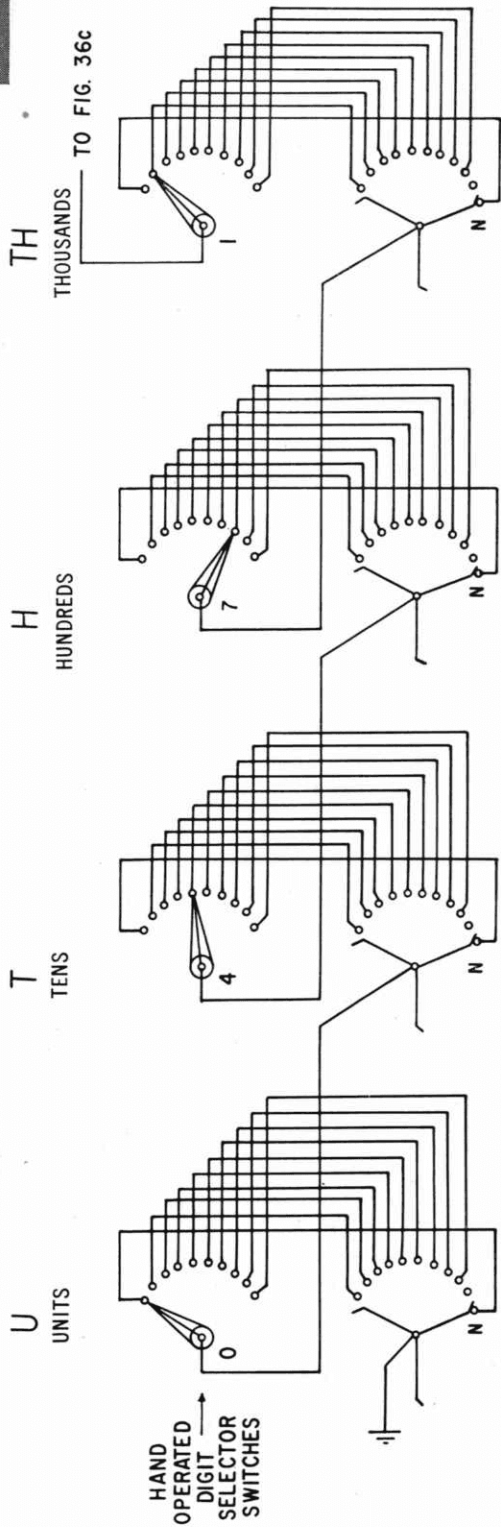


Fig. 36B. Predetermined count chain circuit.

PREDETERMINED COUNTER

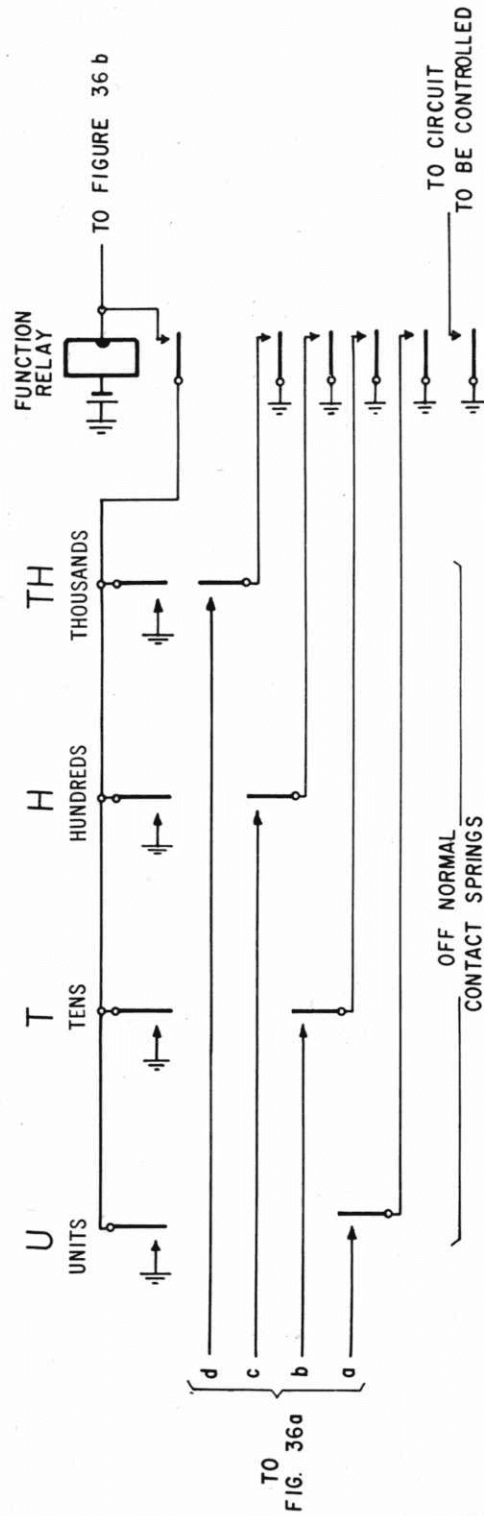


Fig. 36C. Count complete function output and reset circuit.

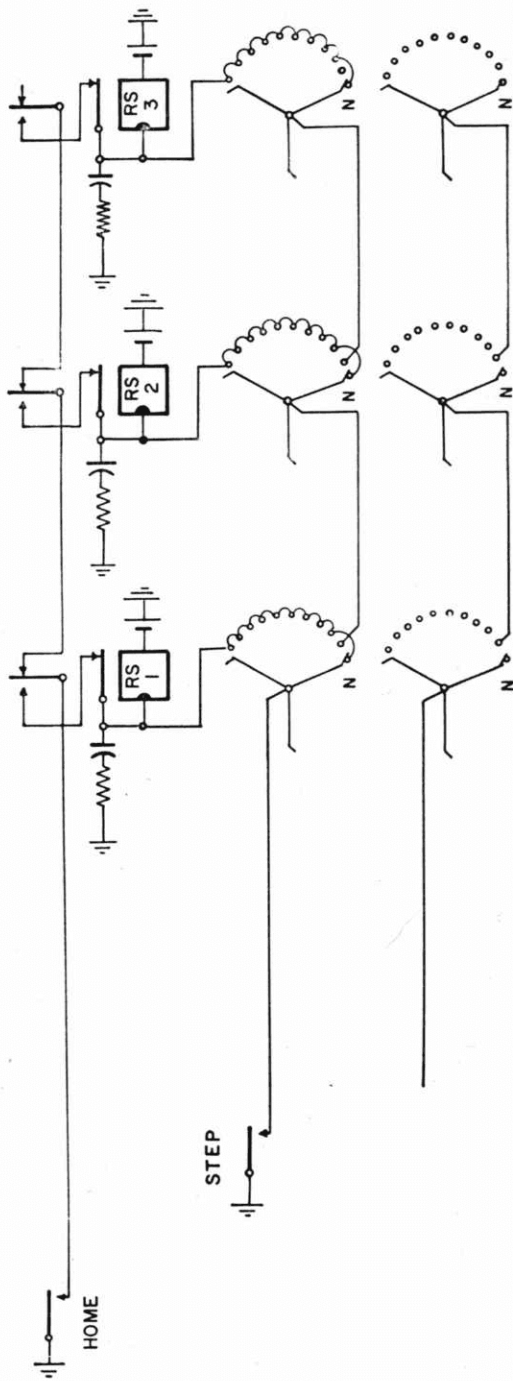


Fig. 37. Sequential or tandem stepping of rotary switches.

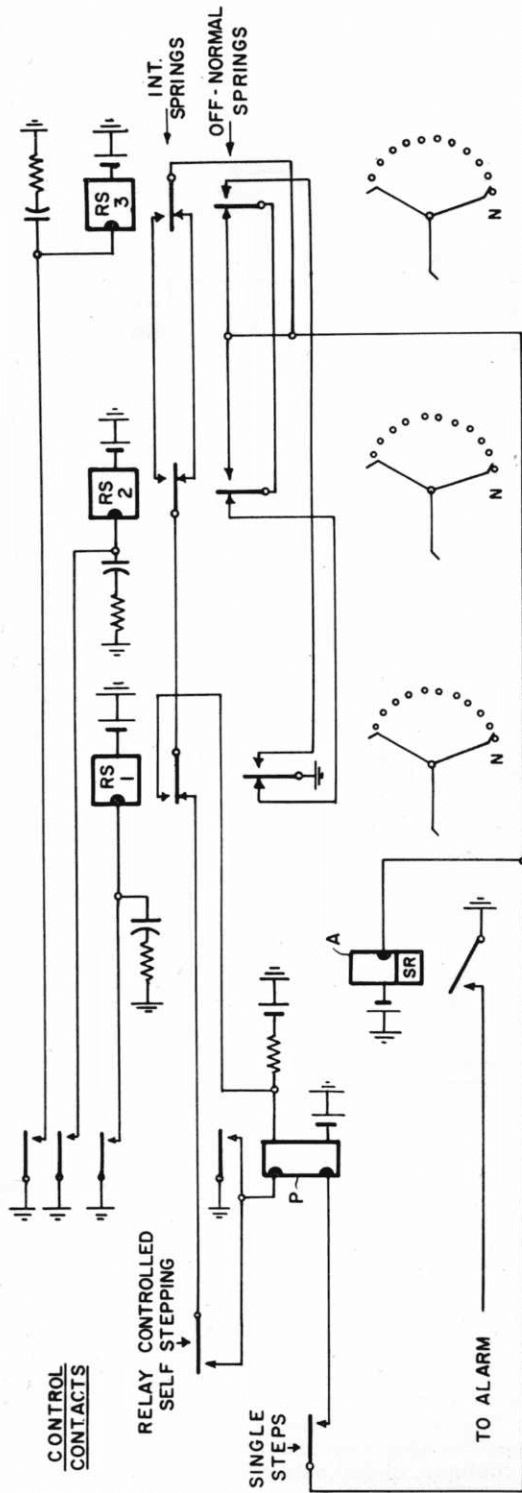


Fig. 38. "Lock step" synchronization of rotary stepping switches for simultaneous stepping.

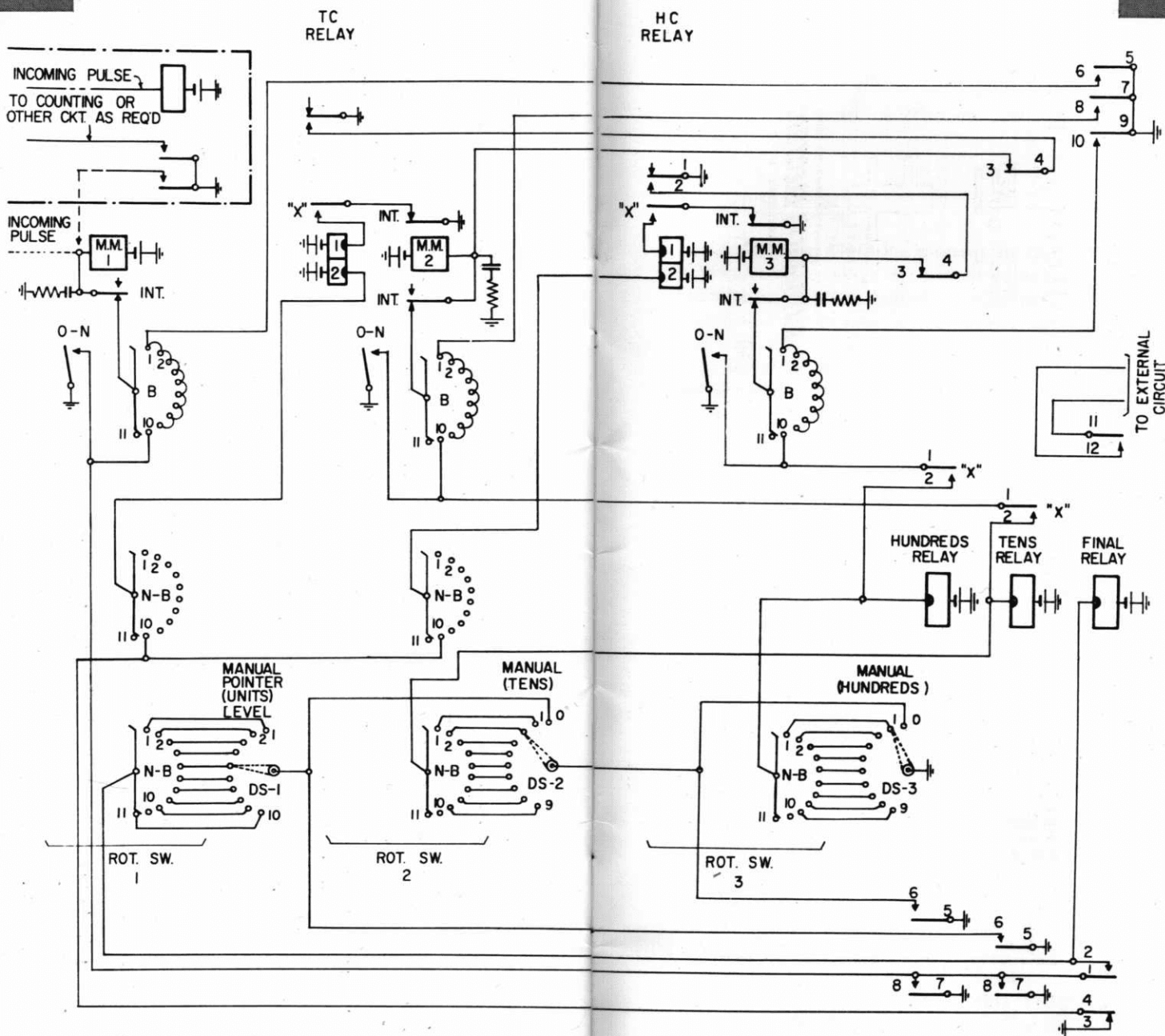


Fig. 39. Typical count, connect, recycle circuit. Manual decade switches DS-1, DS-2, and DS-3 are set to the desired count. Stepping Switch 1 is externally pulsed, stepping commences in sequence, and final relay operates when exact count is reached. If signal pulses continue, circuit automatically recommences

cycle. Key: MM, motor magnet—steps rotating contactors below it; INT, interrupter contacts—open each time MM armature is energized; O-N, off-normal contacts—operated by a lobe on rotating contactor assembly, stays closed 1 to 10, opens at 11; B, bridging, and N-B, non-bridging wipers.

